

# Topic 6: Registers & Counters

-- **Fahimul Haque (FHE)**

\* Slides are used as an aiding tool to teach in the classroom. Not every information/details that will be taught in the classes are mentioned on the slides. Hence, you are expected to follow the given textbook(s) for your course.


# Part 1: Registers

# Registers


- A *register* is a group of flip-flops, each one of which shares a common clock and is capable of storing one bit of information.
- An  $n$ -bit register consists of a group of  $n$  flip-flops capable of storing  $n$  bits of binary information.
- In addition to the flip-flops, a register may have combinational gates that perform certain data-processing tasks.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
  - ❖ retrieve data from register
  - ❖ store/load new data into register (serial or parallel)
  - ❖ shift the data within register (left or right)
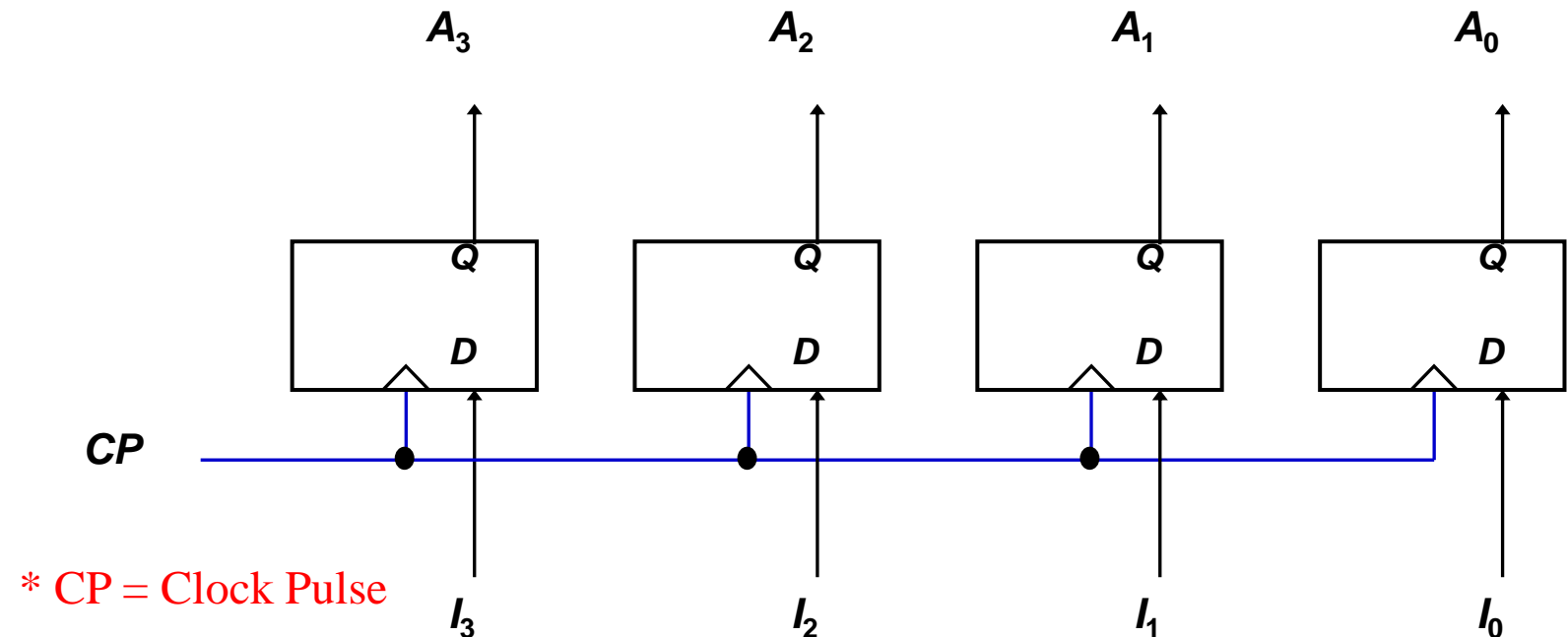
# Simple Registers

- Various types of registers are available commercially. The simplest register is one that consists of only flip-flops, without any gates.
- The transfer of new information into a register/flipflop is referred to as **loading or updating** the register/flipflop. If all the bits of the register are loaded simultaneously with a common clock pulse, we say that the loading is done **in parallel**.
- Example: A 4-bit register. A new 4-bit data is loaded every clock cycle (the common clock input triggers all flip-flops during a positive/negative edge of a pulse).



# Four-bit register with load signal

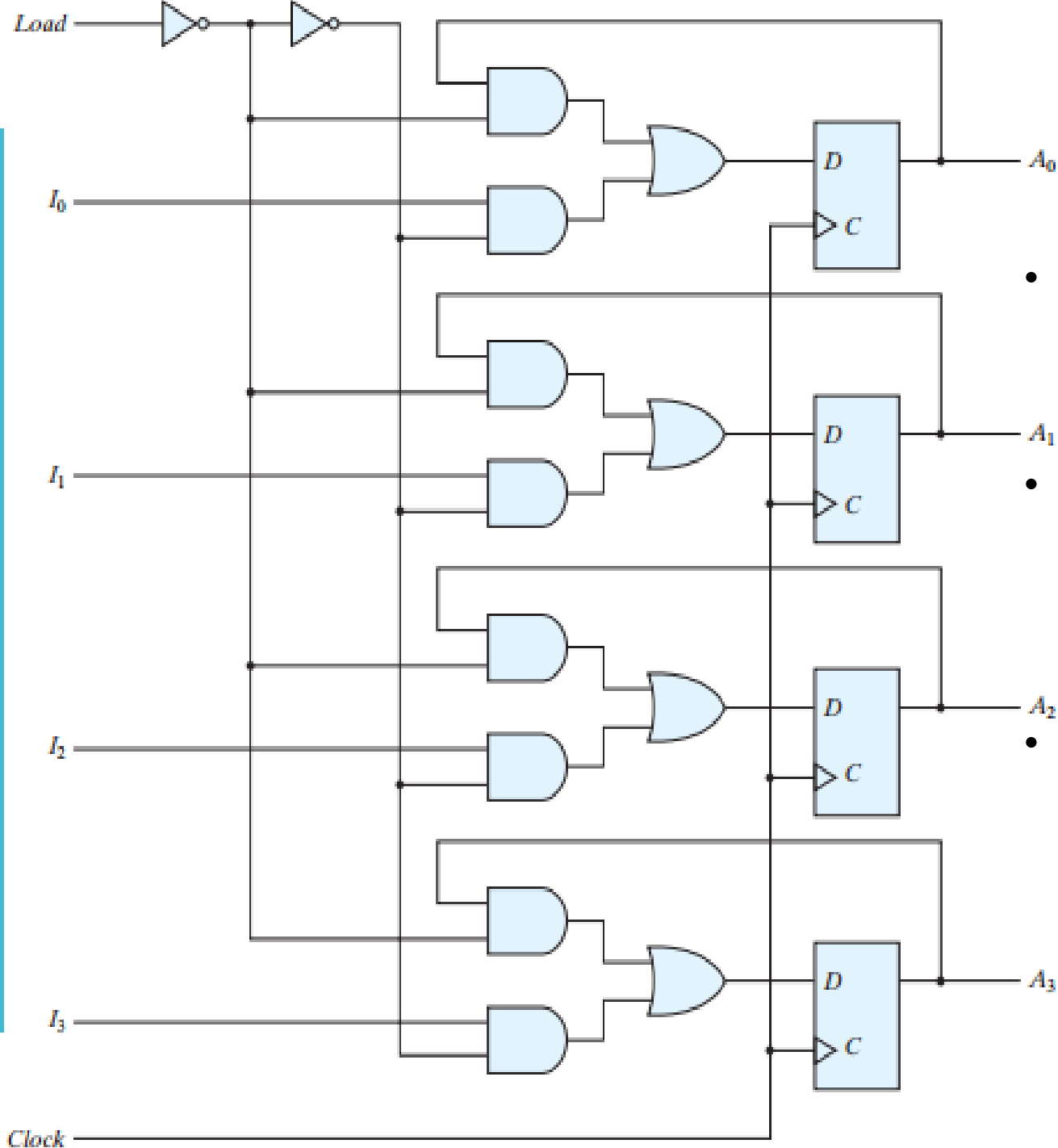


- The load input to the register determines the action to be taken with each clock pulse.
- When the load input is 1, the data at the four external inputs are transferred into the register with the next positive edge of the clock.
- When the load input is 0, the outputs of the flip-flops are connected to their respective inputs to keep the contents of the register unchanged.

# Shift Registers

- Another function of a register, besides storage, is to provide for *data movements*.
- A register capable of shifting the binary information held in each cell to its neighboring cell, in a selected direction, is called a *shift register*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.
- The logical configuration of a shift register consists of a **chain of flip-flops in cascade**, with the output of one flip-flop connected to the input of the next flip-flop. All flip-flops receive common clock pulses, which activate the shift of data from one stage to the next.


# Four-bit Shift Register

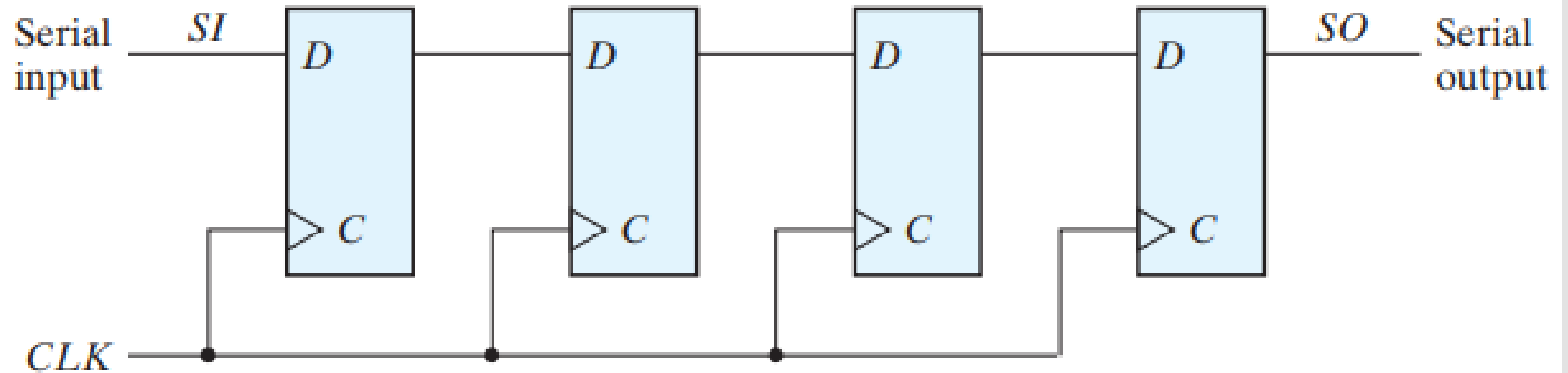


- The simplest possible shift register is one that uses only flip-flops.
- The shown shift register is **unidirectional** (left-to-right).
- The **serial input** determines what goes into the leftmost flip-flop during the shift.
- The **serial output** is taken from the output of the rightmost flip-flop.
 
# Different Shift Register Operations


- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in / parallel out

 

(f) Rotate right

 


(g) Rotate left




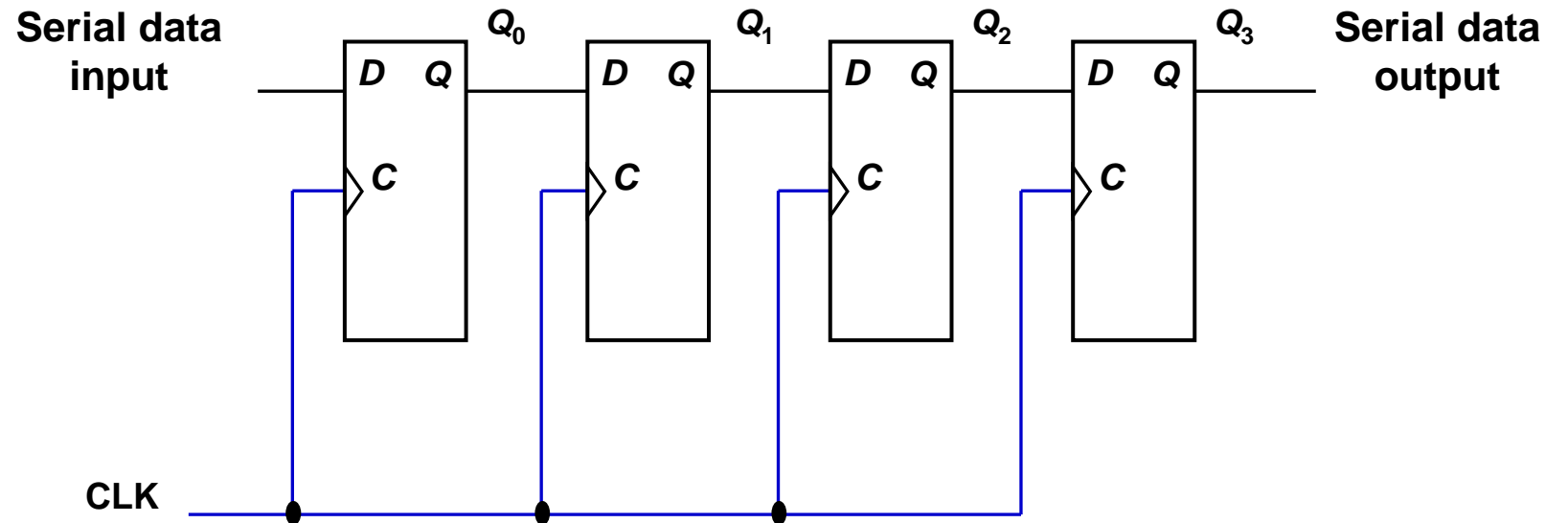
# Serial In/Serial Out Shift Right Registers

- Accepts data serially – one bit at a time – and also produces output serially.



How can we make a 3-bit serial in, serial out, and left shift register?

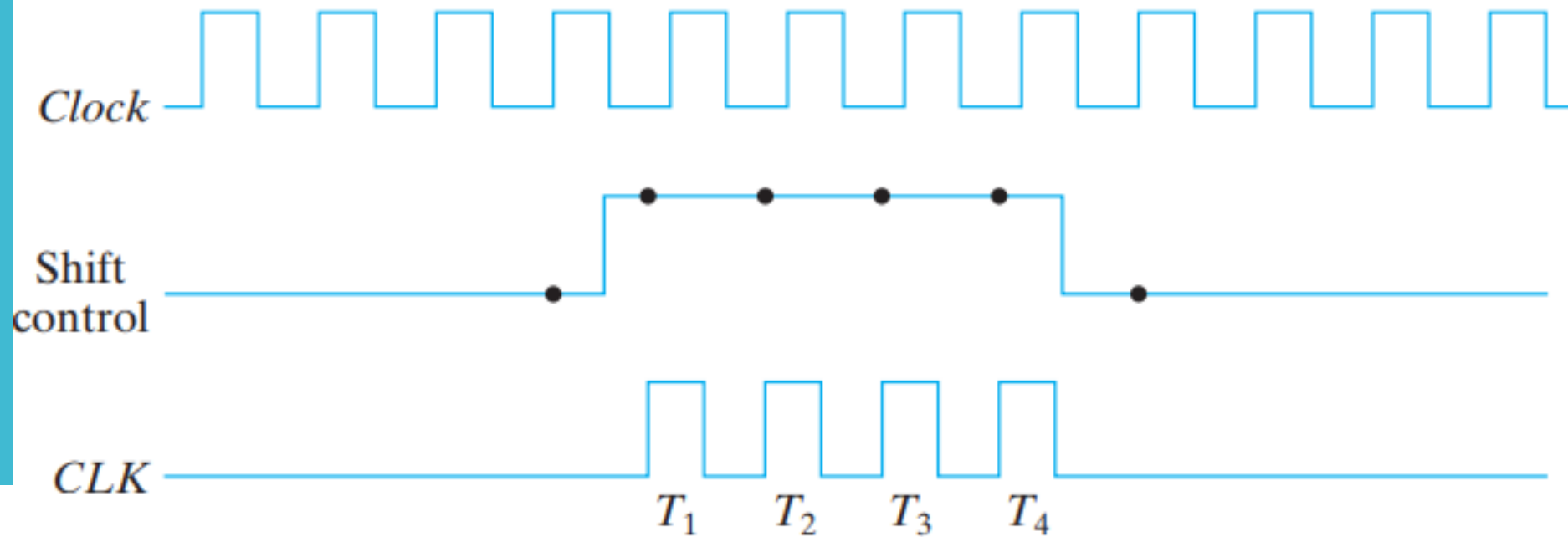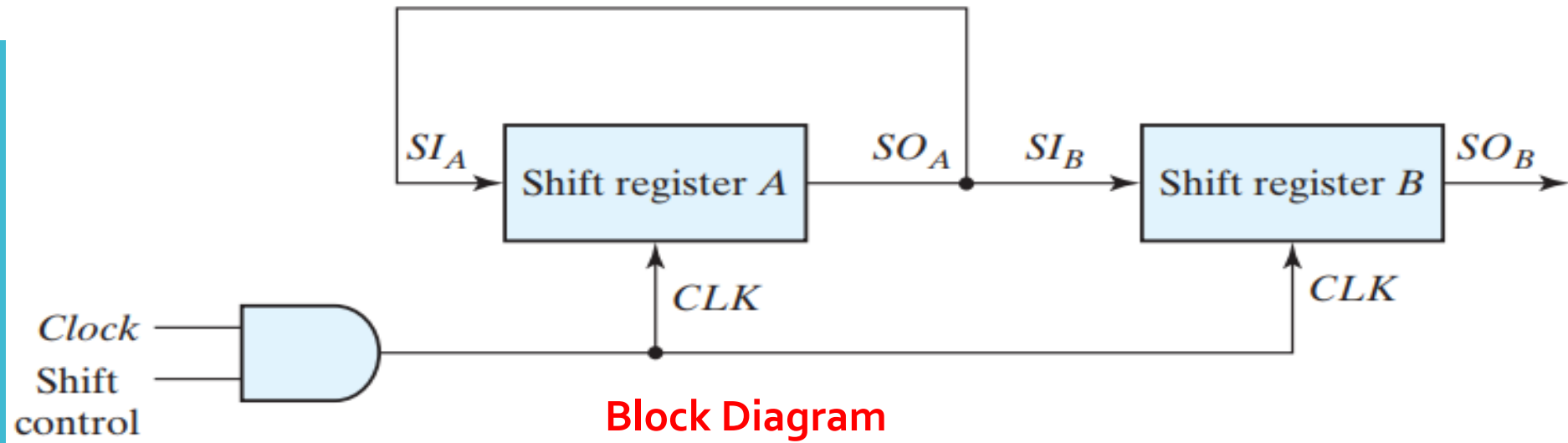**Application:** Serial transfer of data from one register to another.




**Timing Diagram**

# Serial Transfer

# Serial In/Serial Out Shift Registers



- Serial-transfer example.

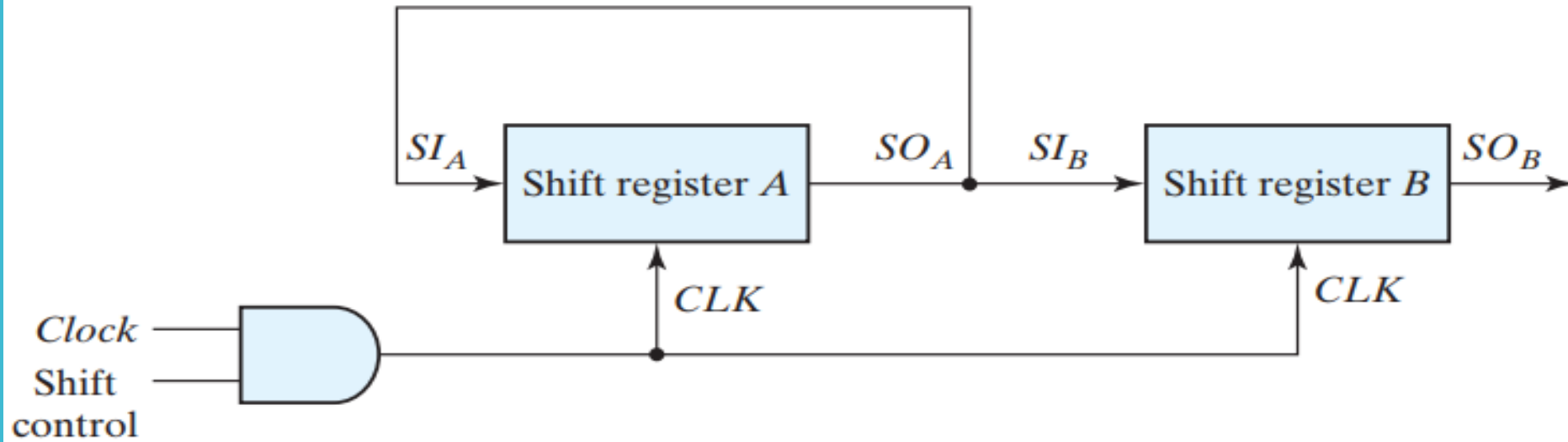

Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After $T_1$	1 1 0 1	1 0 0 1	1
After $T_2$	1 1 1 0	1 1 0 0	0
After $T_3$	0 1 1 1	0 1 1 0	0
After $T_4$	1 0 1 1	1 0 1 1	1

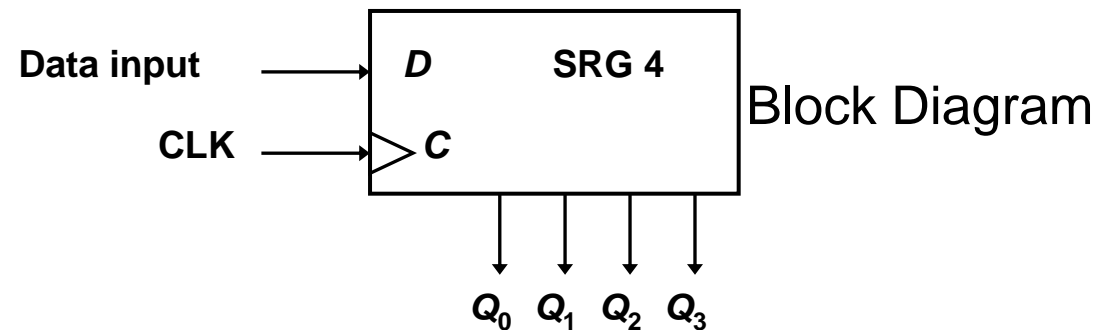 
# Serial In/Parallel Out Shift Registers

- Accepts data serially.
- Outputs of all stages are available simultaneously.



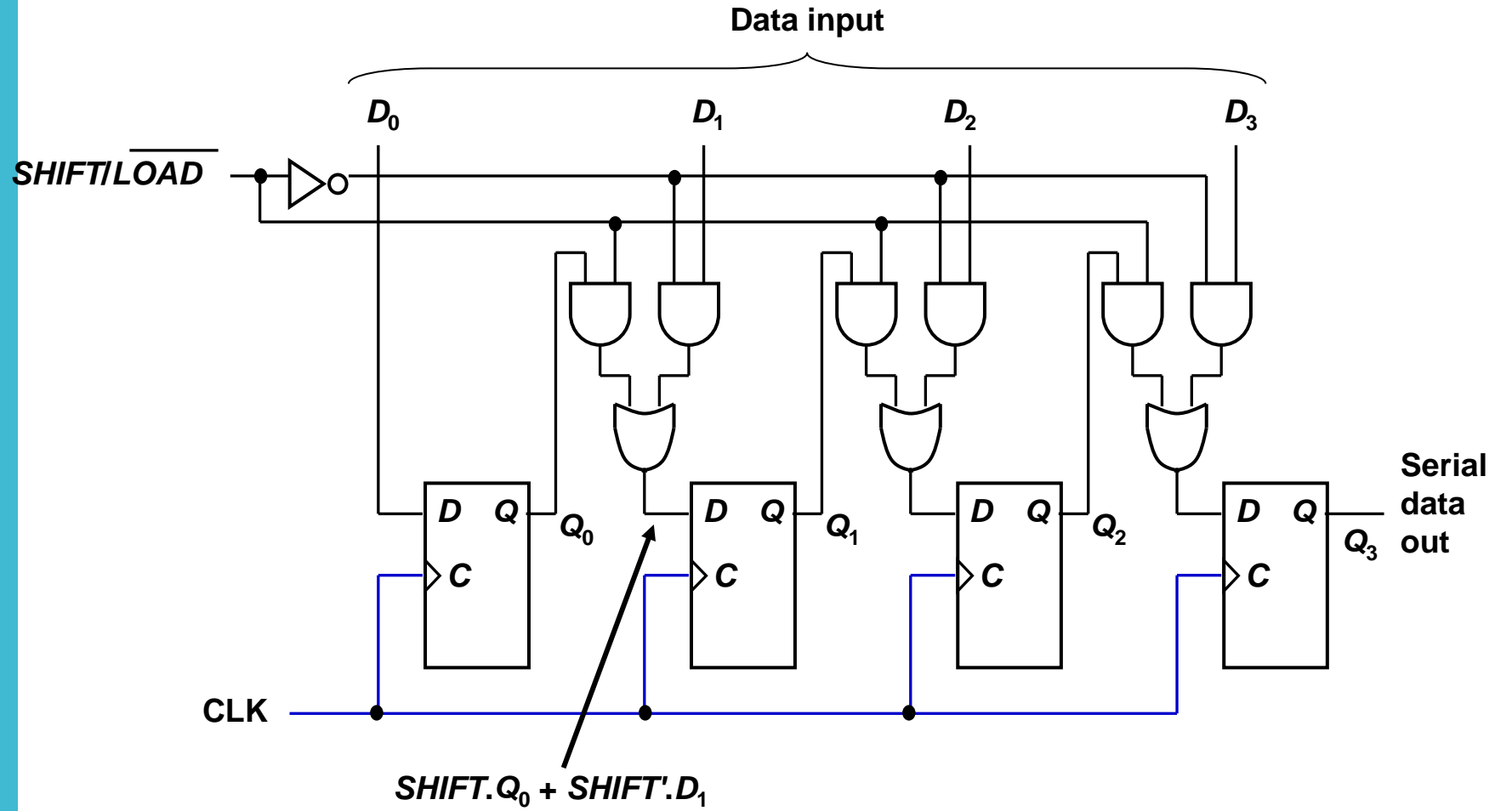
# Parallel In/Serial Out Shift Registers

- Bits are entered simultaneously, but output is serial.



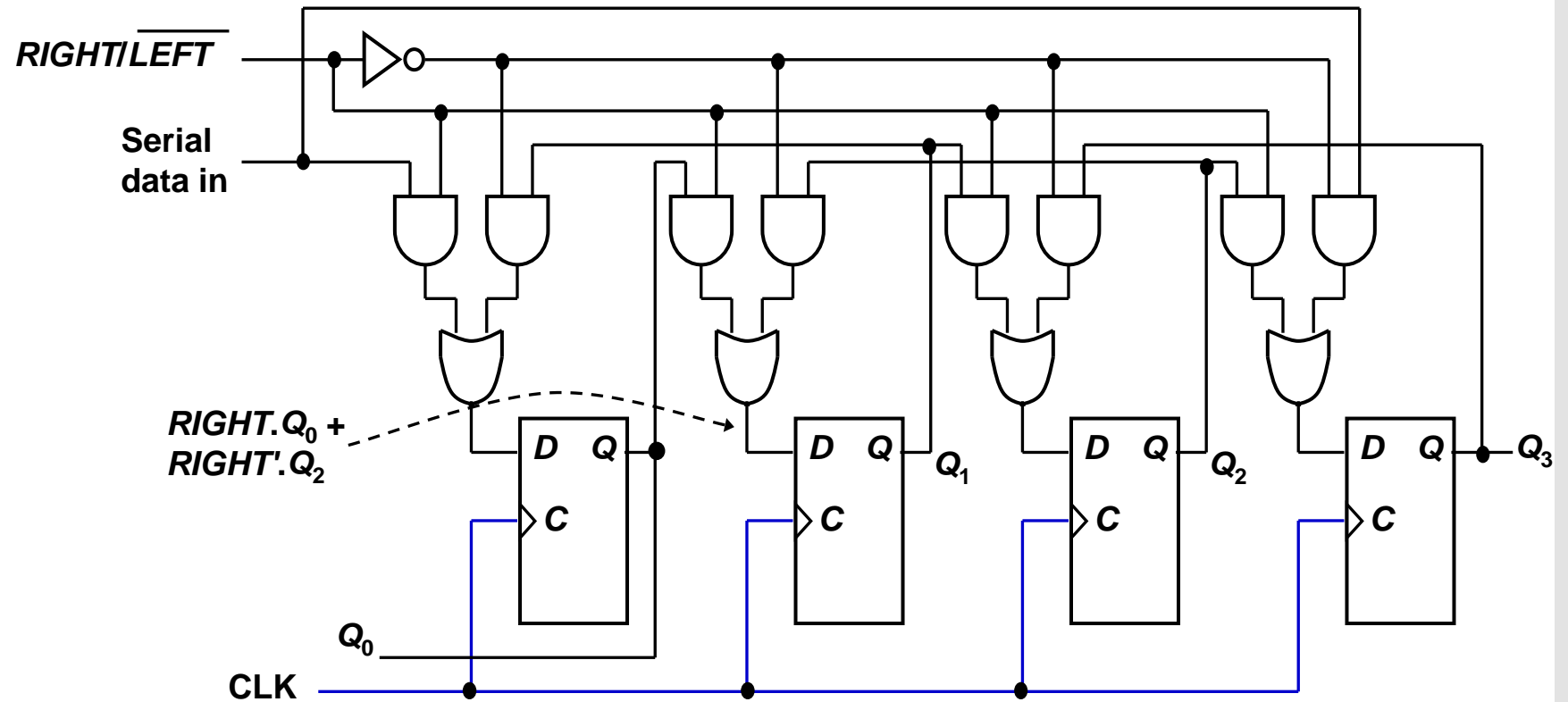
# Bidirectional Shift Registers

- Data can be shifted either left or right, using a control line *RIGHT/LEFT* (or simply *RIGHT*) to indicate the direction.


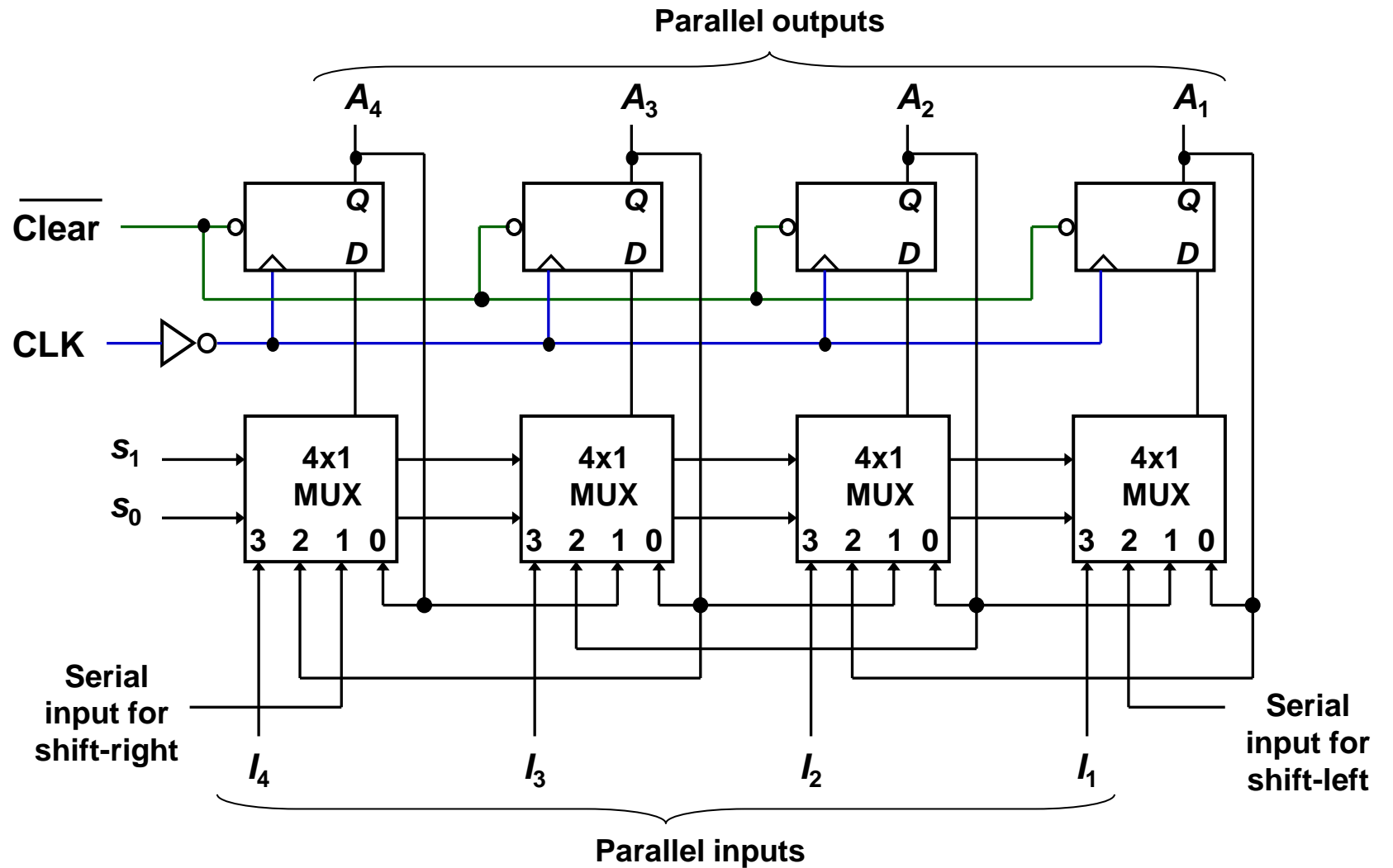
# Bidirectional Shift Registers

- 4-bit bidirectional shift register with parallel load.



# Bidirectional Shift Registers

- 4-bit bidirectional shift register with parallel load.

<i><b>Mode Control</b></i>		<i><b>Register Operation</b></i>
<b><math>s_1</math></b>	<b><math>s_0</math></b>	
<b>0</b>	<b>0</b>	<b>No change</b>
<b>0</b>	<b>1</b>	<b>Shift right</b>
<b>1</b>	<b>0</b>	<b>Shift left</b>
<b>1</b>	<b>1</b>	<b>Parallel load</b>






# Part 2: Counters

# Counters

- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
  - ❖ synchronous (parallel) counters
  - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.
 
# Synchronous (Parallel) Counters

- **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process.
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).




Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

# Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


$$TA_1 = A_0$$
$$TA_0 = 1$$

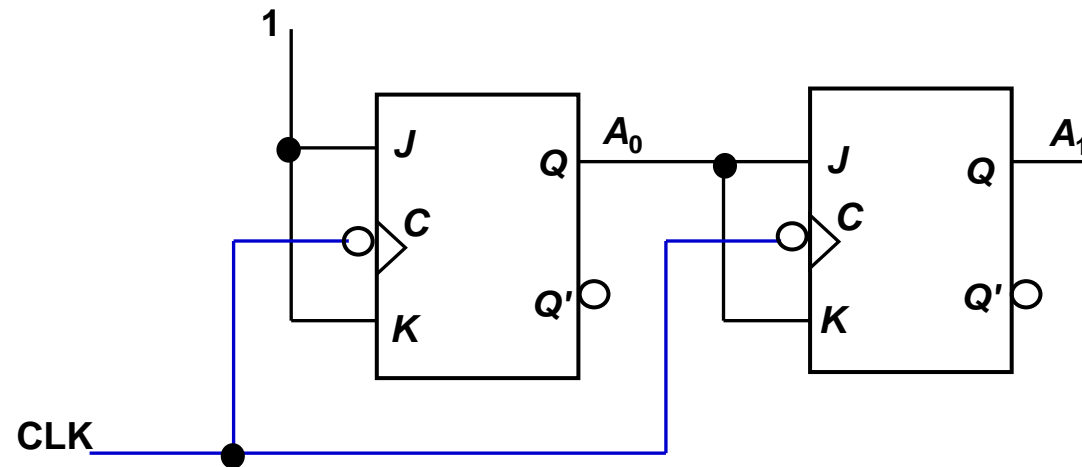

# Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).

Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 


# Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (continued).

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

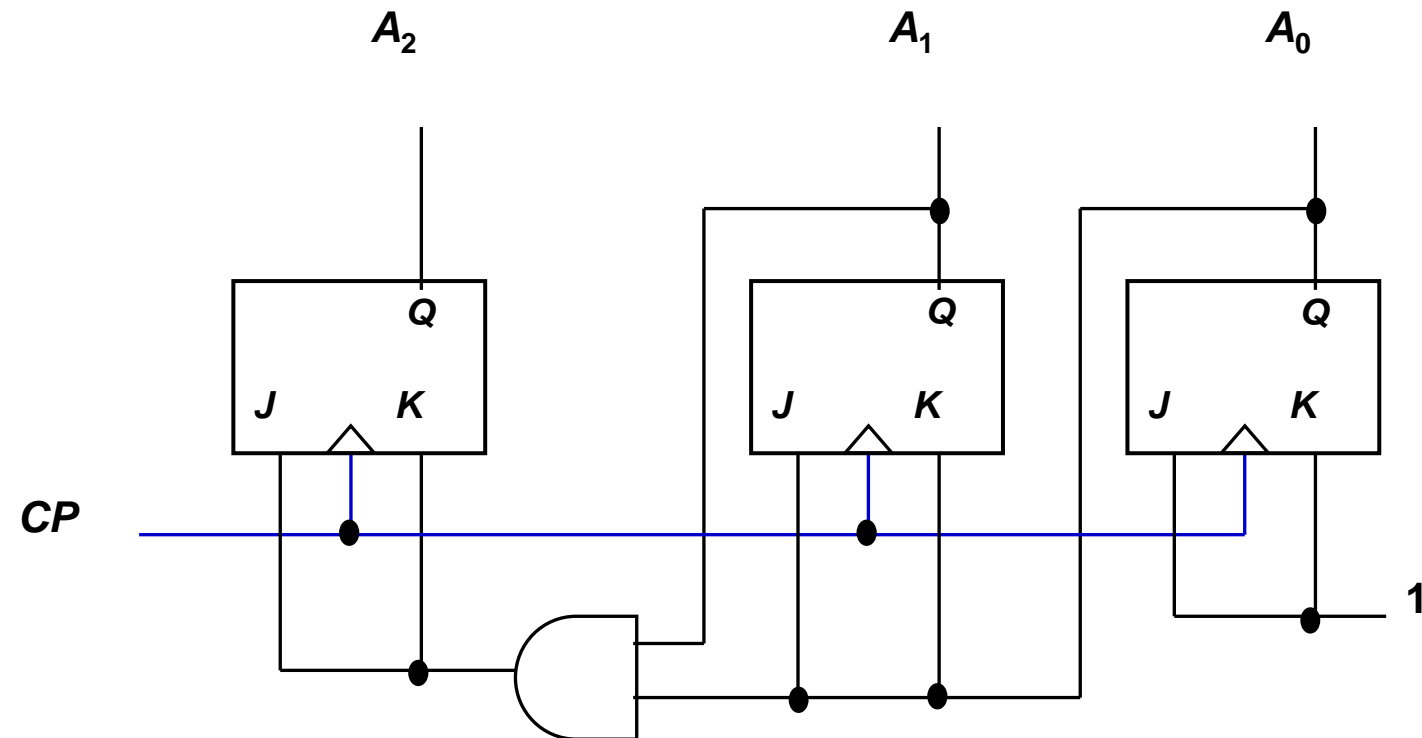

# Synchronous (Parallel) Counters

- Note that in a binary counter, the  $n^{\text{th}}$  bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$

$$\text{or } \underline{1}11\dots11 \rightarrow \underline{0}00\dots00$$

- Hence,  $X_n$  is complemented whenever
$$X_{n-1}X_{n-2} \dots X_1X_0 = 11\dots11.$$
- As a result, if T flip-flops are used, then
$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$

# Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter.

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

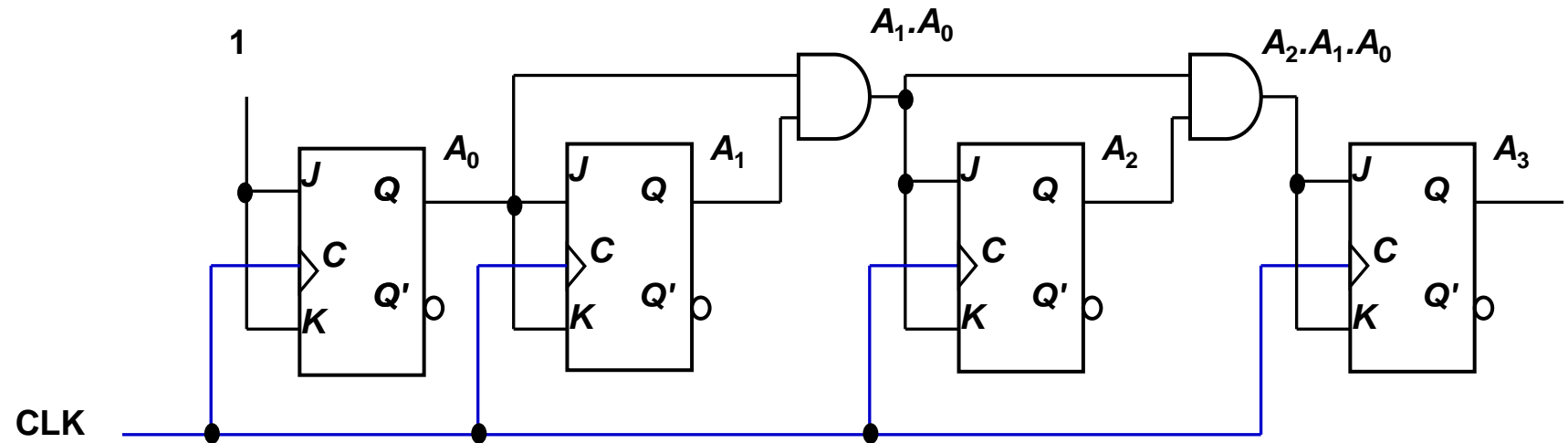



# Synchronous (Parallel) Counters

- Example: Synchronous decade/BCD counter.

Clock pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycle)	0	0	0	0

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$

# Synchronous (Parallel) Counters


- Example: Synchronous decade/BCD counter (continued).

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$
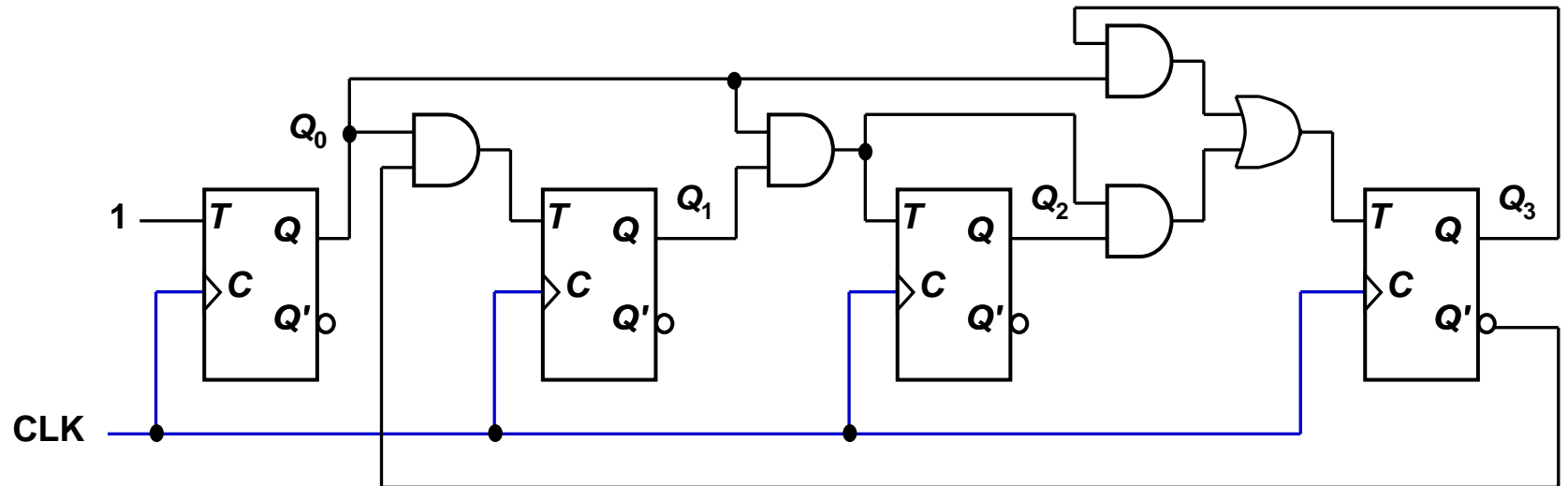
$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$



# Up/Down Synchronous Counters

- **Up/down synchronous counter**: a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line  $Up/\overline{Down}$  (or simply  $Up$ ) specifies the direction of counting.
  - ❖  $Up/\overline{Down} = 1 \rightarrow$  Count upward
  - ❖  $Up/\overline{Down} = 0 \rightarrow$  Count downward

# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	<i>Up</i>	$Q_2$	$Q_1$	$Q_0$	<i>Down</i>
0	↗	0	0	0	↖
1	↘	0	0	1	↗
2	↗	0	1	0	↖
3	↘	0	1	1	↗
4	↗	1	0	0	↖
5	↘	1	0	1	↗
6	↗	1	1	0	↖
7	↘	1	1	1	↗

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (continued).

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$
 
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$





# Asynchronous (Ripple) Counters

- **Asynchronous counters**: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- This counter is also a *frequency divider*.

# Asynchronous (Ripple) Counters

 
 
- Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.



Timing diagram  
00 → 01 → 10 → 11 → 00 ...

- Example: 3-bit ripple binary counter (positive-edge triggered).


# Asynchronous (Ripple) Counters

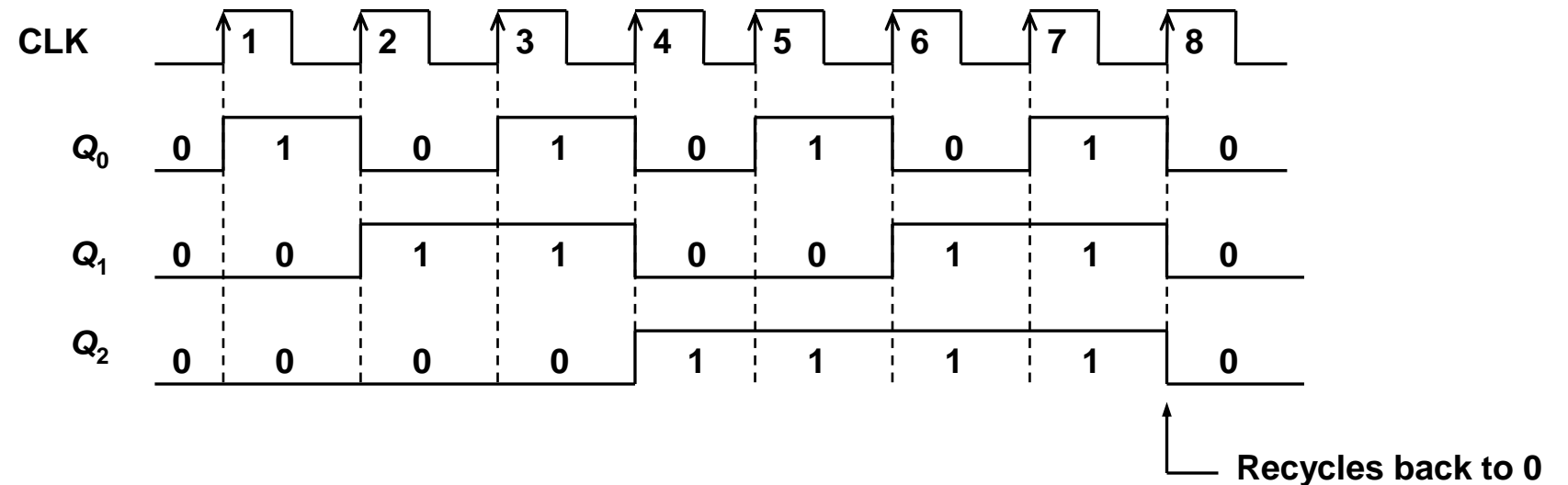 



- Example: 4-bit ripple binary counter (negative-edge triggered).


## Asynchronous (Ripple) Counters

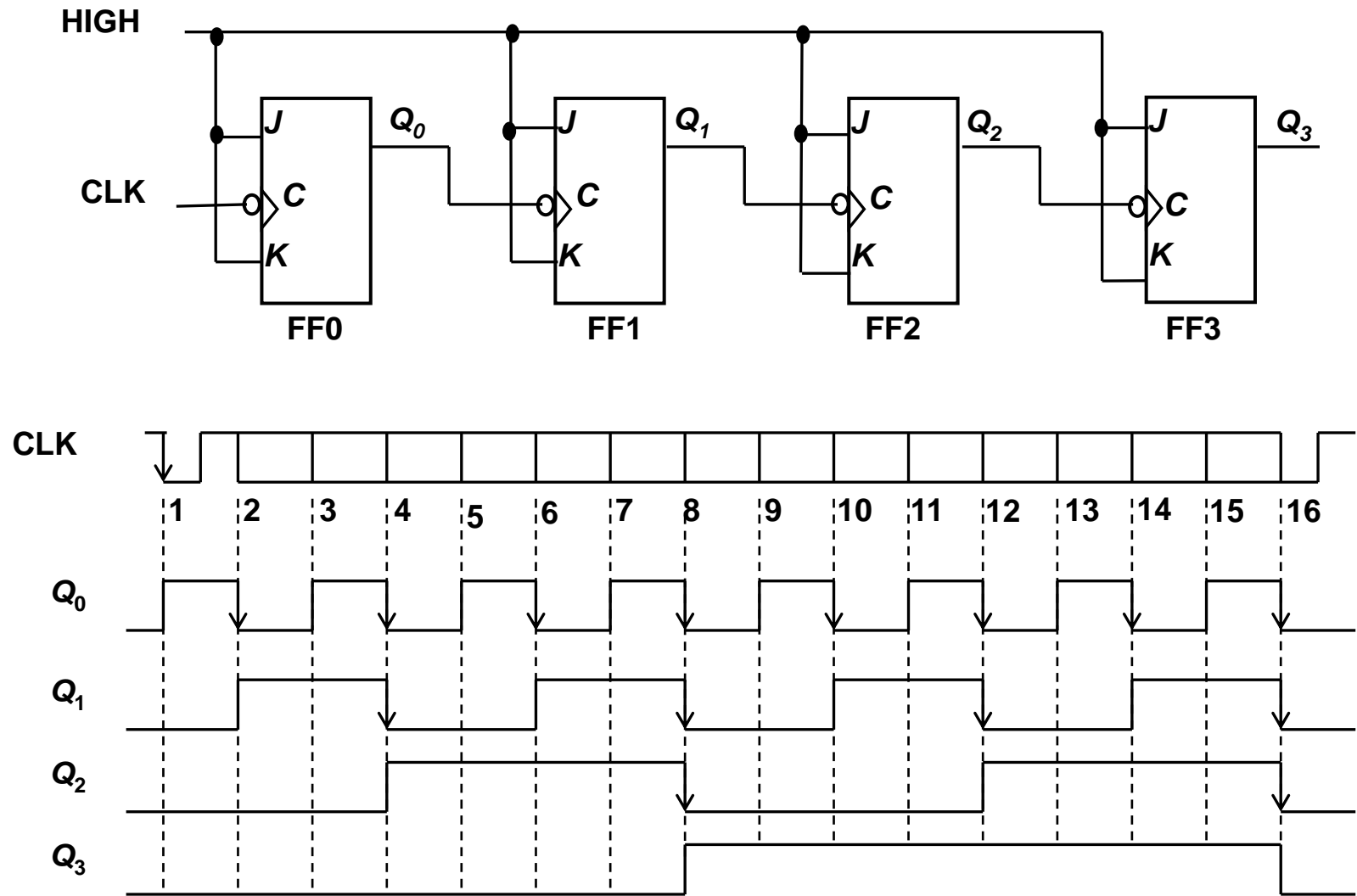

# Asyn. Counters with MOD (modulus) no. $< 2^n$



- States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to *recycle before going through all of the states* in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)

All J, K  
inputs are  
**1 (HIGH)**

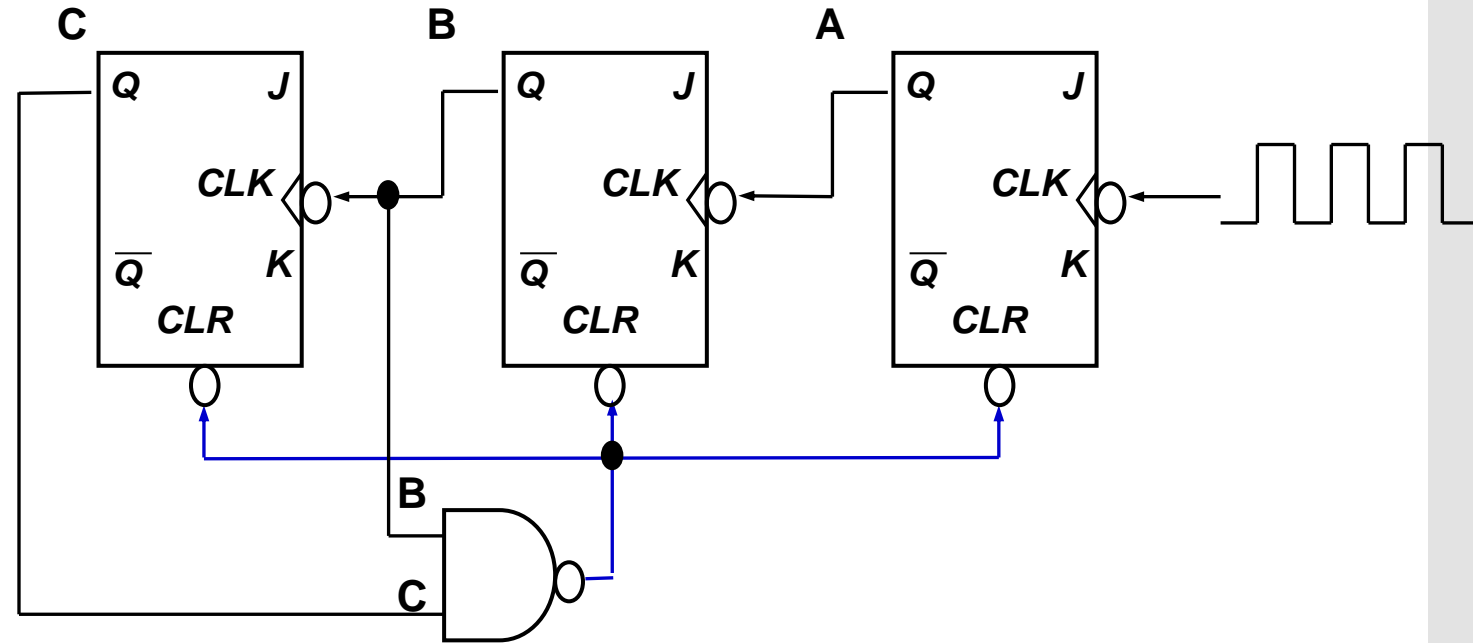

# Asyn. Counters with MOD no. $< 2^n$

## Example (continued):

 
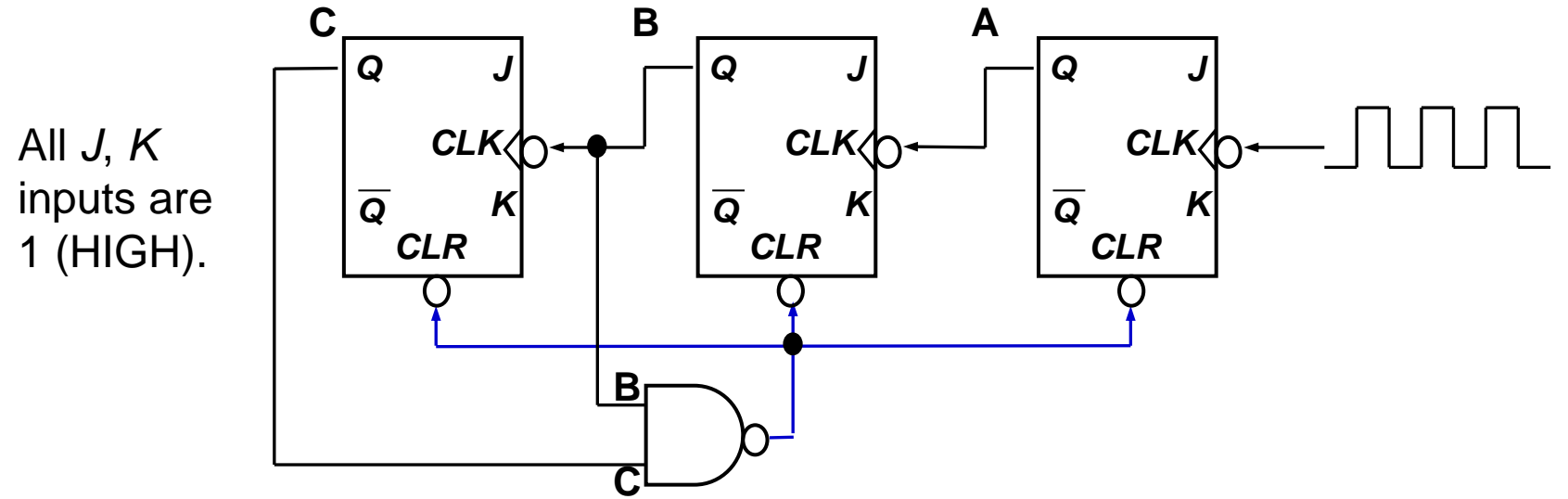


## MOD-6 counter

produced by clearing (a MOD-8 binary counter) when count of six (110) occurs.

- Example (continued): Counting sequence of circuit (in CBA order).

Asyn. Counters  
with MOD no.  
 $< 2^n$

  


## Asyn. Counters with MOD no. $< 2^n$

- *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
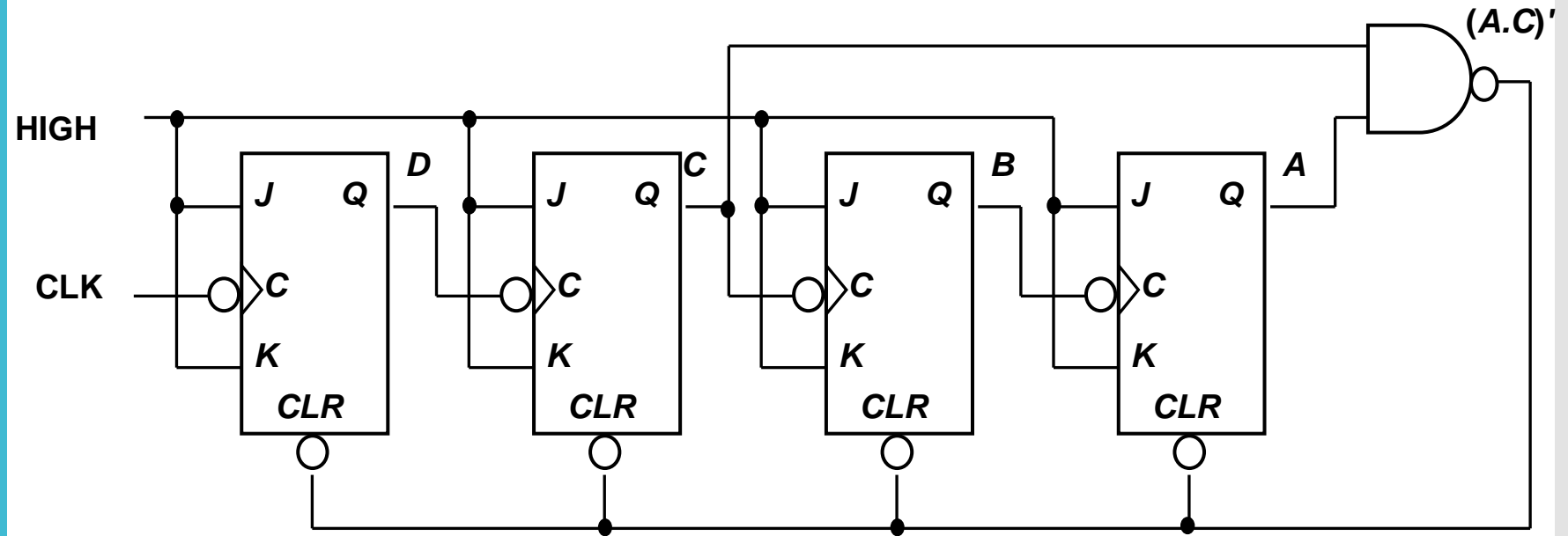
## Asyn. Counters with MOD no. $< 2^n$

- **Decade counters** (or **BCD counters**) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.



# Asyn. Counters with MOD no. $< 2^n$

- Asynchronous decade/BCD counter (continued).

