



North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code : EEE/ETE 241 L

Course Title: Electrical Circuit 2

Course Instructor: NNP

Experiment Number: 03

Experiment Name:

Series RLC Circuit

Date of Experiment: May, 2020

Date of Submission: January, 2021

Section: 02

Group Number: 04

Submitted By			Score
	Student Name	ID	
2.	Kaniz Fatema	1520064045	
3.	Mohammed Mahmudur Rahman	1520386043	

Objective:- To analyze the relationship between the voltage and phase of reactive elements and the source in series RC, RL and RLC circuits.

Background:-

B.1 Voltage and current in an AC circuit:-

An RLC circuit is an electrical circuit consisting of a resistor, an inductor, and a capacitor, connected in series or in parallel. The complex impedance in an AC circuit is represented by Z and expressed in cartesian form by formula $Z = R + jX$ where the real part of impedance is the resistance R and the imaginary part is the reactance X . Here, impedance can also be expressed in magnitude and phase form $|Z| \angle \theta$ where θ is the phase difference between the voltage and the current. The magnitude of the impedance can be expressed as $|Z| = \sqrt{R^2 + X^2}$ and the phase can be expressed as, $\theta = \tan^{-1} \frac{X}{R}$. Ohm's law is true for AC circuits and the current flow caused by a voltage V can be given by:-

$$I = \frac{V}{Z}$$

Here, V_s is the Voltage source and I_s is the source current and V_R , V_L and V_C the voltage across the resistor inductor and capacitor respectively.

circuit:-

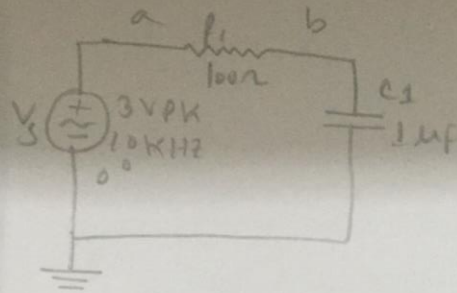


Fig B.1.1: Series RC circuit

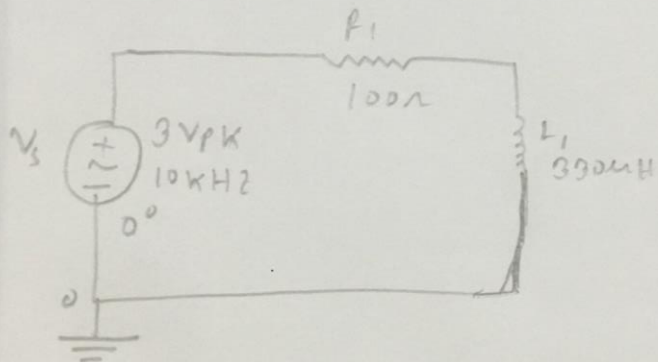


Fig. B.1.2. Series RL circuit

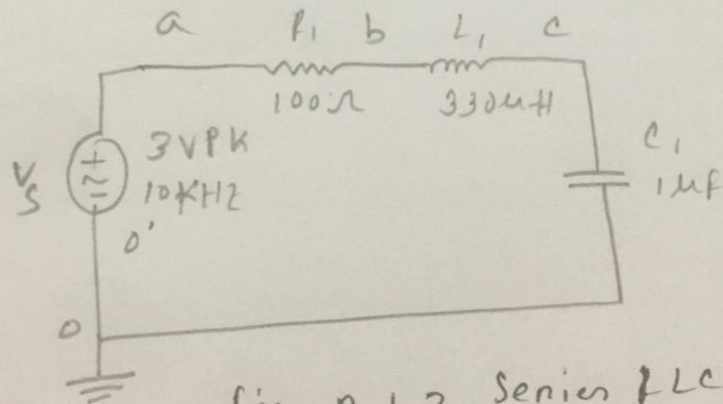


Fig. B.1.3. Series RLC circuit.

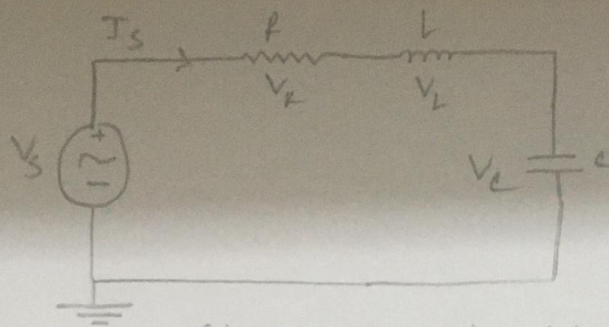


fig B.1.1. Series RLC circuit.

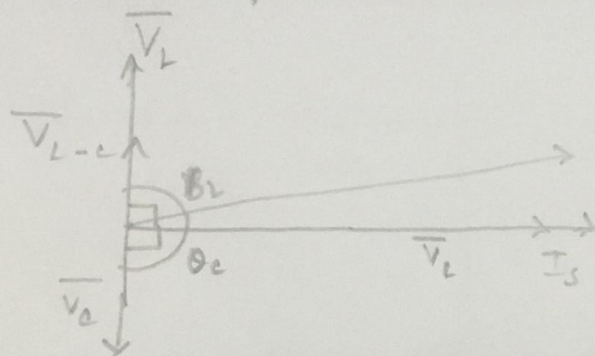


fig B.1.2. Phasor Diagram

A. Apparatus/ Equipment:-

Components	Instruments
<ul style="list-style-type: none"> Resistor: 1x 100 Ω Capacitor: 1x 1 μF Inductor: 1x 330 μH 	<ul style="list-style-type: none"> 1x Bread board 1x function generator 1x digital Storage Oscilloscope (DSO) connecting wires and Probes.

0.09A

Table 1.1.

R (measured) (Ω)	C (measured) (F)	$X_C = \frac{1}{2\pi f C} \Omega$	$Z = \sqrt{R^2 + X_C^2}$ (Ω)	$Z = (\tan^{-1} X_C/R)$ θ
100 Ω	1 μF	15.92	101.26	9.05°

Table 1.2.

V_{Peak} (Theory)	θ (Theory)	$\frac{V_{Peak}}{\Delta T}$ (Practical) (Practical)	V_{Peak} Practical	θ (Practical) $\Delta T \times f \times 360$	% Diff (θ)	% Diff (θ)
V_C 4.7V	86°	24 μs	467.5 mV	86.4°	0.47%	6.5%
V_R 5.5V	18°	5 μs	5.53 V	18°	0%	0.55%

Table 1.3.

R (measured) (Ω)	L (measured) (H)	X_L (Theory) $(2\pi f L) \Omega$	$Z = \sqrt{R^2 + X_L^2}$ (Ω)	$Z = (\tan^{-1} X_L/R)$ θ
100	330 μH	20.73	102.13	11.71°

Table 1.4

V_{Peak} (Theory)	θ (Theory)	V_{Peak} (Practical)	Delay ΔT (Practical)	θ (Practical) $\Delta T \times f \times 360$	% Diff (θ)	% Difference (θ)
V_L 600 mV	357°	608 mV	99.2 μs	357.12°	0.03%	1.16%
V_R 5.4V	5.11°	5.382 V	3.3 μs	11.88°	7.2%	0.33%

3C.65

Table: 1.5.

$R(\Omega)$	$C(F)$	$L(H)$	X_C (Theory) $\frac{1}{2\pi fC} (\Omega)$	X_L (Theory) $\frac{2\pi fL}{} (\Omega)$	$Z = \sqrt{R^2 + X^2}$ (Ω)	$Z = \tan^{-1}(X/R)$ ($^\circ$)
100 Ω	1 μF	330 μH	15.92	20.73	106.565	20.13


Table: 1.6

	V_{Peak} (Theory) (Practical)	ΔT (Theory) (Practical)	$V_{Peak} \theta$ (Practical)
V_L	820 mV	28.3 μS	101.88
V_R	6.06 V	6.06 V 2.8 μS	10.08 μS
V_C	475.028 mV	27 μS	97.2 μS


Question - Answers:

① In step 6 we have used a Math function to obtain the voltage drop in the resistor by substituting V_C from V_S . If we'd switched the position of resistor & capacitor then, we would get the voltage drop across the capacitor again through Math function of Ch1 - Ch2.


① Phasor diagram for RC circuit:

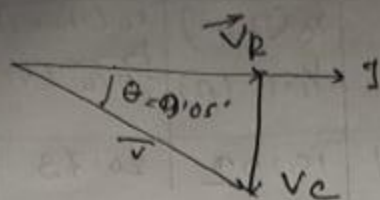


⇒ Phasor diagram for RL circuit:

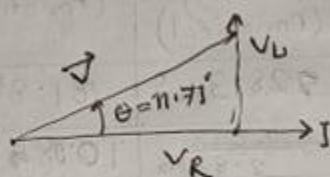

⇒ Phasor diagram for RLC circuit:

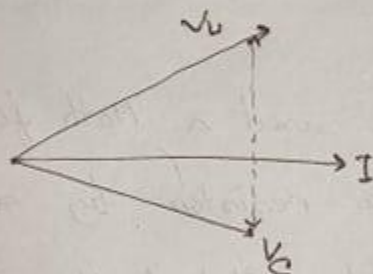


③ For Series RL circuit:

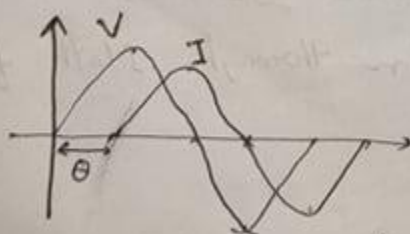


So, if we increase the frequency here as per $(T = \frac{1}{f})$
 T will get smaller which will reduce the θ eventually.

For Series RLC circuit:

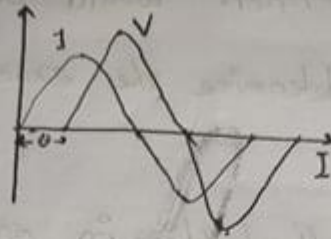

In this case, we can see current leads the voltage by θ . So, if we increase frequency the leading angle would decrease.

For series RLC circuit:

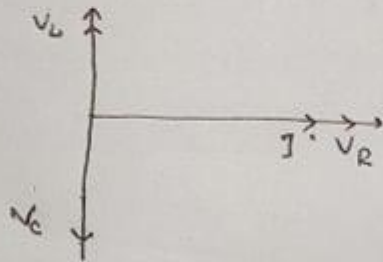

Here, when $X_C > X_L$, voltage will lag the current by θ .

And for $(X_C < X_L)$, voltage will lead the current by θ .

By increasing the frequency we can decrease the angle θ .

①v As we have completed software simulation due to pandemic, we did not noticed ~~was~~ a huge difference between theoretical and practical values. Rather, it was an acceptable difference error. The cause that ~~may be~~ for this error would be:

① We couldn't determine the exact peak values using cursor.

② There was a fluctuation in oscilloscope values.


③ Unavoidable human error.




Discussion:

Due to pandemic, we have completed the lab in online. Through software simulation we've completed the circuit & measured the value. The measurement procedure was a bit complex but we've learned from youtube & a honourable instructor. As, the experiment was done in software thus, value of the component was same as theory & our measured value ~~was~~ had also minimum percentage of error.


RL Circuit

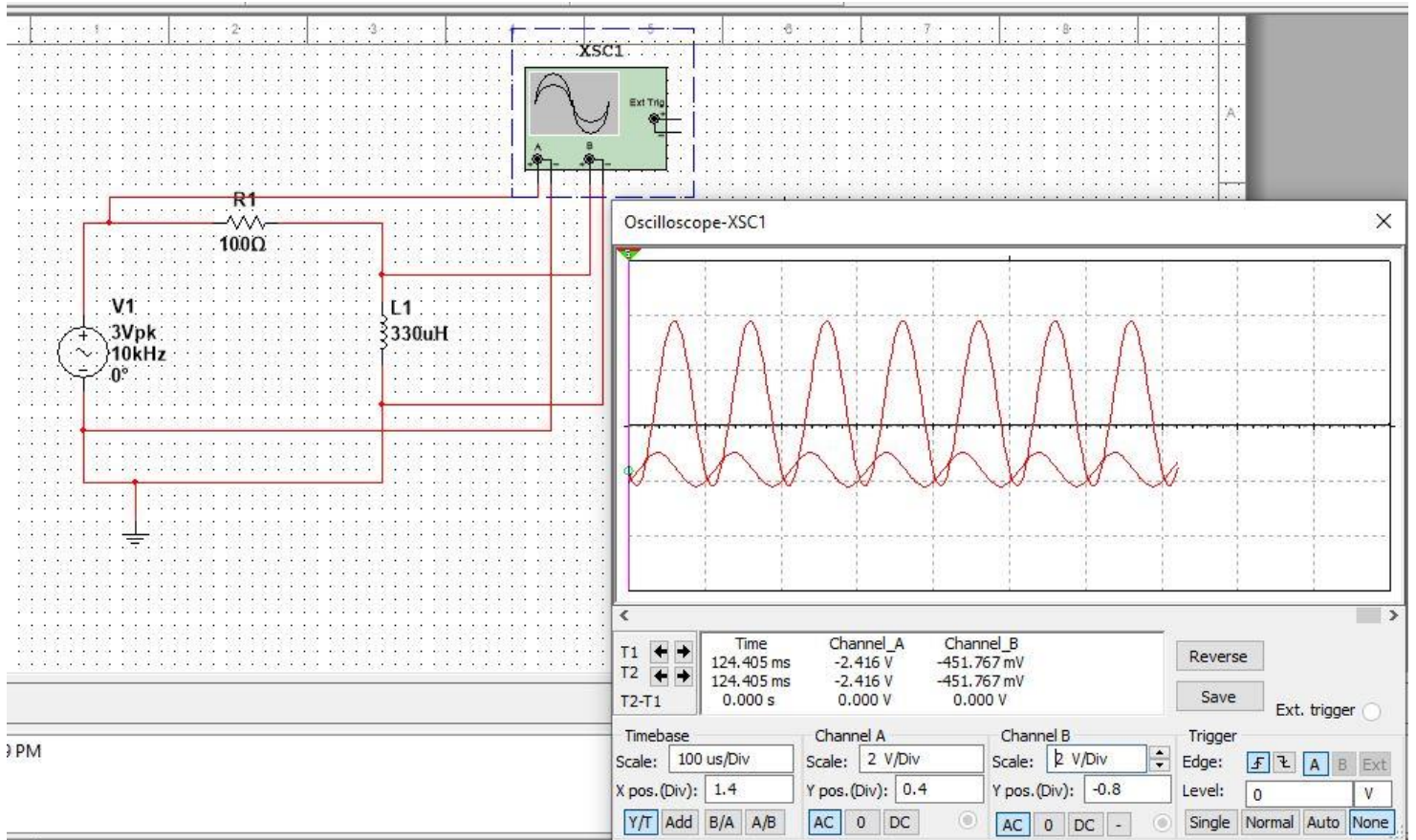


RC Circuit

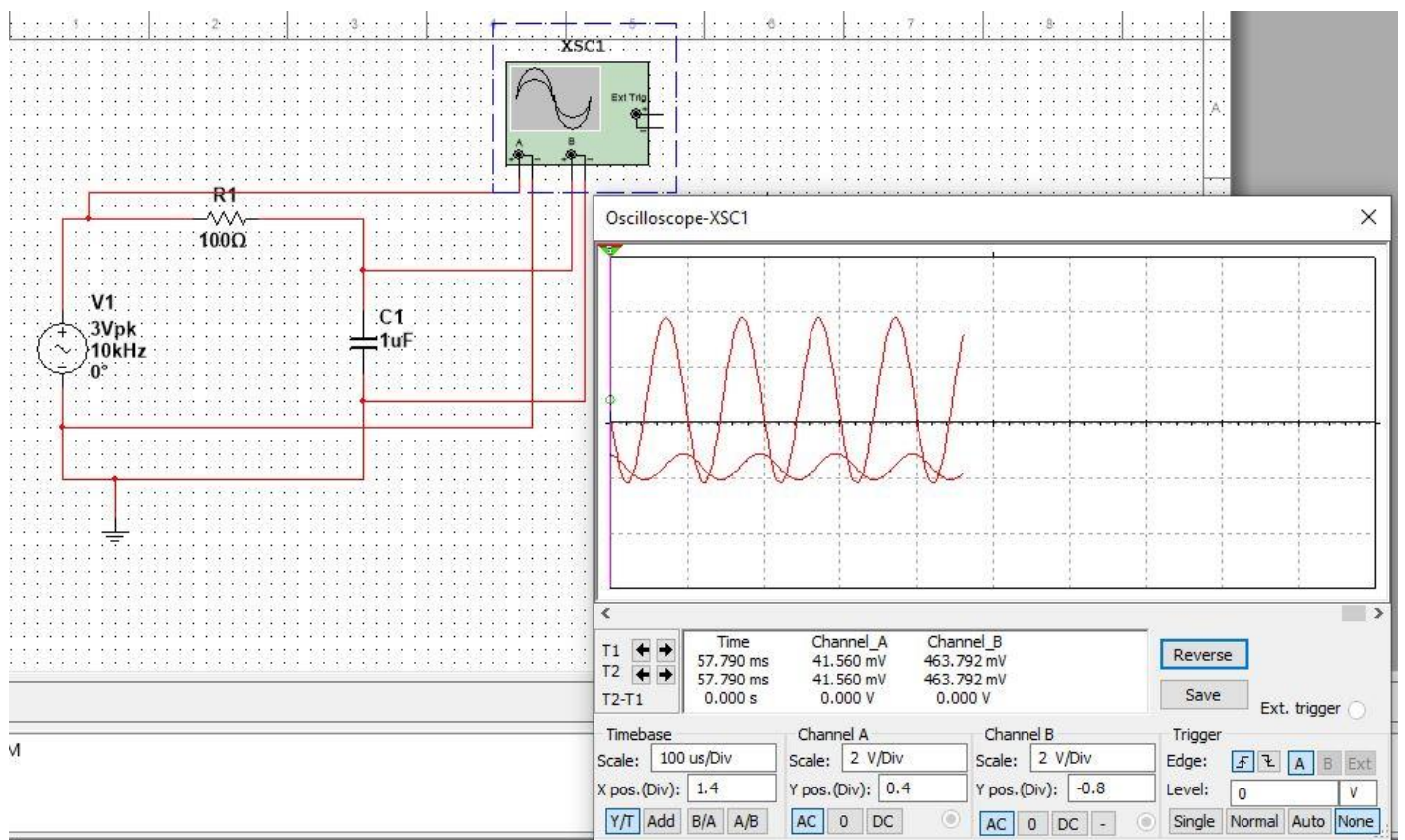

Math Generated Signal in RC Circuit

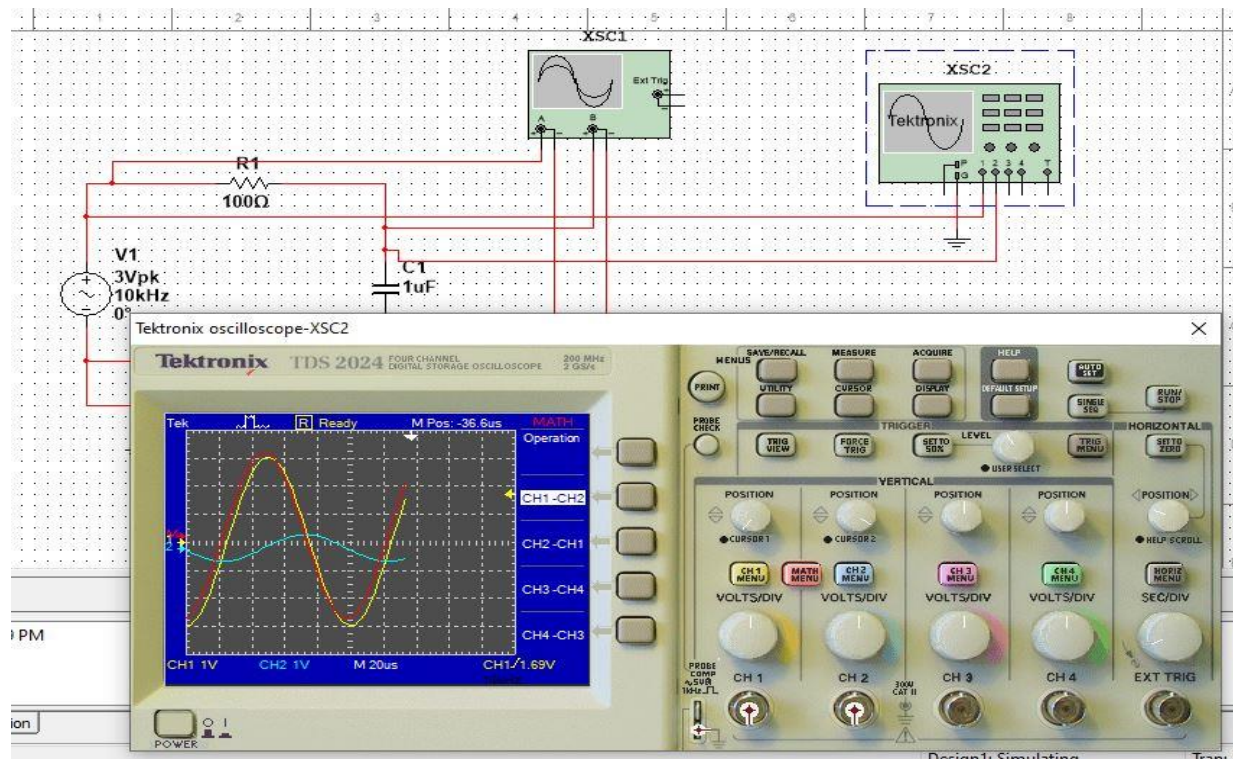

Calculating Del-T for RLC Circuit:

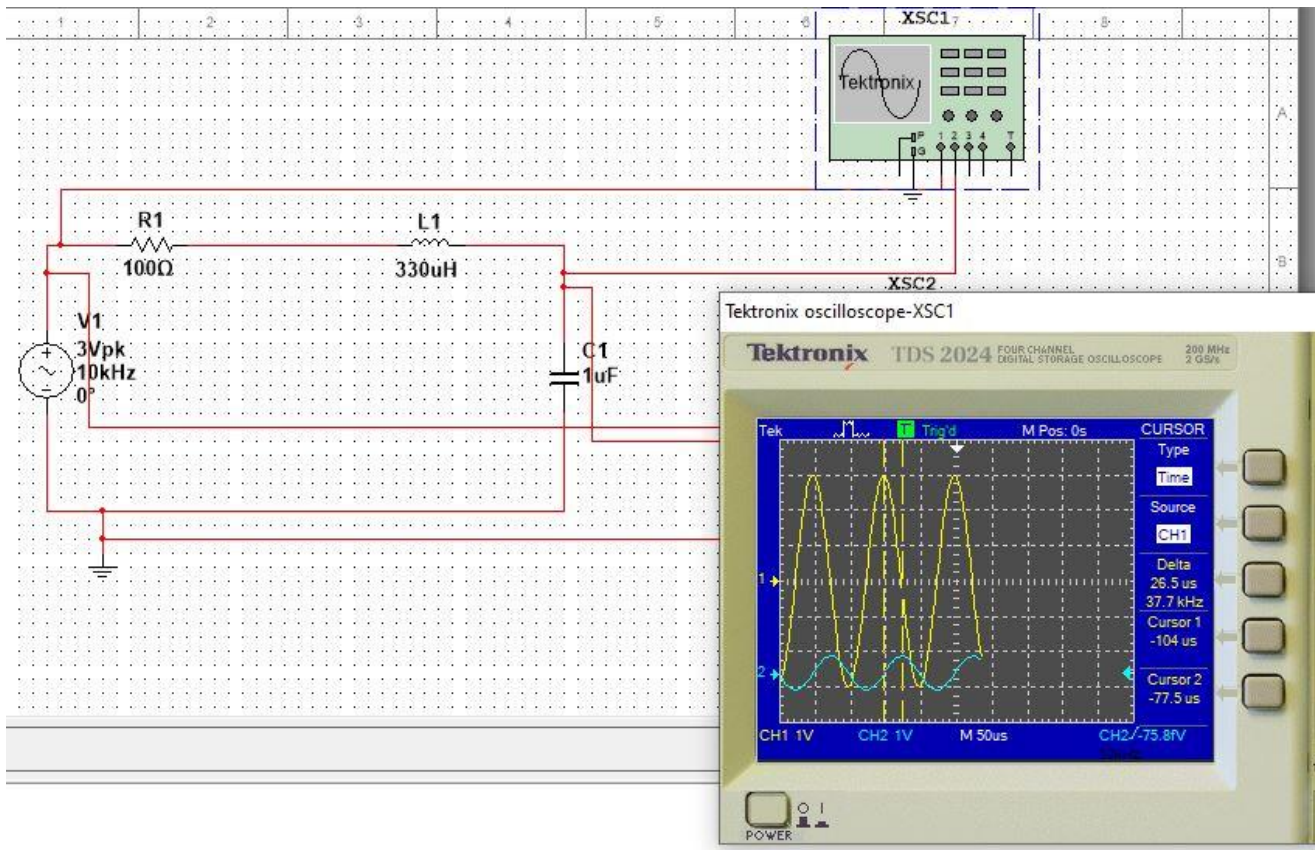

Measuring Del-T for Inductor in RLC Series Circuit

