

Lab 3: Loading Effect of Voltage Divider Circuit

Objective:

- To analyze how the voltage divider circuit behaves when there is no load resistance connected.
- Evaluate the performance of voltage divider circuit due to loading.

List of Equipment:

- Trainer Board
- DMM
- $2 \times 560\Omega$ resistors
- $1 \times (0-10k\Omega)$ variable resistor

Introduction:

Voltage Divider circuit provides a simple way to convert a DC voltage to another lower DC voltage.

Consider the following voltage divider circuit.

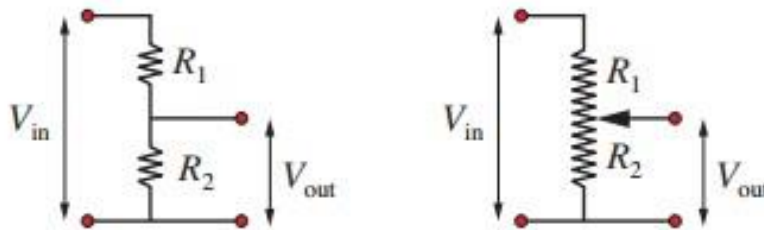


Figure 1: A voltage divider on the left, and potentiometer on the right.

The voltage drop across R_2 is the output voltage, V_{out} . V_{out} is less than V_{in} because the total voltage across R_1 and R_2 must add up to V_{in} . A potentiometer can also be used to change V_{out} by changing the resistance R_2 . As the value of R_2 is changed, it allows the output voltage to be adjusted from 0 to V_{in} .

In Figure 1, there is no output load (R_L) connected in parallel to R_2 hence we call it a No-Load circuit.



According to Voltage Divider Rule: $V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$ (1)

- Say $V_{in}=5v$ and you need $V_{out}= 3v$. How would you set the values of R_1 and R_2 ?

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Choice of resistor value should follow the ratio: $\frac{R_1}{R_2} = \frac{2}{3}$

One possible combination: $R_1 = 2k$ and $R_2 = 3k$

- Now say we connect an output load, R_3 in parallel to R_2 :

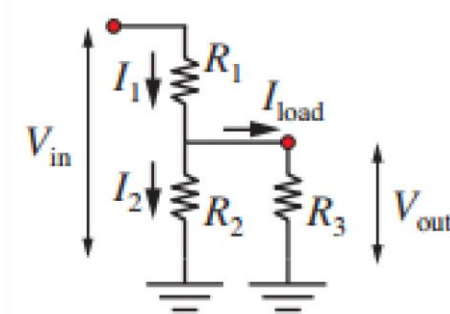


Figure 2: With Output Load Connected.

⇒ Do you think keeping the values of resistors same would still give $V_{out}=3v$ from $V_{in}=5v$?

Let's check:

Since you have a Load resistance parallel to R_2 , your Voltage divider formula to find V_{out} is:

$$V_{out} = V_{in} \frac{(R_2 // R_3)}{R_1 + (R_2 // R_3)} \quad (2)$$

Let $R_3 = 10k$.



$$R_2 // R_3 = 2.31k$$

$$\rightarrow V_{out} = 2.68 \text{ v}$$


So, our Designed value was 3v, but connecting a load resistor reduced it to 2.68v.

Design Criteria:

To minimize the loading effect, choose the load resistor to be much larger than its parallel resistor.

If R_3 is much greater than R_2 then $R_2 // R_3$ (parallel combination of R_2 and R_3) is approximately equal to R_2

Circuit Diagram:

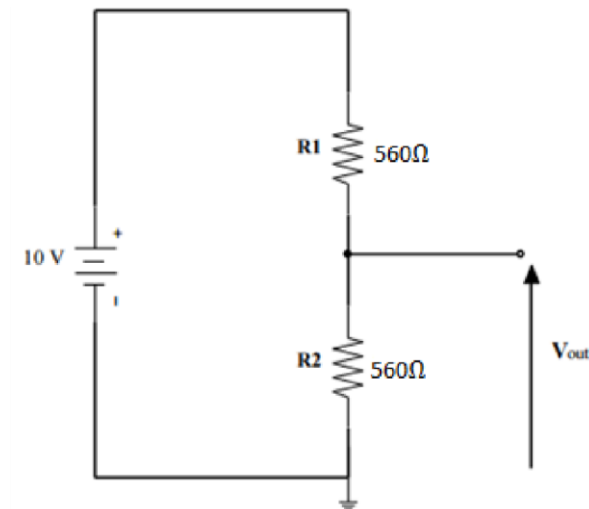

Procedure:

1. Construct the voltage divider circuit as shown in figure above.
2. Measure the unloaded output voltage V_{out} . Record the value in Table 1.
3. Connect 10 kΩ variable load resistor, parallel with R_2 to the circuit. (Connect 1 middle pin of variable resistor and one of the other pins).

North South University

Department of Electrical & Computer Engineering



EEE141/ETE141

4. Change the value of the variable resistor according to Table 1, and record V_{out} for each resistor value in Table 1.



Data Collection for Lab 3:

Group No. _____

Instructor's Signature _____

Table 1:

RL	Vout (Measured)	Vout (Calculated)	%Error
No resistor			
1k			
4k			
7k			
10k			

Report Question:

1. Explain the loading effect of your circuit (i.e. explain how does your V_{out} vary with increasing Load resistor)
2. Showing all steps in details, theoretically calculate the value of V_{out} for each load resistor.
3. Comparing the theoretical data to the experimental data, comment how far the loading effect of your circuit supports.