



Department of Electrical & Computer Engineering

North South University

Final Project

Displaying the word 'FEnCE05'

Submitted By : Group 2

Members:

Name: Rejuan Ahmed Khan

Student ID: 1231121043

Name: Md. Sharuar Zahan Rejon

Student ID: 1431048043

Name: Mohammed Mahmudur Rahman

Student ID: 1520386043

Name: Tamima Nur Khan

Student ID: 1530009045

Course: Digital Electronics

Course Code: EEE211

Section: 01

Faculty Advisor:

Fahimul Haque

Combinational Part

Rejuan Ahmed Khan

ID: 1231121043

EEE/ETE 211

Project

Given word is 'FENCE05'. I have to show each letter and digit in a 7 segment display.

 


Figure: 7 segment display

 


Figure: Pin connection of 7 segment display

Rejuan Ahmed Khan

ID: 1231121043

Date:

Time:

Sat Sun Mon Tue Wed Thu Fri

Truth Table:

Input			DISPLAY	Output						
A	B	C		a	b	c	d	e	f	g
0	0	0	F	1	0	0	0	1	1	1
0	0	1	E	1	0	0	1	1	1	1
0	1	0	n	0	0	1	0	1	0	1
0	1	1	C	1	0	0	1	1	1	0
1	0	0	E	1	0	0	1	1	1	1
1	0	1	D	1	1	1	1	1	1	0
1	1	0	5	1	0	1	1	0	1	1
1	1	1		0	0	0	0	0	0	0

Now, I have to determine the K-map for 7-segment pins (a, b, c, d, e, f, g) to find their respective equations.

K-map

A \ BC	00	01	11	10
0	1	1	1	0
1	1	1	0	1

$$\therefore a = \bar{B} + \bar{A}C + AC$$

Rejuan Ahmed Khan

Sat Sun Mon Tue Wed Thu Fri

ID: 1231121043

Date:

Time:

A \ BC	00	01	11	10
0	0	0	0	0
1	0	1	0	0

$$\therefore b = A\bar{B}C$$

A \ BC	00	01	11	10
0	0	0	0	1
1	0	1	0	1

$$\therefore c = B\bar{C} + A\bar{B}C$$

A \ BC	00	01	11	10
0	0	1	1	0
1	1	1	0	1

$$\therefore d = \bar{A}C + A\bar{B} + A\bar{C} \quad \therefore e = \bar{A} + \bar{B}$$

A \ BC	00	01	11	10
0	1	1	1	1
1	1	1	0	0

A \ BC	00	01	11	10
0	1	1	1	0
1	1	1	0	1

$$\therefore f = \bar{B} + \bar{A}C + A\bar{C}$$

A \ BC	00	01	11	10
0	1	1	0	1
1	1	0	0	1

$$\therefore g = \bar{A}\bar{B} + \bar{C}$$

Rejuan Ahmed Khan

Sat Sun Mon Tue Wed Thu Fri


ID: 1231121043

Date:

Time:


Now, from the determined pin equations I have to draw the circuit diagram using basic gates.

Circuit diagram

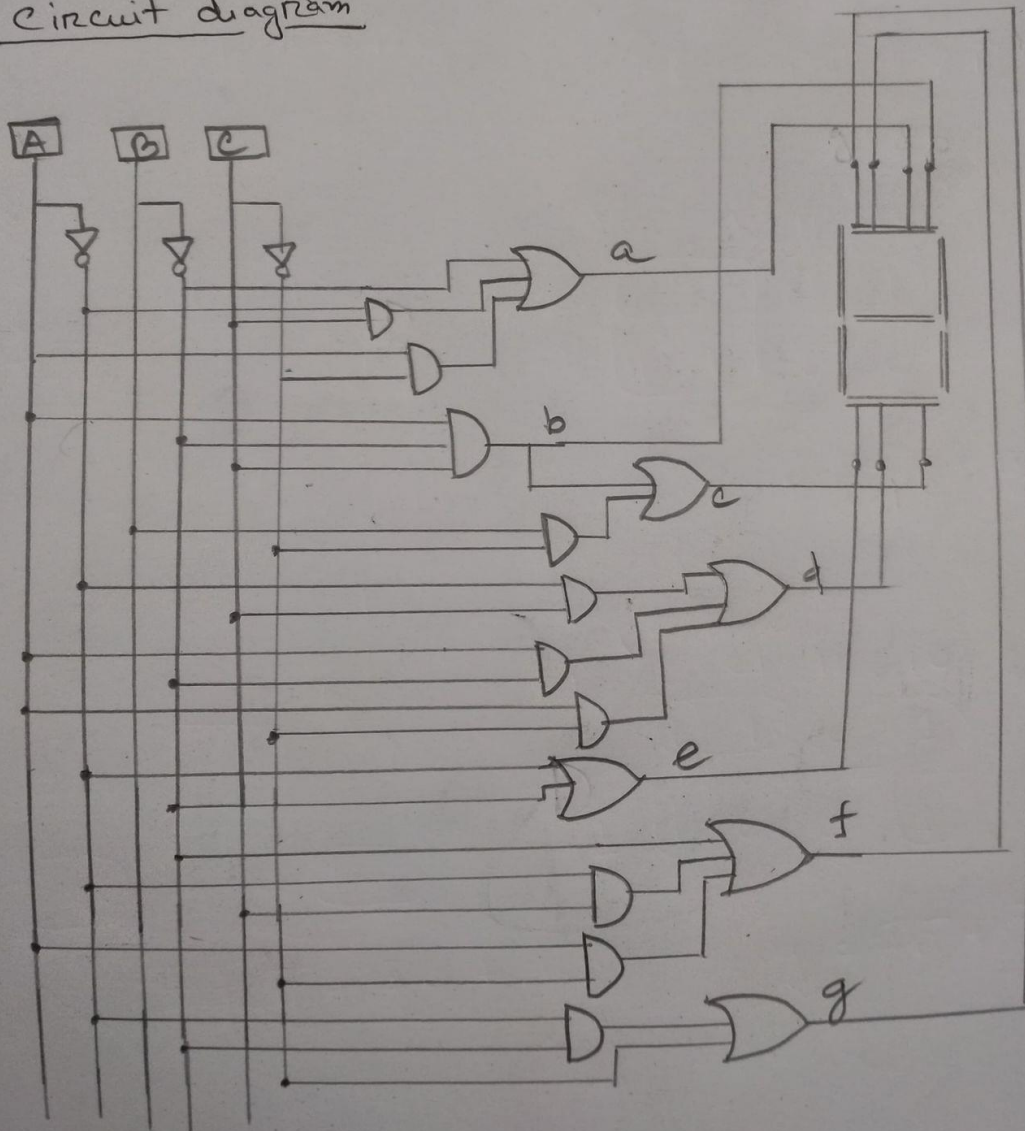

Rejuan Ahmed Khan
ID:1231121043

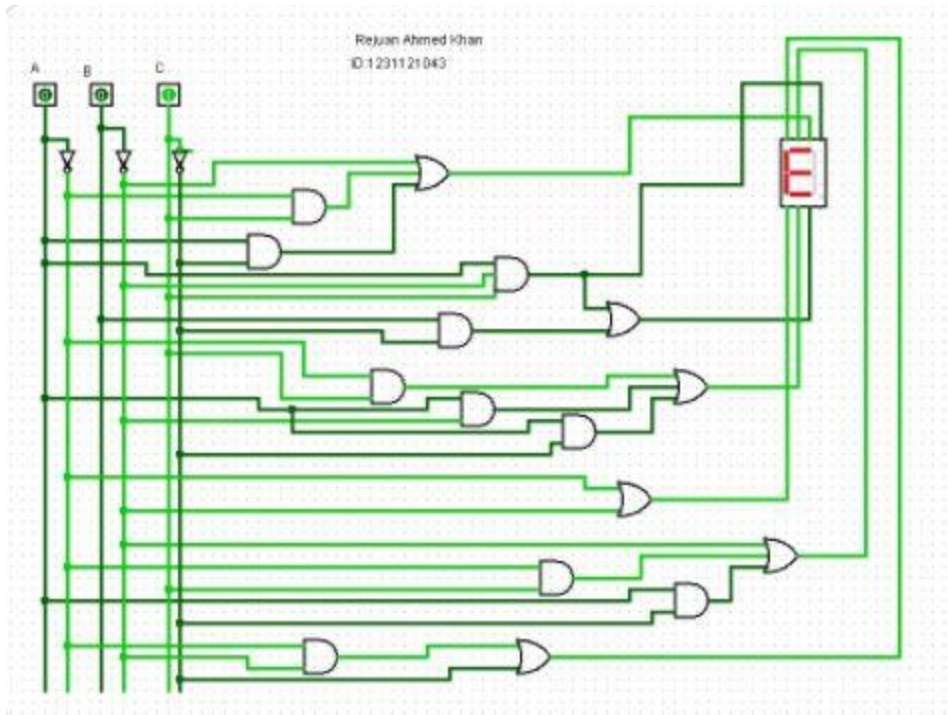The diagram shows a logic circuit for a 3-bit majority gate. Inputs A, B, and C are connected to inverters and a network of AND and OR gates. The output E is the majority function, which is true when at least two inputs are true. The circuit uses 3-input AND gates and 3-input OR gates to implement the majority function.




Name: Md. Sharwar Zahan Pejon

Id: 1431048043

Group code: FENCE05

 Universal gate: Universal gate is the type of gate by which we can implement any boolean function. We can replace any gate by universal gate but the operation will remain same. Using universal gate in a circuit is very much cost effective because when we use universal ~~circuit~~ gate then we need just 1 type IC. There are two types of Universal gate. Nand and Nor.



In this project, we will use seven segment display to show output. In a seven segment display there are 7 different LEDs such as a, b, c, d, e, f, g.

Inputs			Outputs							Output
x	y	z	a	b	c	d	e	f	g	Display
0	0	0	0	0	0	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	1
0	1	0	0	0	1	0	1	0	1	1
0	1	1	1	0	0	1	1	1	0	1
1	0	0	1	0	0	1	1	1	1	1
1	0	1	1	1	1	1	1	1	0	1
1	1	0	1	0	1	1	0	1	1	1
1	1	1	0	0	0	0	0	0	0	0

Truth table

x	yz			
	00	01	11	10
0	1	1	1	0
1	1	1	0	1

$$\therefore a = \bar{y} + \bar{x}z + x\bar{z}$$

Name: Md. Shauvan Zahar Rejon

b

x \ yz	00	01	11	10
0	0	0	0	0
1	0	1	0	0

$$b = x\bar{y}z$$

c

x \ yz	00	01	11	10
0	0	0	0	1
1	0	1	0	1

$$c = y\bar{z} + x\bar{y}z$$

d

x \ yz	00	01	11	10
0	0	1	1	0
1	1	1	0	1

$$d = x'z + xy' + xz$$

e

x \ yz	00	01	11	10
0	1	1	1	1
1	1	1	0	0

$$e = x' + y'$$

f

x \ yz	00	01	11	10
0	1	1	1	0
1	1	1	0	1

$$f = \bar{y} + xz + x\bar{z}$$


g

x \ yz	00	01	11	10
0	1	1	0	1
1	1	0	0	1

$$g = x'y' + z'$$



Nand

 

Nor



Truth Table For Nand

Input		Output
A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


Truth table for NOR

Inputs		Output
A	B	$X = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

  By using a bubble in the Output side we express universal gate.



Circuit: main	
Circuit Name	main
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12

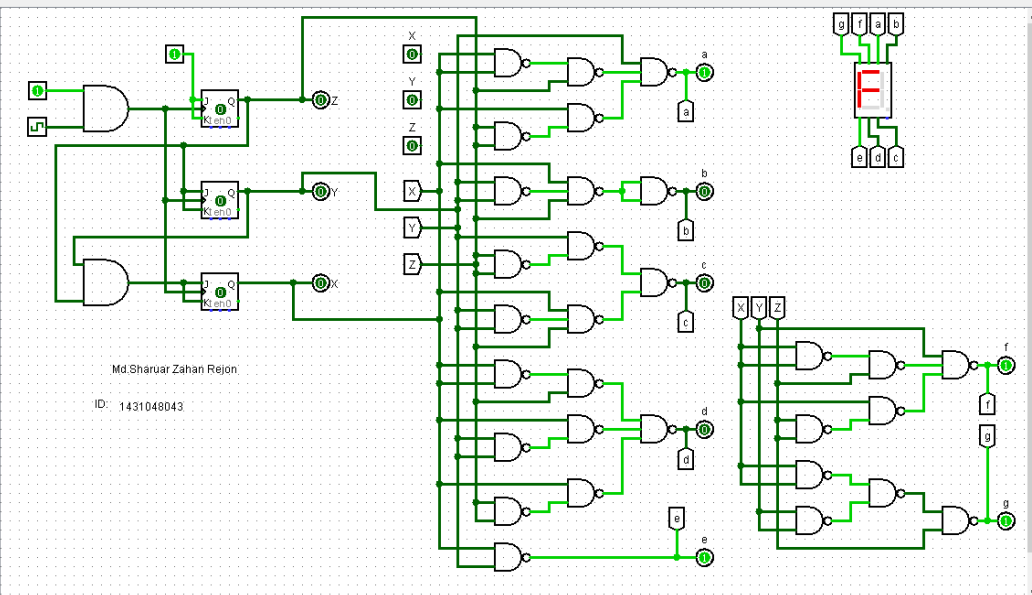

The Name is Mohammed Mahmudur Rahman.

Student ID: 1520386043.

The combinational logic circuit is a type of digital logic circuit implemented using Boolean function, where the output of logic circuit is a pure function of the present inputs only.

A binary decoder is a combination of logical circuit that converts binary information from the n coded inputs to a maximum 2^n unique outputs.

Decoder circuit changes a code into a set of signals. It has maximum of 2^n output lines. One of these outputs will be active high based on the combination of present inputs.

 


Figure: 3x8 decoder.

Name: Mohammed Mahmudur Rahman.

Student ID: 1520386043.

Here, given word to show in a 7-segment display is 'FENCE05'. I have completed the decoder part.

 


Figure: 7-segment display.

 


Figure: Pin-out of a 7-segment display in Logisim.

There ~~was~~ was 6 digit in ~~my~~ our assigned word. To ^{show} display all of them in a single display I had to ~~do~~ build a truth table. If we can ~~in~~ use 7 different display for decoder no truth table would be required. So, here is my truth table:

Decimal value	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	1	1	1
1	0	0	1	0	0	0	1	1	1	1
2	0	1	0	0	0	1	0	1	0	1
3	0	1	1	0	0	0	1	1	1	0
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	1	1	1	1	1	1	0
6	1	1	0	0	0	1	1	0	1	1
7	1	1	1	0	0	0	0	0	0	0

Name: Mohammed Mahmudun Rahman
ID: 1620386043

Expression for 7 pin of the display:

$$a = y' + x'z + xz'$$

$$b = xy'z$$

$$c = yz' + xy'z$$

$$d = x'z + xy' + zz'$$

$$e = x' + y'$$

$$f = \cancel{xz} y' + x'z + xz'$$

$$g = x'y' + z'$$

$$a (0, 1, 3, 4, 5, 6)$$

$$b (5)$$

$$c (2, 5, 6)$$


$$d (1, 3, 4, 5, 6)$$

$$e (0, 1, 2, 3, 4, 5)$$

$$f (0, 1, 3, 4, 5, 6)$$

$$g (0, 1, 2, 4, 6)$$

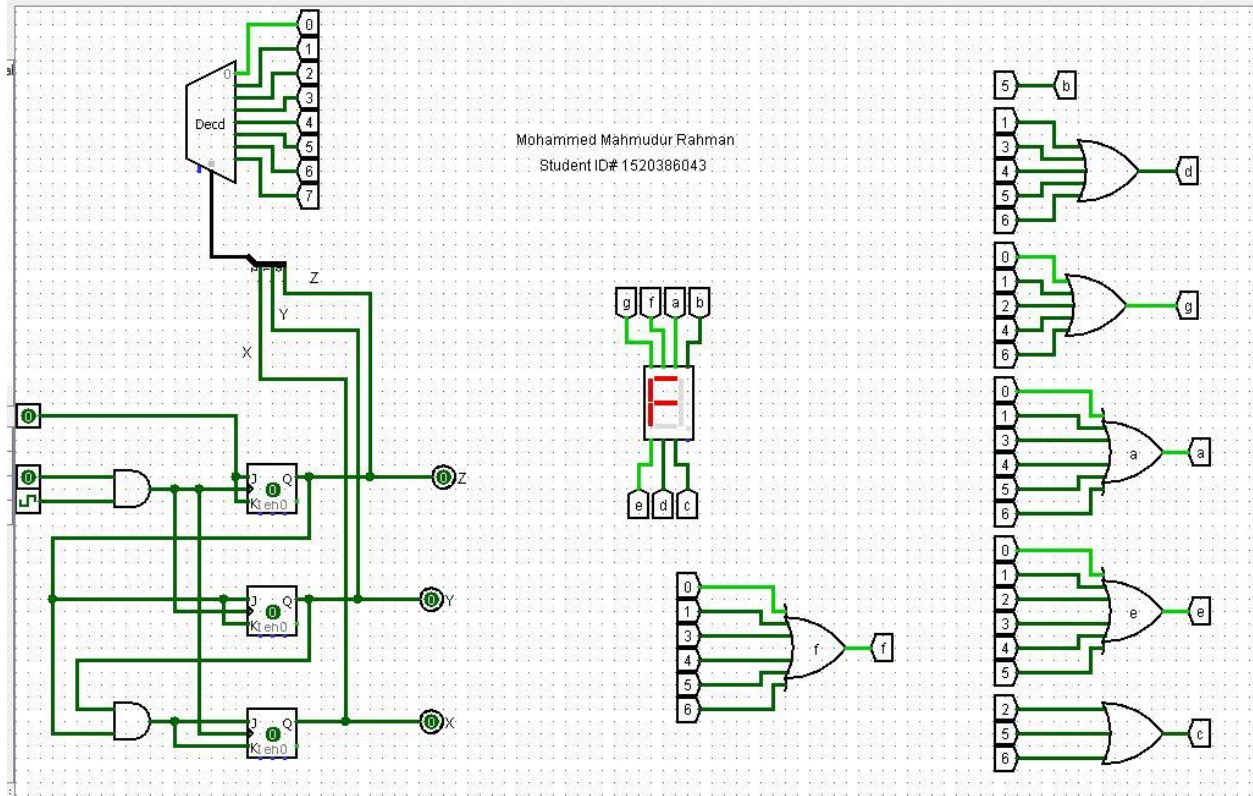To show the mentioned word I have used a 3x8 decoder as there are 7 word alphabet in this that word. As we don't required the 8th output we left it as an open connection; so that no unwanted word alphabet comes at the last.



Report :-

TAMIMA NUR KHAN
1530009045

My part in this project was to design a seven segment display using a multiplexer. In designing this I have taken a 4×1 multiplexer. Truth table for this MUX was derived along with the seven digits from a to g. Later expressions were developed for the MUX inputs I_0, I_1, I_2, I_3 and ~~the~~ in terms of I, O , and C or \bar{C} . and then designed in the logicmin.

A	B	C	a	b	c	d	e	f	g	
0	0	0	1	0	0	0	1	1	1	F
0	0	1	1	0	0	1	1	1	1	E
0	1	0	0	0	1	0	1	0	1	n
0	1	1	1	0	0	1	1	1	0	C
1	0	0	1	0	0	1	1	1	1	E
1	0	1	1	1	1	1	1	1	0	0
1	1	0	1	0	1	1	0	1	1	5
1	1	1	0	0	0	0	0	0	0	x

$$\left. \begin{array}{l} I_0 = 1 \\ I_1 = \bar{c} \\ I_2 = 1 \\ I_3 = \bar{c} \end{array} \right\} \text{for } a$$

$$\left. \begin{array}{l} I_0 = 0 \\ I_1 = \bar{c} \\ I_2 = c \\ I_3 = \bar{c} \end{array} \right\} \text{for } c$$

$$\left. \begin{array}{l} I_0 = 0 \\ I_1 = 0 \\ I_2 = c \\ I_3 = 0 \end{array} \right\} \text{for } b$$

$$\left. \begin{array}{l} I_0 = c \\ I_1 = c \\ I_2 = 1 \\ I_3 = \bar{c} \end{array} \right\} \text{for } d$$


$$\left. \begin{array}{l} I_0 = 1 \\ I_1 = 1 \\ I_2 = 1 \\ I_3 = 0 \end{array} \right\} \text{for } e$$

$$\left. \begin{array}{l} I_0 = 1 \\ I_1 = c \\ I_2 = 1 \\ I_3 = \bar{c} \end{array} \right\} \text{for } f$$

$$\left. \begin{array}{l} I_0 = 1 \\ I_1 = \bar{c} \\ I_2 = \bar{c} \\ I_3 = \bar{c} \end{array} \right\} \text{for } g$$

TAMIMA NUR KHAN

1530009045.

 

Sequential Part

Sequential circuit design report:

A sequential circuit executes one or more inputs & produce one or more outputs. Sequential circuit requires a state table for its execution. These states are related to some definite rules which it depends & generates by its previous states.

To design a sequential circuit we followed some basic steps. Firstly we have created a state transition diagram. Then determined the state transition table. Thirdly, we choose flip-flops & then created excitation table with state transition table. We have chosen ~~JK~~^T flip-flop for this design. By shorting J & K of JK ff we have made T flip-flop.

Flip-flop is a basic building block of a sequential circuit. It is a storage device that can store one bit of data. It has two inputs & two outputs. As in sequential circuit for state transition we need to consider previous state thus for storing that info we must need to

use a flip-flop for sequential circuit.

The J-K flip-flop that we used is the most versatile of the basic flip-flops. It has input following character of the clocked D flip-flop but has two input labeled as J & K.

The J-K flip-flop is basically an SR flip-flop with feedback which enables only one of its two input terminals, either set or reset to be activate at one time. Therefore it eliminates the invalid condition which is found in SR flip-flop circuit.

The T-flip-flop is an edge triggered device. The low to high or high to low transitions on a clock signal of narrow triggers that is provided as input will cause the change in output state of flip-flop.

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0

Fig: Excitation Table of T-flipflop.

T	Q ⁺
0	Q(t)
1	Q'(t)

Fig: Characteristics table of T flip-flop.

Sequential circuit: We have made a counter of 3 bits by using T flip flop. T flip-flop is a toggle flip flop. It changes its output when it gets clock pulse.

Present state			Next state			Flip Flop inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

Here we have used JK flip flop to make T flip flop. Here J and K are shorted to make T flip flop.

P-

