

EEE363


Electrical Machines

Lecture # 14

Dr Atiqur Rahman

3-Phase Transformer

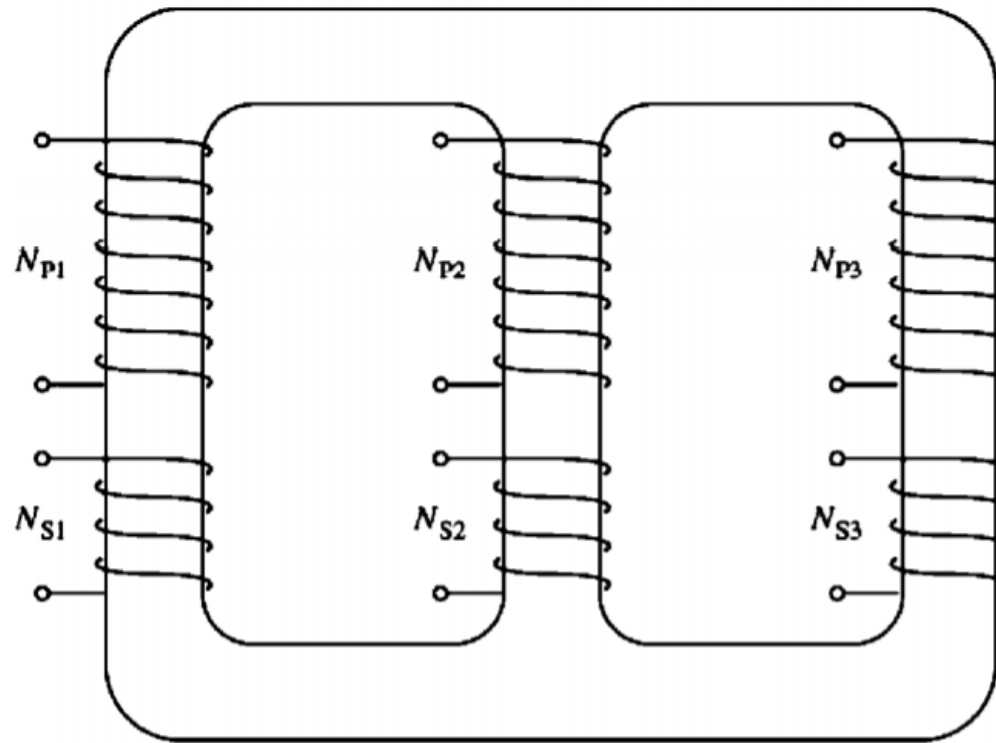
Almost all the major power generation and distribution systems in the world today are three-phase ac systems.



3-phase Transformer connections

1. Wye–wye (Y–Y)
2. Wye–delta (Y– Δ)
3. Delta–wye (Δ –Y)
4. Delta–delta (Δ – Δ)



Y – Y Connection

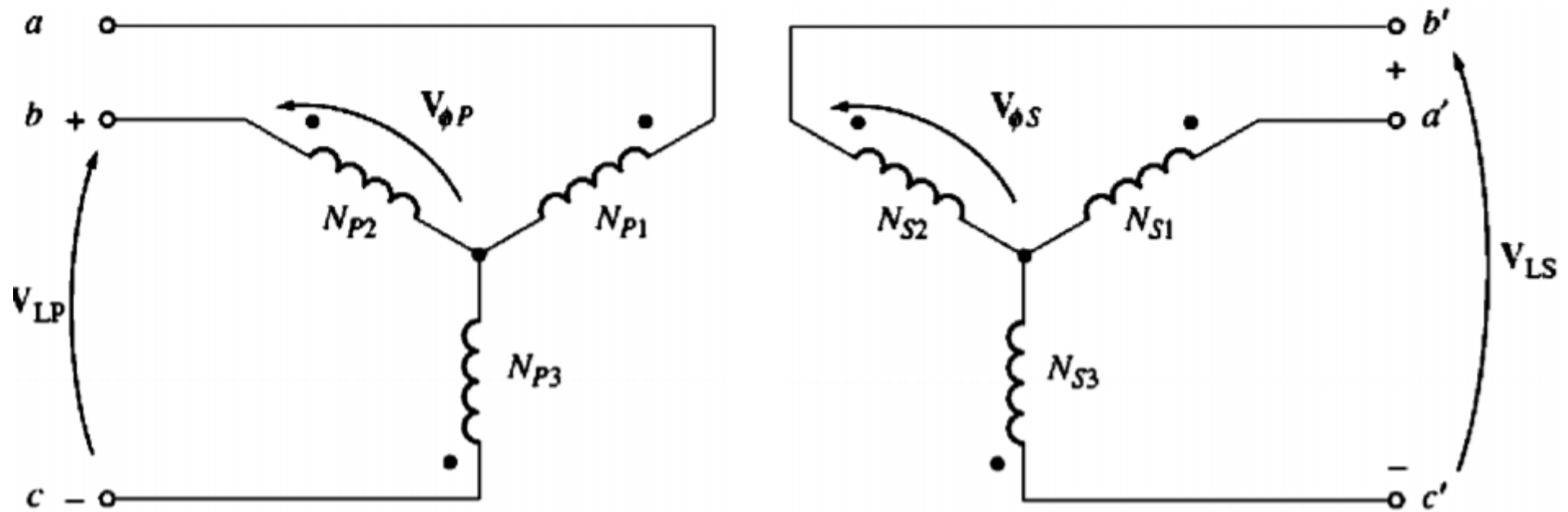

$$\frac{V_{\phi P}}{V_{\phi S}} = a$$

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{\sqrt{3}V_{\phi S}} = a \quad \text{Y-Y}$$

Y – Δ Connection

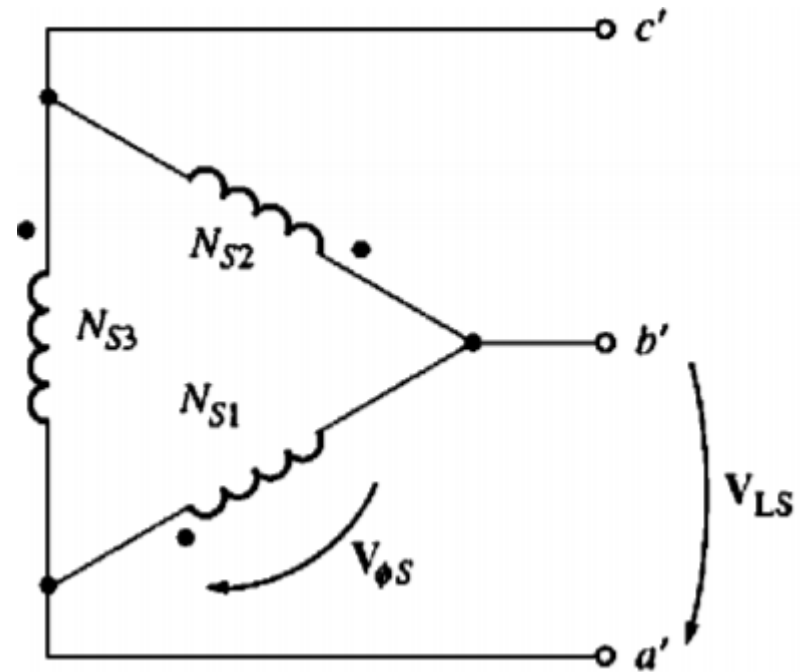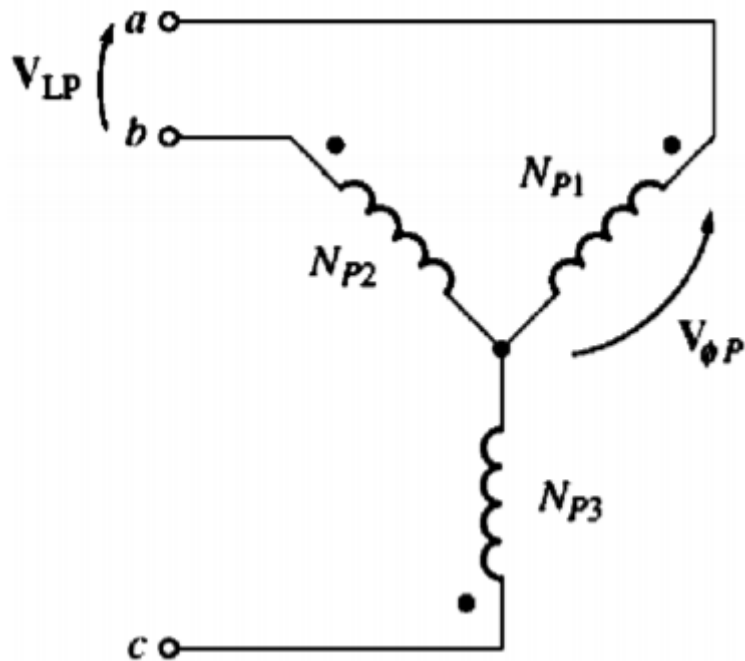



$$\frac{V_{\phi P}}{V_{\phi S}} = a$$

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{V_{\phi S}}$$



$$\boxed{\frac{V_{LP}}{V_{LS}} = \sqrt{3}a \quad Y-\Delta}$$

Other connections
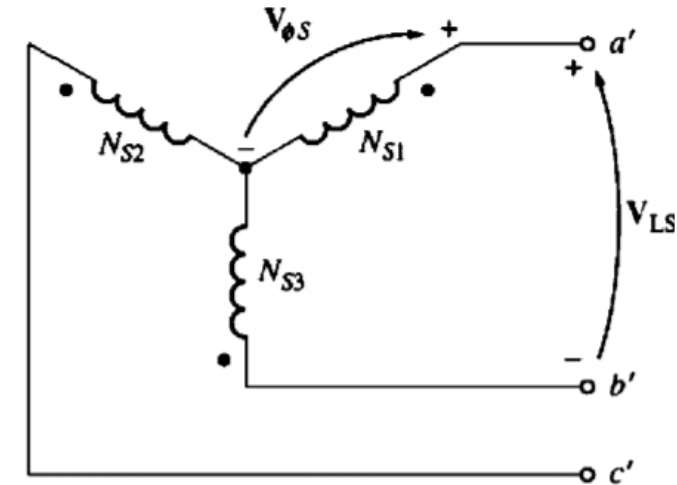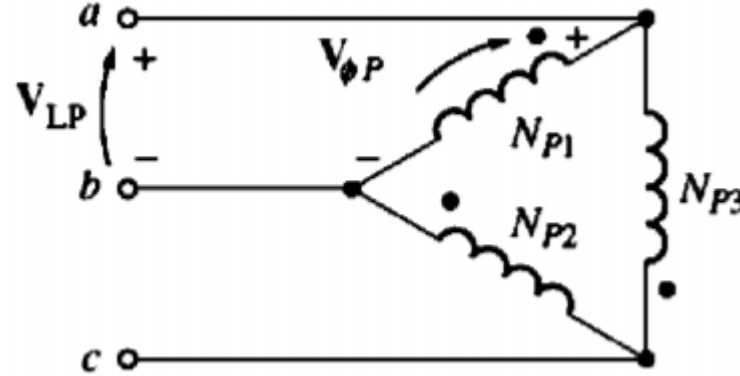
$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}}{a} \quad \Delta-Y$$


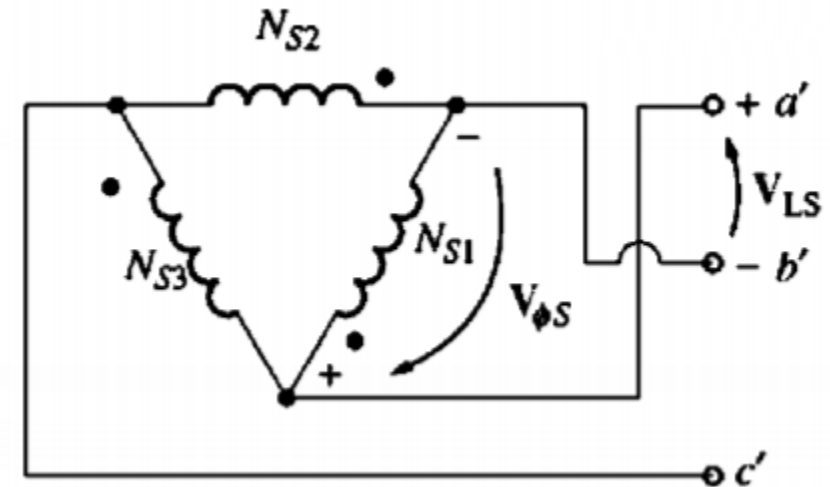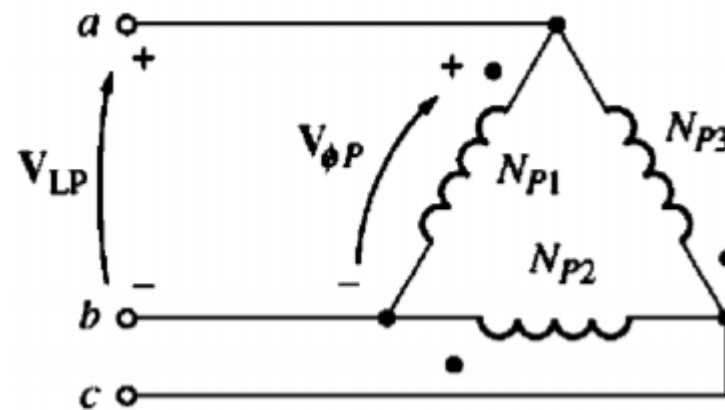
$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a \quad \Delta-\Delta$$



PU system for 3-phase transformer

$$S_{l\phi,base} = \frac{S_{base}}{3}$$

$$Z_{base} = \frac{(V_{\phi,base})^2}{S_{l\phi,base}}$$

$$I_{\phi,base} = \frac{S_{l\phi,base}}{V_{\phi,base}}$$

$$Z_{base} = \frac{3(V_{\phi,base})^2}{S_{base}}$$

$$I_{\phi,base} = \frac{S_{base}}{3 V_{\phi,base}}$$

Problem # 1

Example 2–9. A 50-kVA 13,800/208-V Δ -Y distribution transformer has a resistance of 1 percent and a reactance of 7 percent per unit.

- (a) What is the transformer's phase impedance referred to the high-voltage side?
- (b) Calculate this transformer's voltage regulation at full load and 0.8 PF lagging, using the calculated high-side impedance.
- (c) Calculate this transformer's voltage regulation under the same conditions, using the per-unit system.

$$Z_{\text{base}} = \frac{3(V_{\phi, \text{base}})^2}{S_{\text{base}}} = \frac{3(13,800 \text{ V})^2}{50,000 \text{ VA}} = 11,426 \Omega$$

PU impedance of the transformer is $Z_{\text{eq}} = 0.01 + j0.07 \text{ pu}$

So the high side impedance in ohms is $Z_{\text{eq}} = Z_{\text{eq,pu}} Z_{\text{base}} = (0.01 + j0.07 \text{ pu})(11,426 \Omega)$
 $= 114.2 + j800 \Omega$

Regulation calculation

$$VR = \frac{V_{\phi P} - aV_{\phi S}}{aV_{\phi S}} \times 100\% \quad I_{\phi} = \frac{S}{3V_{\phi}} \quad I_{\phi} = \frac{50,000 \text{ VA}}{3(13,800 \text{ V})} = 1.208 \text{ A}$$

$$\begin{aligned} V_{\phi P} &= aV_{\phi S} + R_{eq}I_{\phi} + jX_{eq}I_{\phi} \\ &= 13,800 \angle 0^{\circ} \text{ V} + (114.2 \, \Omega)(1.208 \angle -36.87^{\circ} \text{ A}) + (j800 \, \Omega)(1.208 \angle -36.87^{\circ} \text{ A}) \\ &= 13,800 + 138 \angle -36.87^{\circ} + 966.4 \angle 53.13^{\circ} \\ &= 13,800 + 110.4 - j82.8 + 579.8 + j773.1 \\ &= 14,490 + j690.3 = 14,506 \angle 2.73^{\circ} \text{ V} \end{aligned}$$

$$VR = \frac{V_{\phi P} - aV_{\phi S}}{aV_{\phi S}} \times 100\% = \frac{14,506 - 13,800}{13,800} \times 100\% = 5.1\%$$



Regulation calculation using PU system

$$\begin{aligned}V_P &= 1 \angle 0^\circ + (0.01)(1 \angle -36.87^\circ) + (j0.07)(1 \angle -36.87^\circ) \\&= 1 + 0.008 - j0.006 + 0.042 + j0.056 \\&= 1.05 + j0.05 = 1.051 \angle 2.73^\circ\end{aligned}$$

$$VR = \frac{1.051 - 1.0}{1.0} \times 100\% = 5.1\%$$

Autotransformer

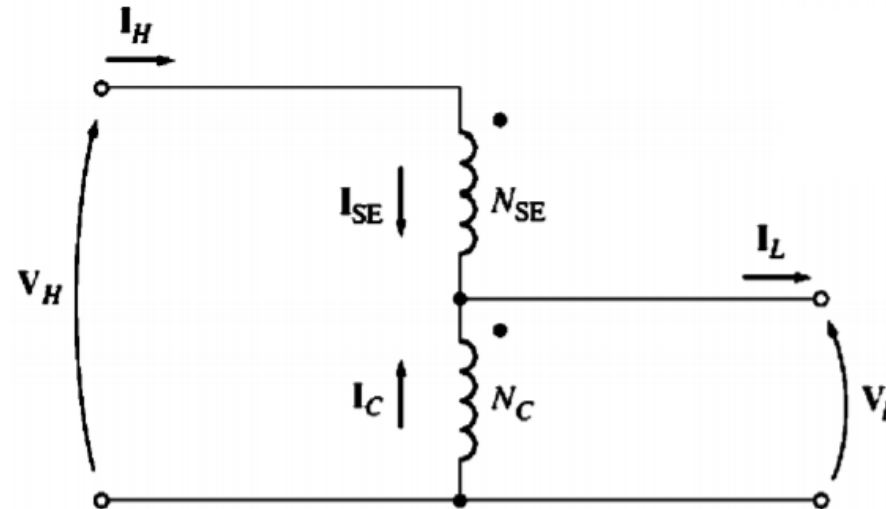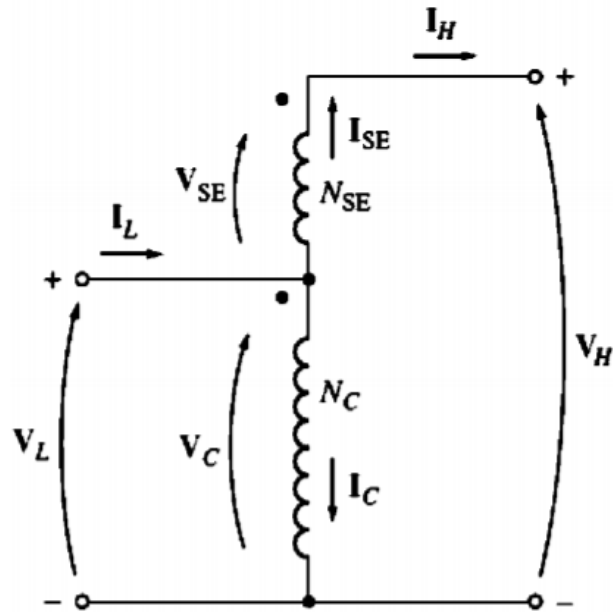- Has one winding only
- To cater for the need to change the voltage slightly.
- To give a small boost to a distribution cable to correct the voltage drop.
- A two-winding transformer is expensive in this case.



Voltage and current relationship

$$\frac{V_C}{V_{SE}} = \frac{N_C}{N_{SE}}$$

$$N_C I_C = N_{SE} I_{SE}$$


$$V_L = V_C$$

$$V_H = V_C + V_{SE}$$

$$V_H = V_C + V_{SE}$$

$$V_H = V_C + \frac{N_{SE}}{N_C} V_C = V_L + \frac{N_{SE}}{N_C} V_L = \frac{N_{SE} + N_C}{N_C} V_L$$

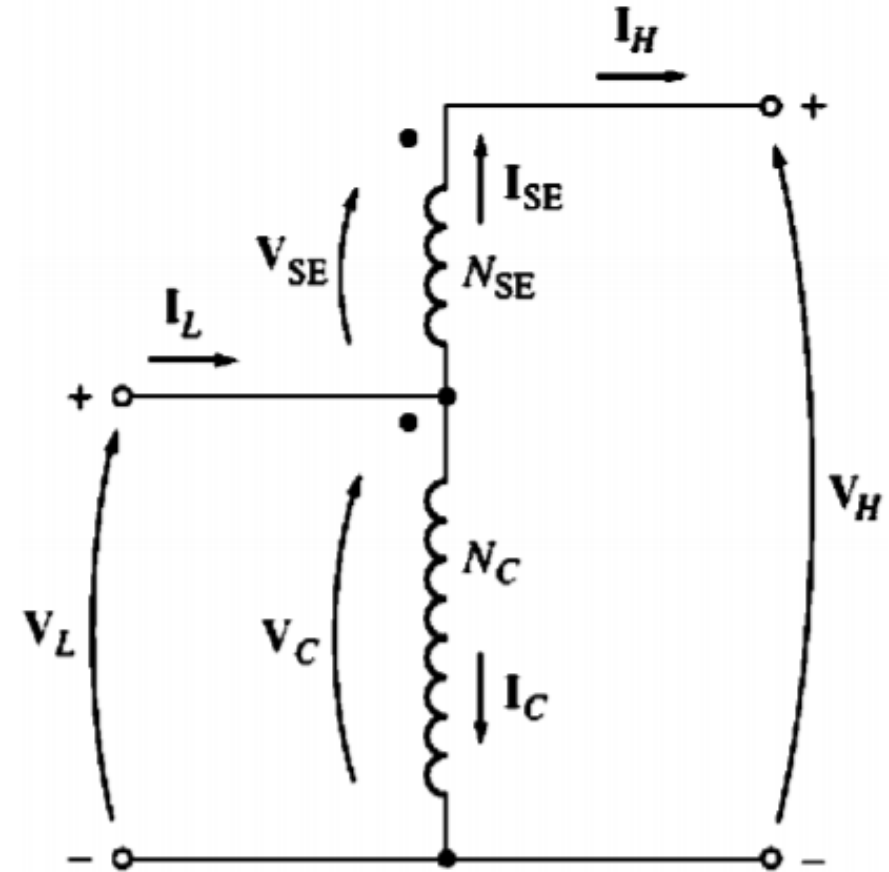
$$\boxed{\frac{V_L}{V_H} = \frac{N_C}{N_{SE} + N_C}}$$



Voltage and current relationship

$$\begin{aligned} I_L = I_C + I_{SE} &= \frac{N_{SE}}{N_C} I_{SE} + I_{SE} \\ &= \frac{N_{SE}}{N_C} I_H + I_H \\ &= \frac{N_{SE} + N_C}{N_C} I_H \end{aligned}$$
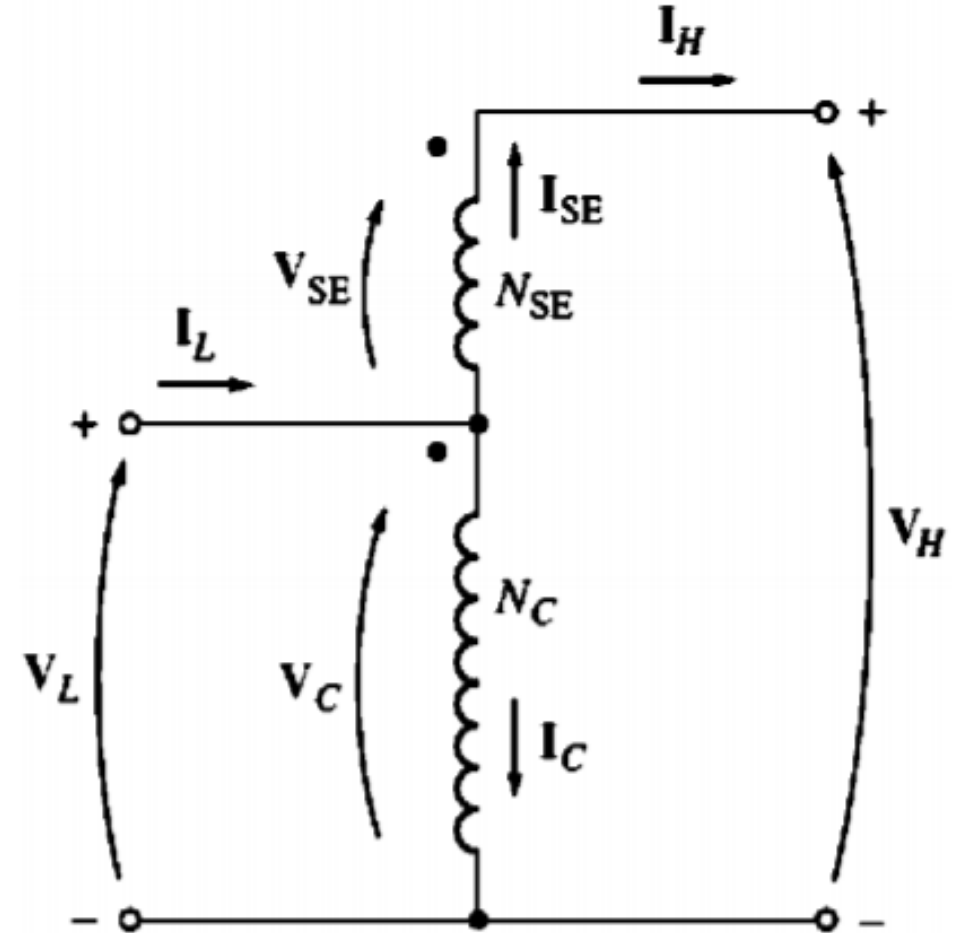
$$\boxed{\frac{I_L}{I_H} = \frac{N_{SE} + N_C}{N_C}}$$




Apparent power rating advantage of Autotransformer

Input apparent power of the transformer $S_{in} = V_L I_L$

Output apparent power of the transformer $S_{out} = V_H I_H$

$$S_{in} = S_{out} = V_L I_L = V_H I_H = S_{IO}$$

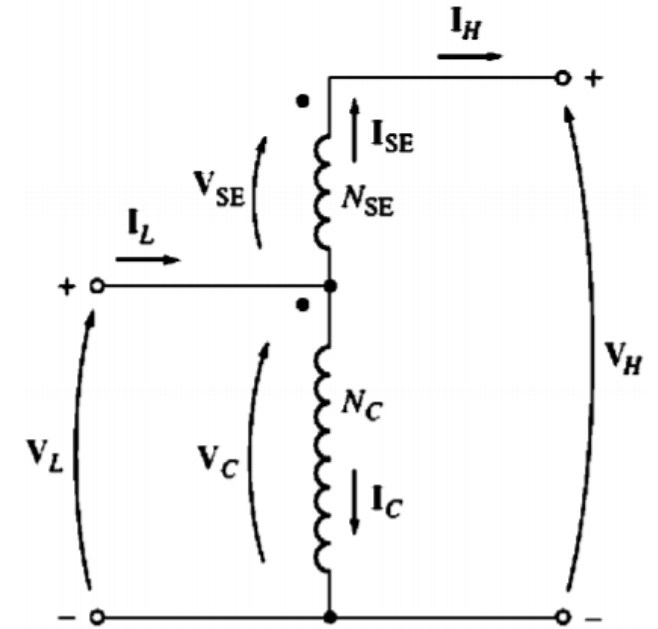The apparent power in the transformer windings is $S_W = V_C I_C = V_{SE} I_{SE}$



$$S_W = V_C I_C = V_L (I_L - I_H)$$

$$= V_L I_L - V_L I_L \frac{N_C}{N_{SE} + N_C} = V_L I_L \frac{(N_{SE} + N_C) - N_C}{N_{SE} + N_C} = S_{IO} \frac{N_{SE}}{N_{SE} + N_C}$$

$$\boxed{\frac{S_{IO}}{S_W} = \frac{N_{SE} + N_C}{N_{SE}}}$$

Problem # 2


Example 2–7. A 100-VA 120/12-V transformer is to be connected so as to form a step-up autotransformer (see Figure 2–34). A primary voltage of 120 V is applied to the transformer.

- (a) What is the secondary voltage of the transformer?
- (b) What is its maximum voltampere rating in this mode of operation?
- (c) Calculate the rating advantage of this autotransformer connection over the transformer's rating in conventional 120/12-V operation.

$$V_H = \frac{N_{SE} + N_C}{N_C} V_L = \frac{12 + 120}{120} 120 \text{ V} = 132 \text{ V}$$

$$\frac{S_{IO}}{S_W} = \frac{N_{SE} + N_C}{N_{SE}} = \frac{12 + 120}{12} = \frac{132}{12} = 11 \quad \leftarrow \text{Rating advantage}$$

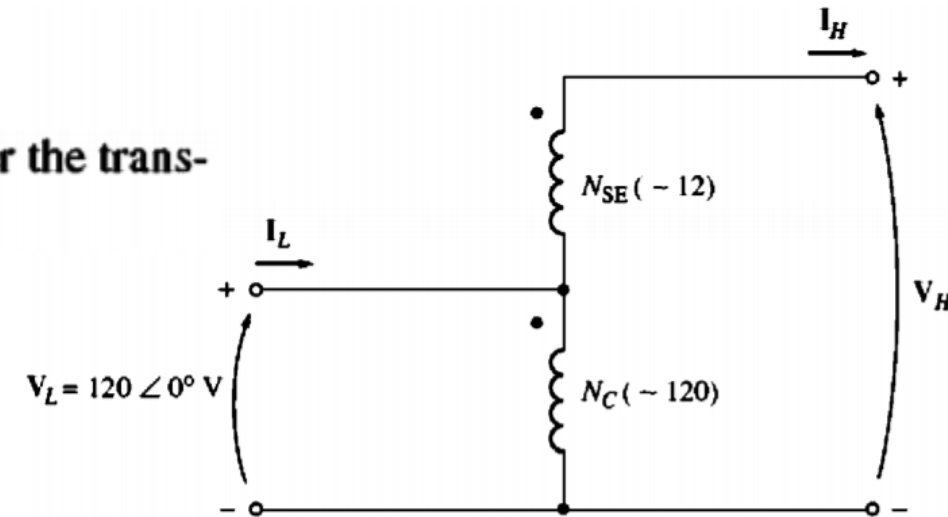Rating of the autotransformer = 11 x 100 = 1100 VA



Problem # 2

The transformer's impedance in a per-unit system when connected in the conventional manner is

$$Z_{eq} = 0.01 + j0.08 \text{ pu}$$

The apparent power advantage of this autotransformer is 11, so the per-unit impedance of the autotransformer connected as described is

$$\begin{aligned} Z_{eq} &= \frac{0.01 + j0.08}{11} \\ &= 0.00091 + j0.00727 \text{ pu} \end{aligned}$$

Problem of initial current inrush

Suppose that voltage $v(t) = V_M \sin(\omega t + \theta)$ is applied at the moment the transformer is first connected to the power line

If the initial voltage is $v(t) = V_M \sin(\omega t + 90^\circ) = V_M \cos \omega t$ and the initial flux in the core is zero, then the maximum flux during the first half cycle will just equal the maximum flux at steady state:

$$\phi_{\max} = \frac{V_{\max}}{\omega N_p}$$

This flux level is just the steady-state flux, so it causes no special problems. But if the applied voltage happens to be


$$v(t) = V_M \sin \omega t$$

$$\phi(t) = \frac{1}{N_p} \int_0^{\pi/\omega} V_M \sin \omega t \, dt = -\frac{V_M}{\omega N_p} \cos \omega t \Big|_0^{\pi/\omega} = -\frac{V_M}{\omega N_p} [(-1) - (1)] \quad \longrightarrow \quad \boxed{\phi_{\max} = \frac{2V_{\max}}{\omega N_p}}$$

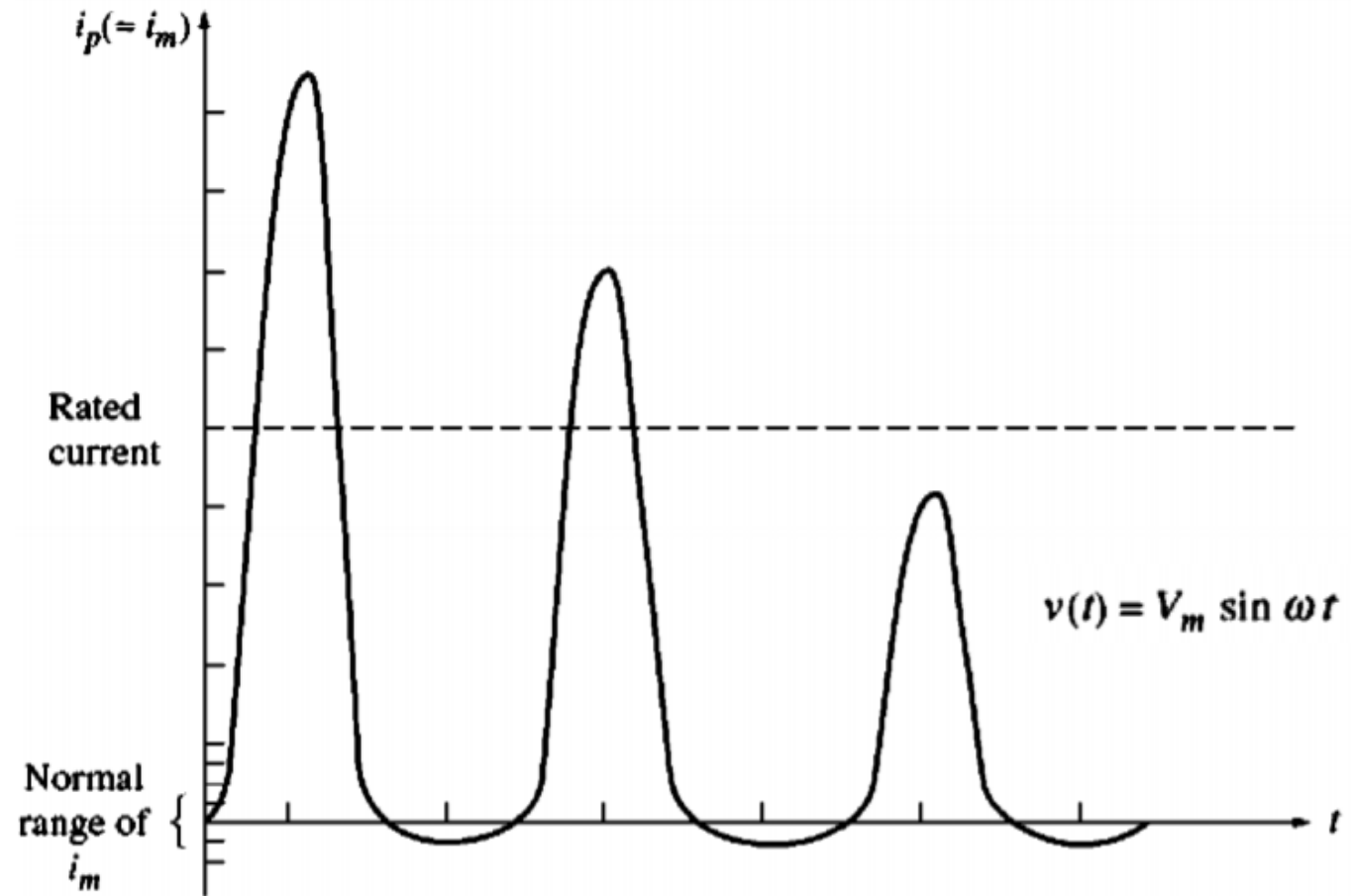Problem of initial current inrush

$$\phi_{\max} = \frac{2V_{\max}}{\omega N_p}$$

- ✓ *This maximum flux is twice as high as the normal steady-state flux.*
- ✓ *This doubling of the flux in the core results in an enormous magnetization current.*
- ✓ *In fact, for part of the cycle, the transformer looks like a short circuit, and a very large current flows*



Maintenance

- Transformers are generally housed in tightly-filled sheet steel metal cage.
- Tanks are filled with special insulating oil. This keeps coil cool.
- Oil should be free from alkalis, sulphur and moisture.
- Sides of the tank is corrugated or are fitted with radiators in order to allow for faster cooling.
- For large transformers, breathers are provided in order to allow for the expansion/contraction of the oil in the tank as the temperature increases or decreases.
- Moisture trapper is provided to block moisture