



Assignment 2

Department of Electrical & Computer Engineering

North South University

Submitted By

Name: Mohammed Mahmudur Rahman

Student ID: 1520386043

Course: Electrical Circuits (EEE141)


Section: 05

Faculty Advisor

Syeda Sarita Hassan (SSH1)

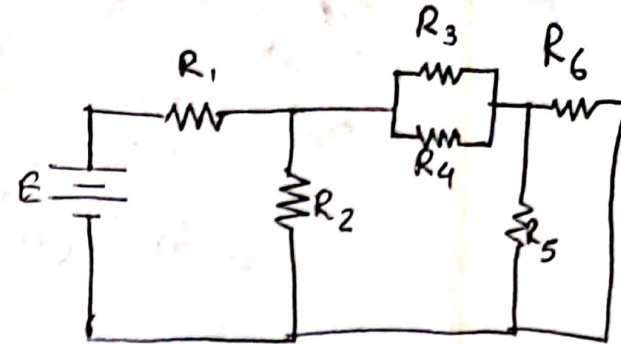Problem: 6.2

② (a) Here R_3 & R_4 are in parallel. Then, R_6 & R_5 are in parallel.



(b) Here, E , R_1 & R_2 are in series.

③ (a) $R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{0.1 \times 18}{0.1 + 18} = 6.044 \Omega$

(b)
$$\frac{1}{R_T} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}$$
$$= \frac{6 + 3 + 2}{6} = \frac{11}{6}$$

$\therefore R_T = \frac{6}{11} = 0.54 k\Omega$

(c)
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{100} + \frac{1}{1 \times 10^3} + \frac{1}{10 \times 10^3}$$

$\therefore \frac{1}{R_T} = \frac{111}{10000} \Omega$

$\therefore R_T = \frac{10000}{111} = 90.09 \Omega$


$$\begin{aligned}
 \textcircled{d} \quad \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \\
 &= \frac{1}{18k\Omega} + \frac{1}{18k\Omega} + \frac{1}{18k\Omega} + \frac{1}{6 \times 10^3 k\Omega} \\
 &= \frac{1001}{6000} k\Omega \\
 \therefore R_T &= \frac{6000}{1001} = 5.994 k\Omega.
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{e} \quad \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} \\
 &= \frac{1}{22} + \frac{1}{10} + \frac{1}{22} + \frac{1}{10} + \frac{1}{22} + \frac{1}{22} \\
 &= 3 \frac{1}{22} (4) + \left(\frac{1}{10} \times 2 \right) \\
 &= \frac{4}{22} + \frac{2}{10} = 0.3818 \Omega.
 \end{aligned}$$

Section 6.3.

⑩ a) For Parallel R_1 & R_2 .
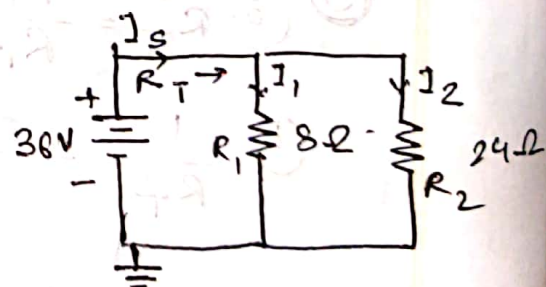
$$\begin{aligned}
 R_T &= \frac{R_1 R_2}{R_1 + R_2} = \frac{8 \times 24}{8 + 24} \Omega \\
 &= 6 \Omega.
 \end{aligned}$$



⑪ As it is a parallel circuit, so, voltage across each branch would be same as source voltage 36V.

⑫ Here $I_1 = \frac{V}{R_1} = \frac{36}{8} = 4.5 A$.

$$I_2 = \frac{V}{R_2} = \frac{36}{24} = 1.5 A$$

$$\therefore I_3 = I_1 + I_2 = (4.5 + 1.5) A = 6 A$$

(d) Here,


$$I_s = \frac{V}{R_T} = \frac{36}{6} A = 6 A = I_1 + I_2$$

(11) (a) $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$$= \left(\frac{1}{3} + \frac{1}{9} + \frac{1}{36} \right) \Omega$$

$$= \frac{17}{36}$$
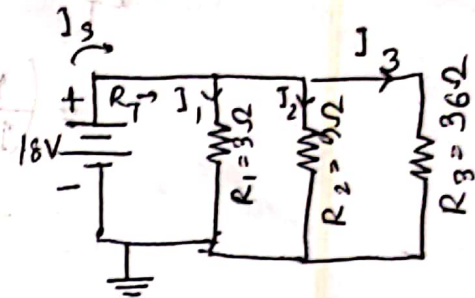
$$\therefore R_T = \frac{36}{17} \approx 2.12 \Omega$$



(b) As, it is a parallel circuit, so voltage in each branch would same as source voltage 18V.

(c) Source current, $I_s = \frac{E}{R_T} = \frac{18}{2.12} A$

$$= 8.49 A$$

$$I_1 = \frac{V}{R_1} = \frac{18}{3} = 6 A$$

$$I_2 = \frac{V}{R_2} = \frac{18}{9} = 2 A$$

$$I_3 = \frac{V}{R_3} = \frac{18}{36} = 0.5 A$$

(d) Here, $I_1 + I_2 + I_3 = (6 + 2 + 0.5) A$

$$= 8.5 A$$

$$I_s = 8.49 A \approx 8.5 A$$

So, $I_1 + I_2 + I_3 = I_s$ [verified]

Section: 6.4

(10) (a) Here,

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \left(\frac{1}{1} + \frac{1}{33} + \frac{1}{8.2} \right) \text{ k}\Omega$$

$$= \frac{1559}{1353} \text{ k}\Omega$$

$$\therefore R_T = 0.868 \text{ k}\Omega$$

Here, $E = V_1 = V_2 = V_3 = 100 \text{ V}$

$$I_1 =$$

$$I_1 = \frac{E}{R_1} = \frac{100 \text{ V}}{1 \text{ k}\Omega} = 100 \text{ mA}$$

$$I_2 = \frac{E}{R_2} = \frac{100 \text{ V}}{33 \text{ k}\Omega} = 3.03 \text{ mA}$$

$$I_3 = \frac{E}{R_3} = \frac{100 \text{ V}}{8.2 \text{ k}\Omega} = 12.195 \text{ mA}$$


(b) As per law,

$$\text{Power } P = VI$$

$$\text{So, Power across } R_1 = P_{R_1} = V_{R_1} \cdot I_{R_1} = (100 \text{ V})(100 \text{ mA}) = 10 \text{ Watt}$$

$$P_{R_2} = V_{R_2} \cdot I_{R_2} = (100 \text{ V})(3.03 \text{ mA}) = 303 \text{ mW} = 0.30 \text{ W}$$
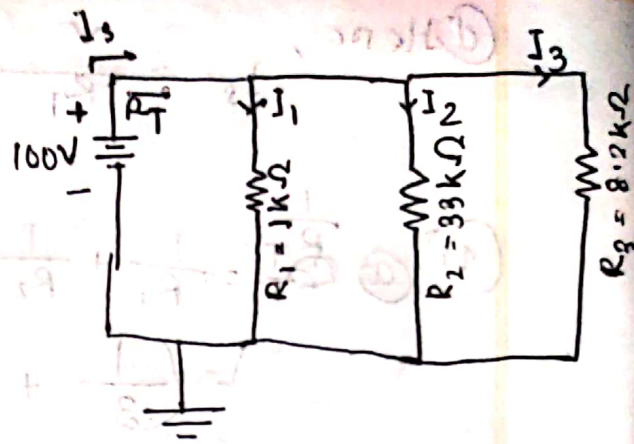
$$P_{R_3} = V_{R_3} \cdot I_{R_3} = (100 \text{ V})(12.195 \text{ mA}) = 1219.5 \text{ mW} = 1.22 \text{ W}$$



$$\textcircled{C} P_{\text{source}} = (F)(I_s)$$

Here, $I_s = \frac{E}{R_T} = \frac{100V}{0.868k\Omega} = 115.21mA$

$$\text{So, } P_{\text{source}} = (100\text{V}) (115.213\text{mA})$$

$$= 11520.74\text{ mW} = 11.52\text{ W}$$

$$(d) P_{R_1} + P_{R_2} + P_{R_3} = (10 + 0.3 + 1.22) \text{ W} \\ = 11.52 \text{ W} = P_{\text{source}} \text{ [Compared]}. \quad \square$$

© Here, Resistor P_R , received most power. As, it has the lowest resistance in this path current was maximum. Thus, it received most power.

23) @ Here, 8Ω & 12Ω are Parallel.

$$So, \frac{1}{R_{(8+12)}} = \frac{1}{8} + \frac{1}{12}$$


$$\therefore \frac{1}{R(8+12)} = \frac{5}{24}$$

$$\therefore R_{(8+12)} = 4 \cdot 8$$

Again, 4Ω is parallel with this 4.8Ω .

So, $\frac{1}{R_{(4||48)}} = \frac{1}{4} + \frac{1}{4.8} = \frac{11}{24}$

$$\therefore R(4114.8) = 2.182 \Omega$$

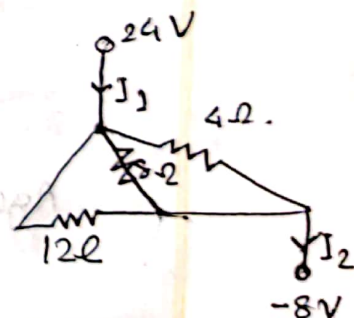

Here, Total Voltage, $V = 24 - (-8) = 24 + 8 = 32V$.

$$\therefore I_1 = \frac{V}{R_T} = \frac{32}{2.182} = 14.67 A$$


(b) Power of 4Ω resistor $= \frac{V^2}{R} = \frac{(32)^2}{4} = 256W$.

(c) Here As there is only one path for output current -
So, output current = input current .

So, $I_2 = I_1 = 14.67 A$.

Section: 6.5

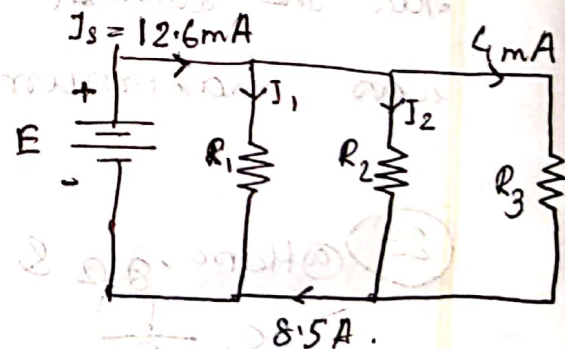(24) Here, $I_1 = I_s - 8.5 mA$
 $= 12.6 - 8.5 mA$
 $= 4.1 mA$.




Again, $I_s = I_1 + I_2 + 4 mA$.

$$12.6 = 4.1 + I_2 + 4$$

$$\therefore I_2 = (12.6 - 4.1 - 4) mA = 4.5 mA$$

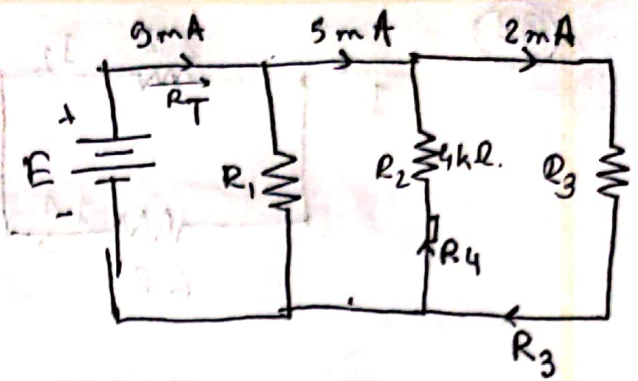(27) Here,
 $I_{R_4} = 5 \text{ mA} - 2 \text{ mA} = 3 \text{ mA}$

$$E = V_{R_2} = (3 \text{ mA})(4 \text{ k}\Omega) = 12 \text{ V}$$



$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{12 \text{ V}}{(5-3) \text{ mA}} = \frac{12 \text{ V}}{2 \text{ mA}} = 6 \text{ k}\Omega$$

$$R_3 = \frac{V_{R_3}}{I_{R_3}} = \frac{12 \text{ V}}{2 \text{ mA}} = 6 \text{ k}\Omega$$

$$\therefore R_T = \frac{E}{I_T} = \frac{12 \text{ V}}{9 \text{ mA}} = 1.33 \text{ k}\Omega$$

Section: 6.6.


(29) Here,
 $I_2 = \frac{4 \Omega}{12 \Omega} \times I_1 = \frac{1}{3} I_1 = \frac{1}{3} \times 6 = 2 \text{ A}$

$$I_3 = \frac{4}{2} I_1 = 2 I_1 = 12 \text{ A}$$


$$I_4 = \frac{4}{40} I_1 = \frac{1}{10} I_1 = 0.6 \text{ A}$$

$$I_T = I_1 + I_2 + I_3 + I_4$$
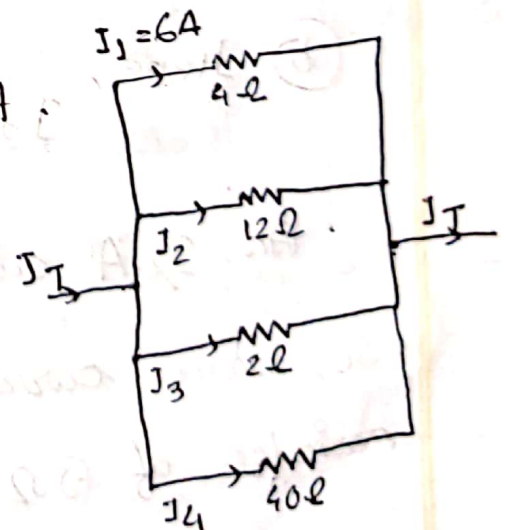
$$= (6 + 2 + 12 + 0.6) = 20.6 \text{ A}$$



32

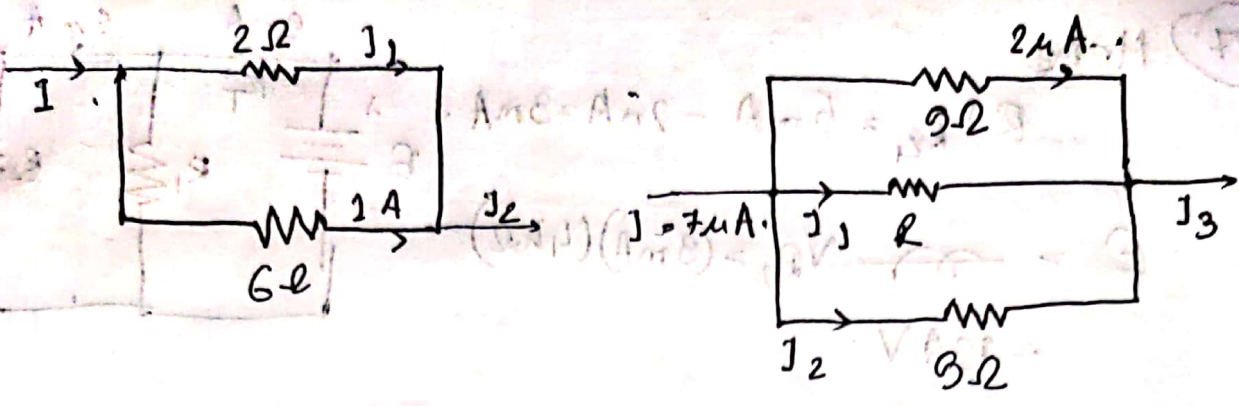

① Applying CDR!

$$I_{6\Omega} = \frac{2\Omega \cdot I}{2\Omega + 6\Omega} = 1A$$

$$I_{3\Omega} = \frac{(1A)(8\Omega)}{2\Omega} = 4A = I_2$$

Again, $I_1 = I - 1A = 3A$

② Here,

$$I_3 = I = 7\mu A$$

As, $2\mu A$ current passes through 3Ω resistor of top
 So, same current would be found at bottom
 resistor of 3Ω .

$$\text{So, } I_2 = 2\mu A$$

$$I_1 = I - 2(2\mu A) = 7\mu A - 4\mu A = 3\mu A$$

$$V_R = (2\mu A)(3\Omega) = 18\mu V$$

$$R = \frac{V_R}{I_R} = \frac{18\mu V}{3\mu A} = 6\Omega$$

Section 6.7.


35) a) $P_L = V_L I_L$

$$\Rightarrow 72 \text{ W} = 12 \text{ V} \cdot I_L$$

$$\therefore I_L = 6 \text{ A}$$

Here,
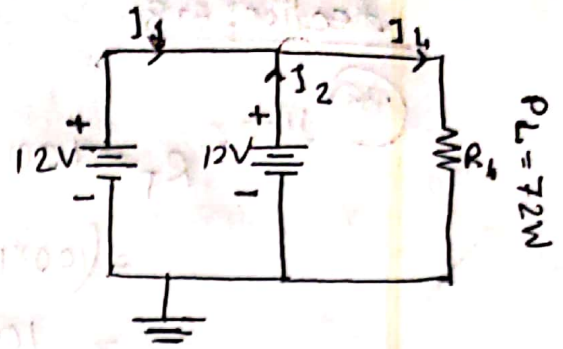
$$I_1 = I_2 = \frac{I_L}{2} = \frac{6 \text{ A}}{2} = 3 \text{ A}$$



b) $P_{\text{source}} = E \cdot I = (12 \text{ V})(3 \text{ A}) = 36 \text{ W}$

c) $P_{S_1} + P_{S_2} = 36 \text{ W} + 36 \text{ W} = 72 \text{ W}$ [As, both source value are same]

d) ~~I drain~~ would be 6A; because if there was only source current available to supply the same power to the load still a load resistance is same. So ~~power~~ current I_L would be same.

36) Here,


$$R_T = (8 \parallel 56) \Omega = \frac{8 \times 56}{8 + 56} \Omega$$

$$= 7 \Omega$$

Here, $I_2 = I_3$ [series circuit; current same]

$$\therefore I_2 = I_3 = \frac{E}{R_T} = \frac{12 \text{ V}}{7 \Omega} = 1.71 \text{ A}$$
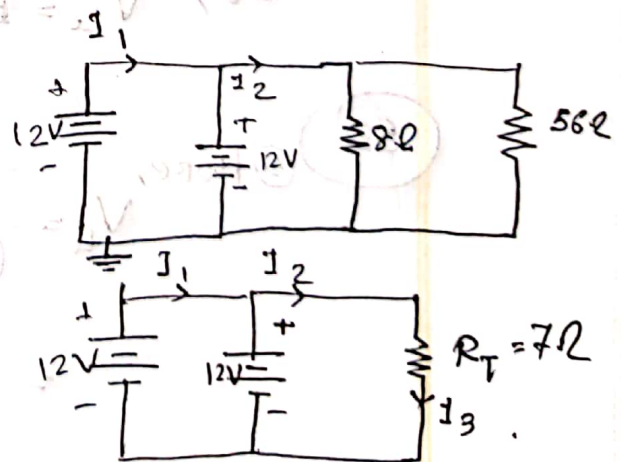
$$I_1 = \frac{1}{2} I_2 = \frac{1}{2} (1.71 \text{ A}) = 0.86 \text{ A}$$



Section: 6.8.

(38) Here $R_T = 100\Omega + 10k\Omega$
 $= (100 \times 10^{-3} + 10)k\Omega$
 $= 10.1k\Omega$

$$I_s = \frac{E}{R_T} = \frac{12V}{10.1k\Omega} = 1.19mA$$

$$V_L = I_s R_L = (1.19mA)(10k\Omega) = 11.9V$$


(b) If R_L is shorted,

$$I_s \text{ would be } \frac{E}{R_i} = \frac{12V}{100\Omega} = 120mA$$


(c) If R_L is replaced by open circuit,

V_L would be same as source voltage.

$$\text{So, } V_L = E = 12V$$

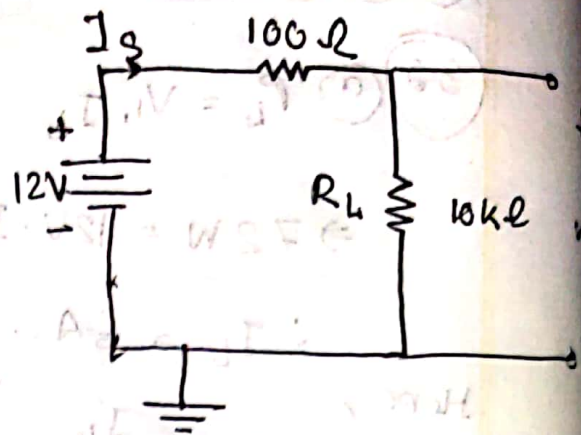

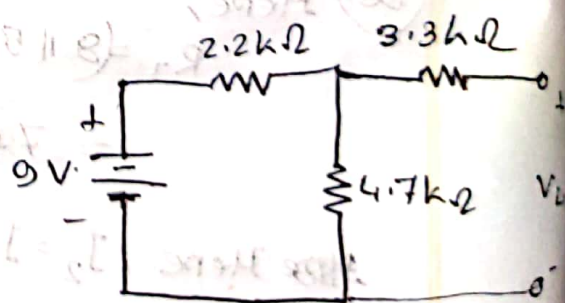(39) Here, $V_L = \frac{4.7k\Omega}{(4.7 + 2.2)k\Omega} \times 9V$
 $= \frac{4.7 \times 9}{6.9} = 6.13V$



(b) If the $2.2k\Omega$ resistor is shorted, then V_L would be same as source voltage. So, $V_L = E = 9V$.

③ If $4.7\text{ k}\Omega$ resistor is replaced by open circuit then the voltage V_u would be same as source voltage. Because, other both are in same node.

$$\text{So, } V_L = E = 9\text{ V}.$$