



North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code : EEE211

Course Title: Digital Electronics

Section: 01

Experiment Number: 08

Experiment Name: Introduction to Flip flop and Sequential Circuit

--

Experiment Date: 04.01.2021

Date of Submission: 10.01.2021

Course Instructor: Fahimul Haque

Submitted To: Fatema Zahra

(1)

Experiment Name:

Introduction to flip-flops & sequential circuits.

Objective:

- Learning the concept of states in digital logic & how flip-flop circuits can be used to store state information.
- Understand the internal logic & relationship among J-K, T & D flip-flops & observe their characteristics.
- Understand & design synchronous sequential circuit as per state diagram.

Theory:

Flip-flop is a storage device which has two stable states & has capability of storing one bit of binary information. The output of the flip-flop can only change if a clock pulse is supplied to flip-flop. There are three types of flip-flops. They are J-K, D & T flip flop. ^{Each} of them has different characteristics.

Sequential logic is a type of logic circuit whose output depends both on the present value of its input & sequence of past input. It is a contrast to combinational logic.

For J_A .

BC	00	01	11	10
A				
0	0	0	1	0
1	x	x	x	x

$$\therefore J_A = BC$$

For J_B

BC	00	01	11	10
A				
0	0	1	x	x
1	0	1	x	x

$$\therefore J_B = C$$

For J_C

BC	00	01	11	10
A				
0	1	x	x	1
1	1	x	x	1

$$\therefore J_C = 1$$

For T_A .

BC	00	01	11	10
A				
0	0	0	1	0
1	0	0	1	0

$$\therefore T_A = BC$$

For T_C

BC	00	01	11	10
A				
0	1	1	1	1
1	1	1	1	1

$$\therefore T_C = 1.$$

For K_A

BC	00	01	11	10
A				
0	x	x	x	x
1	0	0	1	0

$$\therefore K_A = BC$$

For K_B

BC	00	01	11	10
A				
0	x	x	1	0
1	x	x	1	0

$$\therefore K_B = C$$

For K_C

BC	00	01	11	10
A				
0	x	1	1	x
1	x	1	1	x

$$\therefore K_C = 1.$$

For T_B

BC	00	01	11	10
A				
0	0	1	1	0
1	0	1	1	0

$$\therefore T_B = C.$$

For D_A .

A \ BC	00	01	11	10
0	0	0	1	0
1	1	1	0	1

$$\therefore D_A = AC' + AB' + A'BC$$

For D_C

A \ BC	00	01	11	10
0	0	1	0	1
1	1	0	0	1

$$\therefore D_C = C.$$

For D_B .

A \ BC	00	01	11	10
0	0	1	0	1
1	0	1	0	1

$$\therefore D_B = B0' + B'1$$

Circuit Diagram:

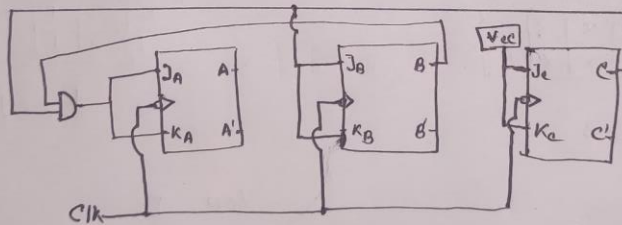


Figure : JK Flip-Flop.

5

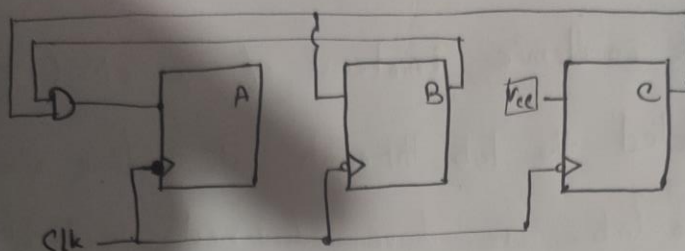


Figure: T-Flip-Flop.

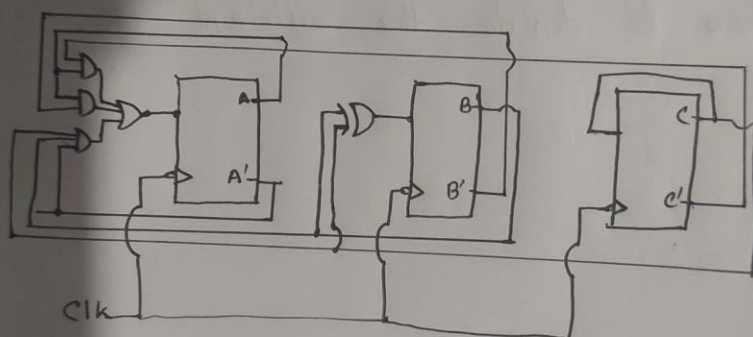


Figure: D Flip Flop

Discussion:

Due to pandemic instead of practical session we completed the lab through ~~an~~ online simulation. Through this lab, we have learned to implement flip-flop & design the sequential circuit. We also learned compare between different flip-flops & decide the efficient one.

Simulation:

