
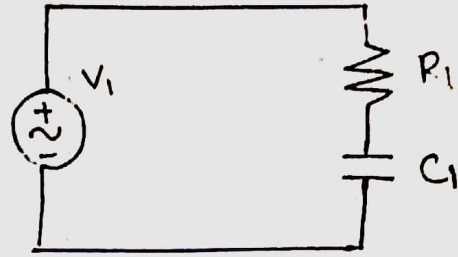


Questions :-

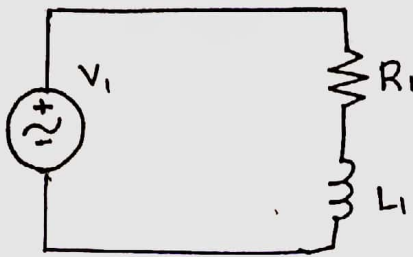


1) How much average power is consumed by the inductor ^{Capacitor?} and ?

Ans: The average power consumed by the inductor and the capacitor is zero. Since the voltage (V) and current (I) are 90° out of phase for all reactive loads, the power factor for them, $Pf = \cos \pm 90^\circ = 0$. Therefore the average power consumed by reactive load is zero. ^{as} and the power received by capacitor and inductor is returned back in the cycle.

2. What is the effect of the inductor and capacitor on the instantaneous power of the R_1

Ans: A circuit element produces or dissipates power according to $p = I \cdot V$ where I is the current ~~across~~ through the element and V is the voltage across it. Since the current and voltage depends on time in a AC circuit, instantaneous power is also time dependent. For R_1 , $I(t)$ and $V(t)$ are in phase ^{and} ~~an~~ therefore Always ~~It~~ have the same sign but for a capacitor and inductor, the relative sign of $V(t)$ and $I(t)$ vary over time due to a cyc cycle due to their phase difference. Consequently, $P(t)$ is positive at times and negative at others indicating that capacitive and inductive element produces power at some instants and absorbs it at other.

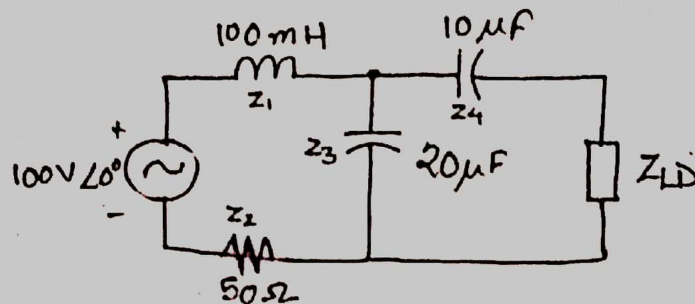3) Determine the load Z_{LD} that will allow maximum power delivered to the load for the following circuit. if the frequency is 192.241 Hz . What should be the maximum power of the load? Construct a final circuit in multisim and measure the power at the load. Is the result similar to the theoretical maximum power. Attach the simulation screenshot in the lab report.



Ans: Maximum power delivered where $Z_{LD} = Z_{TH}$

$$\therefore Z_{LD} = \{(Z_1 + Z_2) \parallel Z_3\} + Z_4 \quad \text{where} \quad Z_1 = j \times 2\pi \times 192.241 \times 100 \times 10^{-3}$$

$$= \{j120.79 + 50\} \parallel -j41.39 + (j82.79) = j120.79 \Omega$$

$$= 0.731 - j139.63$$

$$= 139.98 \angle -86.013^\circ$$

$$Z_2 = 50 \Omega$$

$$Z_3 = -j41.994 \Omega$$

$$Z_4 = -j82.79 \Omega$$

$$\text{Maximum power } P_{max} = \frac{V_{TH}^2}{4R_L}$$

$$= \frac{100^2}{4 \times 139.98}$$

$$V_{TH} = \frac{-j41.394}{j120.79 + 50 + (-j41.394)} \times 100$$

$$= -34.096 - j2.429$$

$$= 34.18 \angle -175.92^\circ$$

$$P_{max} = \frac{|V_{TH}|^2}{8R_{TH}}$$

$$= \frac{34.18^2}{8 \times 139.98}$$

$$= 1.043 \text{ W}$$