



### Assignment

### EEE211/CSE231 (Digital Logic Design)

**Total Points: 60**

**Direction:** Please answer all the questions. You must show the steps of your calculations.

**STUDENT's NAME:** \_\_\_\_\_

**STUDENT's ID:** \_\_\_\_\_ **SECTION:** 10

- [2+6+2 = 10 points]** Convert the following numbers with the indicated base to Decimal
  - (2A3.CE4) Hex to ( )<sub>10</sub>
  - $(110101101110)_2 = ( )_8 = ( )_{16} = ( )_{10}$
  - 5602 = ( )<sub>BCD</sub>
- [3+2+2+3 = 10 points]** Draw the logic diagram of a full adder circuit. Also show the carry propagator (Pi) and carry generator (Gi). What is the purpose of using carry-look-ahead generator? Derive the Boolean equations and draw a 4 bit carry-look-ahead generator circuit.
- [2+2+3+3 = 10 points]** For the Boolean function,  $F = xyz + xy'z + x'y + xy'$ 
  - Obtain the truth table of F
  - Use Boolean algebra to simplify the function to a minimum number of literals
  - Implement the simplified function obtained in (b) using NAND only logic
  - Implement the function F using 2-to-4 Decoder with Enable
- [3 + 2 + 5 = 10 points]**

Consider the following function:

$$F(W, X, Y, Z) = \Sigma(1, 3, 7, 8, 10, 15) + \Sigma_d(0, 2, 9)$$

Using K-Map

  - Express the simplified Boolean expression.
- [10 points]** A **Minority Finder** is a digital circuit that will produce a 1 only if the Majority of the inputs are 0s. Design a logic circuit for a **3-input Minority Finder**. State any assumptions you have made in your design. Your circuit should be as simple as possible in terms of number of literals and/or gate input counts.

6. [ 10 points] Design Problem:



Consider the above chemical plant that has four large tanks with sensors A, B, C, and D. Sensor A and B are *liquid-level sensors* and sensor C and D are *heat sensors*. The value of A and B are 'LOW' if the liquid level is satisfactory and 'HIGH' when the level is in danger. Similarly, the value of C and D are 'LOW' if the temperature is normal and 'HIGH' if the temperature drops below the threshold limit.

Design a logic circuit that will take input from these four sensors and produce an alarm ('HIGH') whenever any of the following conditions is True:

- a) If the level in tank A and tank B is too high (danger) at the same time
- b) If either one of the tank A or tank B is too high (danger) and at the same time that the temperature of tank C or tank D is below the limit.
- c) If the temperature of both tank C and tank D is below the limit.

Implement your logic design using any one of the following two methods:

Using Universal gates only (should be minimized first)

OR

Using 8-to-1 Multiplexer

You must show the step-by-step design procedure