

1. Find the Thevenin equivalent circuit for the portions of the network external to the resistor  $R$ . Find the value of  $R$  for maximum power transfer to  $R$ . Determine the maximum power to  $R$ . Draw all the required circuit, demonstrate all the steps with clear formulas.

