

ASSIGNMENT-06

Name : Monsoor Mofiz Asmani

ID : 1921079642

Course : CSE231

Section : 10.

Submitted to : Dr. Mohammad Moniruzzaman Khan

Date : 29-03-2021

Digital Logic Design

"Don't care" condition:

use of "don't care" conditions to simplify an expression.

Inputs				Output
A	B	C	D	Y
0	0	0	0	X
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

AB/CD		00	01	11	10
00	X				
01					
11	X	X	(1)	X	X
10	1	1	X	X	


without don't cares:

$$Y = A\bar{B}\bar{C} + \bar{A}BCD$$

with don't cares:



$$Y = A + BCD$$

Combinational Logic Circuit:

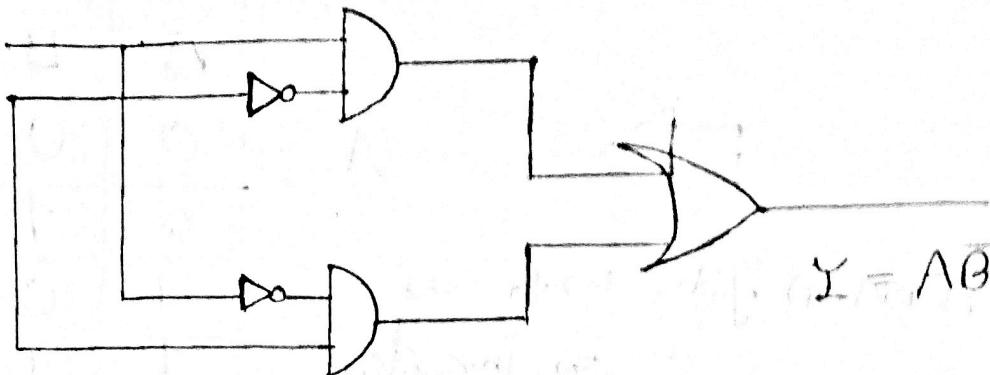


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$\therefore Y = A \oplus B.$$

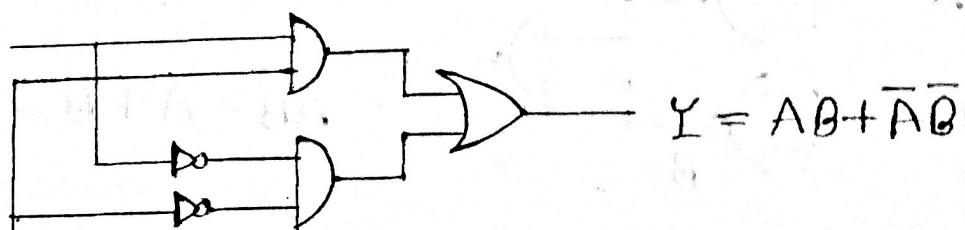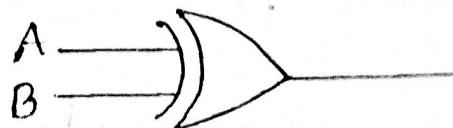

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$\therefore Y = \overline{A \oplus B}$$

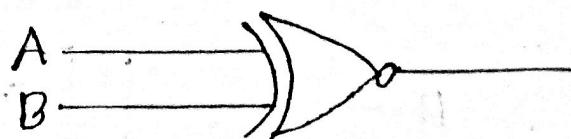

The universal property of NAND and NOR gates.

Truth table for 2 input NAND gate.

(a)



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

fig: A NAND gate used as an inverter.

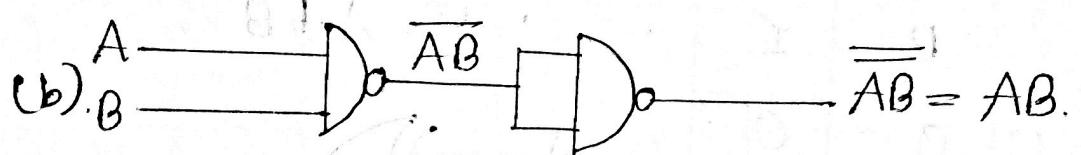


fig: Two NAND gates used as an AND gate.

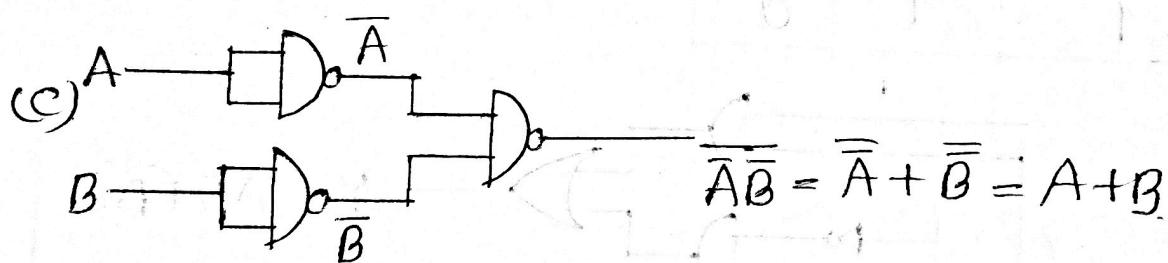


fig: Three NAND gates used as an OR gate.

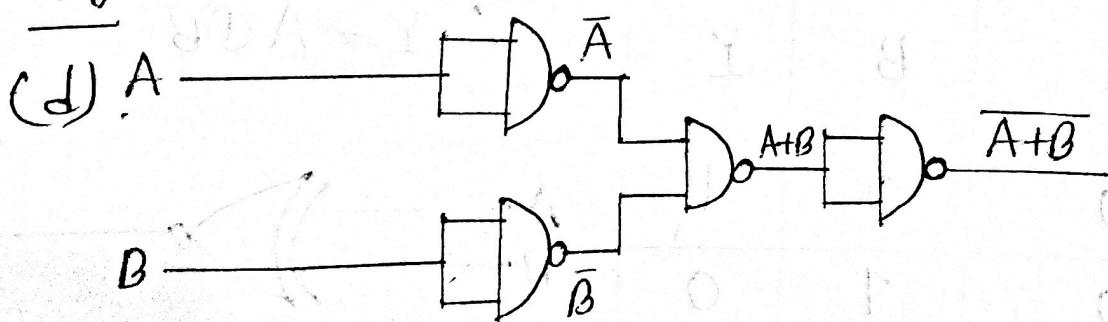


fig: Four NAND gates used as NOR gate.

The NOR Gate as a universal logic element.

Truth table for 2 input NOR Gate.


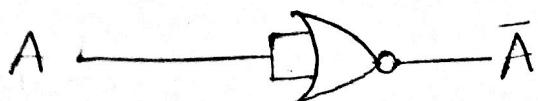


Fig: a NOR gate used as an inverter.

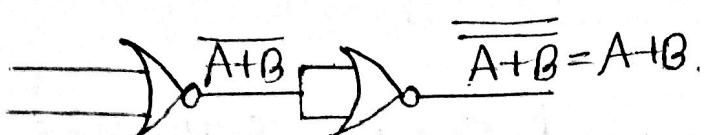

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Fig: Two NOR gates used as an OR gate.

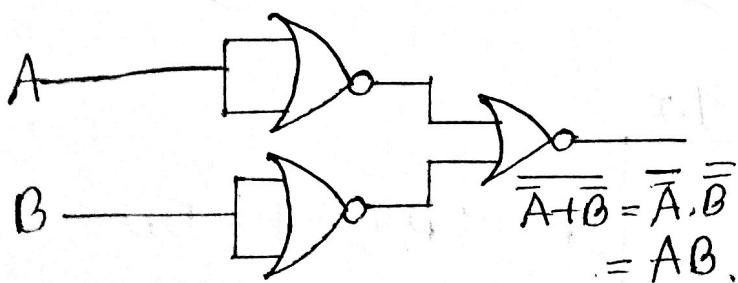


Fig: Three NOR gates used as an AND gate.

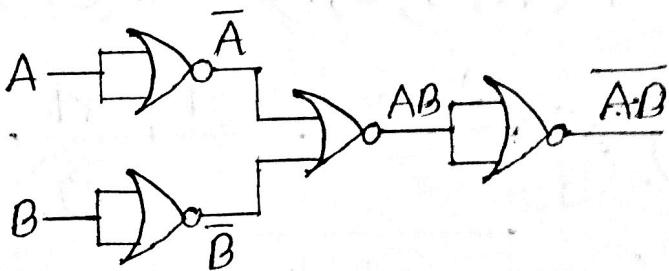


Fig: Four NOR gates used as a NAND gate

Simplify the Boolean Function in :

- (a) Sum of products and
- (b) Product of sum form.

$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$

(a) AB \ CD

		00	01	11	10
		00	01	11	10
B		01	11	11	11
01	11	11	11	11	11
11	12	13	15	14	11
10	12	11	11	11	11

$F = \overline{BC} + \overline{BD} + \overline{ACD}$

In product of maxterms, F can be expressed as

$$F(A, B, C, D) = \prod (3, 4, 6, 7, 11, 12, 13, 14, 15)$$

(b) AB \ CD

		00	01	11	10
		00	01	11	10
B		01	01	01	01
01	01	01	01	01	01
11	01	0	0	0	0
10			0		

$F = \overline{CD} + AB + BD$

$F = \overline{CD} + AB + BD$

$= (\overline{CD}) \cdot (AB) \cdot (BD)$

$= (\overline{C} + \overline{D}) (A+B) (B+D)$

Combinational Logic using NAND and NOR gates:

NAND gate:

using De Morgan's rule :

$$\overline{AB} = \overbrace{\overline{A} + \overline{B}}$$

Negative OR.


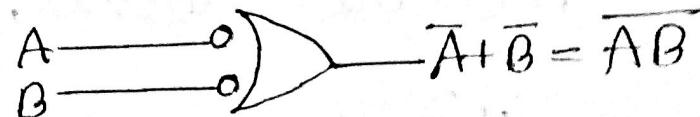
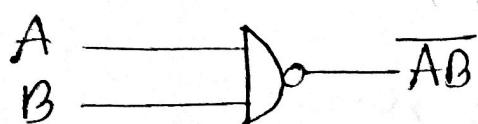


Fig : Two graphic symbols for NAND gate.

$$\overline{A+B} + \overline{AB}$$

Negative AND.

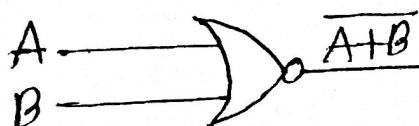

OR-invert.

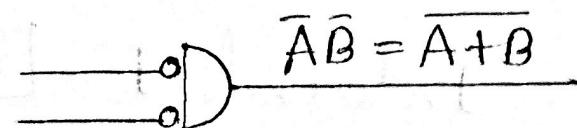


Fig : Two graphic symbols for NOR gate.

Exercise 01 :

$$F(A, B, C, D) = \Sigma (5, 7, 8, 10, 11, 14, 15).$$

$$d(A, B, C, D) = \Sigma (0, 12, 13).$$

A Karnaugh map for a 4-variable function $F(A, B, C, D)$. The variables are labeled A , B , C , and D at the top and left respectively. The rows and columns are labeled as follows:

- Top row: $AB \backslash CD$ (implied), 00, 01, 11, 10.
- Left column: 00, 01, 11, 10.
- Row 00: 0, \times , 0, 0.
- Row 01: 0, 0, 1, 1.
- Row 11: \times , \times , 1, 1.
- Row 10: 1, 0, 1, 1.

Minterms marked as 1 are 5, 12, 13, 14. Minterms marked as \times are 7, 8. Minterms marked as 0 are 0, 10, 11, 15.

$$F = A\bar{D} + BD + AC$$

(Ans).

Exercise 02 :

$$F(w, y, z) = \Sigma (1, 3, 7, 11, 15)$$

$$d(w, n, y, z) = \Sigma (0, 2, 5)$$

W \ YZ

w\yz	00	01	11	10
00	X	1	1	X
01	O	X	1	O
11	O	O	1	O
10	O	O	1	O

A } B }

D. D.

$$F = \bar{w}\bar{x} + yz. \quad (\text{Ans})$$

Exercise 03 :

$$F(A, B, C, D) = \Pi (1, 3, 5, 7, 13, 15)$$

A \ B \ C \ D

A \ B \ C \ D	00	01	11	10
00	0	0	0	
01	0	0	0	
11	0	0	0	
10				

A } B }

D.

$$F = \overline{AD} + BD.$$

$$\therefore F = \overline{\overline{AD} + BD}$$

$$= (\overline{AD}) \cdot (\overline{BD})$$

$$= (\overline{A} + \overline{D}) \cdot (\overline{B} + \overline{D})$$

$$= (A + \overline{D}) \cdot (\overline{B} + \overline{D}).$$

(Ans)

Exercise 04:

		F(A, B, C, D) = \prod (1, 3, 6, 9, 11, 12, 14)			
		00	01	11	10
AB	CD	00	1	0	0
		01	5	2	6
11	12	0	13	15	14
10	8	9	0	11	10

$$F = \overline{BD} + AB + CD$$

$$\therefore F = \overline{\overline{BD} + AB + CD} = (\overline{BD}) \cdot (\overline{AB}) \cdot (\overline{CD})$$

$$= (\overline{B} + \overline{D}) \cdot (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$

$$= (B + \overline{D}) (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$

(Ans)

Exercise 3.15 :

(a) $F(n, y, z) = \Sigma(0, 1, 4, 5, 6)$.

$d(n, y, z) = \Sigma(2, 3, 7)$. y

$n \backslash yz$	00	01	11	10
0	1	1	X	X
1	1	1	X	D

n \downarrow

z

$$F = \bar{n} + n = 1$$

(Ans).

$$(b). F(A, B, C, D) = \sum (0, 6, 8, 13, 14).$$

$$d(A, B, C, D) = \sum (2, 4, 10). c.$$

\backslash	CD	00	01	11	10	
AB	00	1	0	0	X	
	01	X	0	0	1	B
A	11	0	1	0	1	
	10	1	0	0	X	D.

$$F = \bar{B}\bar{D} + C\bar{D} + A\bar{B}\bar{C}D.$$

(Ans).

$$(c) F(A, B, C, D) = \Sigma(5, 6, 7, 12, 14, 15).$$

$$d(A, B, C, D) = \Sigma(3, 9, 11, 15).$$

AB		CD				C	D
		00	01	11	10		
00	0	1	3	X	0	B	1
	4	0	5	1	X	6	1
11	12	1	13	0	X	14	1
	8	0	9	X	11	X	10

$$F = AB\bar{D} + \bar{A}BD + BC.$$

(Ans)

(a)

$$(d). F(A, B, C, D) = \Sigma(4, 12, 7, 2, 10)$$

$$d(A, B, C, D) = \Sigma(0, 6, 8).$$

AB \ CD	00	01	11	10
00	X	0	0	1
01	1	0	1	X
11	1	0	0	0
10	X	0	0	1

$$\text{Ans} = \overline{AB} \overline{D} + \overline{A} \overline{B} C + \overline{B} \overline{D}$$

$$F = \overline{C} \overline{D} + \overline{A} \overline{B} C + \overline{B} \overline{D}$$

(Ans)