

**North South University**  
Electrical and Computer Engineering Department  
**QUIZ 2**



Spring Semester-2021

Course: CSE231

**Marks: 15, Time: 30 minutes**

1. Derive a truth table for Full adder. Write the Boolean equation for full adder and minimize the equation and finally draw a full adder circuit. **5\*1=5 marks**

2. Simplify the Boolean function using K map

1.  $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$  **5\*1 marks=5 marks**

3. Draw a 2 to four line decoder with enable input. Show the truth table and equation for the circuit if we want to use and gate to design it. **5\*1 marks=5 marks**