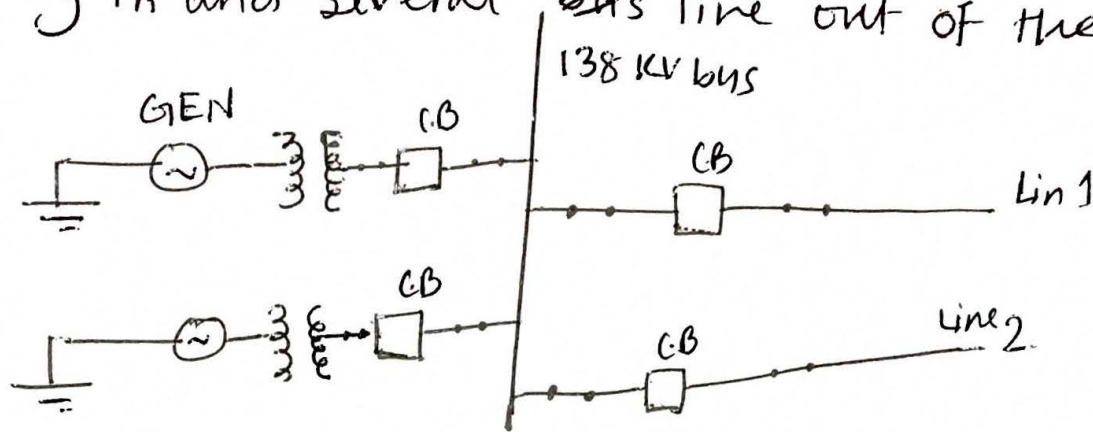


Bus must be use at every junction point of line and Feeder. Normally a bus will have several power source feeding in and several bus line out of the bus.



at various point on Transmission line


Various ckt and Breaker are connected to bus <sup>thru</sup> Breaker so disconnection in either side of Breaker so that due to any fault it can be disconnected or isolated.

at Low voltage bus is made of copper which may be made indoor or outdoor. In this arrangement breaker can be simply disconnect from bus for isolation.
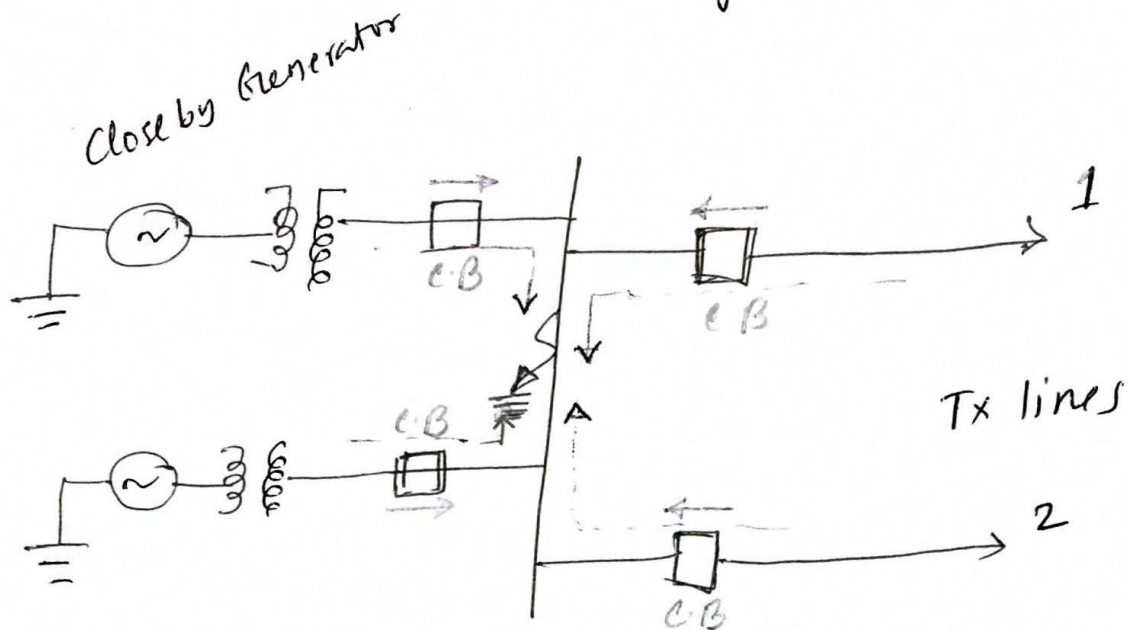
### Common bus Faults:

- animals or birds bridging an insulator
- Lightning Flashover
- flying object bridging across bus bars


Occur it must be clear as quickly as possible otherwise extensive damage may occur.



if reverse current flow prolong, it may cause outage of power generation and 2 Tx line

basis

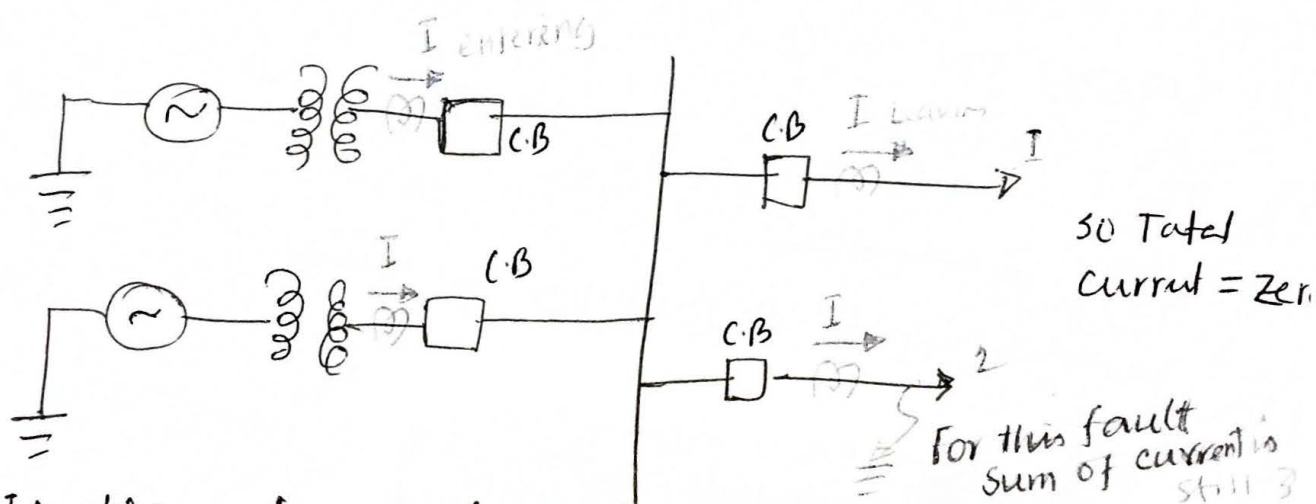
Direction of flows forms <sup>bus</sup> protection using CTs on outboards like following fig




If there is no fault than sum of current

Leaving equal to sum of the current entering

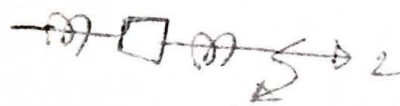so this <sup>downstream</sup> fault is cleared by activating inboard CT by other protection relay



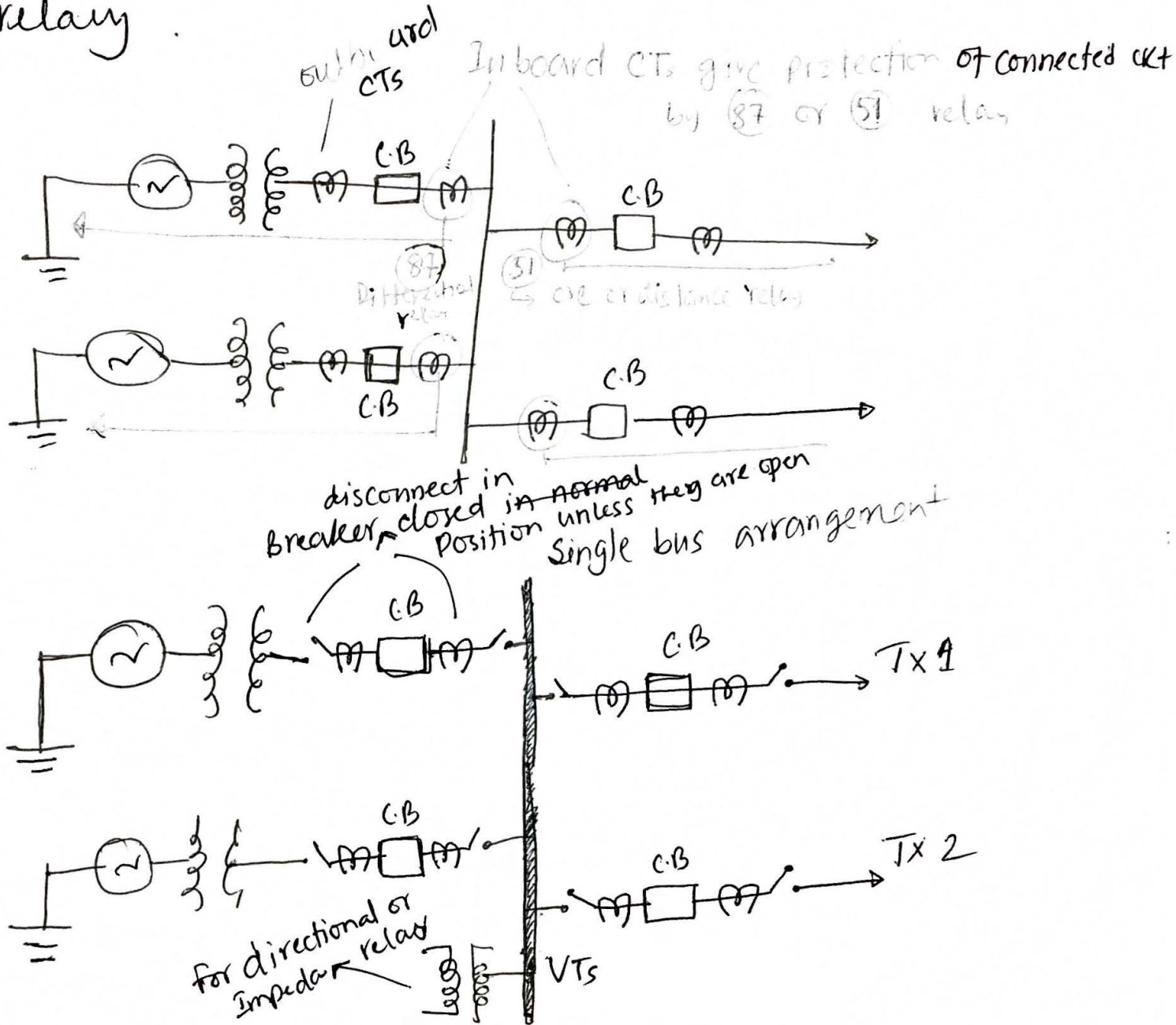If fault does occur in Bus itself  
 of currents will no longer be zero and all current  
 fed to the fault will trip all the breaker  
 This is the well known formula by differential  
 relay.




If there is need of a directional or Impedance relay a voltage transformer is being connected to the bus bar to fulfill the requirement of a voltage signal.



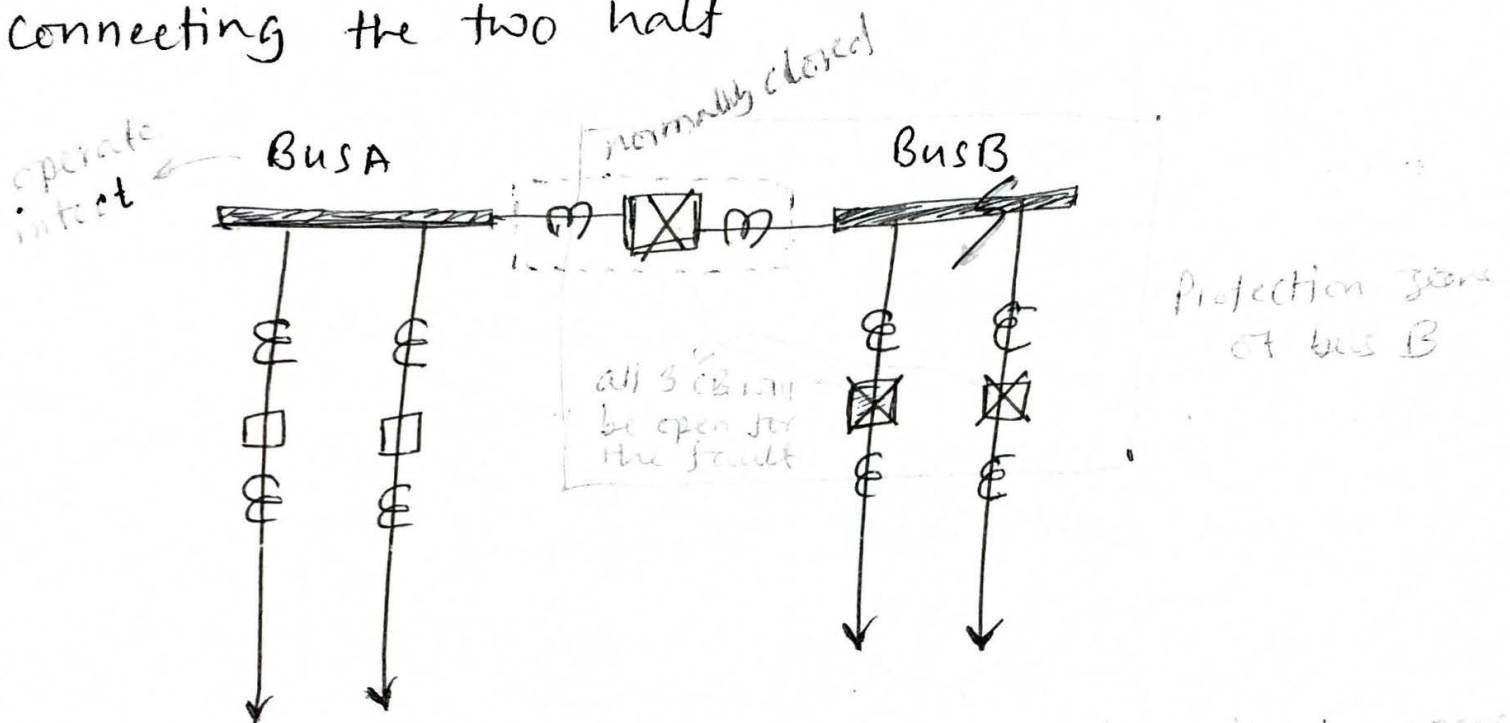
## Disadvantage of single bus arrangement

any fault in bus will necessitate shutting down the whole power system and losing the output from two generator [all four CB will open]


To Improve reliability we need to add a tiebreaker connecting the two half



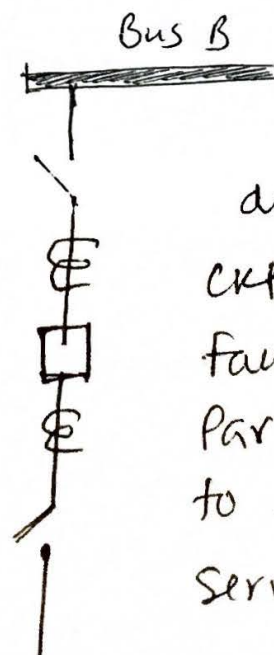Each side of bus including tiebreaker will be operated by separate relay




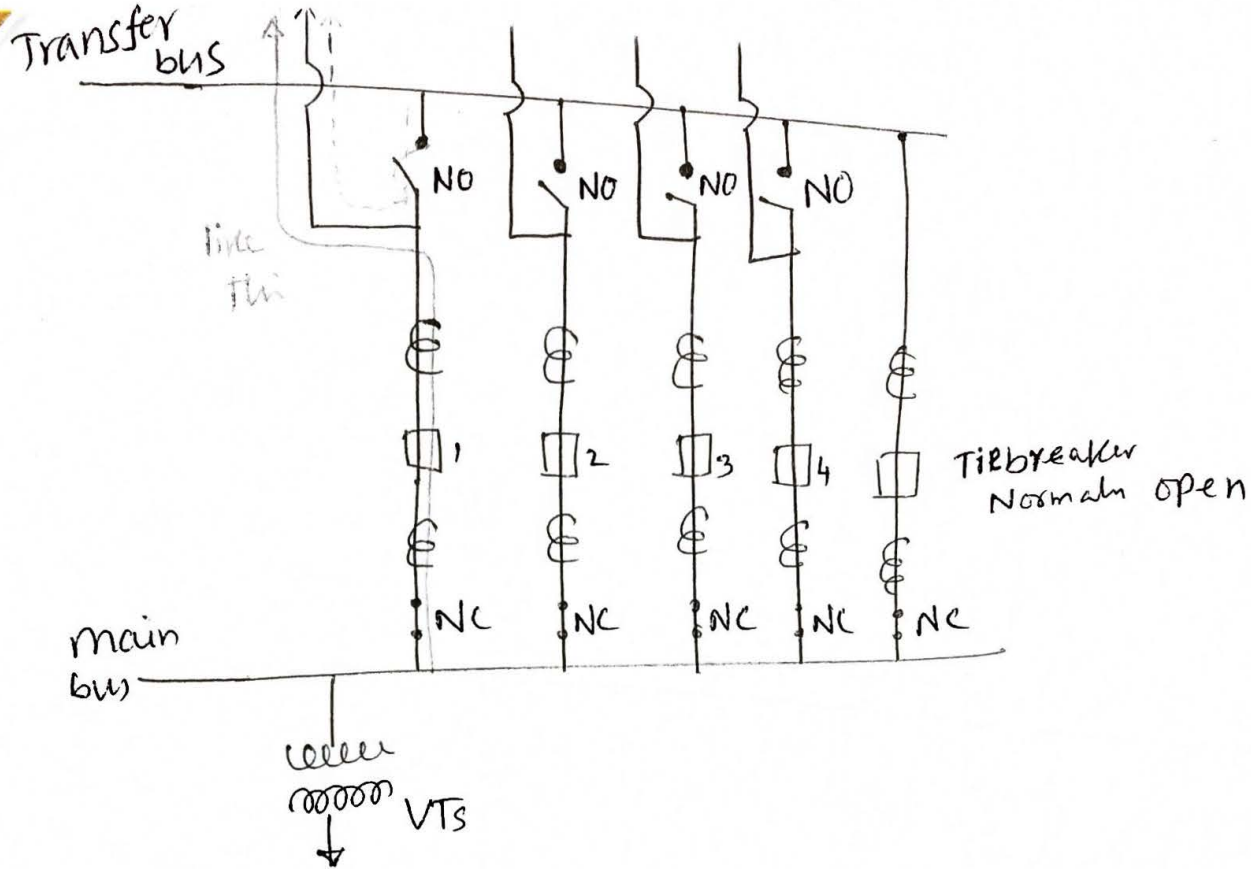as one CB in Each ckt so due to any fault only this Particular line need to be taken out of service for maintenance



The ckt Disconnect are arrange so that any line can feed into the main bus through CB (→) or <sup>Direct to the Trans bus</sup> (---)

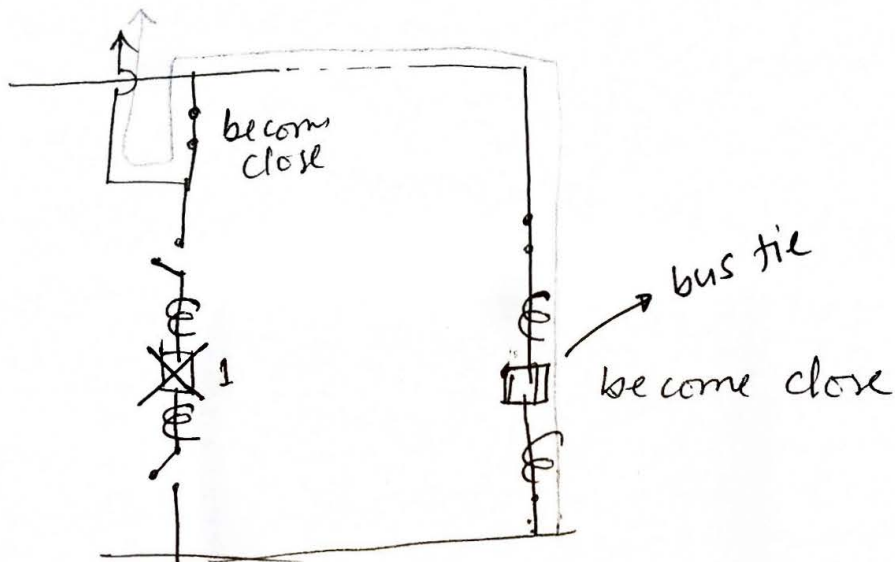suppose we need to isolate CB1 for maintenance  
In this situation




In this config the Transfer bus act as part of protection. so for the line and protected by Line protection. so for the Price of one CB we can substitute any one of line Breakers

Problem  
Cone can easily forget  
to change or  
the incorrect  
settings]


transfor bus bar is not a true bus bar as  
it never can connect more than one ckt

## True double bus arrangement

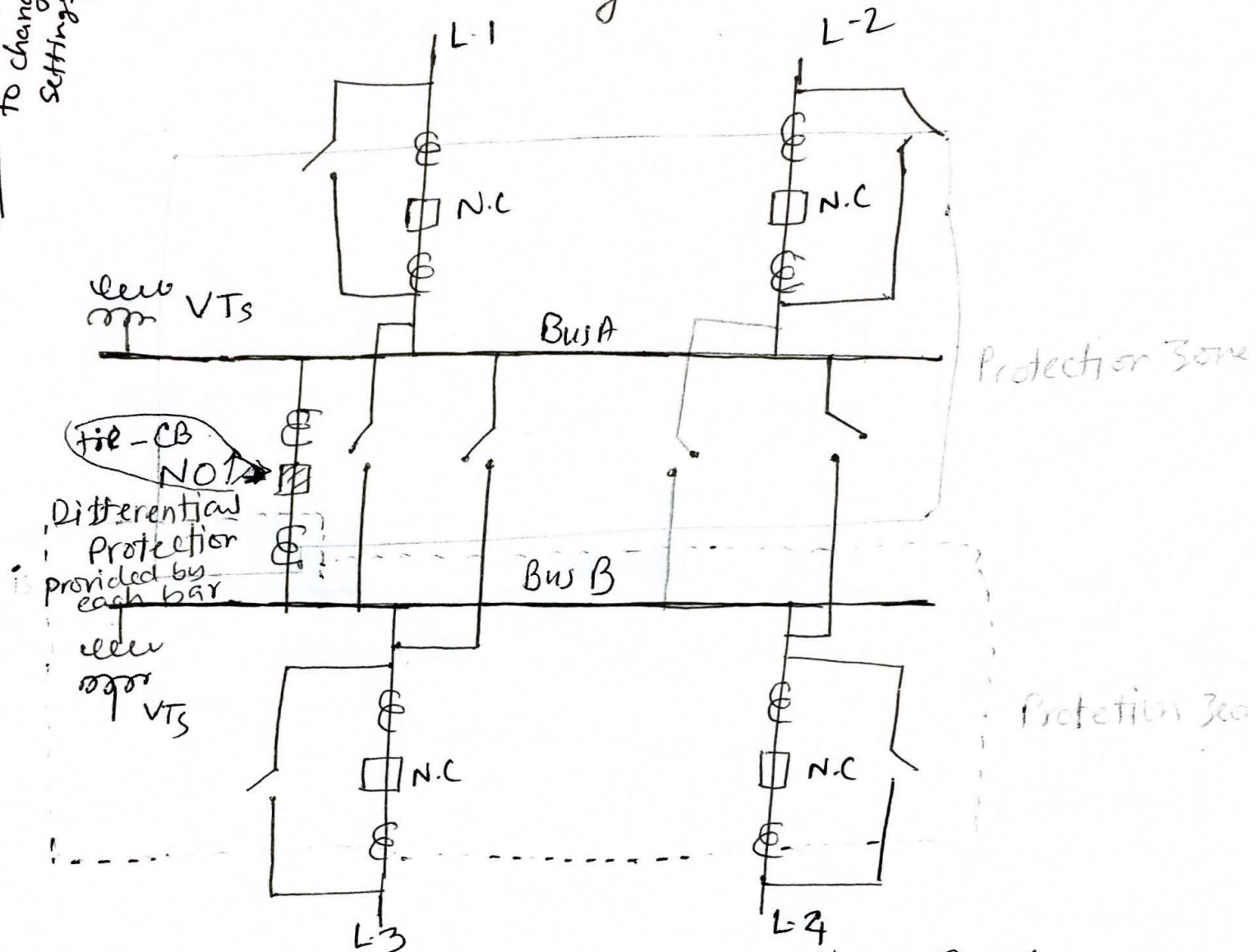

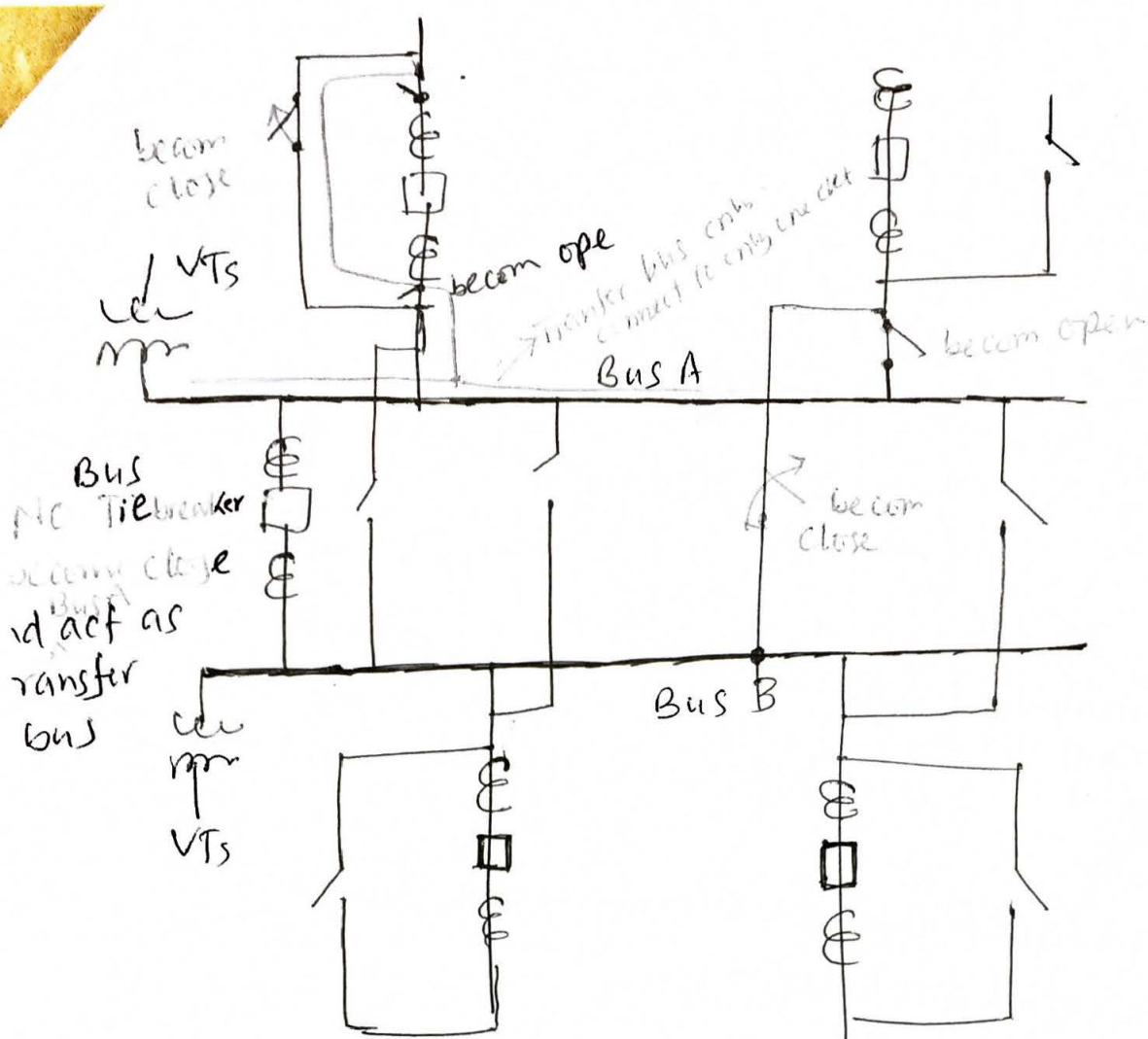Each ckt can be connected to either Bus A or Bus B. For simplicity we are showing only two line to each bus bar. In practice there could be many more.







we wish to remove CB1 So all of the remainin  
ckt is now connected to Bus B.


before closing Tiebreaker differential protection must be closed  
disabled otherwise unbalance current might arise  
and bus tie need to be adaptable for all line
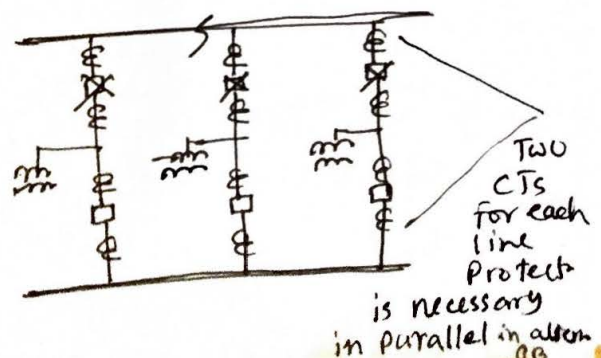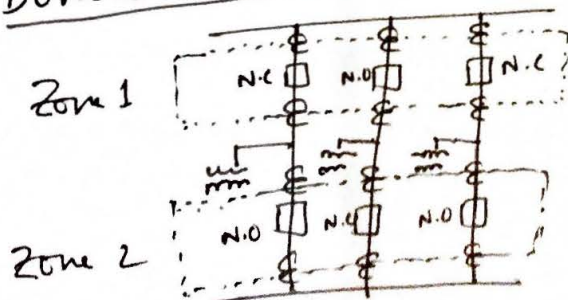
### Double breaker double bus arrangement




Two CTs for each line  
Protect in parallel in all

## Breaker and half diagram

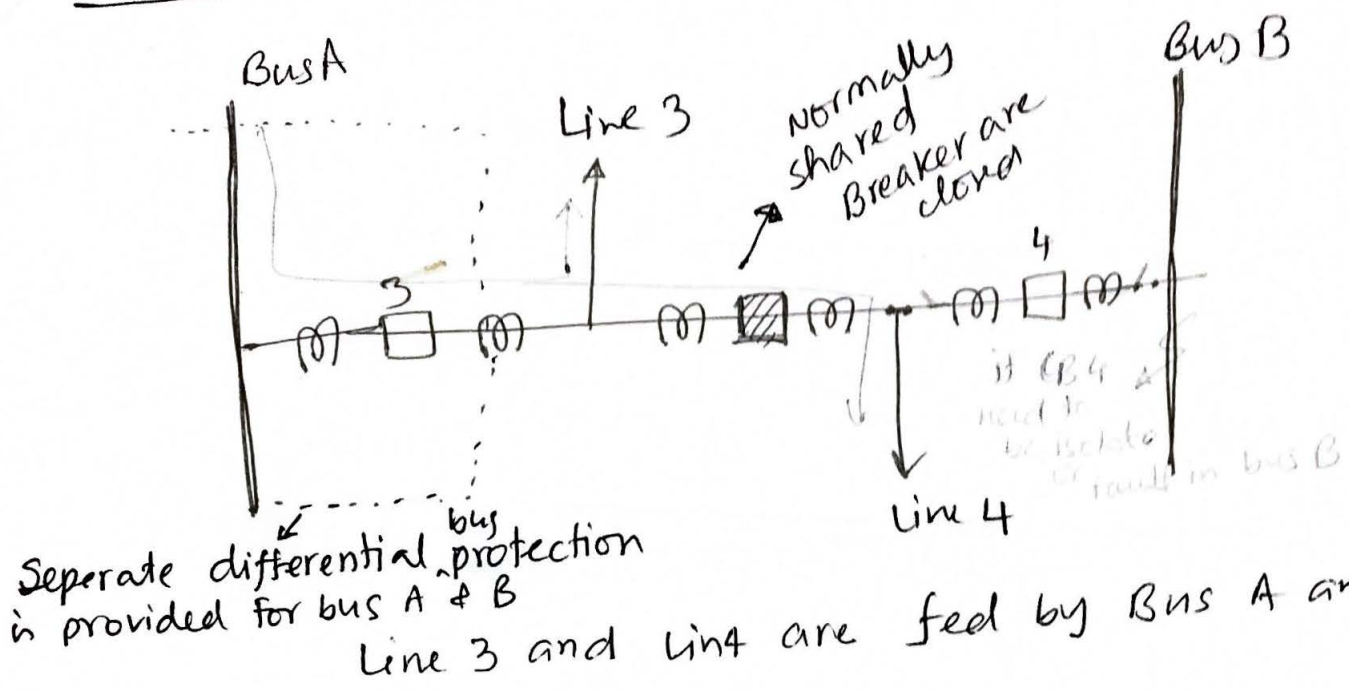

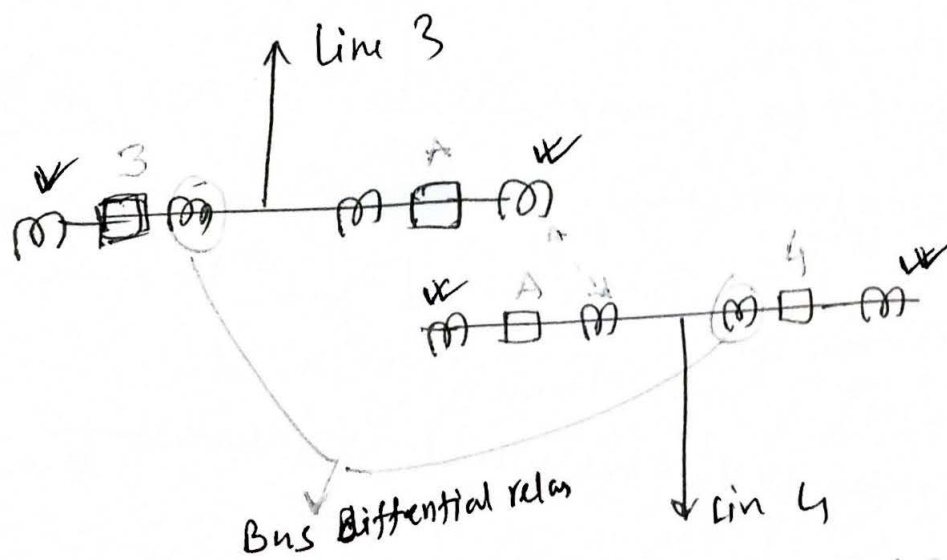
CTs are installed to provide both line and bus differential protection




Bus diff rels are served by outboard CTs of line breakers - bus breakers

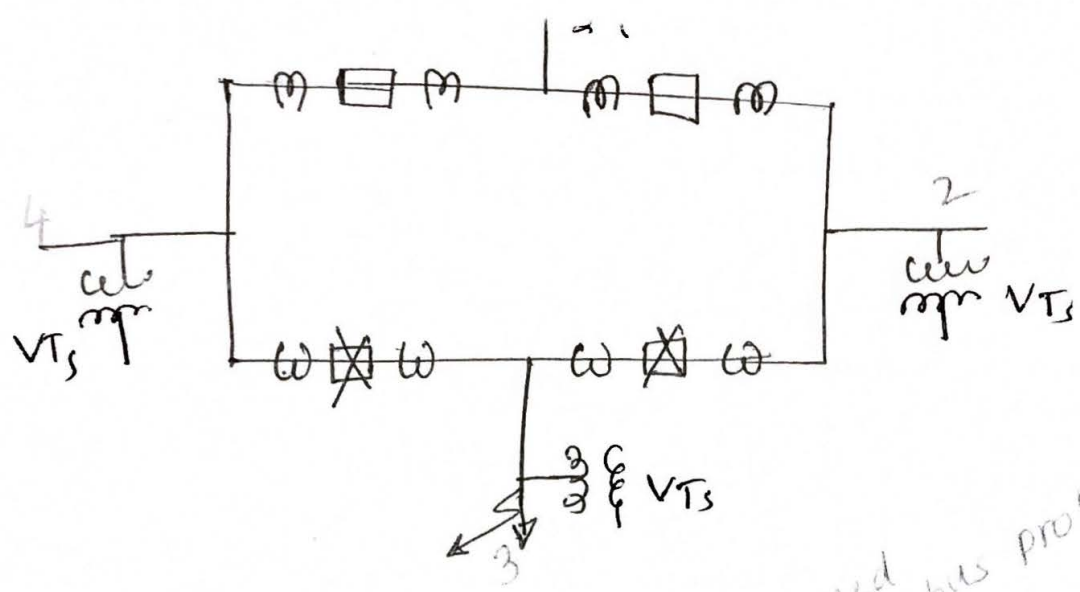if Breaker 4 need to isolate for maintenance purpose  
CB4 will only open. line 3 and 4 will feed by  
bus A.






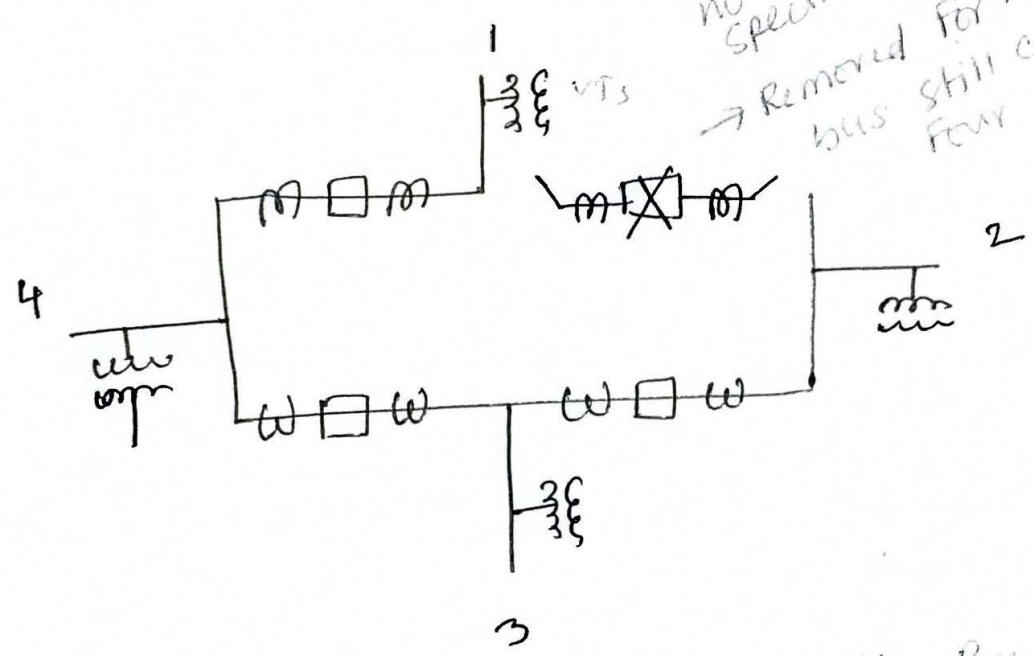
no need special bus protection for this arrangement  
 → Removed for maintaining bus still connected to four ckt  
 so it is now open bus



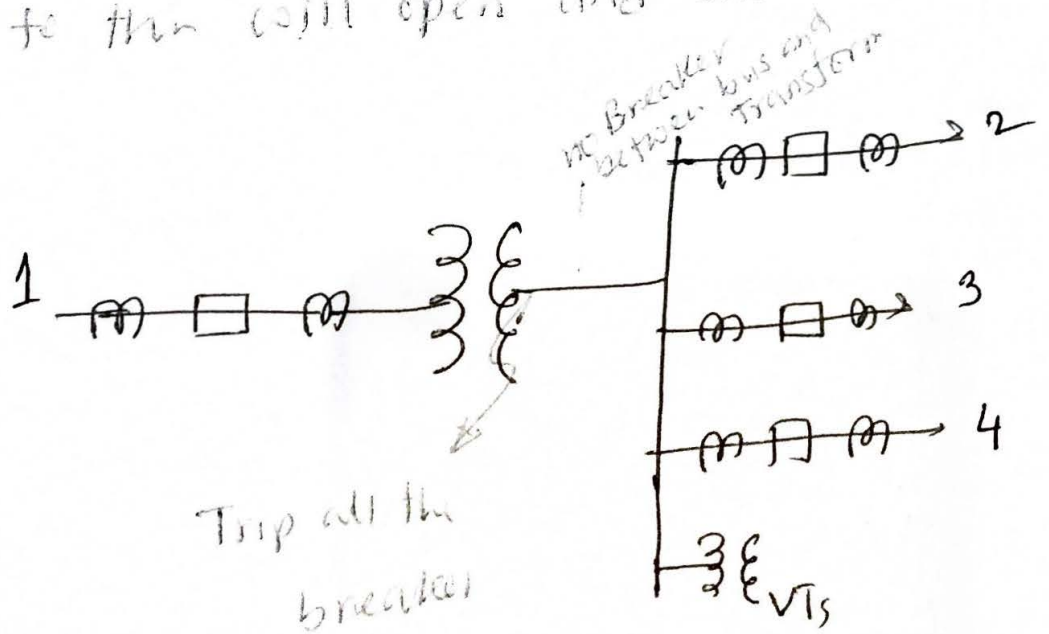
if fault occur at line 3 both Breakers related to this will open and bus will be split.



Trip all the breaker

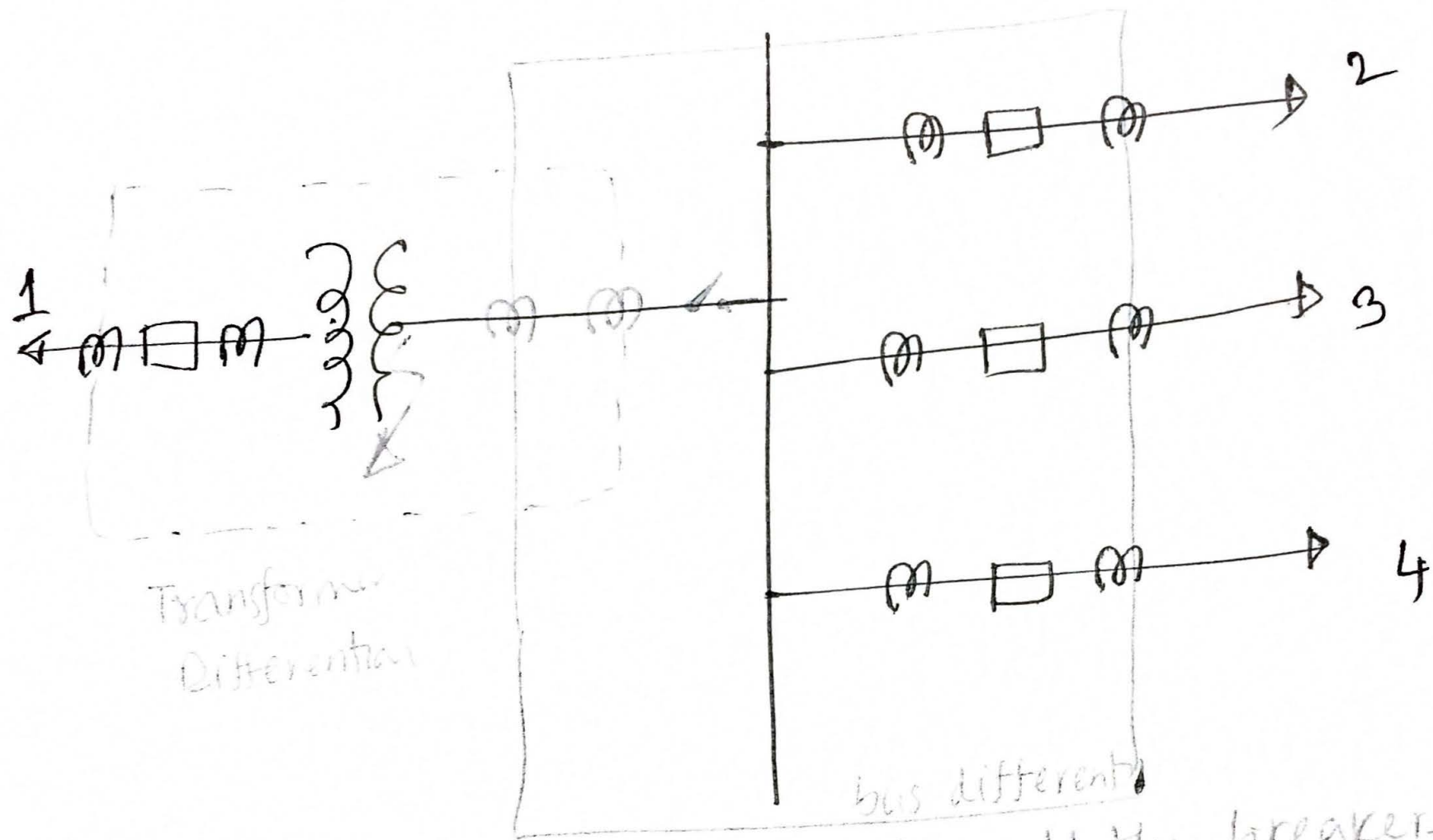

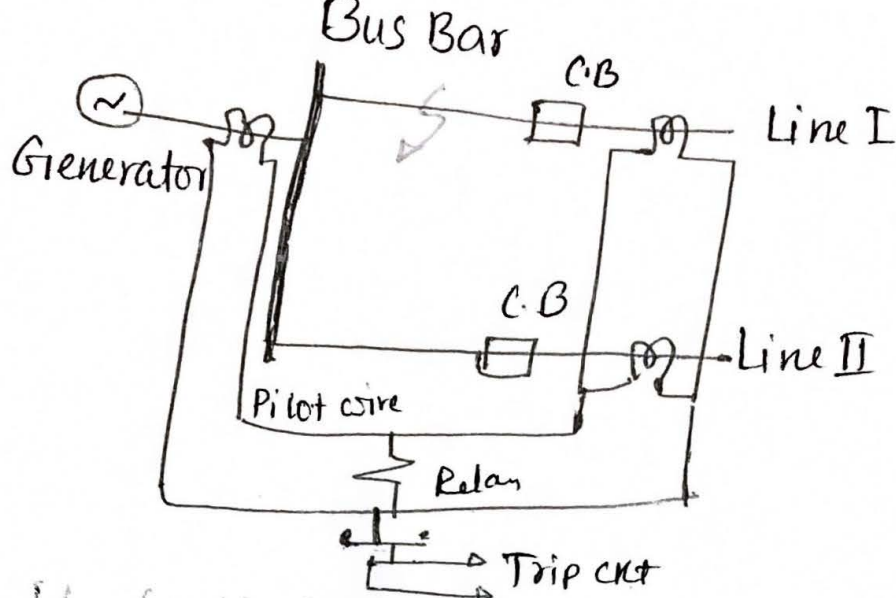fault at Transformer will trip all the breakers as disconnected previous but after that a motor operated switch will be open and the bus put back in the service



If fault occurs at line I, current at bus bar will be greater than rated current.

So current will flow through CTs and relay got excited. So CB will be open and busbar will be protected.

### Time graded system

