

Assignment-2

Marks: $30 \times 4 = 120$

Submission Deadline (18th August Thursday)

No assignment will be marked/accepted after this date

Submission: online submission in canvas only

Attach your cover page and also this Question paper

Book: Introductory Circuit Analysis by Boylestad 11th Edition

Chapter 8 Example

8.11-8.15

8.16-8.18 (Solve the problems using general approach)

8.20-8.21

8.23-8.26 (Solve the problems using general approach)

8.27-8.29

Total 17 problems from chapter 8

Chapter 9 Example

9.1-9.8

9.10-9.13

9.17

Total 13 problems from chapter 9

Total $17+13=30$ Example problem from chapter 8 & 9