



Performance 3

Department of Electrical & Computer Engineering

North South University

Submitted By

Name: Mohammed Mahmudur Rahman

Student ID: 1520386043

Course: Electrical Circuits (EEE141)

Section: 05

Faculty Advisor

Syeda Sarita Hassan (SSH1)


Problem 1.

Here,

$$8\Omega \parallel 8\Omega = 4\Omega$$


$$\text{So, } I = \frac{E}{R_T} = \frac{30V}{4\Omega + 6\Omega} \text{ A}$$

$$= 3A$$

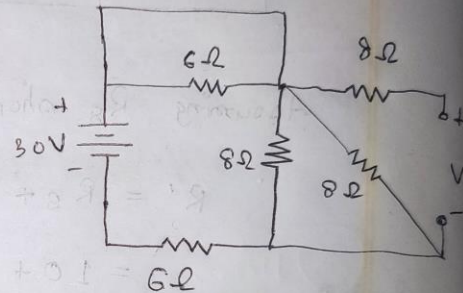

$$\therefore V = I(8\Omega \parallel 8\Omega) = (3A)(4\Omega) = 12V$$

Problem #2

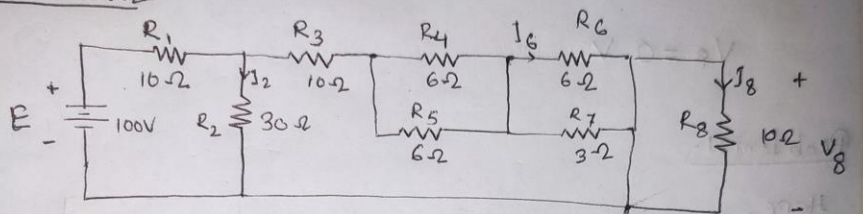

Assuming R_8 shorted,

$$\begin{aligned} R' &= R_3 + (R_4 \parallel R_5) + (R_6 \parallel R_7) \\ &= 10 + (6 \parallel 6) + (6 \parallel 3) \\ &= 15 \Omega \end{aligned}$$

$$\begin{aligned} R_T &= R_1 + R_2 \parallel R' \\ &= 10 \Omega + 30 \parallel 15 = 10 \Omega + 10 \Omega = 20 \Omega \end{aligned}$$

$$I = \frac{E}{R_T} = \frac{100}{20 \Omega} = 5A$$

$$I_2 = \frac{I}{R' + R_2} (R') = \frac{5}{15 + 30} (15) = 1.67A$$

$$\text{So, } I_3 = I - I_2 = 5 - 1.67 = 3.33 \text{ A}$$

$$I_G = \frac{(R_7)(I_3)}{R_7 + R_6} = \frac{(3\Omega)(3.33\text{A})}{3\Omega + 6\Omega} = 1.11 \text{ A}$$

$$I_8 = 0 \text{ A}$$

$$\text{Again, } V_4 = I_3 (R_4 \parallel R_5) = (3.33\text{A})(3\Omega) = 10 \text{ V}$$

$$V_8 = 0 \text{ V}$$