



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Code:EEE362 L

Course Title: Power system

Course Instructor: Mohammed Shafayet Hossain

Experiment Number:05

Experiment Name:

Phase Angle and voltage Drop between Sender and Receiver

Date of Experiment:07/09/2020

Date of Submission: 21/09/2020

Section:02

Group Number:

Submitted By : Mohammad Mahmudur Rahman

Score

	Student Name	ID
1.	Md: Redwan	1512863643
2.	Mohammed Mahmudur Rahman (W)	1520386043
3.	Md: Mynul hasan	1521629043
4.	Zahirul Hasan Zim	1411822043
5.	Md:Mamun alam	1620299643

Objective:

- i) To regulate the receiver end voltage.
- ii) To observe the phase angle between the voltages at the sending and the receiving end of the transmission line.
- iii) To observe the line voltage drop when the sending and receiving end voltages have same magnitude.

Theory:

If there is a voltage drop at the end of a transmission line, this would be harmful in practical conditions. As, motors, relays & lot other equipments work properly under a suitable voltage, thus, to keep the receiving end voltage at a constant value we need to regulate the voltage at receiving end.

Voltage regulation in regulated power supplies refers to maintain voltage at a desired level.

Voltage Regulation can be defined as following equation:

$$\text{percentage VR} = \frac{|V_{nl}| - |V_{fl}|}{|V_{fl}|} \times 100\%$$

Required Equipments:

- ① Resistive load (model 8311)
- ② Three Phase Transmission line (model 8329)
- ③ Capacitive load (model 8331)
- ④ AC Voltmeter (model 8426)
- ⑤ Three Phase Wattmeter/Varmeter (model 8446)
- ⑥ Phase meter (model 8451)
- ⑦ Power Supply (model 8821)
- ⑧ Connection leads (model 9128)

Circuit Diagram:

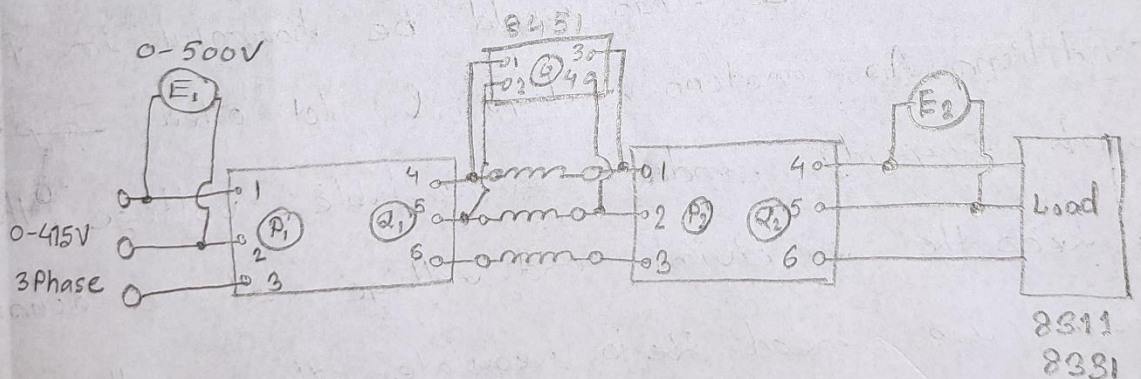


Figure: Circuit Diagram

Data table :

Voltage Regulation with Resistive load.								
R	X_L	E_1	P_1	Q_1	E_2	P_2	Q_2	Angle
Ω	Ω	V	W	Var	V	W	Var	$^\circ$
∞		350	0	0	350	0	0	0
4800		350	12	0	330	0	0	0
2400		350	25	0	305	20	0	0
1600		350	30	0	300	25	0	0
1200		350	80	10	300	75	0	15
960		350	90	20	305	80	0	15
800		350	98	30	290	95	0	16
686		350	100	30	280	92	0	16

Voltage Regulation with Resistive load.									
R	X_L	E_1	P_1	Q_1	E_2	P_2	Q_2	Angle	
Ω	Ω	V	W	Var	V	W	Var	$^\circ$	
∞	0	250							
4800	0	350	28	0	320		0		
2400	685.71	350	28	0	310	20	0	36 $^\circ$	
1600	685.71	350	100	-100	350	80	-255	24 $^\circ$	
1200	342.9	350	180	-150	350	180	-100	33 $^\circ$	
960	1200	350	110	0	340	100	-50	20 $^\circ$	
800	1200	350	130	10	340	110	-60	20 $^\circ$	
686	600	350	150	0	345	135	-75	18 $^\circ$	

Calculations:

(a) Reactive Power

$$Q_c = \frac{E_1 E_2 \cos \delta}{x} - \frac{E_2^2}{x}$$

Now,

$$P = \frac{E_1 E_2 \sin \delta}{x}$$

$$S_0, 50 \times 10^6 = \frac{100 \times 100 \times 10^6}{100} \sin \delta$$

$$\text{So, } \delta = 30^\circ$$

$$\therefore \cos 30 = 0.867$$

$$\therefore Q_c = \frac{100 \times 100 \times 0.87 \times 10^6}{100} - \frac{100^2 \times 10^6}{100} = -13.4 \times 10^6 = -13.4 \text{ MW}$$


(b)

Again,

Reactive Power at sender end,

$$\frac{E_1^2}{x} - \frac{E_1 E_2 \cos \delta}{x} = 13.4 \text{ MW}$$

(c)

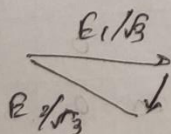

$$E_3 = \text{voltage drop per phase} = \frac{2}{\sqrt{3}} E_1 \sin \frac{\delta}{2} = 29.89 \text{ kV drop}$$

(d) Phase angle between sender & receiver voltage,
 $\delta = 30^\circ$

③ Apparent Power supply by sender.

$$S_1 = \sqrt{P_1^2 + Q_1^2}$$

$$= \sqrt{(50)^2 + (13.4)^2 + 100} = 51.8 \text{ MVA}$$


Answer to question NO:3

Yes, it is possible to raise the receiver end voltage by using static capacitors.

As the transmission line is purely resistive, then, Reactive power absorbed by transmission line is zero.

$$\Rightarrow \Phi_{abs} = 0$$

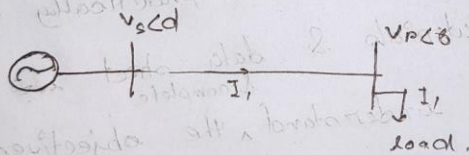As a static capacitor is added at the receiving end of the transmission line, this capacitor supplies reactive power to the transmission line.



Receiving end voltage $= V_r$.

$$|V_r| = |V_s| - \frac{|X|}{|V_s|} Q \quad \left[\begin{array}{l} X = \text{reactance} \\ V_s = \text{sending end voltage} \end{array} \right]$$

$$\Rightarrow |V_r| = |V_s| - \frac{|X|}{|V_s|} (Q_{abs} - Q_{gen} - Q_{sh, cap})$$

$$\Rightarrow V_r = |V_s| - \frac{|X|}{|V_s|} (-Q_{gen} - Q_{sh, cap}) \quad [Q_{abs} = 0]$$

$$\Rightarrow |V_r| = |V_s| + \frac{|X|}{|V_s|} (Q_{gen} + Q_{sh, cap})$$

$Q_{gen} \rightarrow$ Reactive power supplied by generator

Discussion:

The experiment was based on practically observing the regulation of receiver end voltage, & observing the phase angle between the voltages of the sending and the receiving end. Due to pandemic situation, we could not observe practically but, ^{from} ~~as per~~ video lesson, tutorials & data sheet ^{& complete} we we can say we have understood the objectives. We have successfully able to calculate the values of sender and receiving end voltages & also calculated the phase angle between them.

$$[0 = 200^\circ]$$