

Fall 2021  
EEE/ETE 141L  
Electrical Circuits-I Lab(Sec-5)  
Faculty : Md. Abu Obaidah (AbO)  
Instructor: Farhana Atuyar Saleh

Lab No. : 01

Date of Performance : 3/11/2021

Date of Submission : 10/11/2021

**Name:**

- 1. Tahsin Tabassum Ali**
- 2. Tabassoom Rahman**
- 3. Kanta Saha**

**ID:**

- 1. 2011059642**
- 2. 2011062642**
- 3. 2011731642**

## Experiment 1:

### Experiment name: Verification of Ohm's Law


#### Objectives:

- We have to find the resistance of a resistor from its color code.
- We have to measure voltage, current and resistance values using a digital multimeter.
- We have to verify the validity of Ohm's Law.
- We have to test the voltage divider rule in a series circuit.

#### List of equipment:

- Trainer board
- Resistors ( $3.3\text{ K}\Omega$ ,  $5.6\text{ K}\Omega$ )
- Digital Multimeter (DMM)
- Connecting Wire
- Multisim

#### Circuit diagram:

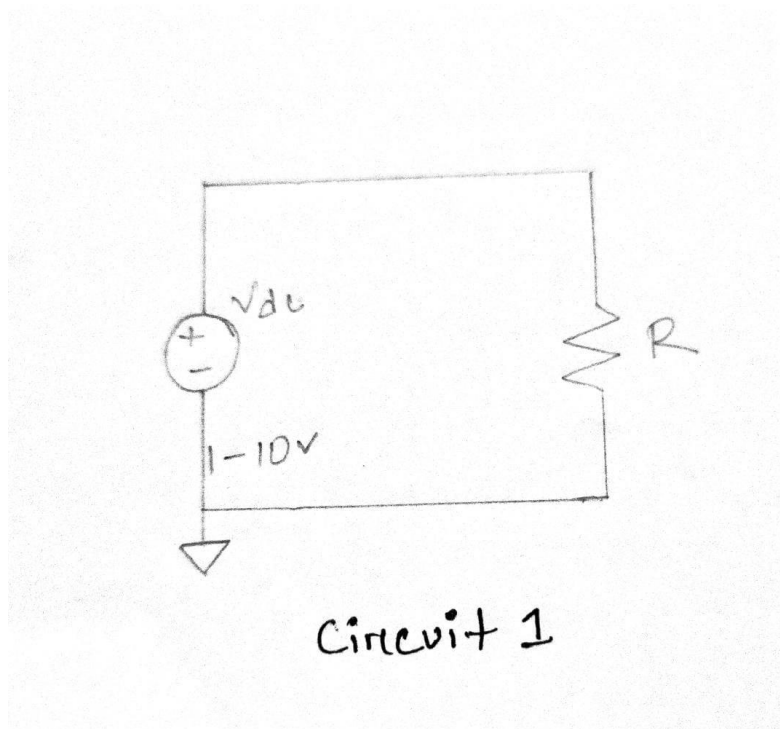

Data table:

Table 1:

Resistance using colour coding					Resistance using DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance $\pm$ tol		
Orange	Orange	Red	Gold	3.3k+-5%	3.3k	0%
Green	Blue	Red	Gold	5.6k+-5%	5.6k	0%

Table 2:

3.3 K $\Omega$ Voltage	Experimental readings		
	Current, I	Voltage, I R	Power, I <sup>2</sup> R (mW)
2	.606 mA	2 V	1.212
4	1.212 mA	4V	4.818
6	1.818 mA	6 V	10.908
8	2.424 mA	8 V	19.392
10	3.03 mA	10 V	30.3

Table 3

5.6 K $\Omega$ Voltage	Experimental readings		
	Current, I	Voltage, I R	Power, I <sup>2</sup> R(mW)
2	.357 mA	2V	.714
4	.714 mA	4V	2.856

6	1.071 mA	6V	6.426
8	1.429 mA	8V	11.432
10	1.786 mA	10V	17.86

Results:

From table 2,

Where  $V=2\text{ V}$ ,  $I = .606\text{ mA}$

Power,  $I^2R = 2*0.606 = 1.212\text{ mW}$

From table 3,

Where  $V=8\text{ V}$ ,  $I = 1.429\text{ mA}$

Power,  $I^2R = 8*1.429 = 11.432\text{ mW}$

Question/Answer:

### 1. State Ohm's law.

**Ans:**

Ohm's law states that the voltage  $v$  across a resistor is directly proportional to the current ( $I$ ) flowing through the resistor.


That is,  $V \propto I$

Ohm defined the constant of proportionality for a resistor to be the resistance,  $R$ . (The resistance is a material property which can change if the internal or external conditions of the element are altered, if there are changes in the temperature.).

So, the equation is  $V = IR$ .

2. Plot V vs I graph for each resistor value in same graph.

Ans:

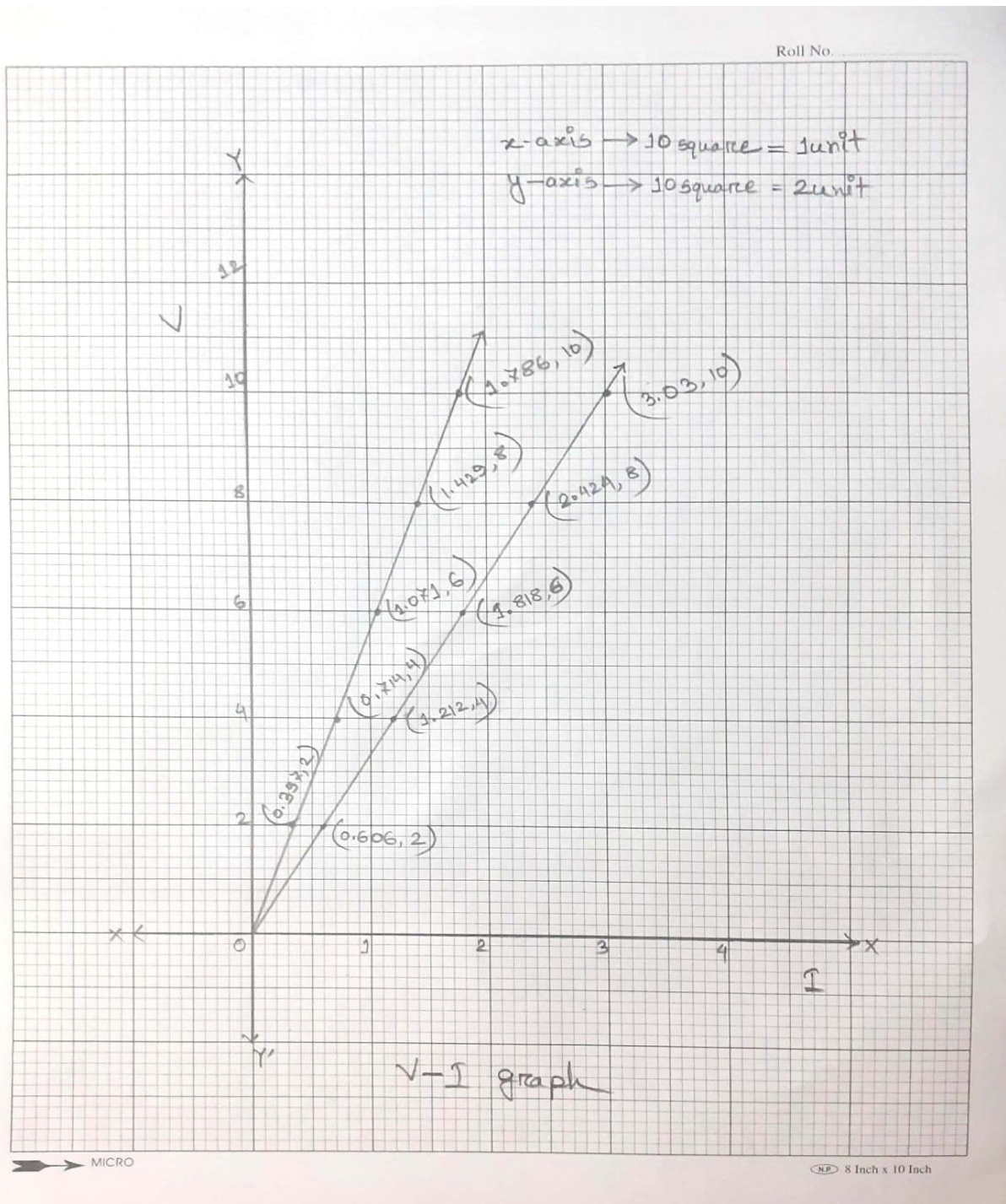

**3. Does your experimental circuit follow ohm's law? Explain how you figured it out.**

**Ans:**

Yes, my experimental circuit follow ohm's law.

Ohm's law states that the voltage  $v$  across a resistor is directly proportional to the current  $I$  flowing through the resistor. From Data table 2, we can see that when voltage is 6 V, current passing through the resistor is 1.818 mA. When the voltage is decreasing to 4 V, current passing is decreasing to 1.212 mA. And when voltage is increasing to 8 V, current passing is also increasing to 2.424 mA.

From data table 3, we can see that when voltage is 6 V, current passing through the resistor is 1.071 mA. When the voltage is decreasing to 4 V, current passing is decreasing to 0.714 mA. And when voltage is increasing to 8 V, current passing is also increasing to 1.429 mA. So, it's following  $V \propto I$ .

**4. Calculate the resistance of each circuit using the slope of your V vs I graphs. Compare these R<sub>graph</sub> values to the measured R values using DMM. Find the percentage difference.**

**Ans:**

**Slope = Rise/Run**

For, the data table 2,

Using the slope of V vs I graphs,

$$\text{Resistance, } R = 2/.606 = 3.3\text{k}\Omega$$

$$R = 4/1.212 = 3.3\text{k}\Omega$$

$$R = 6/1.818 = 3.3\text{k}\Omega$$

$$R = 8/2.424 = 3.3\text{k}\Omega$$

$$R = 10/3.03 = 3.3\text{k}\Omega$$

R value from DMM is 3.3k $\Omega$ .

So, Error = 0%

For, the data table 3,

Using the slope of V vs I graphs,

$$\text{Resistance, } R = 2/.357 = 5.6\text{k}\Omega$$

$$R = 4/.714 = 5.6\text{k}\Omega$$

$$R = 6/1.071 = 5.6\text{k}\Omega$$

$$R = 8/1.429 = 5.6\text{k}\Omega$$

$$R = 10/1.786 = 5.6\text{k}\Omega$$

R value from DMM is 5.6kOhm.

So, Error = 0%

## Experiment 2

### Experiment name: Series Circuit


#### Objectives:

- We have to learn how to connect a series circuit on breadboard.
- We have to validate the voltage divider rules.
- We have to verify Kirchhoff's voltage law.

#### List of Components:

- Trainer board
- Resistors ( $3.3\text{ K}\Omega$ ,  $4.7\text{ K}\Omega$ ,  $5.6\text{ K}\Omega$ )
- Digital Multimeter (DMM)
- Connecting Wire
- Multisim

#### Circuit Diagram:

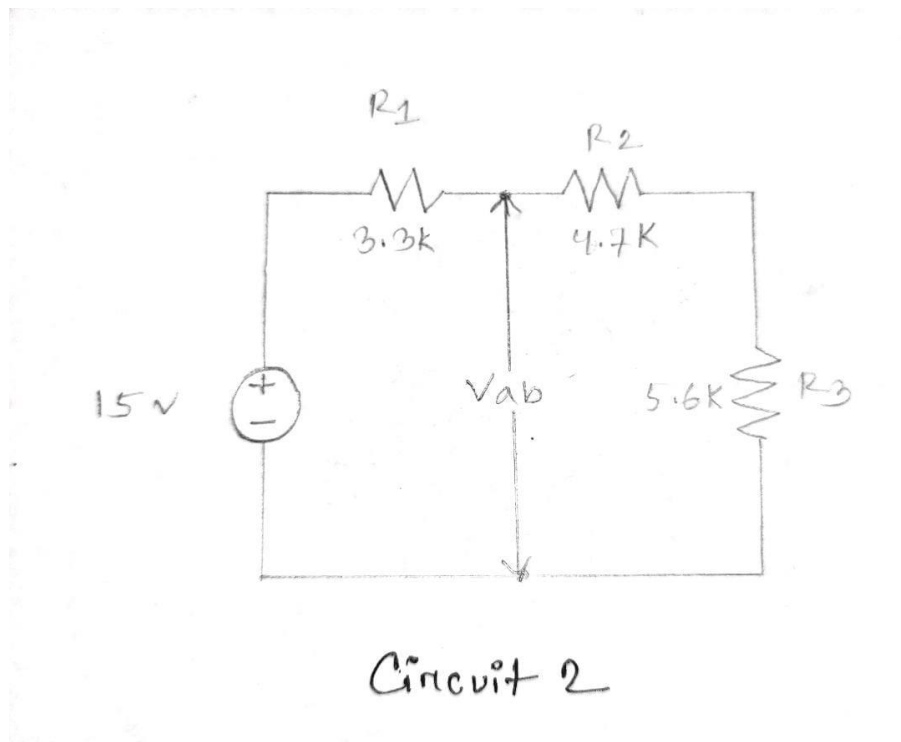



Data Table:

Table 1:

Resistance using colour coding					Resistance using DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance $\pm$ tol		
Orange	Orange	Red	Gold	3.3k $\pm$ 5%	3.3k	0%
Yellow	Violet	Red	Gold	4.7k $\pm$ 5%	4.7k	0%
Green	Blue	Red	Gold	5.6k $\pm$ 5%	5.6k	0%

Table2:

Experimental readings				Theoretical values			
$V_s$	$V_{R1}$	$V_{R2}$	$V_{R3}$	$V_s$	$V_{R1}$	$V_{R2}$	$V_{R3}$
15V	3.64V	5.184 V	6.176 V	15V	3.64V	5.18V	6.176
% Error							
$V_s$		$V_{R1}$		$V_{R2}$		$V_{R3}$	
0%		0%		0.077%		0.065%	

Table 3:

Potential rise $V_s$	15 V	Are the voltage rises and drops equal?
Potential drops ( $V_{R1} + V_{R2} + V_{R3}$ )	(3.64+5.184+6.176)=15V	Yes

Table 4

Experimental readings		Theoretical values	
$V_{ab}$	$R_{eq}$	$V_{ab}$	$R_{eq}$
11.36V	13.6k	11.36 V	13.6k
% Error			

$V_{ab}$	$R_{eq}$
0%	0%

Results:

$$V_X = (E \cdot R_X) / R_T$$

$$R_T = 3.3 + 4.7 + 5.6 = 13.6$$

$$V_{R1} = (3.3 \cdot 15) / 13.6 = 3.64$$

$$V_{R2} = (4.7 \cdot 15) / 13.6 = 5.18$$

$$V_{R3} = (5.6 \cdot 15) / 13.6 = 6.18$$

$$\% \text{ Error} = (\text{Theoretical value} - \text{Experimental Value}) / \text{Theoretical Value}$$

For  $V_s$ ,

$$\% \text{ Error} = (15 - 15) / 15 \cdot 100\% = 0\%$$

For  $V_{R1}$ ,

$$\% \text{ Error} = (3.64 - 3.64) / 3.64 \cdot 100\% = 0\%$$

For  $V_{R2}$ ,

$$\% \text{ Error} = ((5.184 - 5.18) / 5.18) \cdot 100\% = 0.077\%$$

For  $V_{R3}$ ,

$$\% \text{ Error} = ((|6.176 - 6.18|) / 6.18) \cdot 100\% = 0.065\%$$

$$V_{ab} = 5.18 + 6.18 = 11.36 \text{ V}$$

$$R_{eq} = 3.3k + 4.7k + 5.6k = 13.6k$$

Question/Answer:

**1. State the voltage division rule.**

**Ans:**

Voltage division rule states that the voltage is divided between two resistors which are connected in series in direct proportion to their resistance.

The equation is,  $V_x = (E \cdot R_x) / R_T$

**2. State the Kirchhoff's voltage law (KVL).**

**Ans:**

Kirchhoff's voltage law (KVL) states that the voltages around a closed path algebraically sum to zero. In other words, the sum of voltage rises equals the sum of voltage drops.

So, the equation is,

$$\sum_{m=0}^m V_m = 0$$

**3. Showing all steps, calculate the theoretical values in Table 2. Compare theoretical values to your experimental values and explain whether your circuit follows KVL or not.**

**Ans:**

$$V_X = (E \cdot R_X) / R_T$$

$$R_T = 3.3 + 4.7 + 5.6 = 13.6$$

$$V_{R1} = (3.3 \cdot 15) / 13.6 = 3.64$$

$$V_{R2} = (4.7 \cdot 15) / 13.6 = 5.18$$

$$V_{R3} = (5.6 \cdot 15) / 13.6 = 6.18$$

% Error = (Theoretical value – Experimental Value) / Theoretical Value  
For  $V_S$ ,

$$\% \text{Error} = (15 - 15) / 15 \cdot 100\% = 0\%$$

For  $V_{R1}$ ,

$$\% \text{Error} = (3.64 - 3.64) / 3.64 \cdot 100\% = 0\%$$

For  $V_{R2}$ ,

$$\% \text{Error} = ((5.184 - 5.18) / 5.18) \cdot 100\% = 0.077\%$$

For  $V_{R3}$ ,

$$\% \text{Error} = ((|6.176 - 6.18|) / 6.18) \cdot 100\% = 0.065\%$$

Here, Voltage rise = 15 V

Voltage drop =  $V_{R1} + V_{R2} + V_{R3} = (3.64 + 5.18 + 6.18) \text{ V} = 15 \text{ V}$

So, Voltage rise = Voltage drop

Which follows KVL.

**4. Showing all the calculations, theoretically calculate  $V_{ab}$ . Compare with the experimental value and verify the voltage division rule at the terminal a-b.**

**Ans:**

According to Voltage division rule,

$$V_X = (E \cdot R_X) / R_T$$

$$V_a = (15 \cdot 4.7) / (3.3 + 4.7 + 5.6)$$

$$= 5.18 \text{ V}$$

$$V_b = (15 \cdot 5.6) / (3.3 + 4.7 + 5.6)$$

$$= 6.18 \text{ V}$$

$$V_{ab} = 5.18 + 6.18 = 11.36 \text{ V}$$

From the experimental value of multisim we see that,  $V_{ab} = 11.36 \text{ V}$ .

Here, the error is 0%

So, Voltage division rule at the terminal a-b is verified.

**5. Showing all the steps, calculate  $R_{eq}$ . Compare with the experimental value.**

**Ans:**

By experimenting from multisim,  $R_{eq} = 13.6 \text{ k}\Omega$

$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$= (3.3 \text{ k} + 4.7 \text{ k} + 5.6 \text{ k}) \Omega$$

$$= 13.6 \text{ k}\Omega$$

So, Theoretical and experimental values for  $R_{eq}$  are the same.

So, there is 0% error.

**Discussion:**

From the lab 1, we learned about Ohm's law, Kirchoff's voltage law, and voltage divider rule using series circuit.

As, it was an online lab, we had to use multisim to do the experiments. So, we didn't have to face many errors or faults. We could find the theoretical values easily.

If we would have done the lab offline, we could have faced many errors such human errors, environmental errors or mechanical errors. Also, we could have faces errors using DMM, cables, breadboard connection etc.