
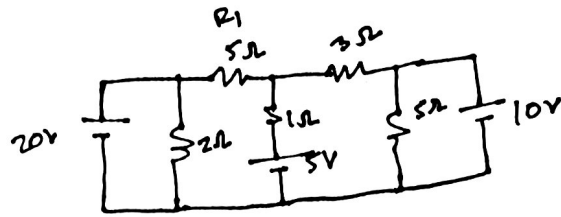




# Solution to Problem 1

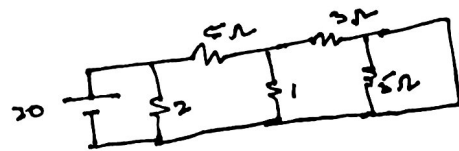

Using superposition and considering 20V source:



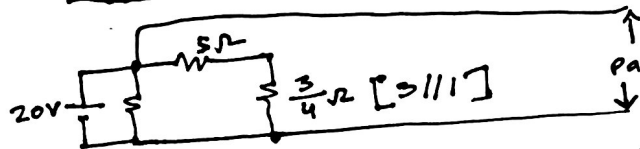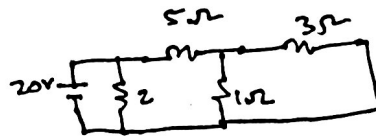
due to this short circuit the resistance  $R_4$  is ignored



Parallel to 20V



∴ drop across 5Ω and  $\frac{3}{4}\Omega$  is 20V.

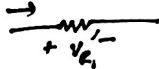∴ Applying VDR,  $V_{R1}' = \frac{5}{5 + \frac{3}{4}} \times 20 = 17.4V$



considering the 10V source:

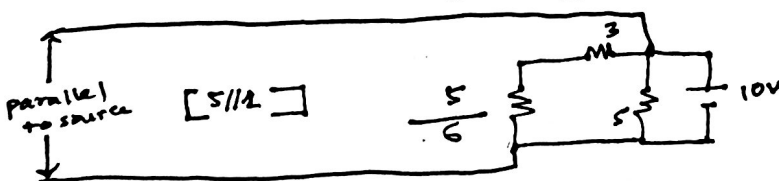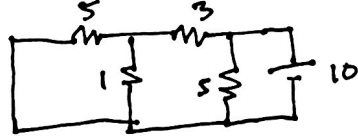due to this short the 2Ω resistance is shorted






drop across  $5/6\Omega$

$\frac{\frac{5}{6}}{3 + \frac{5}{6}} \times 10 = 2.17V$

$V_{R1}'' = 2.17V$




considering 5V source:

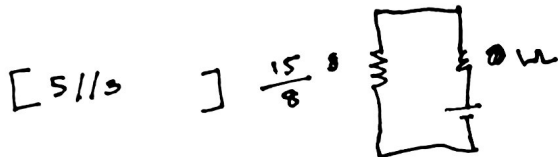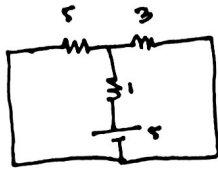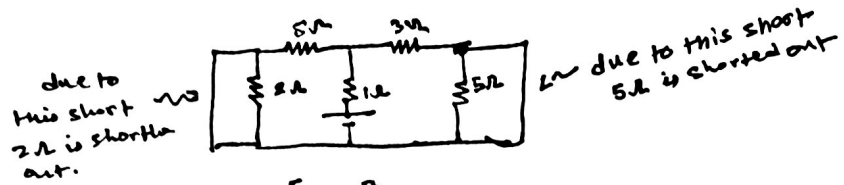

$$V_{R1}''' = \frac{15/8}{1 + 15/8} \times 5$$

$$\approx 3.26V$$

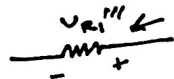

$$V_{R1} = \frac{V_{R1}'}{+ -} + \frac{V_{R1}''}{- +} + \frac{V_{R1}'''}{- +}$$

$$\therefore V_{R1} = 17.4 - 2.17 - 3.26$$

$$\approx 11.97V$$

