

Quiz - 03

Name: Masroor Mofiz Arman

ID: 1921079642

Course: CSE231

Section: 10

Date: 23-05-2021

Ans to the Q No: 01

Synchronous counter:

The flip flops within synchronous counters are all clocked at the same time by a common clock pulse.

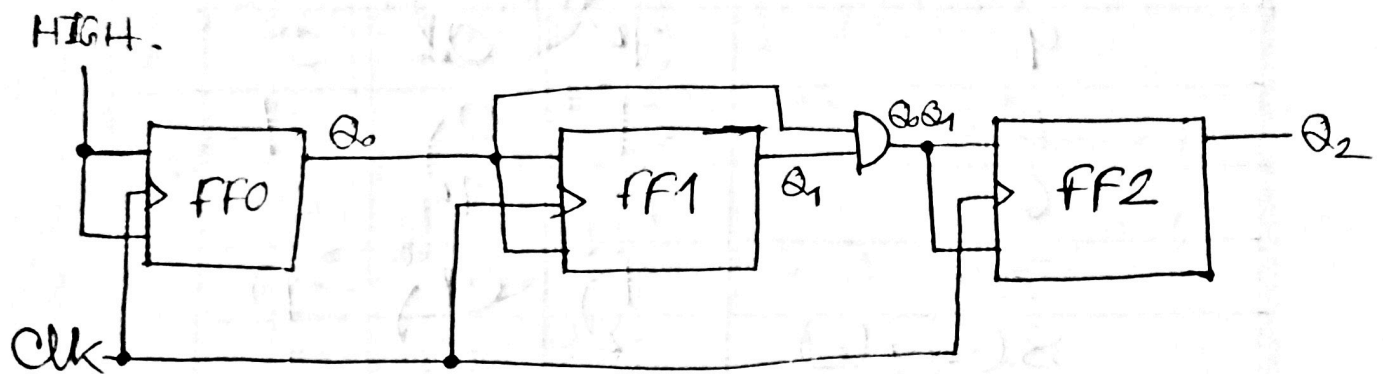


Figure : 3-bit synchronous counter.

where, $J_1 = K_1 = Q_0$

$$J_2 = K_2 = Q_0 Q_1$$

State sequence:

Clock phase	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

Ans to the Q NO: 03 (a)

(i) $256k \times 32$.

Number of words = $256k$.

Number of bits per word = 32

So, in $256k \times 32$ the number of address lines is an obtained number of words. that is,

$$256k = 2^8 \times 2^{10} = 2^{18}$$

Therefore, it requires 18 ~~lines~~, address lines.

\therefore The sum of address lines and the number of bits (data lines):

$$18 + 32 = 50.$$

\therefore it requires 50 I/O lines.

(Ans).

(ii) $16M \times 16$.

Number of words = $16M$.

Number of bits = 16 . (per word).

\therefore The number of address line is obtained number of words. that is:

$$16M = 2^4 \times 2^{20} = 2^{24}$$

\therefore it requires 24 address lines.

\therefore The sum of address lines and the number of bits:

$$24 + 16 = 40.$$

\therefore therefore, it requires 40 I/O lines.
(Ans).

(iii). $8k \times 8$.

Number of words = 8.

Number of bits per word = 8.

\therefore The number of address line is obtained number of words, that is,

$$8k = 2^3.$$

\therefore it requires 3 address lines.

\therefore The sum of address lines and the number of bits, that is,

$$3 + 8 = 11$$

Therefore, it requires 11/0 lines.

Ans to the Q No: 3 (b)


DFF requires 1 bit.

So, No of DFF requires for.

$$2^{18} \times 32 =$$

$$2^{24} \times 16 = 256 \text{ Million DFF}$$

$$2^{13} \times 8 = 64K \text{ DFF.}$$

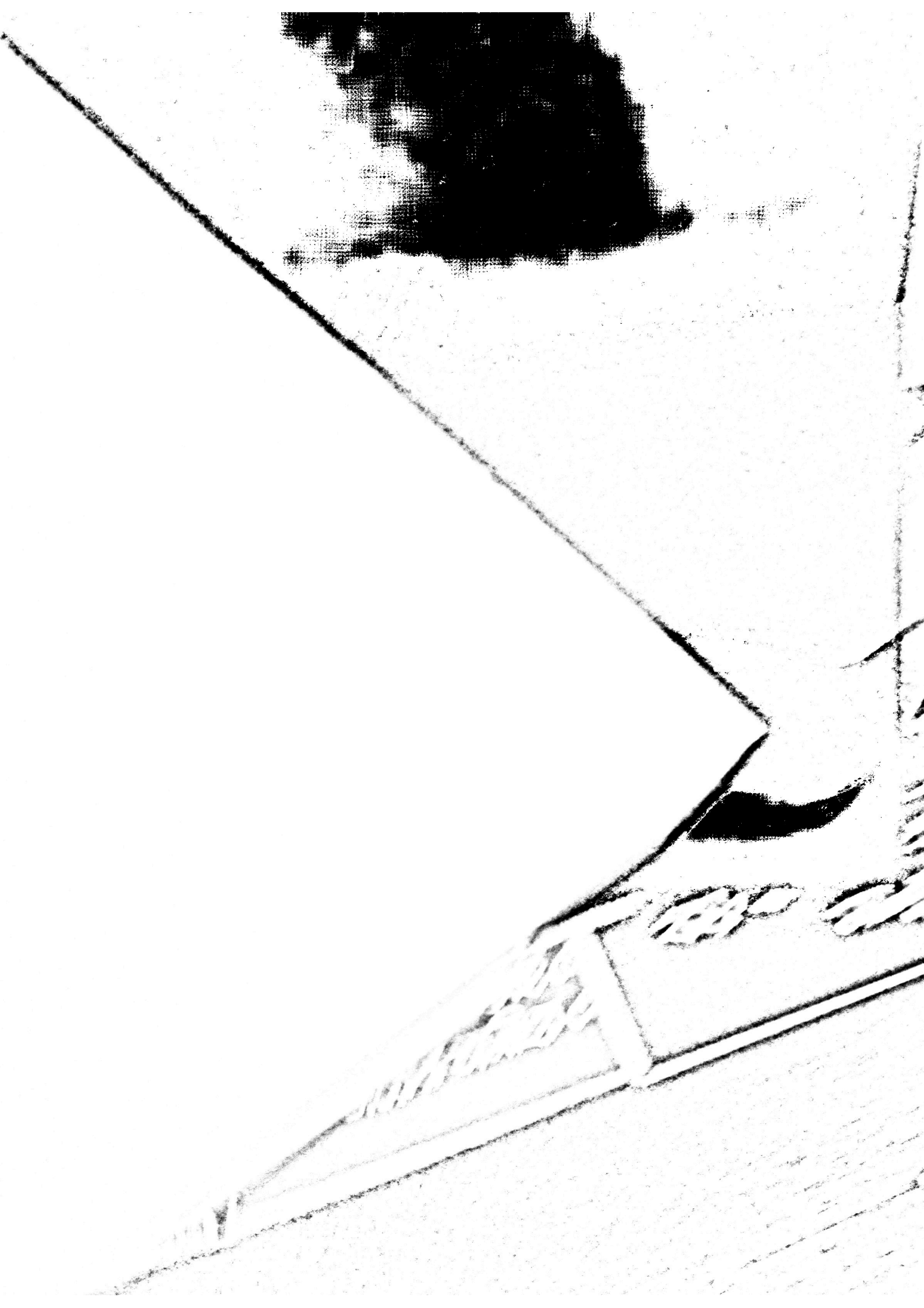

Ans to the Q No : 02

	<u>w</u>	<u>x</u>	<u>y</u>	<u>z</u>
Initial output	0	0	0	0
After T_1	1	0	0	0
After T_2	1	1	0	0

the value of wxyz after

2 successive cycles is 1100.