

SOLUTION


North South University
Fall 2021
EEE141 (sec - 5)
Midterm exam

Marks = 30

Time = 1 hour 15 minutes

1. (a) Calculate I_o in the following circuit.
(b) Calculate the power supplied by the source and absorbed by the $10\text{-}\Omega$ resistor.

[8]

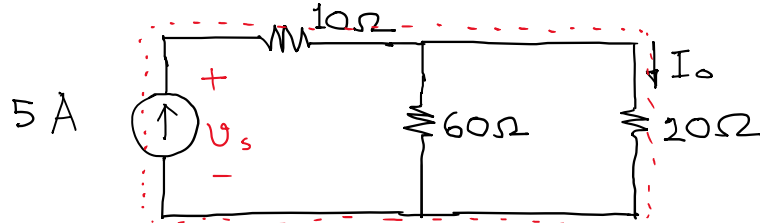

SOLUTION :

$$I_o = \frac{5 \times 60}{60 + 20} = 3.75 \text{ A}$$

$$P_R = 5^2 \times 10 = 250 \text{ W}$$


KVL at the outer loop.

$$-V_s + 5 \times 10 + 3.75 \times 20 = 0 \Rightarrow V_s = 125 \text{ V}$$

$$P_s = 125 \times 5 = 625 \text{ W}$$

2. In the following circuit, find the mesh currents using the mesh analysis.

[10]

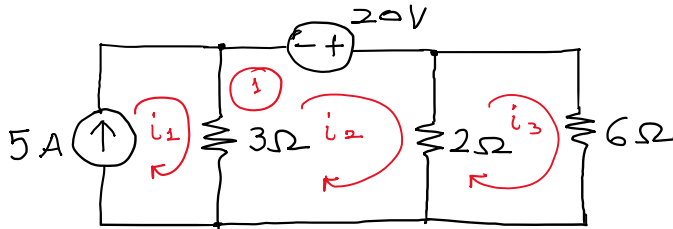

SOLUTION :

$$i_1 = 5 \text{ A}$$

KVL at mesh #2,

$$3(i_2 - i_1) - 20 + 2(i_2 - i_3) = 0$$

$$\Rightarrow -3i_1 + 5i_2 - 2i_3 = 20$$

$$\Rightarrow 5i_2 - 2i_3 = 35 \quad \text{--- (i)}$$

KVL at mesh #3,

$$2(i_3 - i_2) + 6i_3 = 0$$

$$\Rightarrow 8i_3 - 2i_2 = 0$$

$$\Rightarrow 4i_3 - i_2 = 0 \quad \text{--- (ii)}$$


$$\text{From (ii)} \Rightarrow i_2 = 4i_3 \text{ in (i)} \Rightarrow 20i_3 - 2i_3 = 35$$

$$\Rightarrow 18i_3 = 35$$

$$\Rightarrow i_3 = 1.94 \text{ A} \quad i_2 = 7.78 \text{ A}$$

3. Calculate the node voltages in the following circuit, using nodal analysis.

[12]

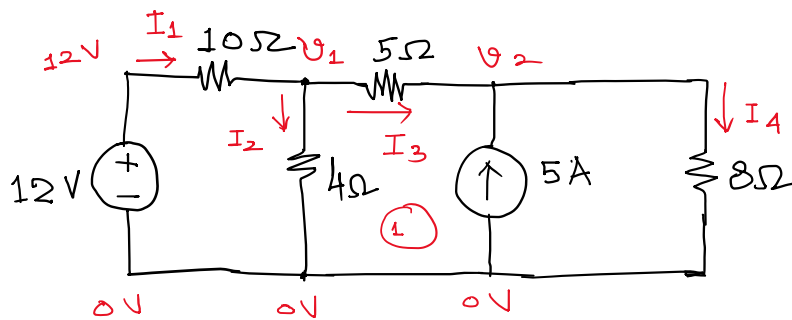

SOLUTION

$$\left\{ \begin{array}{l} I_1 = \frac{12 - V_1}{10} ; I_2 = \frac{V_1}{4} ; \\ I_3 = \frac{V_1 - V_2}{5} ; I_4 = \frac{V_2}{8} ; \end{array} \right.$$

KCL at node 1, $I_1 = I_2 + I_3$

$$\textcircled{1} \Rightarrow \frac{12 - V_1}{10} = \frac{V_1}{4} + \frac{V_1 - V_2}{5}$$

$$(\times 20) \Rightarrow 24 - 2V_1 = 5V_1 + 4V_1 - 4V_2$$

$$\Rightarrow 11V_1 - 4V_2 = 24 \dots \textcircled{i}$$

KCL at node 2, $I_3 + 5 = I_4$

$$\textcircled{2} \Rightarrow \frac{V_1 - V_2}{5} + 5 = \frac{V_2}{8}$$

$$(\times 40) \Rightarrow 8V_1 - 8V_2 + 200 = 5V_2$$

$$\Rightarrow 8V_1 - 13V_2 = -200 \dots \textcircled{ii}$$

$$\textcircled{3} \quad \textcircled{i} \times 13 \Rightarrow 143V_1 - 52V_2 = 312$$

$$\textcircled{ii} \times 4 \Rightarrow 32V_1 - 52V_2 = -800$$

$$(-) \quad 111V_1 = 1112 \Rightarrow$$

$$V_1 = 10.02V$$

$$\textcircled{i} \Rightarrow$$

$$V_2 = 21.55V$$

END