

Assignment-1

Marks: $21 \times 2 = 42$

Submission Deadline (18th November Wednesday)

No assignment will be marked/accepted after this date

1. Solve any three exercise problems from each of the following sections of Chapter-5 (Series DC Circuits)
5.2, 5.3, 5.4, 5.5, 5.6, 5.7, 5.9

Total 21 exercise problems from all the above sections

Note:

1. You have to write the Question and then write the Answer.
2. Do Not Copy Paste others problems. Your selection of problems should be different from others.
3. Attach your cover page and also this Question paper.