

<p>Fall 2021 EEE/ETE 141L Electrical Circuits-I Lab(Sec-5) Faculty : Md. Abu Obaidah (AbO) Instructor: Farhana Atuyar Saleh</p>
<p>Lab No. : 02</p>

<p>Date of Performance :10.11.2021</p> <p>Date of Submission :17.11.2021</p>	<p><b>Name:</b> <b>1. Tahsin Tabassum Ali</b> <b>2. Tabassoom Rahman</b> <b>3. Kanta Saha</b></p> <p><b>ID:</b> <b>1. 2011059642</b> <b>2. 2011062642</b> <b>3. 2011731642</b></p>
--	--

## Lab2: KCL, Current Divider Rule with Parallel and Ladder Circuit.

### Experiment 1


#### Objectives

- We have to connect a parallel circuit on a breadboard.
- We have to validate the current divider rules.
- We have to verify Kirchhoff's current law.
- We have to verify KCL and KVL in ladder circuit.

#### List of Components:

- Trainer board
- Resistors (1K, 3.3k, 4.7 K $\Omega$ , 5.6K, 10K)
- Digital Multimeter (DMM)
- Connecting Wire
- Multisim

#### Circuit Diagram:

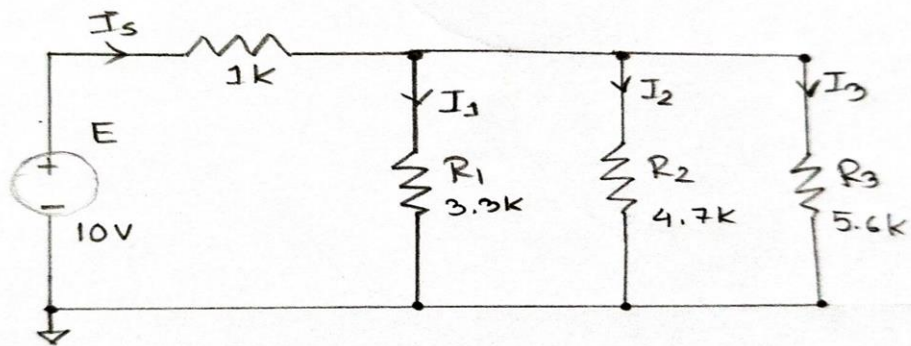

circuit 1

Data Table:

Table 1:

Resistance using colour coding					Resistance using DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance $\pm$ tol		
Brown	Black	Red	Gold	1 k $\Omega$ $\pm$ 5%	1 k $\Omega$	0%
Orange	Orange	Red	Gold	3.3 k $\Omega$ $\pm$ 5%	3.3 k $\Omega$	0%
Yellow	Violet	Red	Gold	4.7 k $\Omega$ $\pm$ 5%	4.7 k $\Omega$	0%
Green	Blue	Red	Gold	5.6 k $\Omega$ $\pm$ 5%	5.6 k $\Omega$	0%
Brown	Black	Orange	Gold	10 k $\Omega$ $\pm$ 5%	10 k $\Omega$	0%

Table 2:

Experimental readings				Theoretical values			
$I_s$	$I_{R1}$	$I_{R2}$	$I_{R3}$	$I_s$	$I_{R1}$	$I_{R2}$	$I_{R3}$
4.098mA	1.788mA	1.256mA	1.053mA	4.1mA	1.8mA	1.258mA	1.06mA
% Error							
$I_s$		$I_{R1}$		$I_{R2}$		$I_{R3}$	
0.0079%		0.017%		0.00158%		0.0060%	

Table 3:

$I_s$	4.098	Is Total Current equal to sum individual current?
Sum of individual Current ( $I_{R1} + I_{R2} + I_{R3}$ )	(1.788+1.256+1.053)k=4.098k	Yes

Table 4:

Experimental Req	Theoretical Req	% Error
2.44k	2.44k	0%

Result:

From table 2,

Here,

$$R_T = 3.3k // 4.7k // 5.6k = 1.44k$$

$$I_s = 10V / 2.44k = 4.1mA$$

$$R_{eq} = 1.44k + 1k = 2.44k$$

Now using  $I_X = I_s \cdot R_T / R_X$  we get theoretical values ,

$$I_{R1} = (4.1 \cdot 1.44) / 3.3k = 1.8 \text{ mA}$$

$$I_{R2} = (4.1 \cdot 1.44) / 4.7k = 1.258 \text{ mA}$$

$$I_{R3} = (4.1 \cdot 1.44) / 5.6k = 1.06 \text{ mA}$$

Again using % Error = (Theoretical value – Experimental Value) / Theoretical Value we get,

$$\% \text{ Error of } I_s = (4.1\text{mA} - 4.098\text{mA}) / 4.1\text{mA} = 0.0079\%$$

$$\% \text{ Error of } I_{R1} = (1.8\text{mA} - 1.788\text{mA}) / 1.8\text{mA} = 0.017\%$$

$$\% \text{ Error of } I_{R2} = (1.258\text{mA} - 1.256\text{mA}) / 1.258\text{mA} = 0.00158\%$$

$$\% \text{ Error of } I_{R3} = (1.06\text{mA} - 1.053\text{mA}) / 1.06\text{mA} = 0.0060\%$$

From table 3,

$$I_s = 4.098$$

$$\text{Sum of individual Current } (I_{R1} + I_{R2} + I_{R3}) = (1.788 + 1.256 + 1.053) \text{ mA} = 4.098 \text{ mA or } 4.1 \text{ mA}$$

From table 4,

$$\text{Experimental Req} = 2.44k$$

Now Theoretical Req,

$$R_T = 3.3k // 4.7k // 5.6k = 1.44k$$

$$R_{eq} = 1.44k + 1k = 2.44k$$

So,

Experimental Req = Theoretical Req with 0% Error.

## Experiment 2

### Objectives


- We have to connect a parallel circuit on a breadboard.

- We have to validate the current divider rules.
- We have to verify Kirchhoff's current law.
- We have to verify KCL and KVL in ladder circuit.

#### List of Components:

- Trainer board
- Resistors (1K, 3.3k, 4.7 K $\Omega$ , 5.6K, 10K)
- Digital Multimeter (DMM)
- Connecting Wire
- Multisim

#### Circuit Diagram:

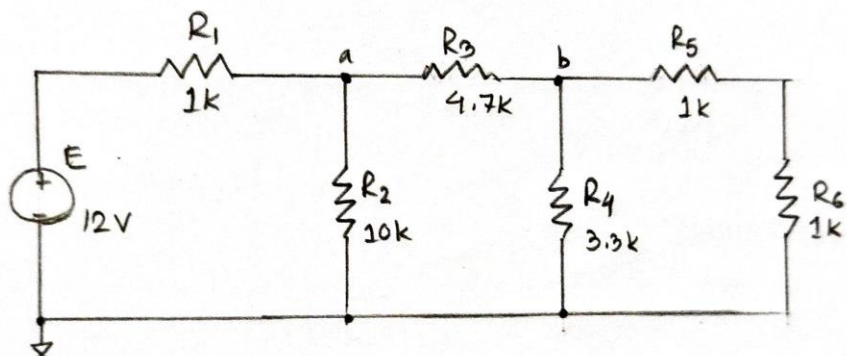

Circuit 2

Table 5:

Component	Voltage	Current
E	12	2.538A
R1	2.538V	2.538A
R2	9.462V	946.223uA
R3	7.48V	1.592mA
R4	1.982V	600.586uA
R5	990.967mV	990.996uA
R6	990.967mV	990.996uA

### Question/Answer

#### 1. State the current division rule.

**Answer:** Current Division rule states that the entire current separated into either of the parallel combination of two resistance or impedance is conversely corresponding to the esteem of resistance. It fundamentally tells us how the current is isolated within the parallel associated resistance.

#### 2.State the Kirchhoff's current law (KCL).

**Answer:** Kirchhoff's Current Law (KCL) states that “the algebraic sum of the currents entering and leaving a node is equal to zero.” This law is utilized to depict how a charge enters and takes off a wire junction point or node on a wire.

#### 3. With the experimental data, verify Kirchhoff's voltage law in Circuit 1 within each independent closed loop of the circuit.

**Answer:** We have to Kirchhoff's voltage law in Circuit 1 within each independent closed loop of the circuit.

Here,  $V=10V$

Now,

$$(10-V_x)/1k = V_x/3.3k + V_x/4.7k + V_x/5.6k$$

$$\rightarrow 10-V_x = (1/3.3k + 1/4.7k + 1/5.6k)V_x$$

$$\rightarrow 10 = V_x(1 + 0.303k + 0.21276k + 0.17857k)$$

So,  $V_x = 5.90 V$

$$I_s = (10 - 5.902)/1k = 4.098mA$$

Again,  $I = V_x/3.3k$

$$I_{R1} = 5.902V/3.3k = 1.788mA$$

$$I_{R2} = 5.902V/4.7k = 1.256mA$$

$$I_{R3} = 5.902V/5.6k = 1.053 mA$$

**4. With the experimental data, verify Kirchhoff's current law at nodes *a* and *b* of circuit 2.**

**Answer:** We have to apply KCL at node a,

$$2.538mA = 0.946mA + 1.592mA$$

$$\rightarrow 2.538mA = 2.538mA$$

So, Input current = Output Current

KCL is verified at node a.

Now, We have to apply KCL at node b,

$$\rightarrow 1.592 = 600.5 + 990.9$$

$$\rightarrow 1.592 = 1591.4$$

$$1.592 = 1.592$$

So, Input current = Output Current

KCL is verified at node b.



We can say that, Kirchhoff's current law is verified at nodes *a* and *b* of circuit 2.

Because output Current is equal to input Current.

**5. Showing all steps, calculate the theoretical values in Table 2. Compare theoretical values to your experimental values and explain whether your circuit follows KCL or not.**

**Answer:** We have to calculate the theoretical values in Table 2.

Here,

$$R_T = 3.3k // 4.7k // 5.6k = 1.44k$$

$$I_s = 10V / 2.44k = 4.1 \text{ mA}$$

$$R_{eq} = 1.44k + 1k = 2.44k$$

Now using  $I_X = I_s \cdot R_T / R_X$  we get theoretical values ,

$$I_{R1} = (4.13 \cdot 1.44) / 3.3k = 1.8 \text{ mA}$$

$$I_{R2} = (4.13 \cdot 1.44) / 4.7k = 1.258 \text{ mA}$$

$$I_{R3} = (4.13 \cdot 1.44) / 5.6k = 1.06 \text{ mA}$$

Sum of individual Current ( $I_{R1} + I_{R2} + I_{R3}$ ) of theoretical value =  $(1.8 \text{ mA} + 1.258 \text{ mA} + 1.06 \text{ mA}) = 4.1 \text{ mA} = I_s$

Now we can get the experimental values using multisim. They are,

$$I_s = 4.1 \text{ mA}$$

$$I_{R1} = 1.778 \text{ mA}$$

$$I_{R2} = 1.256 \text{ mA}$$

$$I_{R3} = 1.053 \text{ mA}$$

Sum of individual Current ( $I_{R1} + I_{R2} + I_{R3}$ ) of experimental value =  $(1.778 \text{ mA} + 1.258 \text{ mA} + 1.053 \text{ mA}) = 4.098 \text{ mA}$  or  $4.1 \text{ mA} = I_s$

So, analyzing the theoretical values and experimental values we can say that the circuit follows KCL.

**6. Showing all the steps, theoretically calculate Req of circuit 1. Compare with the experimental value.**

**Answer:** Experimental Req=2.44k

Now Theoretical Req,

$$R_T = 3.3k // 4.7k // 5.6k = 1.44k$$

$$R_{eq} = 1.44k + 1k = 2.44k$$

After analyzing the experimental Req and theoretical Req , we can say that both has same value and it is 2.44k which means there are 0% error.

### **Discussion:**

From the lab 2, we learned about Kirchoff's Current law or KCL, Current Divider Rule using Parallel and Ladder Circuit.

As, it was an online lab, we had to use multisim to do the experiments. So, we didn't have to face many errors or faults. We could find the theoretical values easily.

If we would have done the lab offline, we could have faced many errors such human errors, environmental errors or mechanical errors. Also, we could have faces errors using DMM, cables, breadboard connection etc.