

North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code : EEE211

Course Title: Digital Electronics

Section: 01

Experiment Number: 05

Experiment Name: Binary Arithmetic

--

Experiment Date: 07.12.2020

Date of Submission: 10.01.2021

Course Instructor: Fahimul Haque

Submitted To: Fatema Zahra

Experiment Name:

Binary Arithmetic.

Objectives:

- Minimize combinational logic circuits using K-maps.
- Learn various numerical representation systems.
- Implement circuits using 1st & 2nd canonical minimal forms.
- Implement circuit using universal logic.

Theory:

The addition & subtraction of the binary number system are similar to that of the decimal number system. The only difference is that decimal number system consists the digit from 0-9 & their base 10 whereas the binary number system consists only two digits (0 & 1) which make operation easier.

Apparatus:

① Trainer board.

② 1 x 7483 IC (4 bit binary adder).

③ 1 x 7486 IC (quadruple 2-input XOR gates).

Circuit Diagram:


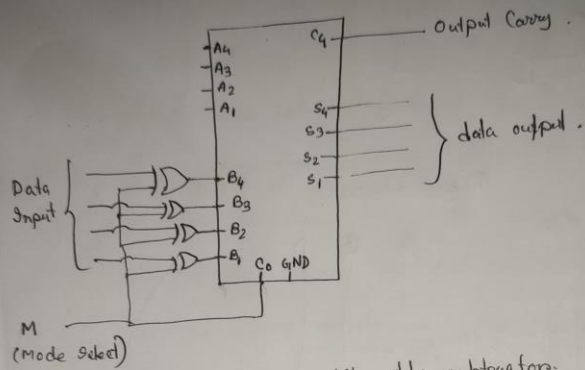


Figure: 4-bit adder subtractor.

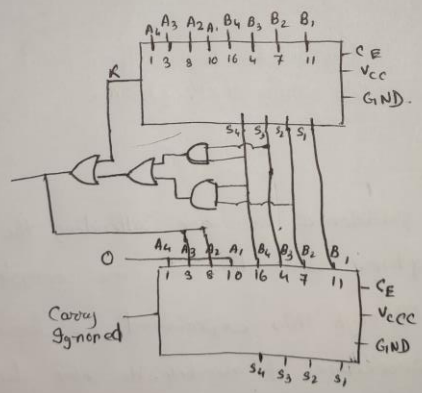

(3)

Here, input = 8

Table:

Operation	M	A	B	C ₄	S ₄ S ₃ S ₂ S ₁
7+5	0	0111	0101	0	1100
4+6	0	0100	0110	0	1010
9+11	0	1001	1011	1	0100
15+15	0	1111	1111	1	1110
7-5	1	0111	0101	1	0010
4-6	1	0100	0110	0	1110
11-2	1	1011	0010	1	1001
15-15	1	1111	1111	1	0000

Operation	A	B	Over flow Carry	Sum
7+5	0111	0101	0	1100
18+10	10010	10011	1	00101
72+83	1001006	1010011	1	0011011
129+255	10000001	11111111	1	10000000

(4)

Operation	A	B	Overflow carry	Sum
0+0	1001	0000	0	1001
0+1	1001	0001	1	00000
0+2	1001	0010	1	0001
0+3	1001	0011	1	0010
0+4	1001	0100	1	0011
0+5	1001	0101	1	0100
0+6	1001	0110	1	0101
0+7	1001	0111	1	0110
0+8	1001	1000	1	0111
0+9	1001	1001	1	1000

Observation Report:

Here M bit used a mode select which control the mode in this circuit. For $M=0$, the circuit executes addition & for $M=1$, the circuit executes subtraction.

M is connected as input in XOR. Truth Table for the XOR gates is:

A	B	output
0	0	0
0	1	1
1	0	1
1	1	0

Here, $B=M$ when $B=M=0$, then output will be either 0 or 1. And, for $M=1=B$, output is $A'=0$ or 1.

Discussion:

Due pandemic we could not attend in practical lab session. But, through ~~sim~~ software simulation we have completed this lab. We have learned binary addition & subtraction ~~within~~ at a time using adder-subtractor. Besides, we also learned BCD addition in cases where decimal number are larger than 9 is ~~is~~ being used.

Simulation:

Mohammed Mahmudur Rahman
Student ID# 1520386043

