

Experiment - 05: Verification of Superposition Theorem

Objective:

In this experiment we have learnt

- Verifying Superposition Theorem
- Building Circuit with multiple power source

List of Equipment:

- Bread Board
- DC power source
- DMM
- 1 x $3.3\text{k}\Omega$ resistor
- 1 x $4.7\text{k}\Omega$ resistor
- 1 x $1\text{k}\Omega$ resistor

Theory:

Superposition Theorem: The current or voltage passing through any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.

Circuit Diagram:

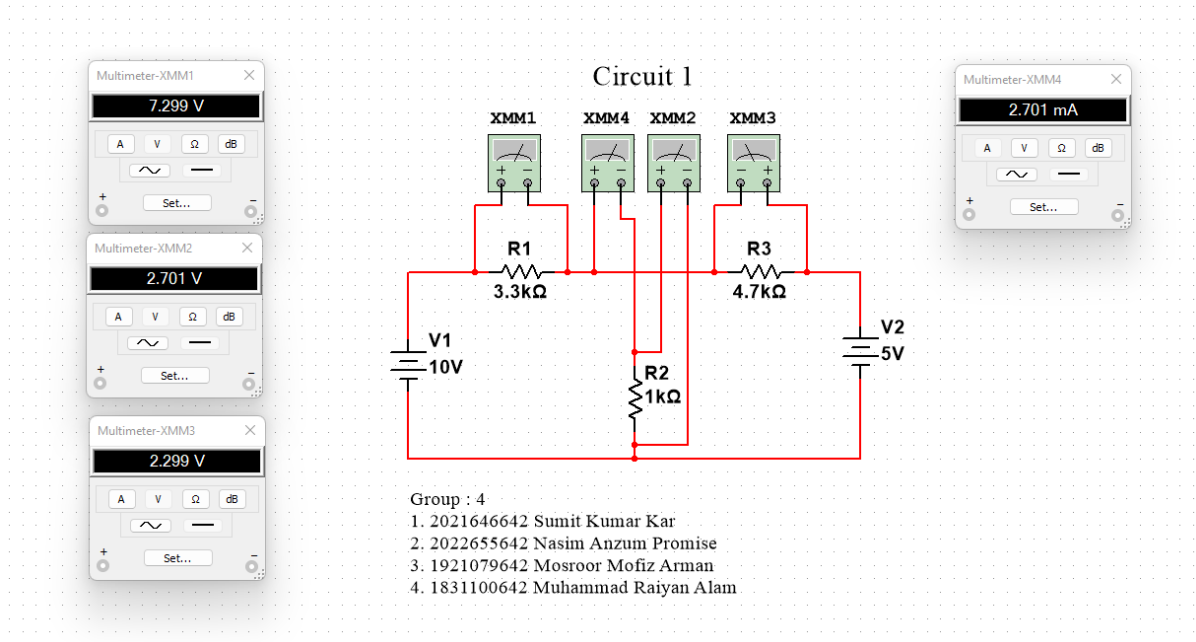


Figure 1: Circuit 1

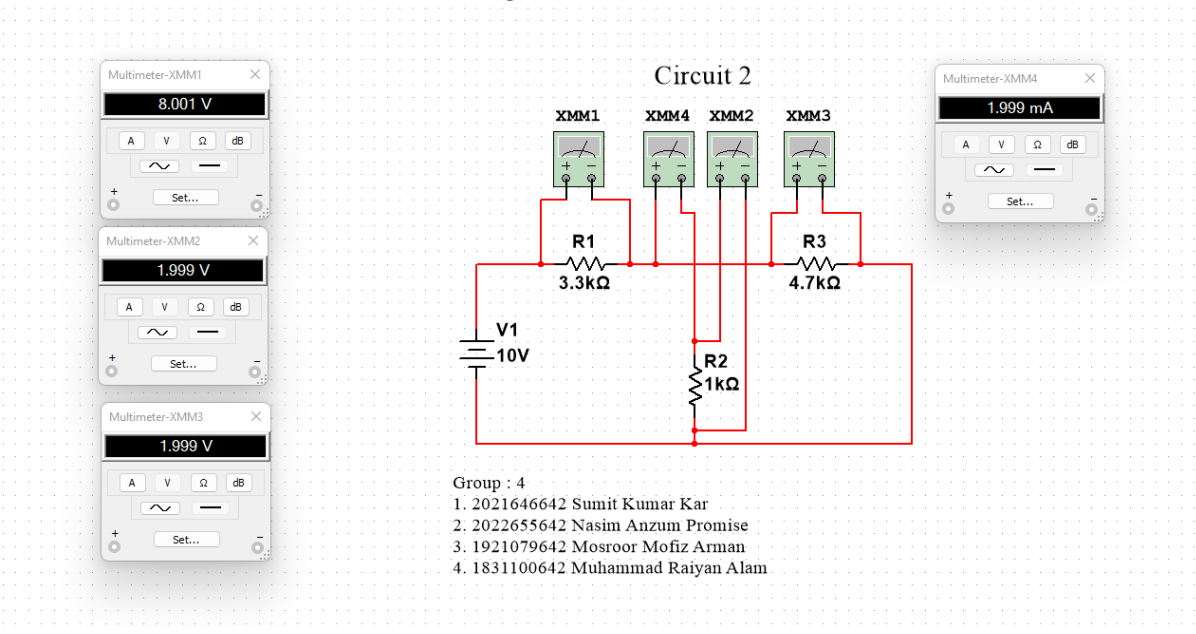


Figure 2: Circuit 2

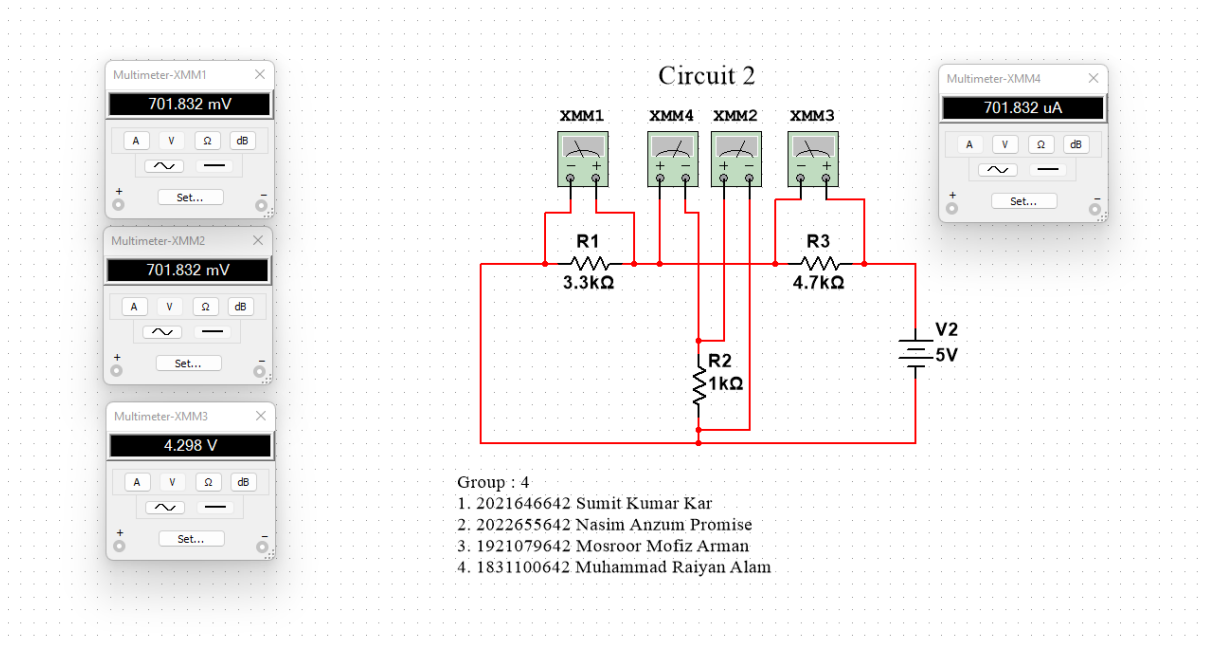


Figure 3: Circuit 3

Question and Answers:

1. What is Superposition Theorem?

Answer: The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.

2. Theoretically calculate all values of Table 1 to Table 4. Show all the steps in details.

Answer: Here for Circuit 2

$$R'_T = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 3.3K\Omega + \frac{1K\Omega \times 4.7K\Omega}{1K\Omega + 4.7K\Omega} = 4.12K\Omega$$

Now,

$$I' = \frac{V}{R'_T} = \frac{10V}{4.12K\Omega} = 2.43mA$$

Again for I'_2 and I'_3

$$I'_2 = \frac{I' R_3}{R_2 + R_3} = \frac{2.43mA \times 4.7K\Omega}{1K\Omega + 4.7K\Omega} = 2mA$$

$$I'_3 = \frac{I' R_2}{R_2 + R_3} = \frac{2.43mA \times 1K\Omega}{1K\Omega + 4.7K\Omega} = 0.43mA$$

Here,

$$\begin{aligned} V'_{R1} &= I' \times R_1 = 2.43mA \times 3.3K\Omega \\ &= 8.02V \end{aligned}$$

$$\begin{aligned} V'_{R2} &= I'_2 \times R_2 = 2mA \times 1K\Omega \\ &= 2V \end{aligned}$$

$$\begin{aligned} V'_{R3} &= I'_3 \times R_3 = 0.43mA \times 4.7K\Omega \\ &= 2V \end{aligned}$$

Here for Circuit 3

$$R''_T = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 4.7K\Omega + \frac{3.3K\Omega \times 1K\Omega}{3.3K\Omega + 1K\Omega} = 5.47K\Omega$$

Now,

$$I'' = \frac{V}{R''_T} = \frac{5V}{5.47K\Omega} = 0.91mA$$

Again for I''_2 and I''_1

$$I''_2 = \frac{I'' R_1}{R_1 + R_2} = \frac{0.91mA \times 3.3K\Omega}{3.3K\Omega + 1K\Omega} = 0.70mA$$

$$I''_1 = \frac{I'' R_2}{R_1 + R_2} = \frac{0.91mA \times 1K\Omega}{3.3K\Omega + 1K\Omega} = 0.21mA$$

Here,

$$\begin{aligned} V''_{R1} &= I''_1 \times R_1 = 0.21mA \times 3.3K\Omega \\ &= 0.7V \end{aligned}$$

$$\begin{aligned} V''_{R2} &= I''_2 \times R_2 = 0.70mA \times 1K\Omega \\ &= 0.7V \end{aligned}$$

$$\begin{aligned} V''_{R3} &= I'' \times R_3 = 0.91mA \times 4.7K\Omega \\ &= 4.27V \end{aligned}$$

Finally for Circuit 1, Using Superposition Theorem

$$\begin{aligned} I_2 &= I'_2 + I''_2 \\ &= 2mA + 0.7mA \\ &= 2.7mA \end{aligned}$$

$$\begin{aligned} V_{R1} &= V'_{R1} + V''_{R1} \\ &= |8.02V - 0.7V| \\ &= 7.32V \end{aligned}$$

$$\begin{aligned} V_{R2} &= V'_{R2} + V''_{R2} \\ &= |2V + 0.7V| \\ &= 2.7V \end{aligned}$$

$$\begin{aligned} V_{R3} &= V'_{R3} + V''_{R3} \\ &= |2V - 4.27V| \\ &= 2.27V \end{aligned}$$

3. Using measured data, show that your circuit followed superposition theorem.

Answer: From the measured data we get,

$$I_2, V_{R1}, V_{R2}, V_{R3}, I_2' + I_2'', V_{R1}' + V_{R1}'', V_{R2}' + V_{R2}'', V_{R3}' + V_{R3}''$$

Here,

$$\begin{aligned} I_2 &= 2.76mA, & I_2' + I_2'' &= 2.79mA \\ I_2 &\approx I_2' + I_2'' \\ V_{R1} &= 7.34V, & V_{R1}' + V_{R1}'' &= 7.29V \\ V_{R1} &\approx V_{R1}' + V_{R1}'' \\ V_{R2} &= 2.71V, & V_{R2}' + V_{R2}'' &= 2.63V \\ V_{R2} &\approx V_{R2}' + V_{R2}'' \\ V_{R3} &= 2.23V, & V_{R3}' + V_{R3}'' &= 2.13V \\ V_{R3} &\approx V_{R3}' + V_{R3}'' \end{aligned}$$

From the above equation we can say that our circuit follows the superposition theorem

4. Find the % Error between your theoretical and experimental values

Answer: Now we calculate the error percentage

$$\frac{|ExperimentalValue - TheoreticalValue|}{TheoreticalValue} \times 100\%$$

$$I_2 = \frac{|2.76mA - 2.7mA|}{2.7mA} \times 100\% = 2.22\%$$

$$V_{R1} = \frac{|7.34V - 7.32V|}{7.32V} \times 100\% = 0.27\%$$

$$V_{R2} = \frac{|2.71V - 2.7V|}{2.7V} \times 100\% = 0.37\%$$

$$V_{R3} = \frac{|2.23V - 2.27V|}{2.27V} \times 100\% = 1.76\%$$

$$I_2' = \frac{|2.10mA - 2mA|}{2mA} \times 100\% = 5.00\%$$

$$V_{R1}' = \frac{|7.91V - 8.02V|}{8.02V} \times 100\% = 1.37\%$$

$$V_{R2}' = \frac{|2.02V - 2.00V|}{2.00V} \times 100\% = 1.00\%$$

$$V_{R3}' = \frac{|2.02V - 2.00V|}{2.00V} \times 100\% = 1.00\%$$

$$I_2'' = \frac{|0.69mA - 0.7mA|}{0.7mA} \times 100\% = 1.42\%$$

$$V_{R1}'' = \frac{|0.62 - 0.7V|}{0.7V} \times 100\% = 11.42\%$$

$$V_{R2}'' = \frac{|0.62V - 0.7V|}{0.7V} \times 100\% = 11.42\%$$

$$V_{R3}'' = \frac{|4.15V - 4.27V|}{4.27V} \times 100\% = 2.81\%$$

Result analysis and Discussion

In this lab we have learnt about Superposition theorem. And how we can use superposition theorem to calculate current and voltage passing through each element in a circuit with multiple power sources. In the lab we were provided $1K\Omega$, $3.3K\Omega$ and $4.7K\Omega$ resistors with a Digital Multi meter(DMM) and Breadboard. We figured out the resistance of the resistors using color coding and we verified the actual resistance using DMM.

Then we built Circuit 1 first and measured voltage across R_1 , R_2 and R_3 . To measure the voltage we connected the probes of DMM in parallel to the resistors. Then we measured the current passing through R_2 , to measure the current we connected the probes of DMM in serial to R_2 . Then we wrote down V_{R1} , V_{R2} , V_{R3} and I_{R2} .

Then we built the Circuit 2. For this we just removed the 5V power source and shorted the path where it was connected. Then we measured V'_{R1} , V'_{R2} , V'_{R3} and I'_{R2} and wrote down the values we found.

After that we built the Circuit 3. For this we re-connected 5V power source and removed the 10V power source and shorted the path where it was connected. Then we measured V''_{R1} , V''_{R2} , V''_{R3} and I''_{R2} and wrote down the values we found.

Then after calculating $I'_2 + I''_2$, $V'_{R1} + V''_{R1}$, $V'_{R2} + V''_{R2}$, $V'_{R3} + V''_{R3}$. We can see that these values are almost equal to I_{R2} , V_{R1} , V_{R2} , V_{R3} . This proves that our experiment follows the superposition theorem. The values we measured are all written in Table-1, Table-2, Table-3, Table-4

We also faced few problems during the experiment. One of our power supply had issues maintaining a steady voltage output. So, we had to measure every value more than once.

Table of Contributions

During the experiment in class:

- 2021646642 Sumit Kumar Kar and 2022655642 Nasim Anzum Promise :
Building the Circuit
- 1831100642 Muhammad Raiyan Alam:
Wrote data in Lab Manual and helped group members with the steps
- 1921079642 Mosroor Mofiz Arman:
Checked whether all the circuits were built correctly or not and whether all the data were written carefully and accurately or not.

During Lab Report:

- 2022655642 Nasim Anzum Promise:
Wrote objective, theory part and Discussion.
- 2021646642 Sumit Kumar Kar:
Drew Multisim and Solved Questions and Answers
- 1831100642 Muhammad Raiyan Alam:
Helped with Question and Answer
- 1921079642 Mosroor Mofiz Arman:
Report Writing according to the Guideline given in the canvas.