

Time: 75 Minutes

Marks: 50

Please read the questions very carefully and answer accordingly. All the answers should be written in the answer script that is provided. Calculators/pens/pencils are allowed. Adopting any unfair means during the exam will automatically result in expulsion without any prior/post notice. You must return back your question paper with your answer script.

Q1. Please answer all the following questions:

[CO 1]

(a) Express the following output function $F(x, y, z)$ in **minterms** and **maxterms**.

4

I. $F(x, y, z) = x$

II. $F(x, y, z) = x + xy$

(b) Draw the output function in relation to the inputs in a table and express the following output function in **minterms**.

3

$$F(A, B, C) = M_0 \cdot M_2 \cdot M_4 \cdot M_7$$

(c) Write the expression of output function $F(A, B, C)$ in **maxterms** for **XNOR** logic-gate.

3

Q2. Please answer all the following questions:

[CO2]

(a) Apply **K-map** to find out both **Sum of Product (SOP)** and **Product of Sum (POS)** for the following functions:

16

i. $F(A, B, C, D) = \sum(0, 5, 10, 15) + \sum d(2, 7, 8, 13)$

ii. $F(A, B, C, D) = \sum(0, 1, 2, 3, 7, 9, 10, 11, 15)$

iii. $F(A, B, C, D) = (A + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + \bar{D})$

iv. $F(A, B, C, D, E) = \prod(0, 1, 4, 5, 12, 13, 18, 19, 22, 23, 30, 31)$

(b) Find the **Prime Implicant (PI)** and **Essential Prime Implicants (EPI)** for the following functions and also please indicate/mark clearly the **PI** and **EPI** in the K-map for the following functions.

4

I. $F(w, x, y, z) = \sum(0, 1, 5, 7, 10, 14, 15)$

II. $F(A, B, C, D) = \prod(4, 6, 8, 9, 12, 14)$

Q3. Please answer all the following questions:

[CO3]

- (a) Draw the truth table of a full-subtractor and implement it using a decoder. **3**
 - (b) Implement a higher order decoder $n \times 2^n$, using lower order decoder $n \times 2^n$. Here, the order of $n = 1$, and **4**
3.
 - (c) Implement a three-input variable XOR gate using 4×1 multiplexer. **5**
 - (d) Draw the truth table for 8×3 priority encoder. **3**
 - (e) Implement the higher order multiplexer $2^n \times 1$ using lower order multiplexer $2^n \times 1$. Here, the order of **5**
 $n = 2$, and 3. Basic gates i.e. AND, NOT, and OR gates can be incorporated with the design, if necessary.
-