





Lab1 exp1 - Multisim - [Lab1 exp1 *]

File Edit View Place MCU Simulate Transfer Tools Reports Options Window Help

Design Toolbox

- Design1
- Lab1 exp1(2)
- Lab1 exp1(2)
- Lab1 exp1
- Lab1 exp1
- Lab1 exp2
- Lab1 exp2

Multimeter-XMM1

1.818 mA

A V Ω dB

Set...

Multimeter-XMM2

6 V

A V Ω dB

Set...

V 6V

R 3.3k Ω

XMM1 XMM2

Kanta Saha
2011731642

Multisim - Monday, November 8, 2021, 7:55:20 PM

Results Nets Components Copper layers Simulation

Lab1 exp1: Simulating... Tran: 4.727 s

08:04 PM 08-Nov-21

Lab1 exp1(2) - Multisim - [Lab1 exp1(2) *]

File Edit View Place MCU Simulate Transfer Tools Reports Options Window Help

Design Toolbox

- Design1
 - Lab1 exp1(2)
 - Lab1 exp1(2)
 - Lab1 exp1
 - Lab1 exp2
 - Lab1 exp2

Multimeter-XMM3

1.429 mA

A V Ω dB

Set...

Multimeter-XMM4

8 V

A V Ω dB

Set...

V1 8V

R1 5.6k Ω

XMM3 XMM4

Kanta Saha
2011731642

Hierarchy Visibility Pr

Design1 Lab1 exp1(2) * Lab1 exp1 * Lab1 exp2

Multisim - Monday, November 8, 2021, 7:55:20 PM

Results Nets Components Copper layers Simulation

Lab1 exp1(2): Simulating... Tran: 3.577 s

08:05 PM 08-Nov-21

Lab1 exp2 - Multisim - [Lab1 exp2]

File Edit View Place MCU Simulate Transfer Tools Reports Options Window Help

Design Toolbox

- Design1
- Lab1 exp1(2)
- Lab1 exp1(2)
- Lab1 exp1
- Lab1 exp1
- Lab1 exp2
- Lab1 exp2

Multimeter-XMM5: 3.64 V

Multimeter-XMM6: 5.184 V

Multimeter-XMM7: 6.176 V

V2 15V

R2 3.3k Ω

R3 4.7k Ω

R4 5.6k Ω

XMM5

XMM6

XMM7

Kanta Saha
2011731642

Hierarchy Visibility Pr

Design1 Lab1 exp1(2) Lab1 exp1 Lab1 exp2

Multisim - Monday, November 8, 2021, 7:55:20 PM

Results Nets Components Copper layers Simulation

Lab1 exp2: Simulating... Tran: 3.599 s

08:05 PM 08-Nov-21