
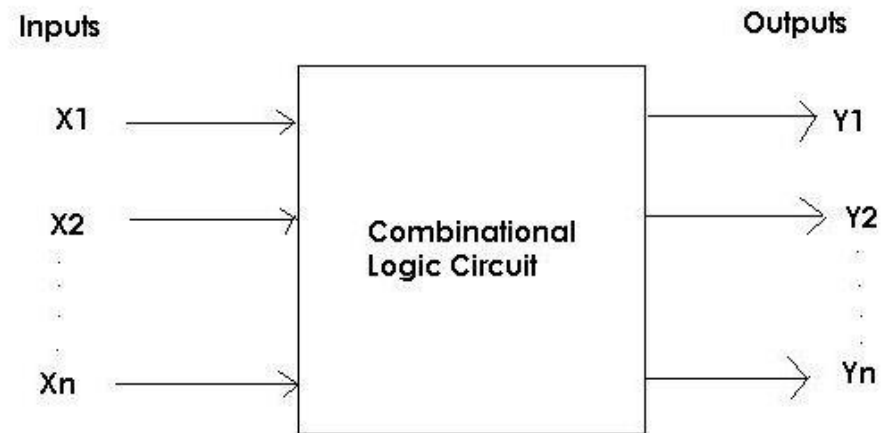


Combinational logic circuit cont..

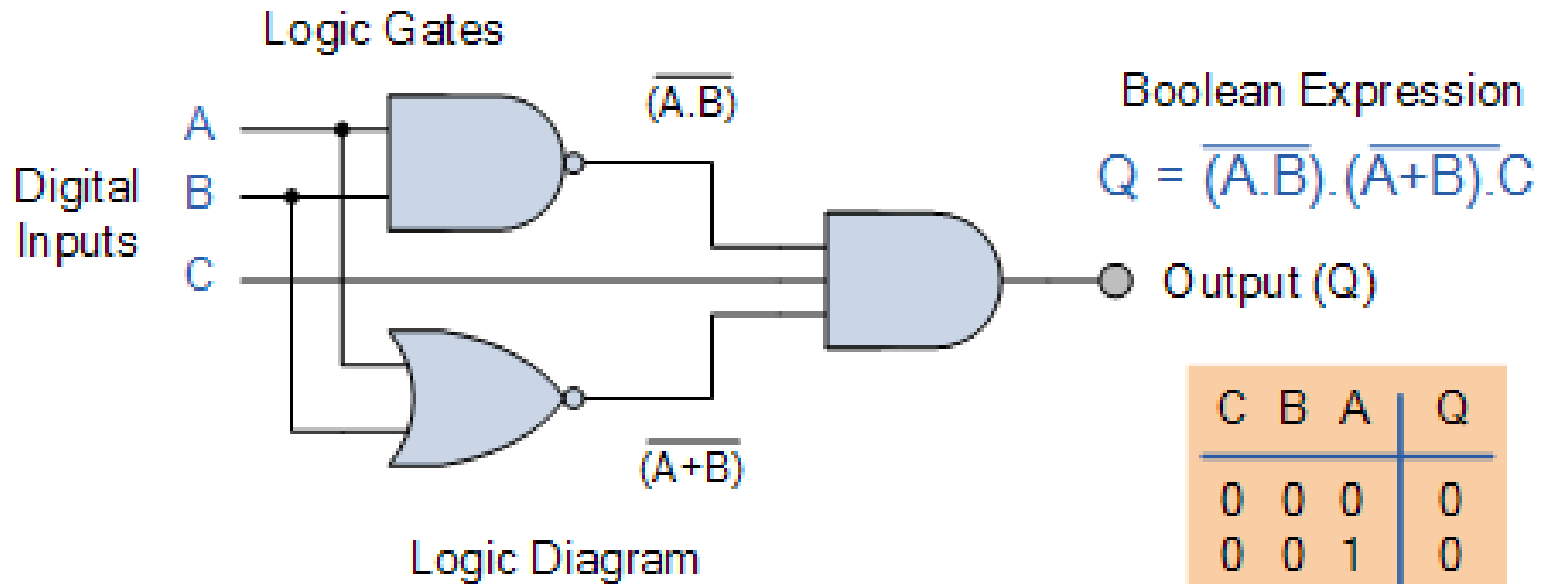


Combinational logic circuit cont..



Typical
Truth Table

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Combinational logic circuit

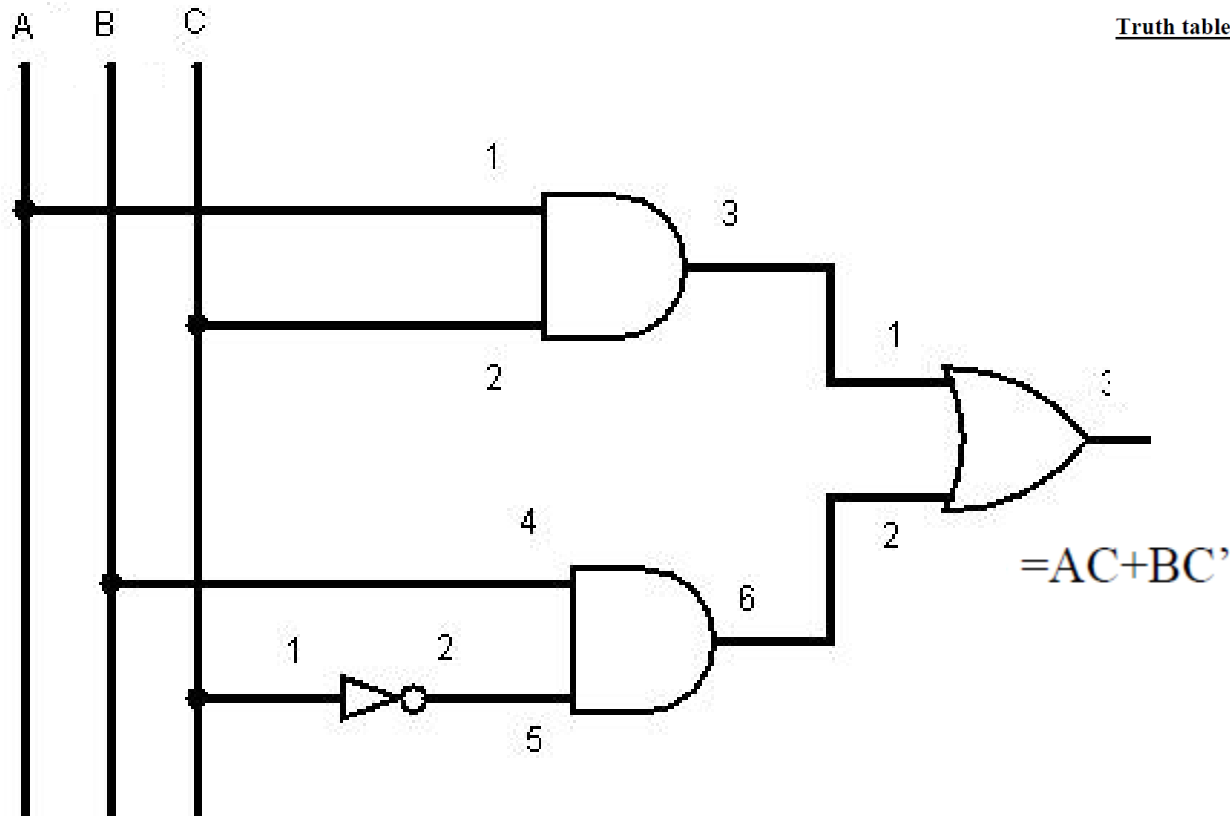

Truth table:


A	B	C	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit

Truth table:

A	B	C	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

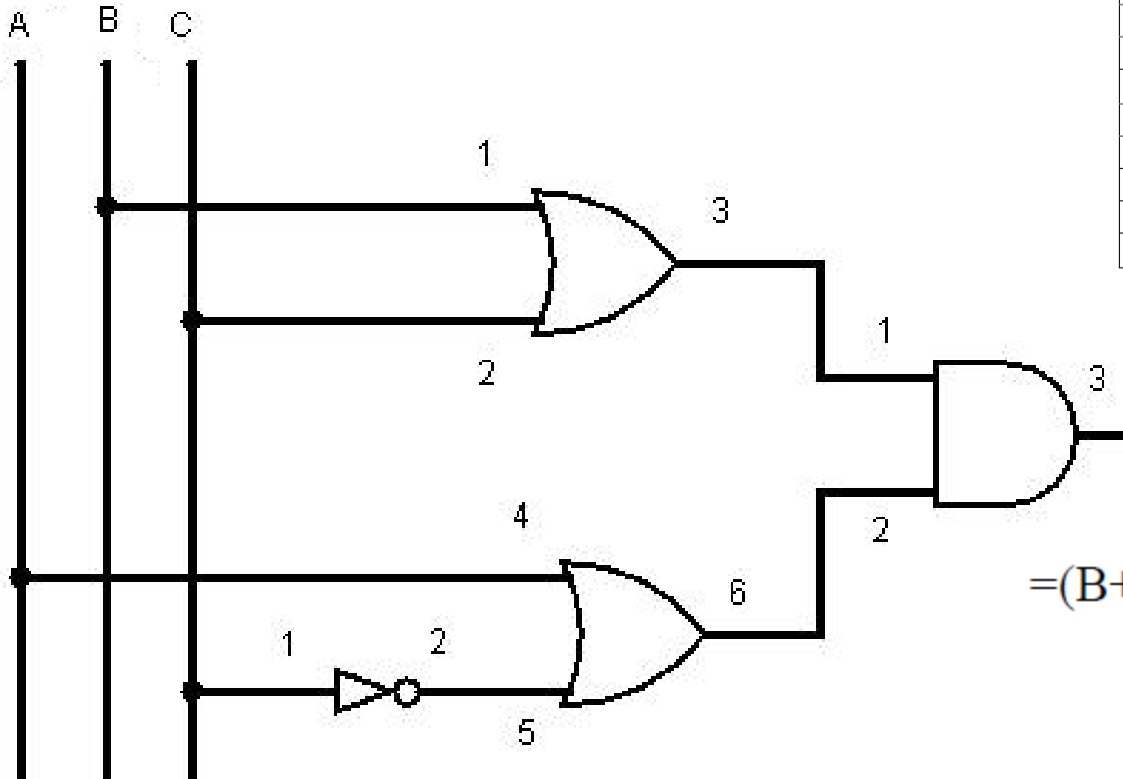


$$=(B+C) (A+C')$$

❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit


Truth table:

A	B	C	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

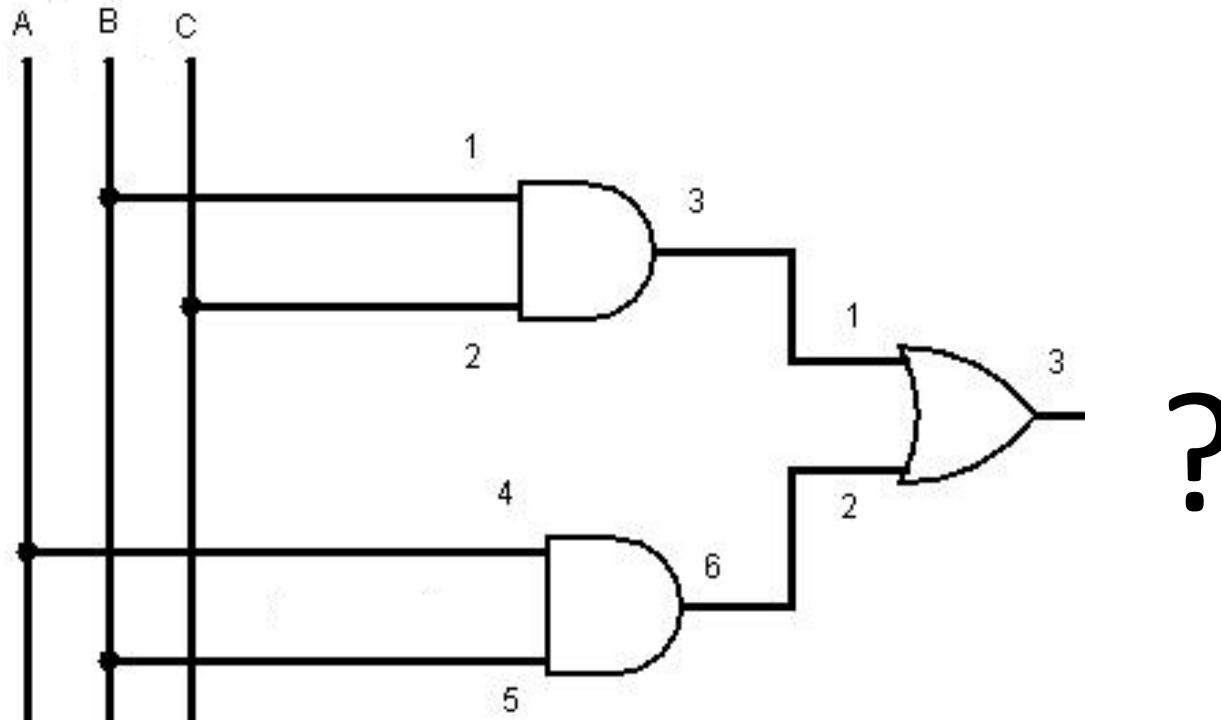

❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit

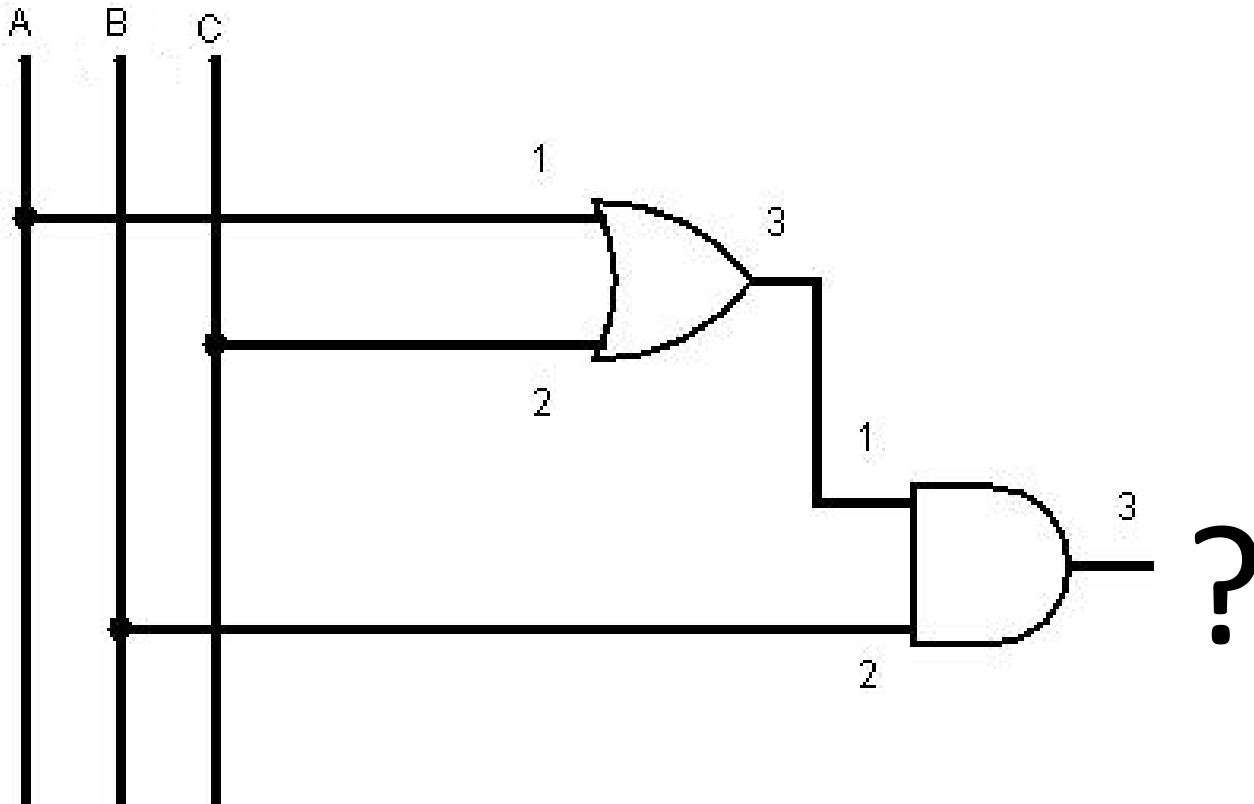


❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit cont..


Implementation of function $f = (AB+B).(C+A).(AC+B)$

Combinational logic circuit

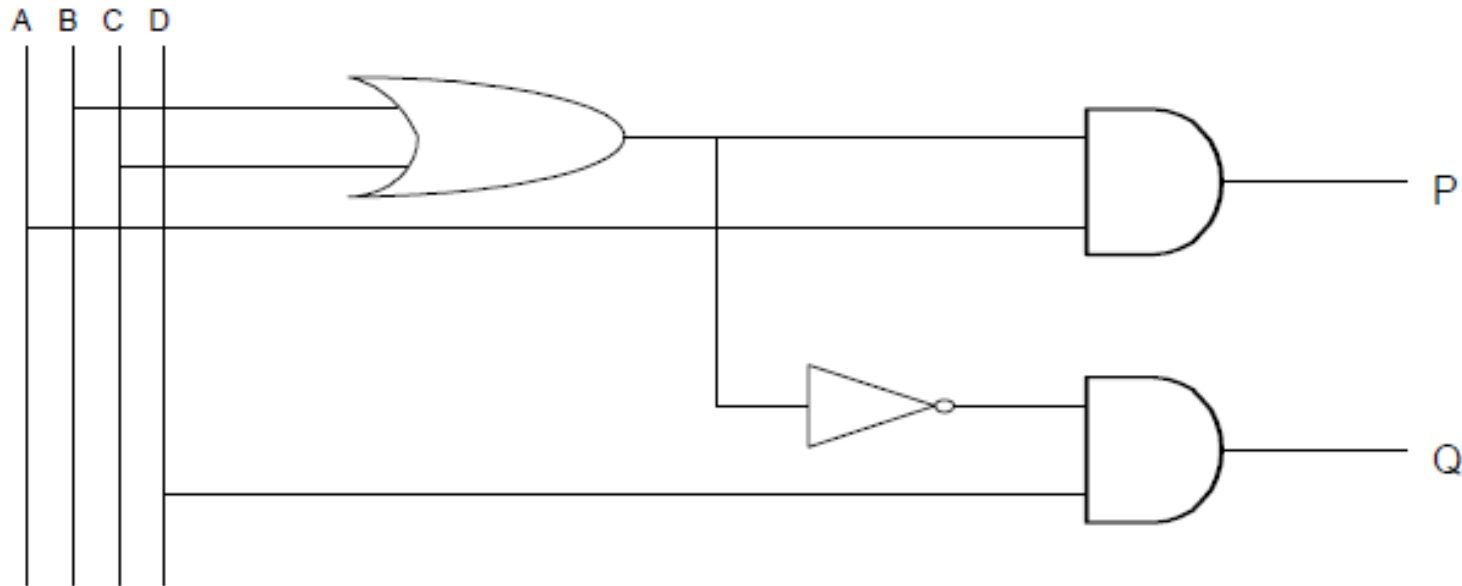


❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit cont..

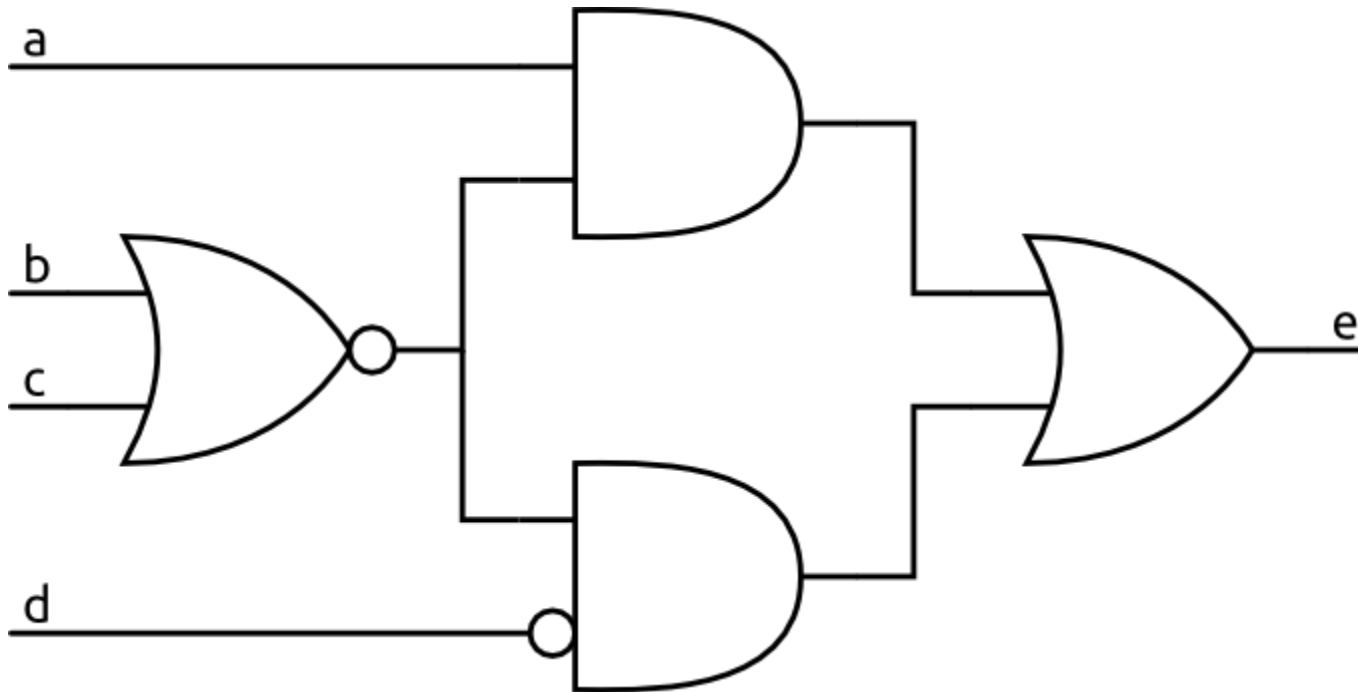


❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit cont..

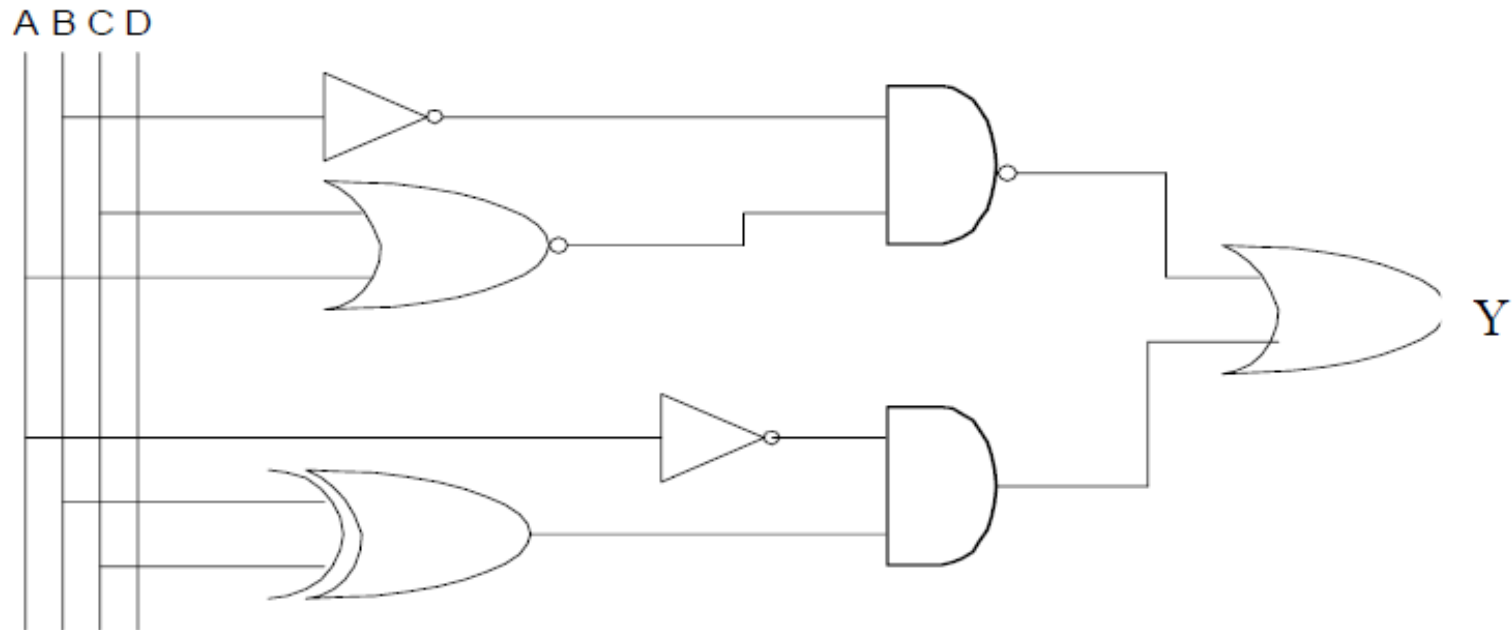

❖ Derive the equations for the circuits and then construct the truth table.

Combinational logic circuit cont..

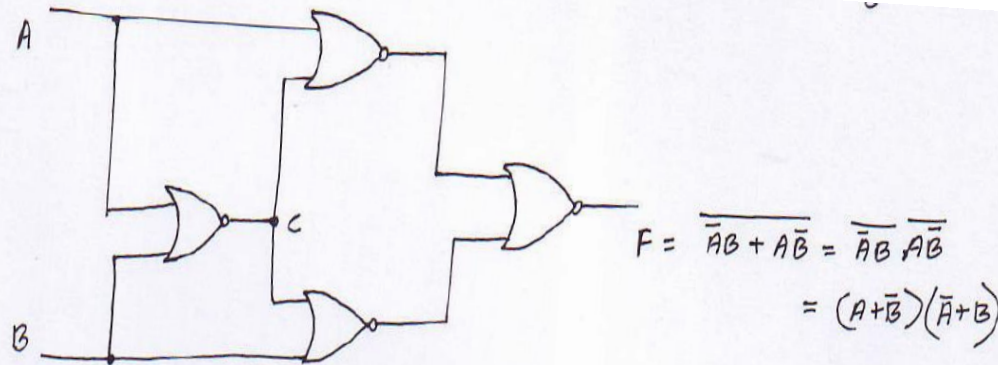

$$F = \overline{AB + AB} = \overline{AB} \overline{AB} \\ = (A + \overline{B})(\overline{A} + B)$$

$$C = \overline{A+B} = \overline{A} \overline{B}$$

$$\begin{aligned} \overline{A+C} + \overline{B+C} &= (A+C)(B+C) \\ &= C + AB \\ &= \overline{AB} + AB \\ &= A \odot B \end{aligned}$$

Truth table

❖ Derive the equations for the circuits and then construct the truth table.

Try with four inputs