
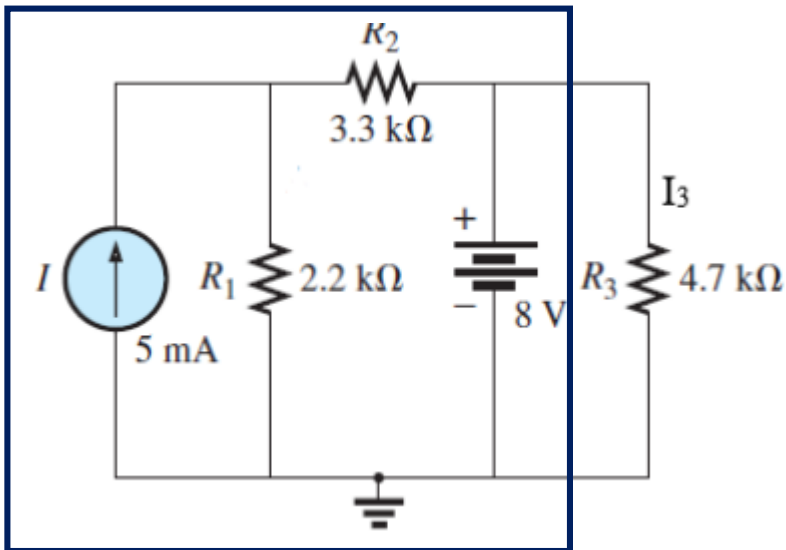


- (a) Using superposition theorem, find the current through  $R_3$  for the network below. Draw the circuits for each source (2 circuits), write all the formulas properly and also provide the current direction.

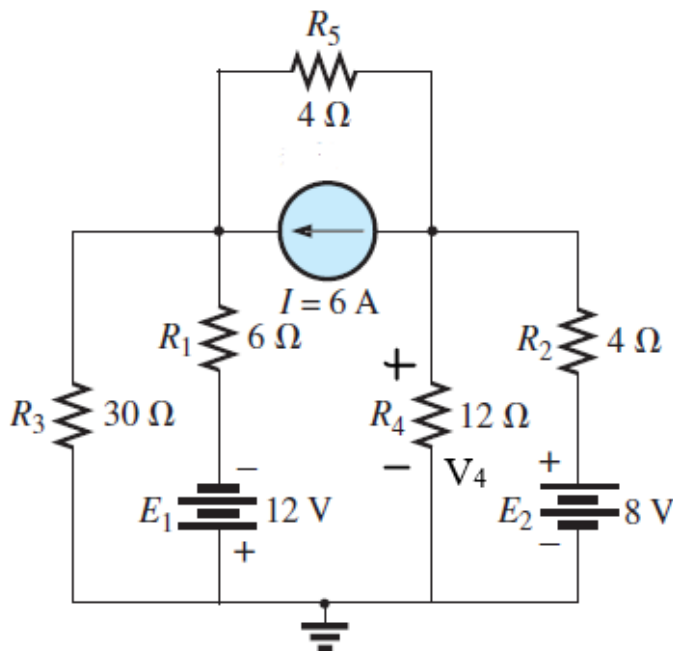
(b) Apply thevenin's theorem for the network external to  $R_3$ . Draw the circuits required to find  $E_{th}$  and  $R_{th}$ . Finally draw the thevenin equivalent circuit and find the current through  $R_3$ . Compare the results with (a).




- Using superposition theorem, find the voltage across  $R_4$  for this network with all necessary steps, formula and diagram.



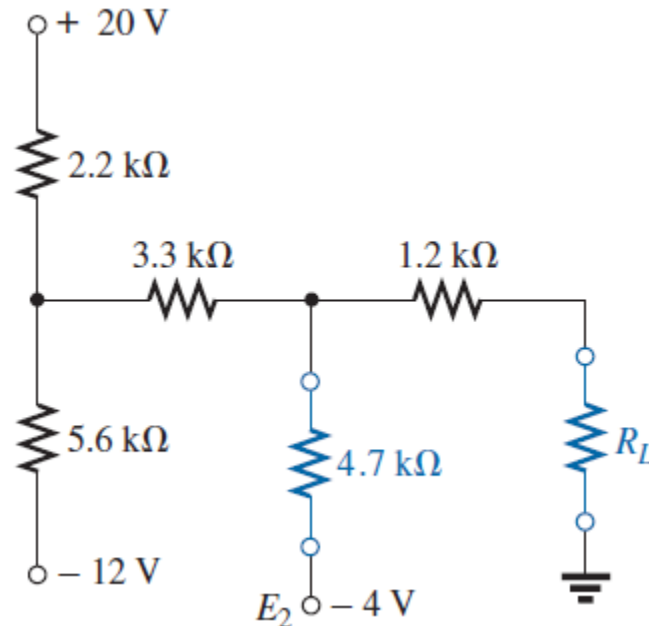3. Apply thevenin's theorem for the network external to  $R_L$  with all necessary steps and formula. Draw the circuits required to find  $E_{th}$  and  $R_{th}$ . Finally draw the thevenin equivalent circuit and find the current through  $R_L$  if  $R_L = 10$  kilo ohm.




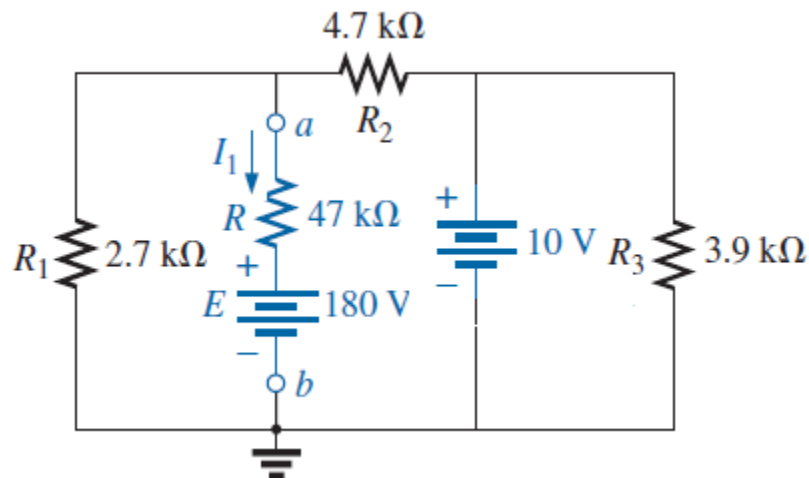4. a) Find the Thévenin equivalent circuit for the portions of the networks external to points  $a$  and  $b$ . Show all necessary steps, formula and diagram. Also find the current  $I_1$  flowing through this portion  $a$  and  $b$  (or flowing through  $R = 47$  kilo ohm resistor).  
 b) Find the Norton's equivalent circuit for the portions of the networks external to the points  $a$  and  $b$  with all necessary steps, formula and diagram.



5. a. Find the mathematical expressions for the transient behavior of the voltage  $v_C$  and the current  $i_C$  if the capacitor was initially uncharged and the switch is thrown into position 1 at  $t = 0$  s.
- b. Find the mathematical expressions for the voltage  $v_C$  and the current  $i_C$  if the switch is moved to position 2 at  $t = 8\tau$ .
- c. Find the mathematical expressions for the voltage  $v_C$  and the current if the switch is thrown into position 3 at  $t = 12\tau$ .
- d. Plot the waveforms obtained in parts (a)–(c)

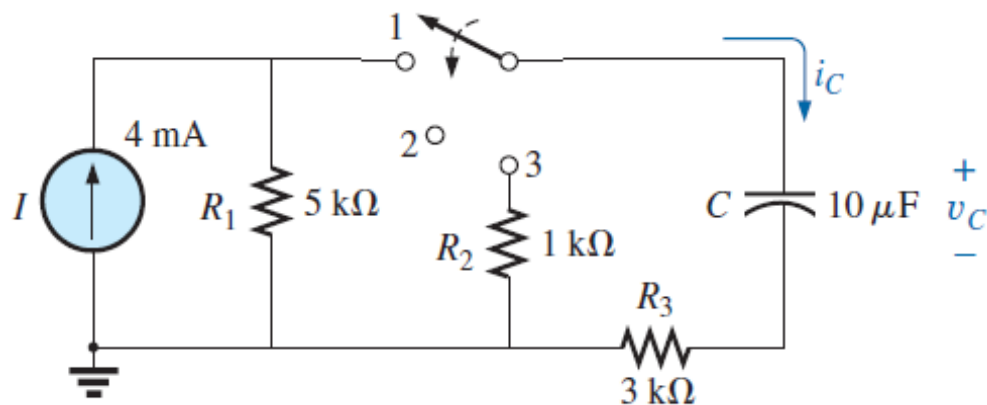**Demonstrate all necessary steps, formulas and calculations properly.**



6. Find currents  $I_1$  and  $I_2$  and voltages  $V_1$  and  $V_2$  for the network below. Also determine the charge stored by the capacitor  $C_2$  and energy stored by the inductor  $L_1$ .

