

Ans to the Q. No 1 (a)

Number of commutator segments = 16

Number of coil sides =  $16 \times 2 = 32$

Pole pitch,  $= 32/4 = 8$

$$Y_F = \frac{Z}{P} - 1 = \frac{32}{4} - 1 = 7$$

$$Y_B = \frac{Z}{P} + 1 = \frac{32}{4} + 1 = 9$$

Simple winding table given below:


<u>Back conn.</u>		<u>Front conn.</u>
1 to $(1+9) = 10$	→	10 to $(10-7) = 3$
3 to $(3+9) = 12$	→	12 to $(12-7) = 5$
5 to $(5+9) = 14$	→	14 to $(14-7) = 7$
7 to $(7+9) = 16$	→	16 to $(16-7) = 9$
9 to $(9+9) = 18$	→	18 to $(18-7) = 11$
11 to $(11+9) = 20$	→	20 to $(20-7) = 13$
13 to $(13+9) = 22$	→	22 to $(22-7) = 15$
15 to $(15+9) = 24$	→	24 to $(24-7) = 17$
17 to $(17+9) = 26$	→	26 to $(26-7) = 19$
19 to $(19+9) = 28$	→	28 to $(28-7) = 21$
21 to $(21+9) = 30$	→	30 to $(30-7) = 23$
23 to $(23+9) = 32$	→	32 to $(32-7) = 25$
25 to $(25+9) = (34-32) = 2$	→	2 to $(34-7) = 27$



$$27 \rightarrow (27+9)=36 = (36-32)=4 \rightarrow 4 \rightarrow (36-7)=29$$


$$29 \rightarrow (29+9)=38 = (38-32)=6 \rightarrow 6 \rightarrow (38-7)=31$$
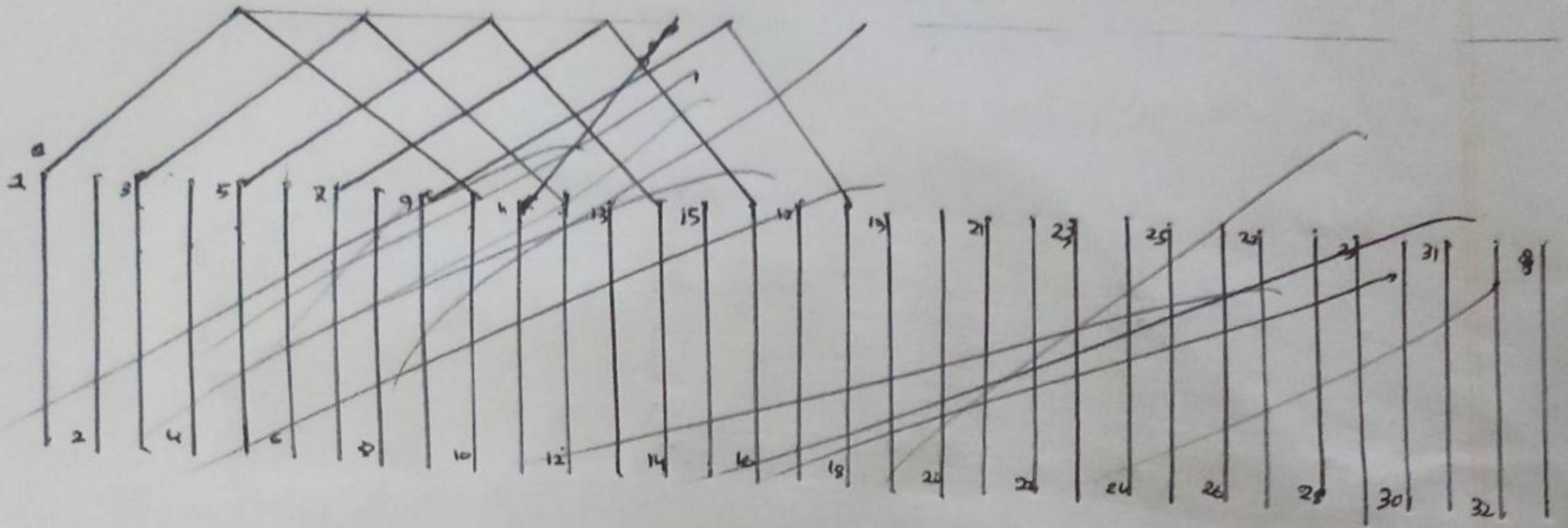
$$31 \rightarrow (31+9)=40 = (40-32)=8 \rightarrow 8 \rightarrow (40-7)=33 = (33-32)=1$$



Back

Rotation ←

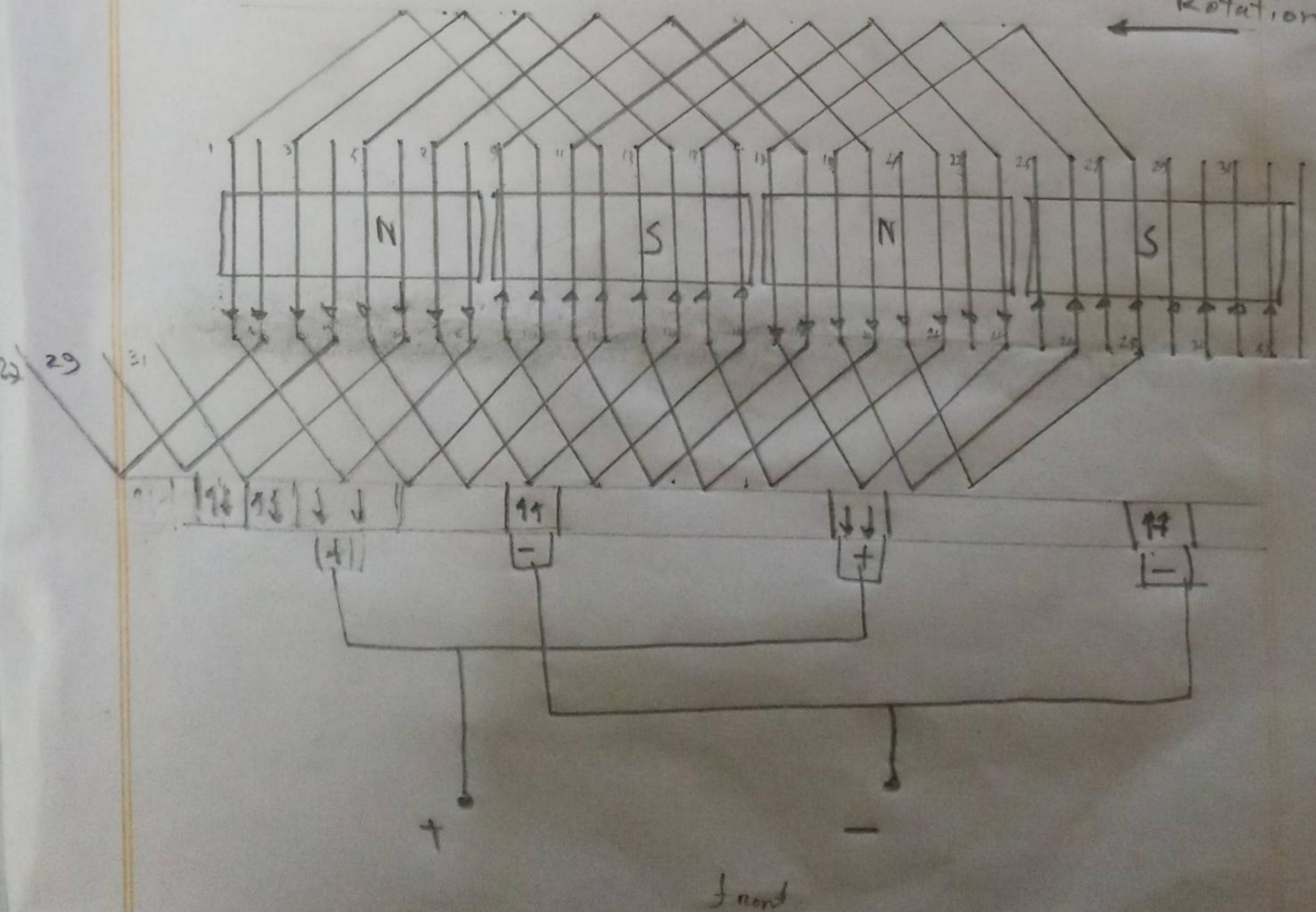



Ans to the Q. No-2 (b)

50 kW generator

$$\text{F.L. voltage drop} = 500 \times 0.06 = 30 \text{ V}$$

$$\text{F.L. current} = 50000 / 500 = 100 \text{ A}$$

$$\text{Drop per } \cancel{\text{ampere}} \text{ ampere} = 30 / 100 = \frac{3}{10} \text{ V/A}$$

100 kW generator:

$$\text{F.L. drop} = 500 \times 0.04 = 20 \text{ V}$$

$$\text{F.L. current} = 100,000 / 500 = 200 \text{ A}$$

$$\text{Drop per ampere} = 20 / 200 = \frac{1}{10} \text{ V/A}$$

If  $I_1$  and  $I_2$  are current supply by ~~two~~  
two gen and  $V$  the terminal voltage, then

$$\begin{aligned} \text{1st gen} \rightarrow V &= \left[ 500 - \left( \frac{3}{10} I_1 \right) \right] \quad \text{--- (i)} \\ \text{2nd gen} \rightarrow &= \left[ 500 - \left( \frac{1}{10} I_2 \right) \right] \quad \text{--- (ii)} \end{aligned}$$

$$0 = \text{--- (iii)}$$

$$500 - \frac{3}{10} I_1 = 500 - \frac{1}{10} I_2$$



Also we know that,

a) Total current,  $I_1 + I_2 = 240$  ——— (iii)

$$\Rightarrow 3I_2 + I_2 = 240$$

$$\Rightarrow 4I_2 = 240$$

$$\Rightarrow I_2 = 60 \text{ A}$$

Put them in eq<sup>n</sup> (i) (ii)

$$I_1 + I_2 = 240$$

$$\Rightarrow I_1 = (240 - 60) \text{ A}$$
$$= 180 \text{ A}$$

Ans

~~Ans~~  $\rightarrow I$

b) Terminal voltage,  $V = 500 - \left(\frac{3}{10} \times 60\right)$

$$= 482 \text{ V}$$

Ans.



## Ans to the Q. No - 2(a)

Armature reaction: The armature reaction represents the armature flux on the main field flux. The armature field is produced by the armature conductors when current flows through them.

We can also say that:  
The effect of magnetic field set up by the armature current on the distribution of main pole flux.

It has two effects:


- (i) It demagnetises or weakens the main flux.
- (ii) It cross-magnetizes or <sup>distorts</sup> ~~distorts~~ the flux.



Geometric  
magnetic


Neutral axis (GNA)  
Neutral axis (MNA)

MNA/GNA

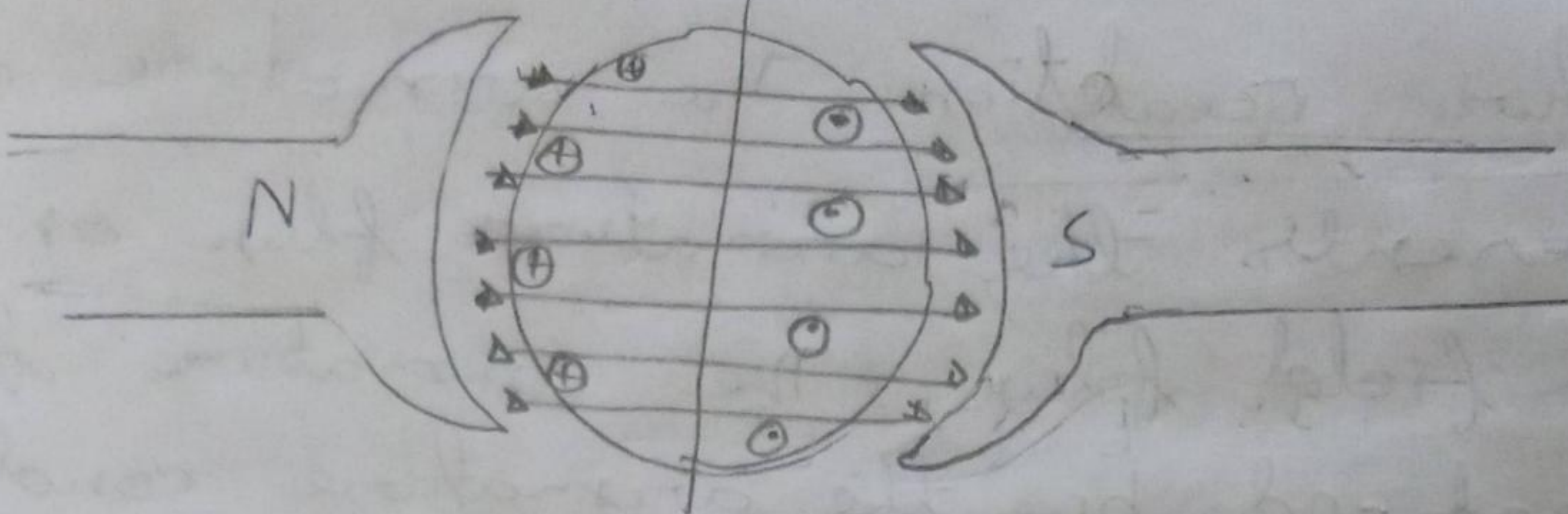

Flux due to pole only

MNA/GNA  $\omega$

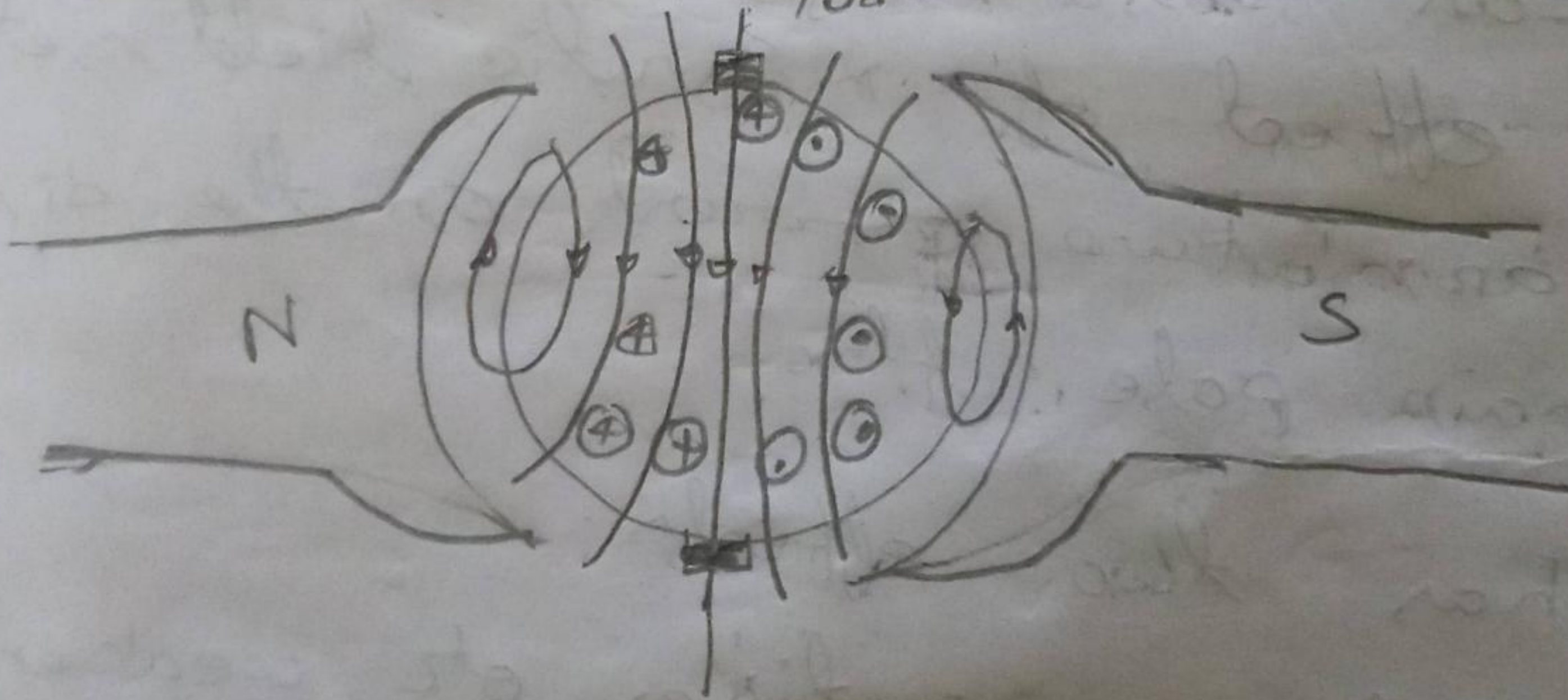


Brush Axis

flux due to armature current only




# Armature reaction

GNA / MNA

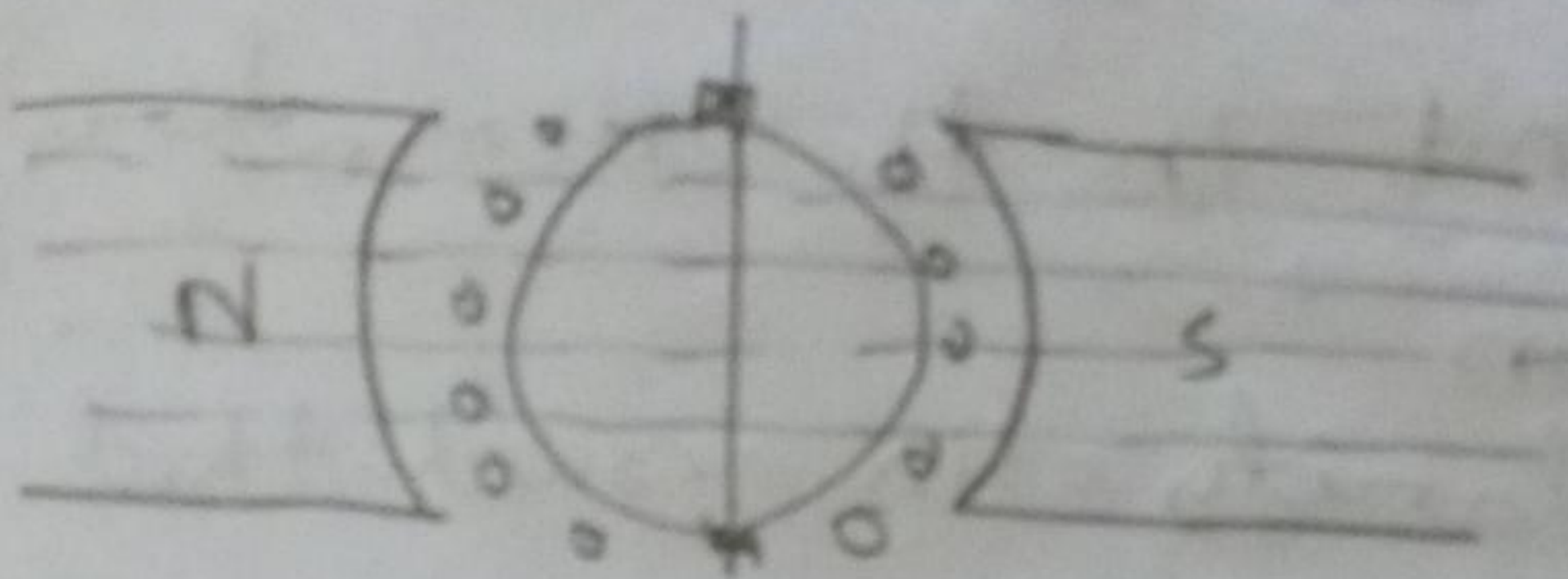

(1)


GNA / MNA

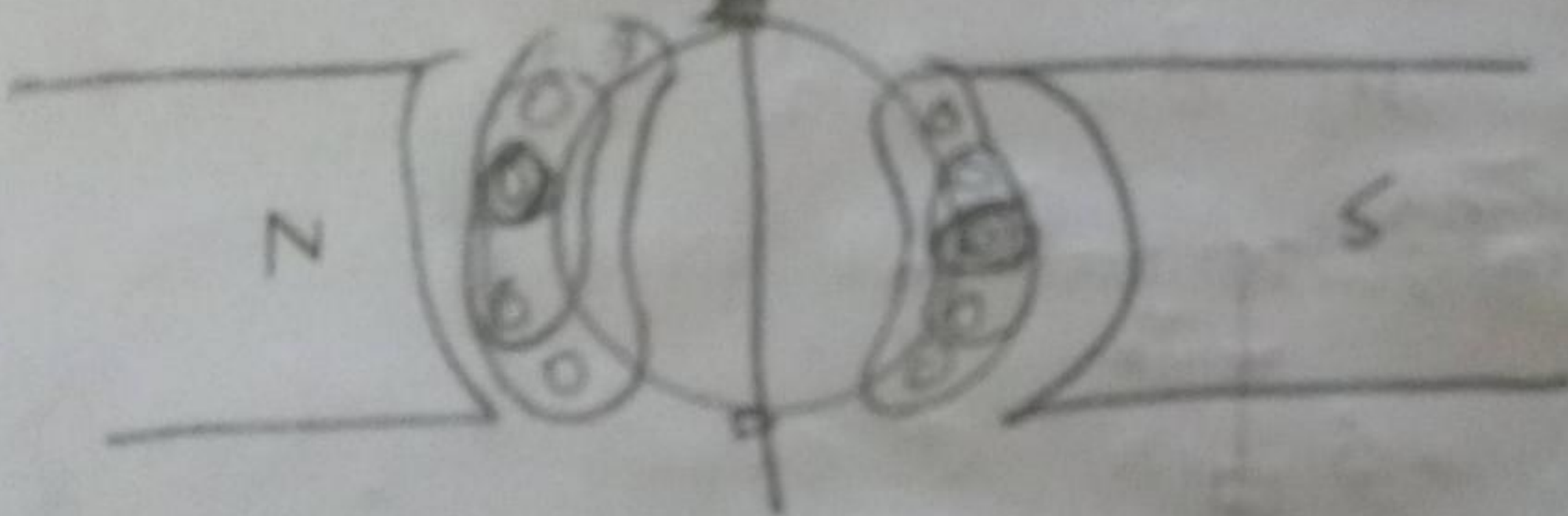

(2)

Rotation

GNA

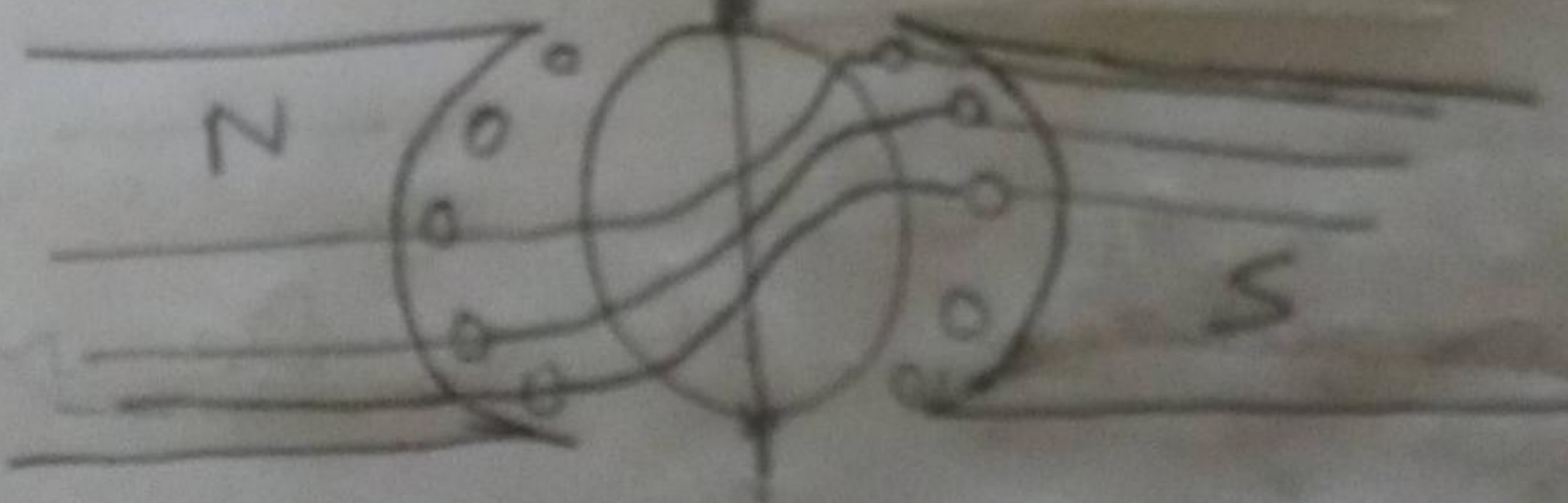

(3)




## Ans to the Q.No-3(a)

Back EMF: Is the

- Induced e.m.f in the armature due to the rotation.
- Its polarity is such that it opposes the applied voltage (Lenz's rule)

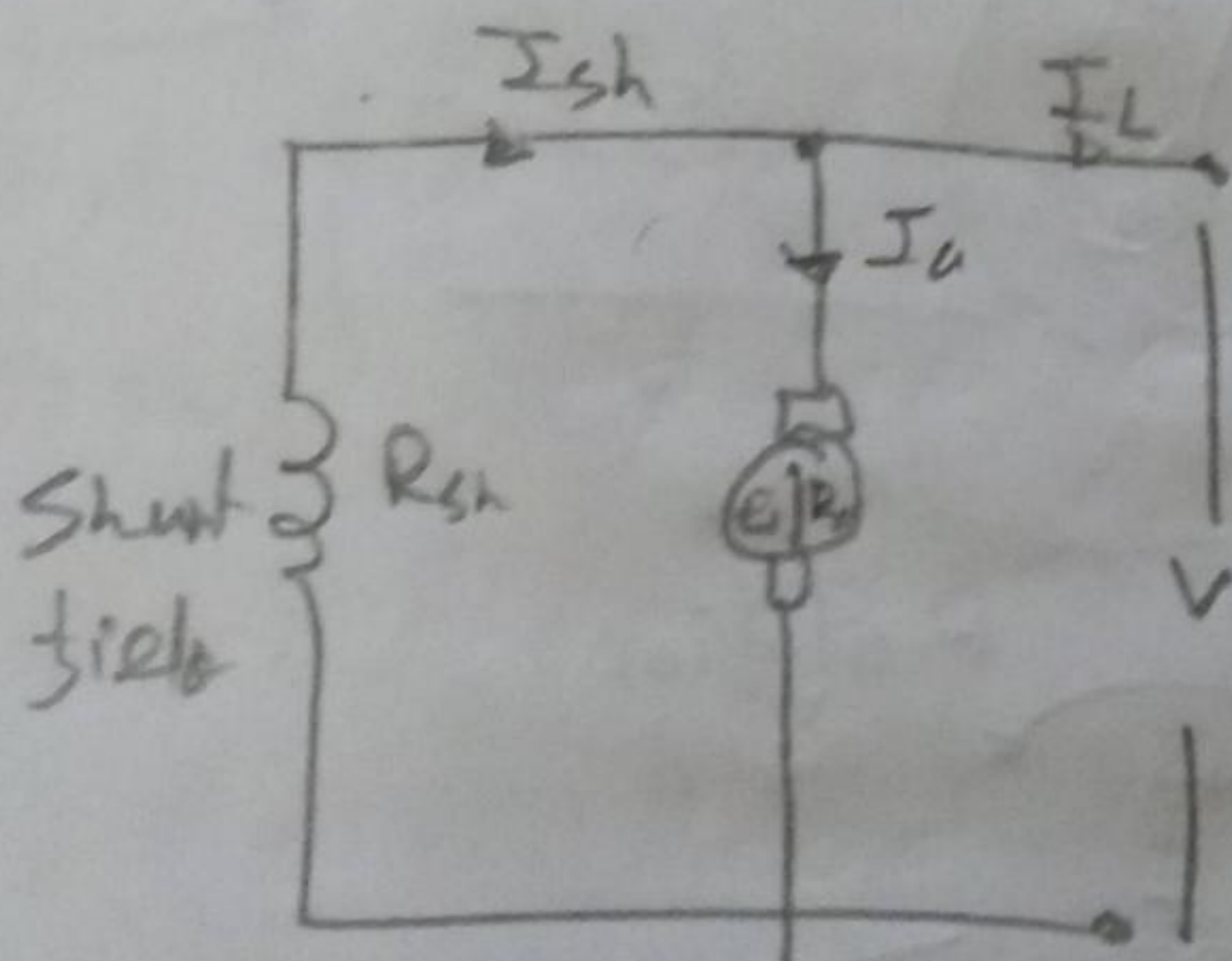~~It is the induced e.m.f in the armature due to the rotation of the armature in the magnetic field.~~



④ Speed regulation of a DC motor is defined as the change in speed from no load to full load.



Ans. to the Q. No - 4(a)

Merits and Demerits.

① Speed changes with every change in load, ~~to~~

② Maximum power developed is diminished in the same ratio as speed

③ Maximum power developed is diminished in the same ratio as speed.

④ It needs expensive arrangement for dissipation of heat produced in the controller resistor



Ans to the Q. No - 4(b)

Losses in a rotating DC machine

① Copper losses.

① Arm. cu loss

② Field cu "

③ Loss due to ~~the~~ brush contact.

• Iron losses

① Hysteresis loss

② Eddy current loss

• Mechanical loss.

① Friction loss


② windage loss


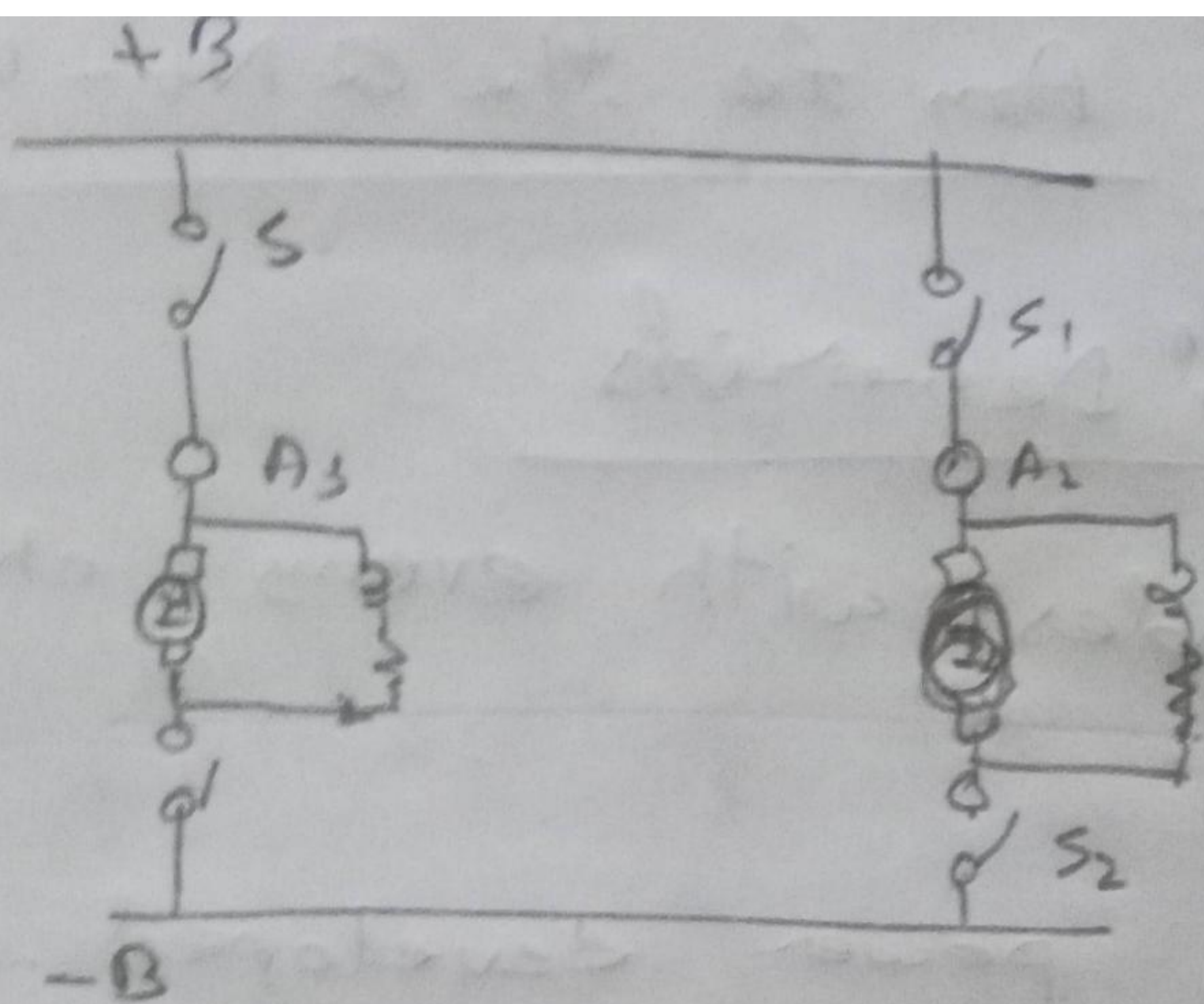
## Ans to the Q No - 1 (b)

- The +ve and -ve terminal of generator must be connected to +ve of bus bars.
- Induced e.m.f of generators should be preferably same.
- Armature is speeded up to the rated speed and then switch  $S_2$  close.
- Excitation of the  $G_2$  is changed until voltmeter  $V$  reads zero.
- Switch  $S_1$  is closed after that.
- Under this condition  $G_2$  is not taking any load (floating condition).
- Excitation of  $G_2$  is increased until it takes the proper share of load.





Load sharing:

