



Lab 4: Verification of Superposition Theorem.


Objective:

- To verify Superposition Theorem.


List of Equipment

- Trainer Board
- DMM
- 1 x 3.3k Ω resistor
- 1 x 4.7k Ω resistor
- 1 x 1K Ω resistor


Circuit Diagram

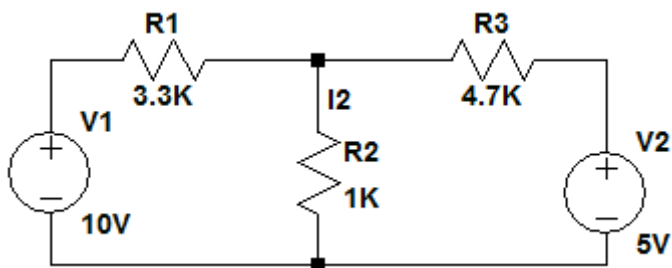

Circuit 1

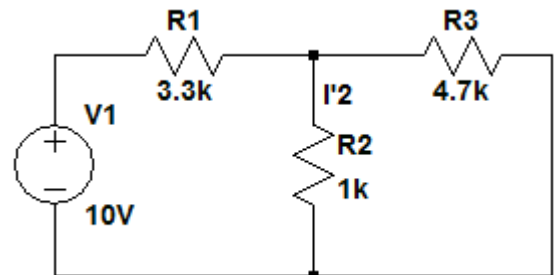

Circuit 2

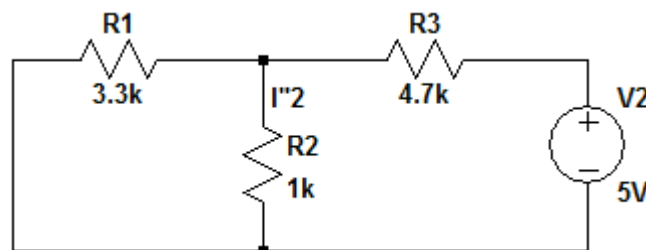

Circuit 3

Procedure:

- Set up Circuit 1.
- With both the voltage source connected to the circuit, measure I_2 , V_{R1} , V_{R2} , V_{R3} and record the values in appropriate tables.
- Setup Circuit 2. Measure and record I'_2 , V'_{R1} , V'_{R2} , V'_{R3} .
- Setup Circuit 3. Measure and record I''_2 , V''_{R1} , V''_{R2} , V''_{R3} .



Data Collection for Exp 4:

Group No. _____

Instructor's Signature _____

Table 1:

I_2	I'_2	I''_2	$I'_2 + I''_2$

Table 2:

V_{R1}	V'_{R1}	V''_{R1}	$V'_{R1} + V''_{R1}$

Table 3:

V_{R2}	V'_{R2}	V''_{R2}	$V'_{R2} + V''_{R2}$

Table 4:

V_{R3}	V'_{R3}	V''_{R3}	$V'_{R3} + V''_{R3}$

Report:

1. What is Superposition Theorem?
2. Theoretically Calculate all values of Table 1 to Table 4. **Show all the steps in details.**
3. Find the %Error between each value.
4. Show that your circuit followed superposition theorem.