

Lec - 1

Machine :- It is an object which convert energy to energy.

Classification

(1) Stationary \rightarrow mobile

(2) Rotational \rightarrow form. (rotational energy convert m)

→ Transformer :- (stationary machine)

* power transformer:- power in
the system transmits high power
to or low power to convert it.



Intro to Magnetic circuits

~~Motor~~ or generator :- power
generate m_p , &

both are conversion of energy.

Energy 1

Energy 2

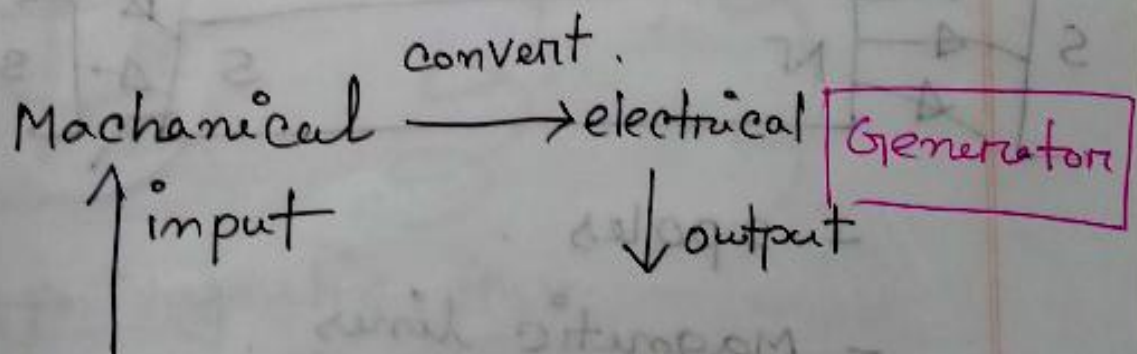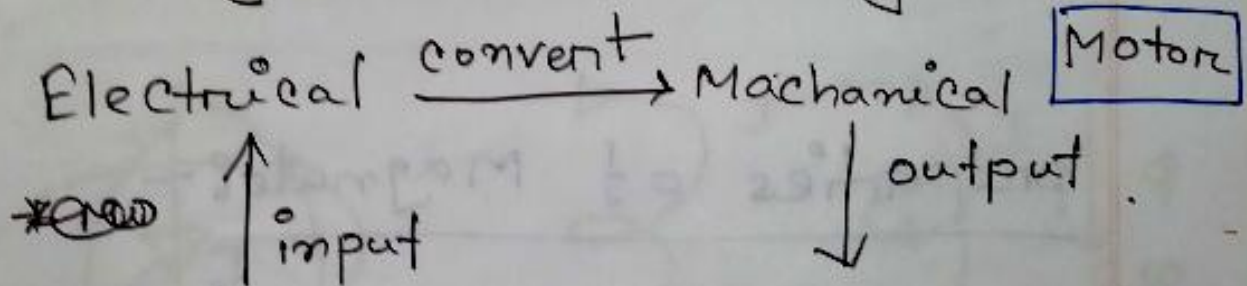


* Magnate \Rightarrow ~~two~~ ^{two} polar poles. ~~with~~ ^{find in nature} naturally permanent & temporary.

Magnetic circuit:-

* electro magnate:- solinoid.
(temporary magnate)


why ^{do} we need electromagnetic?:

properties of Magnate:-

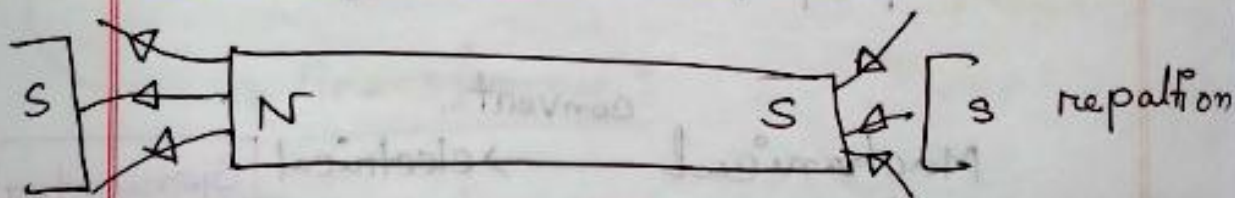

- 2 poles .
- Magnetic lines .
exit from North
entry to south .
- opposite pole attraction .
- same ~ Repulsion .


thumb is 2m current direction.

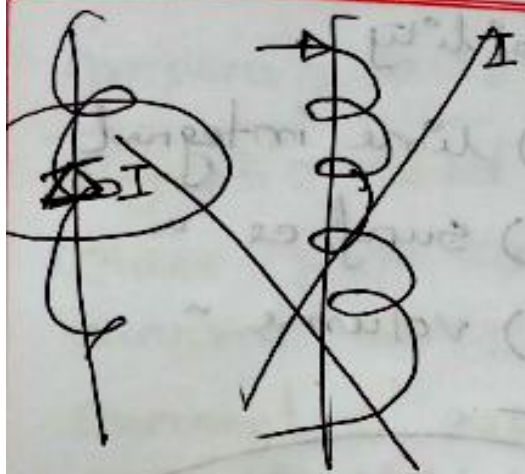

* Right hand rules

google or youtube.

Fleming right hand rule

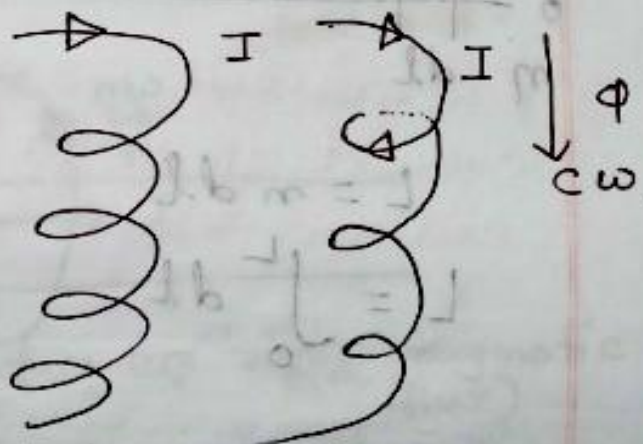

$\Phi \rightarrow$ Magnetic flux.

$B \rightarrow$ Magnetic flux density.


$$= \Phi/A$$

$H = \frac{B}{\mu} \rightarrow$ Magnetic field or
Magnetic field • Intensity.

* electromagnetic trump rule:


μ = mag permeability

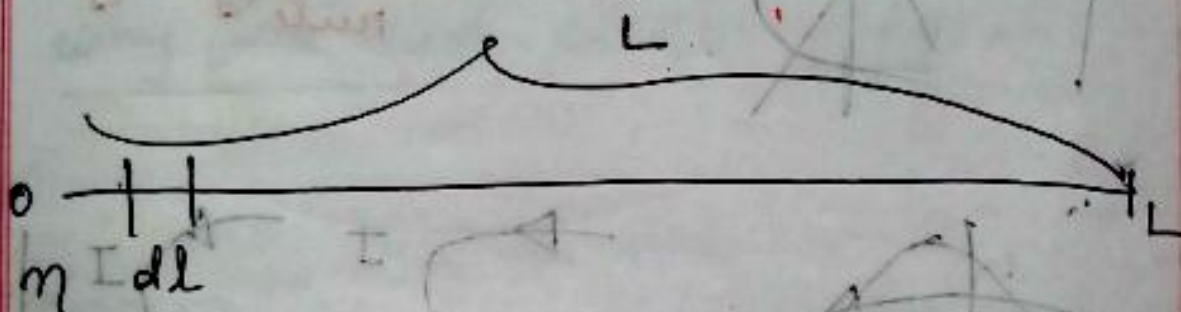* Integral \rightarrow (1) line integral
(2) surface \sim
(3) volume \sim



$$L = \eta dl$$

$$L = \int_0^L dl$$

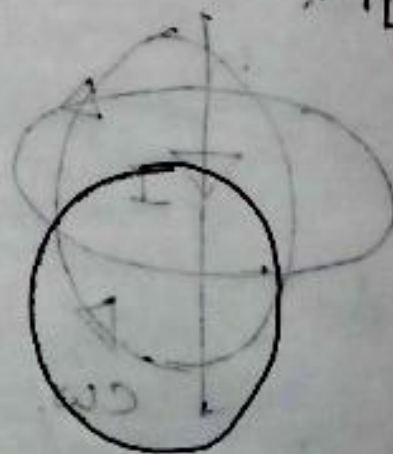

group: — EEE 363.3 SRD1 FALL 2018.

Lec:-2

H. dl નિમ્ન
o alpo current
જાણ્યું માગો,


Ampere's law:- Relation between

magnetic field and electric current.

Close path એ ડિગ્રી ચક્રીયાના electric
current માટે,

Current \Rightarrow cause

Magnetic field \Rightarrow effect.

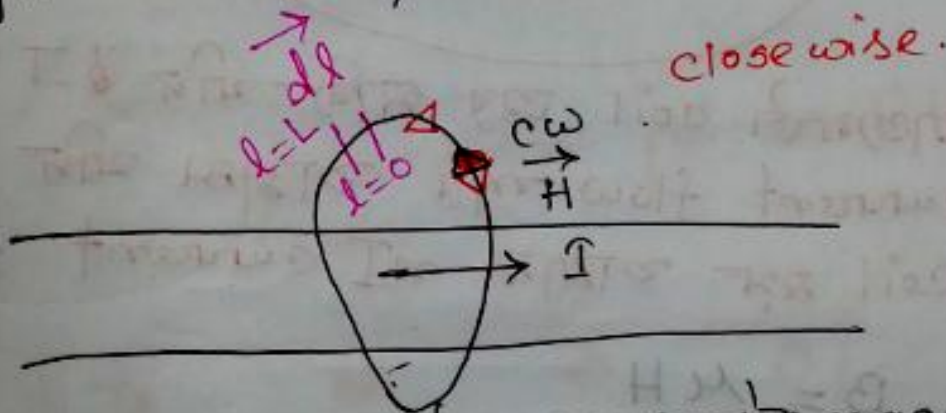


$\phi = BA$ (surface એ ચક્રીયાના magnetic flux)

$$\vec{B} = \mu \vec{H}$$

$\vec{H} \Rightarrow$ vector quantity
 \Rightarrow magnetic field intensity.

$\vec{B} =$ magnetic flux density.

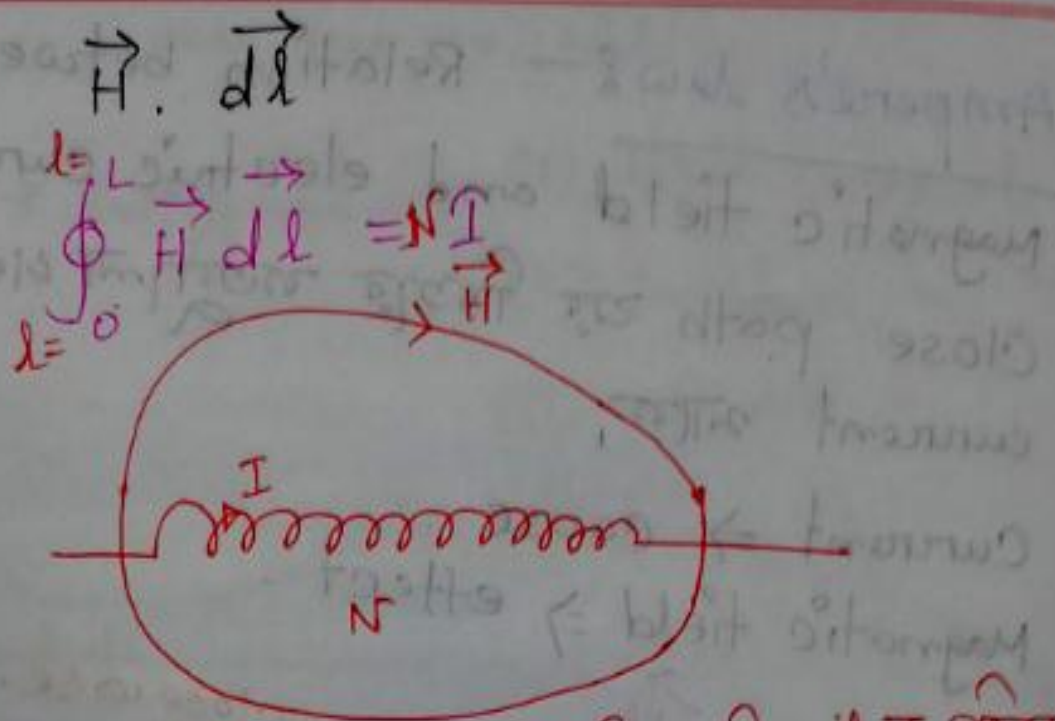

જાન્યારી coil પર સર્કિટ-ચીડ I પારિસ્થાન-
 current flow થી તારાલ ચીડ n સંજ્ઞા
 coil થી તારાલ nI current flow થી,

$$B = \mu H$$

μ = permeability of a medium/
 material.

* ferromagnetic material :- Fe
 (આણ લૂર સર્કિટ magnet થી)

Flux density in free space:-

(air)

$$B = \mu_0 H$$

$$4\pi \times 10^{-7}$$

μ_i = permeability of iron.


= $\mu_0 \mu_r$
 μ_r → Relative permeability of iron.



↓
 magnetic field lines under the core.

Magnetic circuit

electrical circuit :-

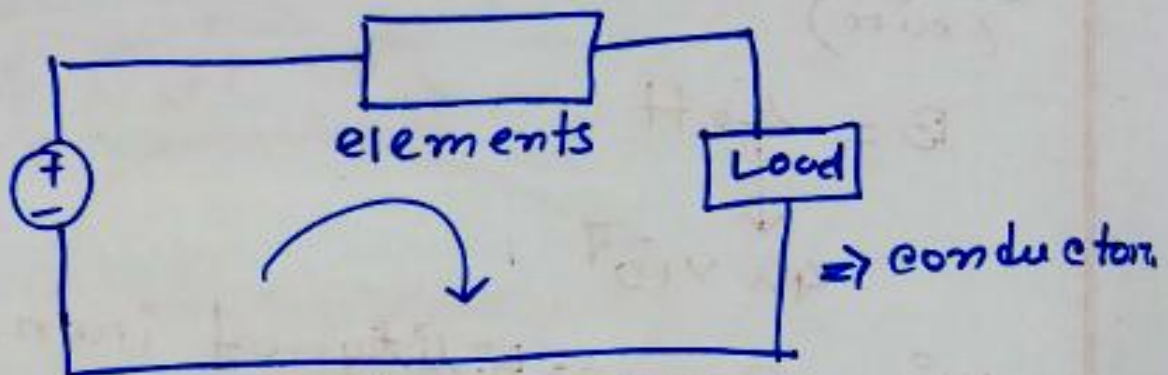


* Close path.

* conductor जिस close path बनाए

अर्थात्,

Magnetic circuit :-

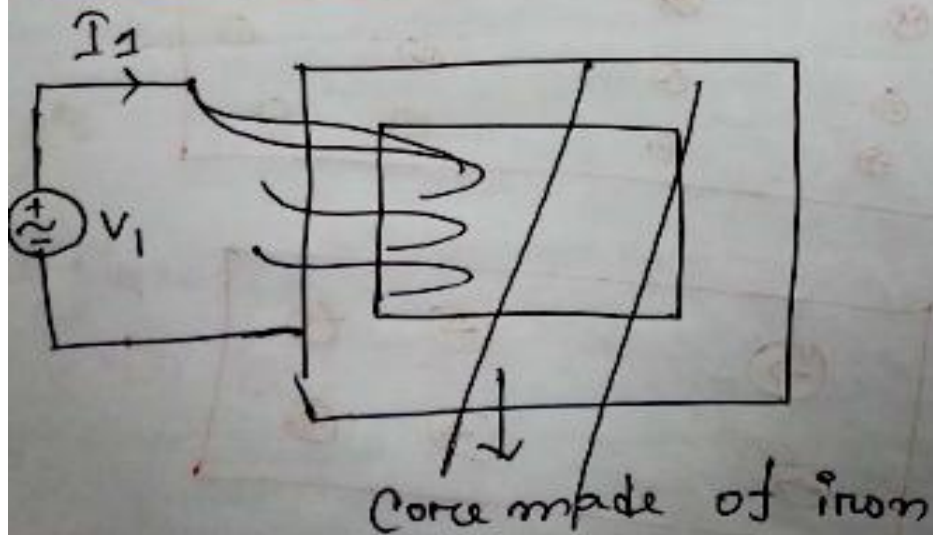


* reluctance :- $\frac{l}{\mu_r \mu_0}$ which is the flow of flux.
* permeability :- $\mu_r \mu_0$ help flux flow easily.

* Permeability :- $\frac{\text{flow rate}}{\text{area} \times \text{thickness}}$

$$NI = M MF$$


$$= \mathcal{F}$$

Problem


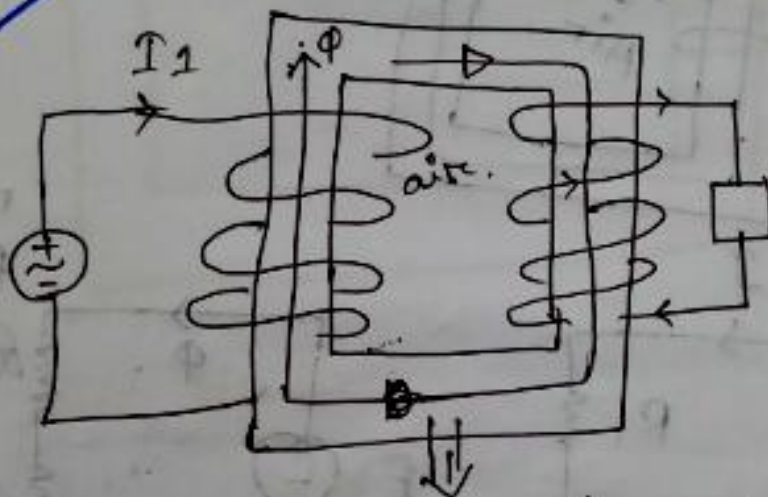


core ~~of~~ made of iron


Magnetic circuit + electric circuit :-

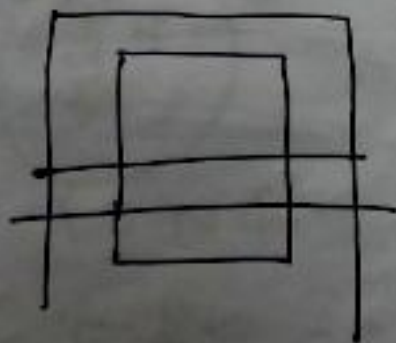

Problem

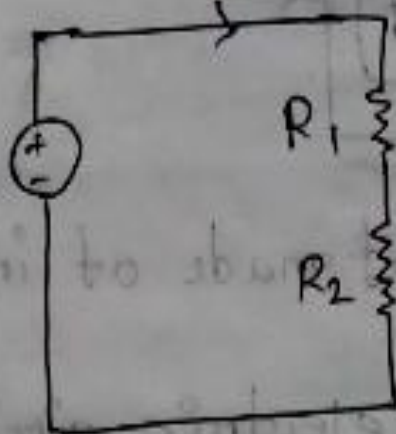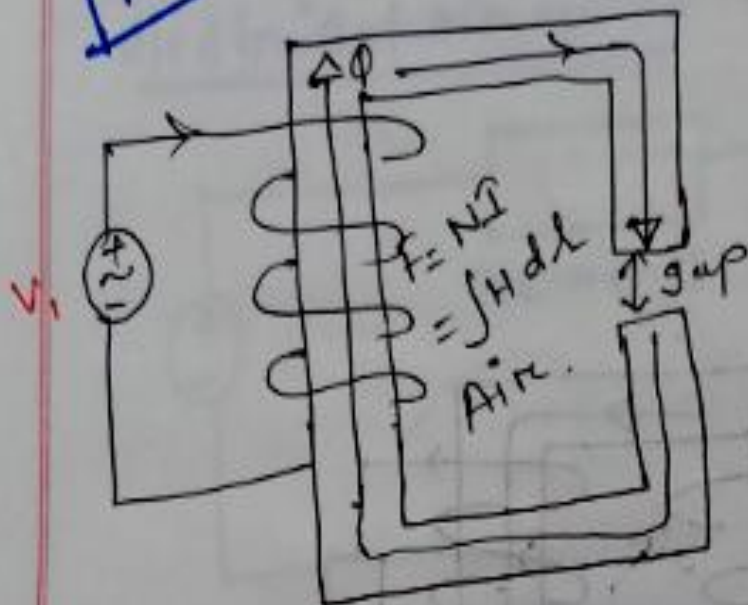

$$I = \frac{V}{R_1 + R_2}$$

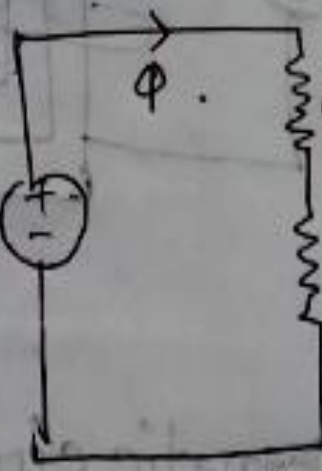

$$\Phi = \frac{F}{R_1 + R_2}$$

reluctance

reluctance

\Rightarrow core

reluctance


$R_2 \Rightarrow$

air

reluctance

Laws of electromagnetic induction


1st law

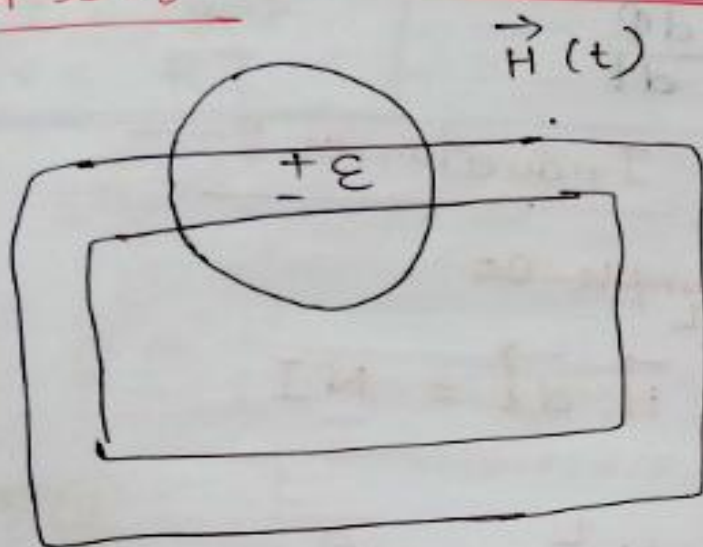

$$\epsilon = \frac{d\lambda}{dt}$$

2nd law

$$|\epsilon| = \frac{d\lambda}{dt}$$

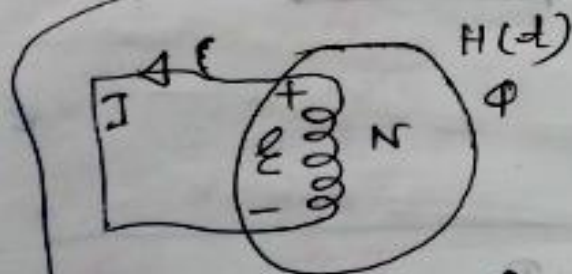

$$\lambda = N\phi$$

$$H(t)$$

$$B(t)$$

$$\phi(t)$$

$\lambda(t)$ = Total flux linkage with the coil/conductor.

$$|\epsilon| = N \frac{d\phi}{dt}$$

$$\begin{aligned} & \frac{dN\phi}{dt} \\ &= N \frac{d\phi}{dt} \end{aligned}$$

$$\mathcal{E} = - N \frac{d\phi}{dt}$$

Inductance

* for simple co
 $l = L$

$$\oint_{l=0} \vec{H} \cdot d\vec{l} = NI$$

$$\Rightarrow H(l)_0^L = NI$$

$$\Rightarrow \boxed{HL = NI}$$

$$NI = \mathcal{F}$$

$$\Rightarrow H = NI/L \quad \boxed{B = \mu H}$$

$$\phi = BA$$

$$= \mu H A$$

$$= \mu \frac{NI}{L} \cdot A$$

$$\phi = \frac{\mu A}{L} \cdot NI$$

$$\Rightarrow \left(\frac{L}{\mu A} \right) \cdot \phi = NI = \mathcal{F}$$

$$\Rightarrow \boxed{\mathcal{R} \phi = NI = \mathcal{F}}$$

$$\oint f = \mathcal{R}\Phi$$

$$V = RI$$

$$R = \frac{\rho L}{A}$$

$$= \frac{L}{\sigma A}$$

$\sigma \rightarrow$ conductivity

$$\rightarrow \mathcal{R} = \frac{L}{\kappa A}$$

Inductance :-

$$\mathcal{R}\Phi = NI$$


$$\Rightarrow \Phi = \frac{NI}{\mathcal{R}}$$

$$= \frac{NI}{\frac{L}{\kappa A}}$$

$$\Phi = \frac{\kappa A}{L} \cdot NI$$

Inductance :-

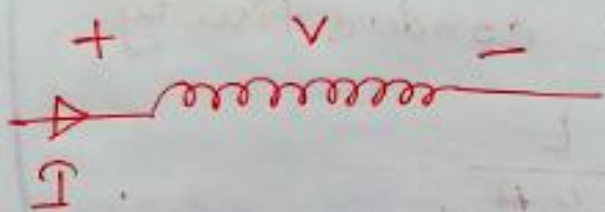* Induction change of current in
opposite direction, that's why
voltage produced



$$V \propto \frac{di}{dt}$$

$$\Rightarrow V = L \frac{di}{dt}$$

→ particular conductor
or conductance

$$\Rightarrow L = \frac{V}{\frac{di}{dt}}$$

→ cause effect

→ effect cause

* Cause & effect :-

electromagnetism :- ~~current & field~~
current flow with flux

Q. Inductance, $L = \frac{\lambda}{I}$


$$= \frac{N\Phi}{I}$$

$$= \frac{N(\mu AN/I)}{l}$$

$$= \frac{\mu N^2 A}{l}$$

Magnetic circuit of basic:-
Core & Load, magnetic
magnate.

Problem
used by now

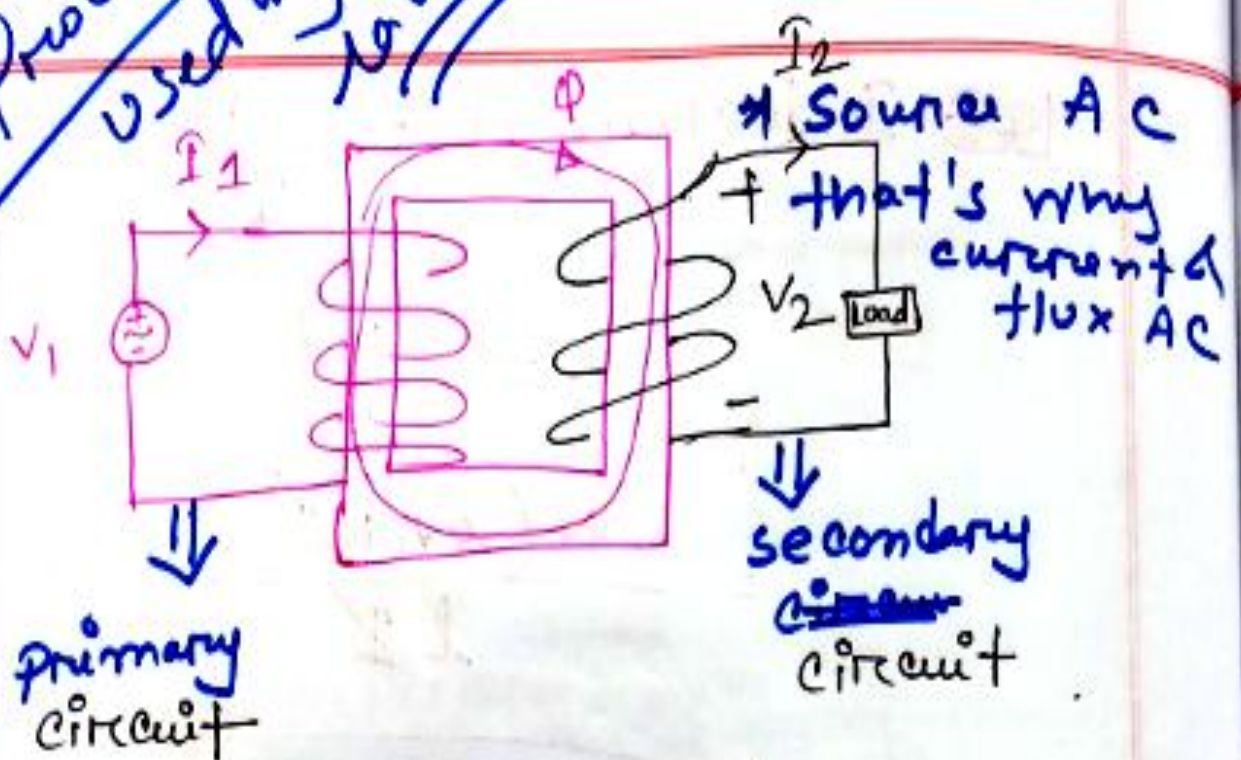

Energy conversion
Charles I Hubert

⇒ book

Electric Machine

* Next 2nd ~~class~~ week class shuru na,
* 4th class shuru na;

Lec:-3


Transformer Lecture:-

electro magnetic induction follow
જાણ.

Transformer:-

Make possible
power transformer, ~~inst~~ instrument transformer.

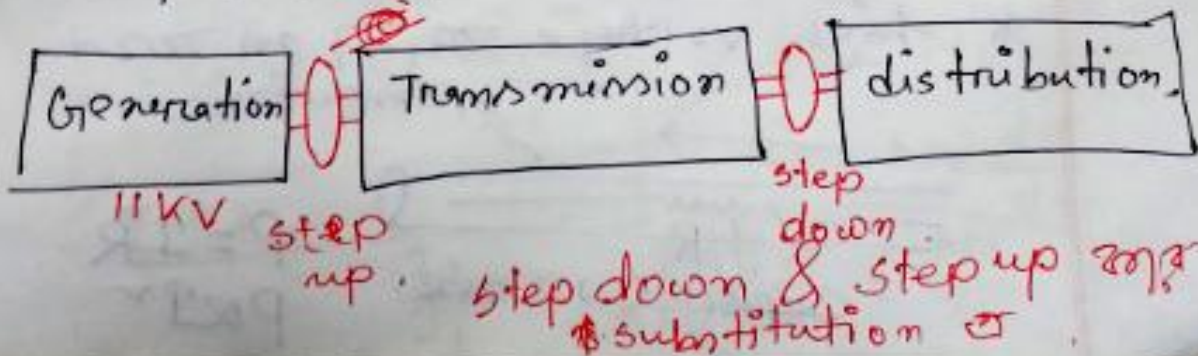- * Transformer ની પાવર રીટી ૩-
જાણ ના destroy જાણ,
- * voltage ન ~~convert~~ convert જાણ,
- * voltage level change જાણ system.
- * transformer power section
જાણ વ્યવસ્થા રૂપ
power system



* electrical energy secondary energy.

* power plant power generate કરાવે.

* આશુગઢ, અમીર, તળાકાલ power plant આર.

* તળાકાલનું primary સિસ્ટમ gas use કરા રહે.


* 11KV voltage use કરા રહે, power generate કરા રહે.

* Transmission લે- voltage 230KV.

* generation થી 11KV.

* that's why step up transformer use કરા રહે.

* high voltage આવી રહે.

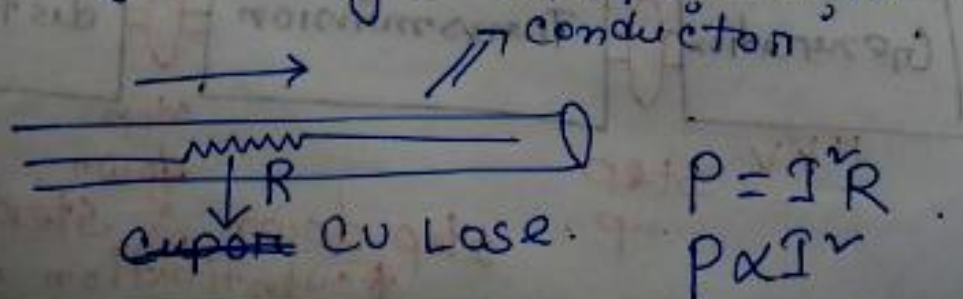

$$V = IR$$

~~But~~

$$P = VI$$


* current and voltage are power loss
are same.

* current and voltage are same
therefore voltage and current are same,

$$P = \uparrow V \downarrow I$$

History:-

principle:-

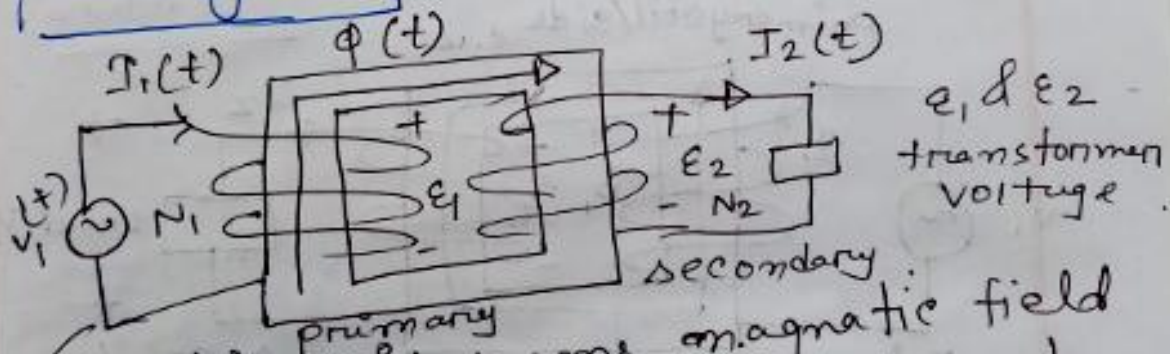


* Both coil same magnetic field
are under the same current
follow each other, couple coil.

$$\begin{aligned} E_1 I_1 &= E_2 I_2 \\ \Rightarrow \frac{E_1}{E_2} &= \frac{I_2}{I_1} \end{aligned}$$


$$\begin{aligned} E_1 &= N_1 \frac{d\Phi}{dt} \\ E_2 &= N_2 \frac{d\Phi}{dt} \end{aligned}$$

$$\frac{I_2}{I_1} = \frac{|E_1|}{|E_2|} = \frac{N_1}{N_2} = \text{turns ratio} = a$$

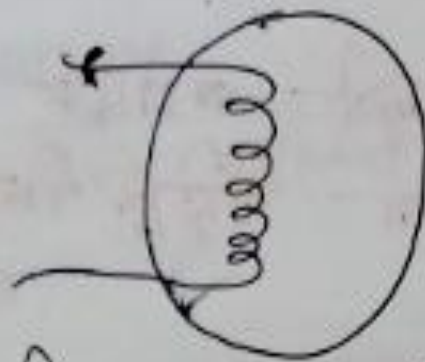

* મોટી rms value પસંદ કરવા સુધી,

Lec:- 4 (Transformer Lecture)

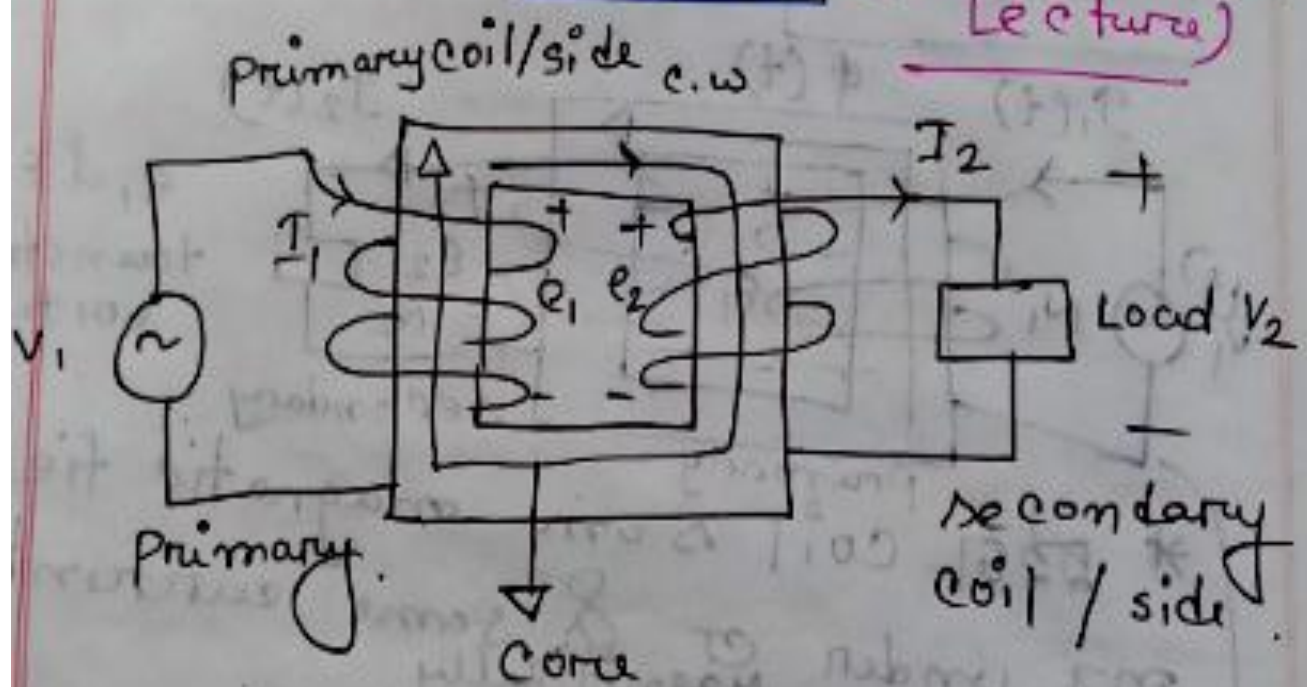

* loop ની close રહે તેથી I & V
produce રહે,

construction of single phase transformer \Rightarrow core type.

construction of three phase transformer \Rightarrow core type.

single phase transformer: \Rightarrow core type.

Classification of Transformer:-

(1) Based on phase.

\rightarrow single- ϕ .

\rightarrow 3- ϕ .

(2) Based on voltage level.

— step up

— step down.

(3) Based on power Rating.

\rightarrow High voltage XFR / Transmission.

\rightarrow Distribution XFR.

* XFR 2 line and 3 phase transformer.
रेखाचिह्न (line symbol).

$$\phi = \phi_{max} \sin \omega t$$

$$e_1 = \frac{d\lambda}{dt}$$

where,

λ = Total flux linkage with coil-1.

$$= N_1 \phi$$

$$e_1 = N_1 \frac{d\phi}{dt}$$

[Primary]

$$e_2 = N_2 \frac{d\phi}{dt}$$

[secondary]

$$\Rightarrow e_1 = N_1 \phi_{max} \omega \cos \omega t$$

\Downarrow

rms value of $\cos \omega t$.


$$\Rightarrow E_1 = \frac{N_1 \phi_{max} \omega}{\sqrt{2}}$$

$$e_2 = \frac{N_2 \phi_{max} \omega \cos \omega t}{\omega \cos \omega t}$$

\Downarrow

$$E_2 = \frac{N_2 \phi_{max} \omega}{\sqrt{2}}$$
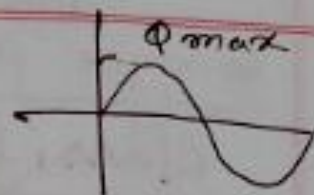
$$\frac{E_1}{E_2} = \frac{\frac{N_1 \phi_{max} \omega}{\sqrt{2}}}{\frac{N_2 \phi_{max} \omega}{\sqrt{2}}} = \boxed{\frac{N_1}{N_2}}$$



$$\omega = 2\pi f$$

\Downarrow
Angular frequency.

→ ~~turns~~ ~~the~~ turns ratio ~~is~~ a on
K.

$$F_1 = F_2$$

$$F = NI$$

$$N_1 I_1 = N_2 I_2$$


$$\Rightarrow \frac{I_1}{I_2} = \frac{N_2}{N_1} = E_1/E_2$$

$$\Rightarrow \frac{E_1}{E_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2} = \text{Turns Ratio}$$

* Ideal transformer \hookrightarrow ~~flux~~ ^{flux} change
losses 2%.

* leakage ^{flux} change?

Problem

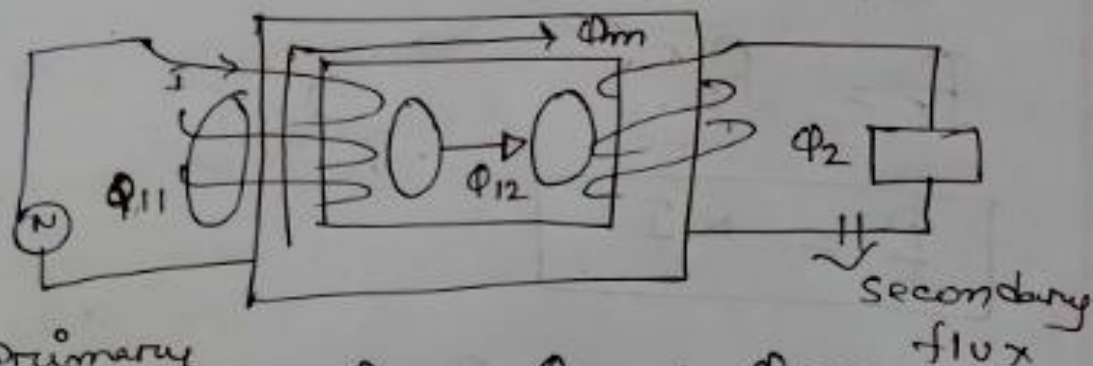


primary
flux,

$$\Phi_1 = \Phi_{11} + \Phi_m$$

↓
Leakage flux

$$\Phi_2 = \Phi_{12} + \Phi_m$$

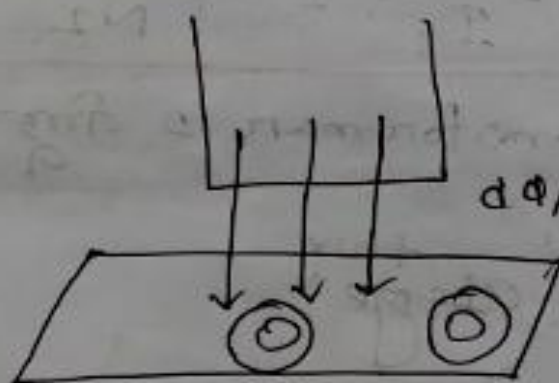

[magnetic
time lag or magnetic
variable].
iron
conductor


core is current low.

(1) hysteresis loss

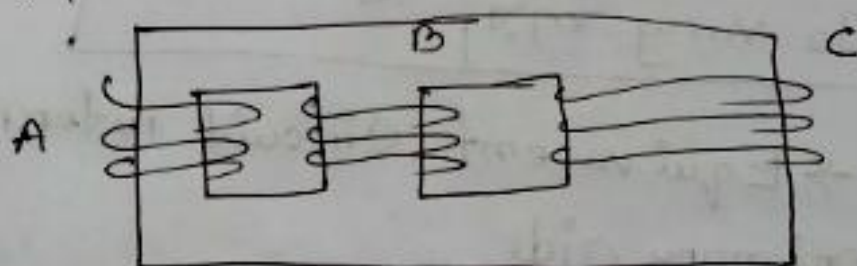(2) ed loss.


এই ১০ম সমস্যাটির জন্য core ৬ সিসিডিন লেয়ার
এর sheet তৈরি করা ২০,

Flash point: ~~the~~ liquid ko jaldi temp. badhane ke liye air ko jaldi induce krna. transformer ko 160° ka flash point. ko jaldi badhane ke liye, freezing point ko 15° C ko jaldi badhane ke liye.



Equivalent circuit of transformer:

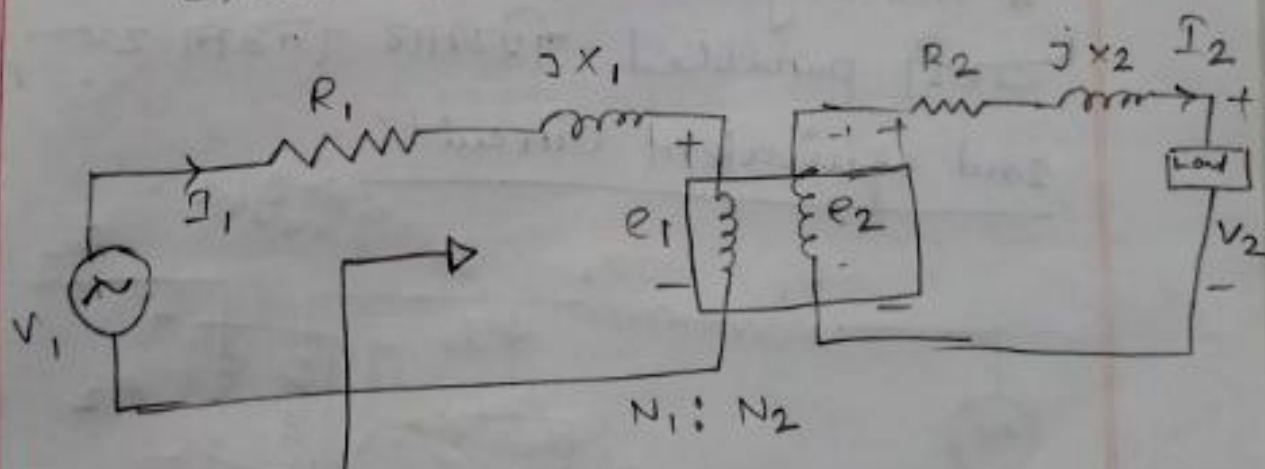Coil is nothing but inductor.
So, ko jaldi badhane ke liye, transformer ko basic krke puri krna.
(1) coil & (2) core.



$$X = j\omega L$$


$$X_C = \frac{1}{j\omega C}$$

- * V_2 fixed voltage 220V,
- * I_2 vary 0.1A,


→ Equivalent circuit referred to primary side.

→ secondary side.

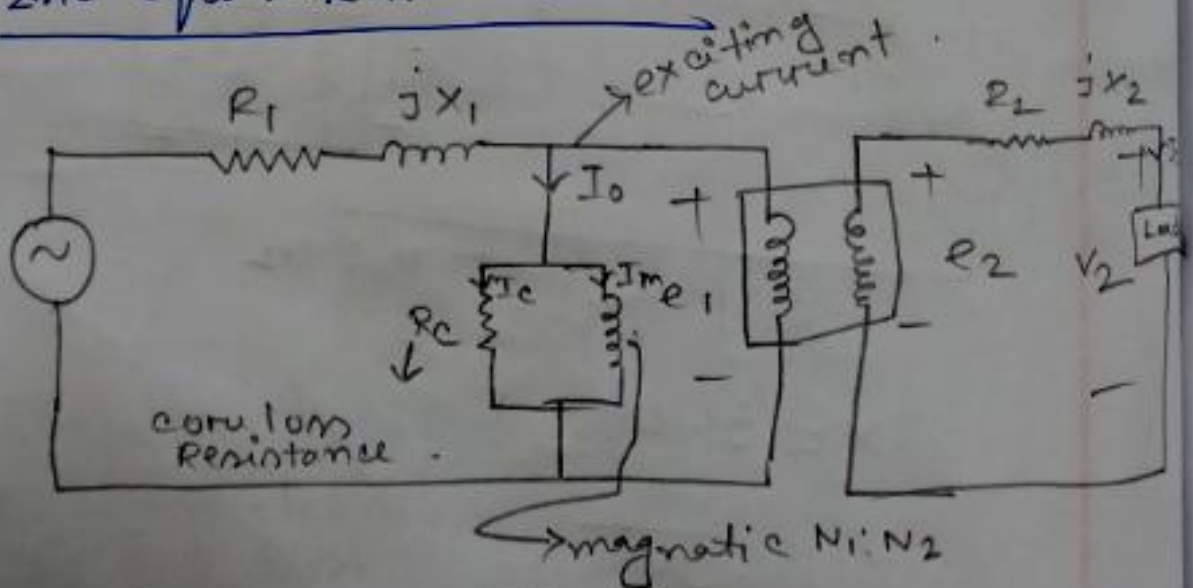* Hysteresis loss & ed current loss are parallel resistance referred to 2nd equivalent circuit:



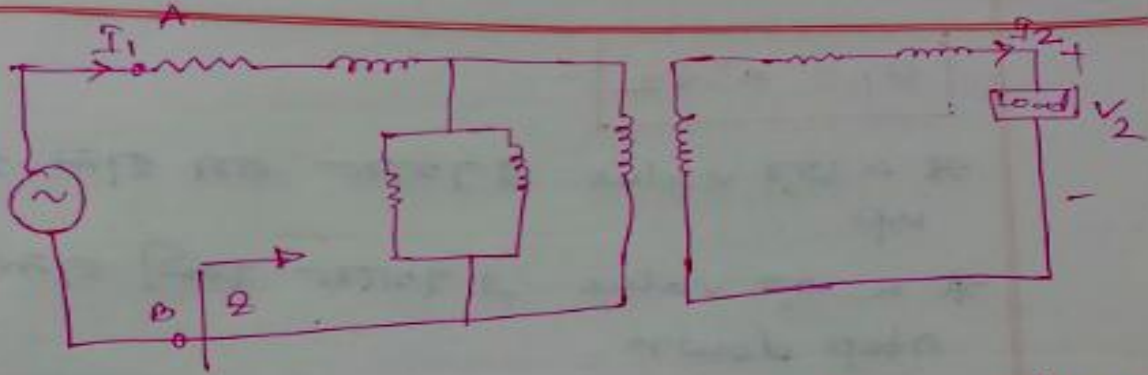reluctance $\mu_0 \mu_r$, basically current flow for



Z_2 = Actual Impedance of secondary side.

Z_1 = Impedance ~~referred~~ ^{referred} to primary side.

$$Z_1 = \frac{V_1}{I_1} ; Z_2 = \frac{V_2}{I_2}$$

$$\frac{Z_1}{Z_2} = \frac{V_1}{I_1} \bigg/ \frac{V_2}{I_2}$$

$$\Rightarrow \frac{V_1}{V_2} \times \frac{I_2}{I_1} = a \times a = a^2$$

$$Z_1 = a^2 Z_2$$

* a > 1 value \Rightarrow step up.


* a < 1 value \Rightarrow step down.

$$Z_1 = a^2 Z_2$$

- * a value 17778 નમ સ્ટેપ up.
- * a value 17778 નમ સ્ટેપ down.

Lec:- 5

Equivalent circuit of a XFR:

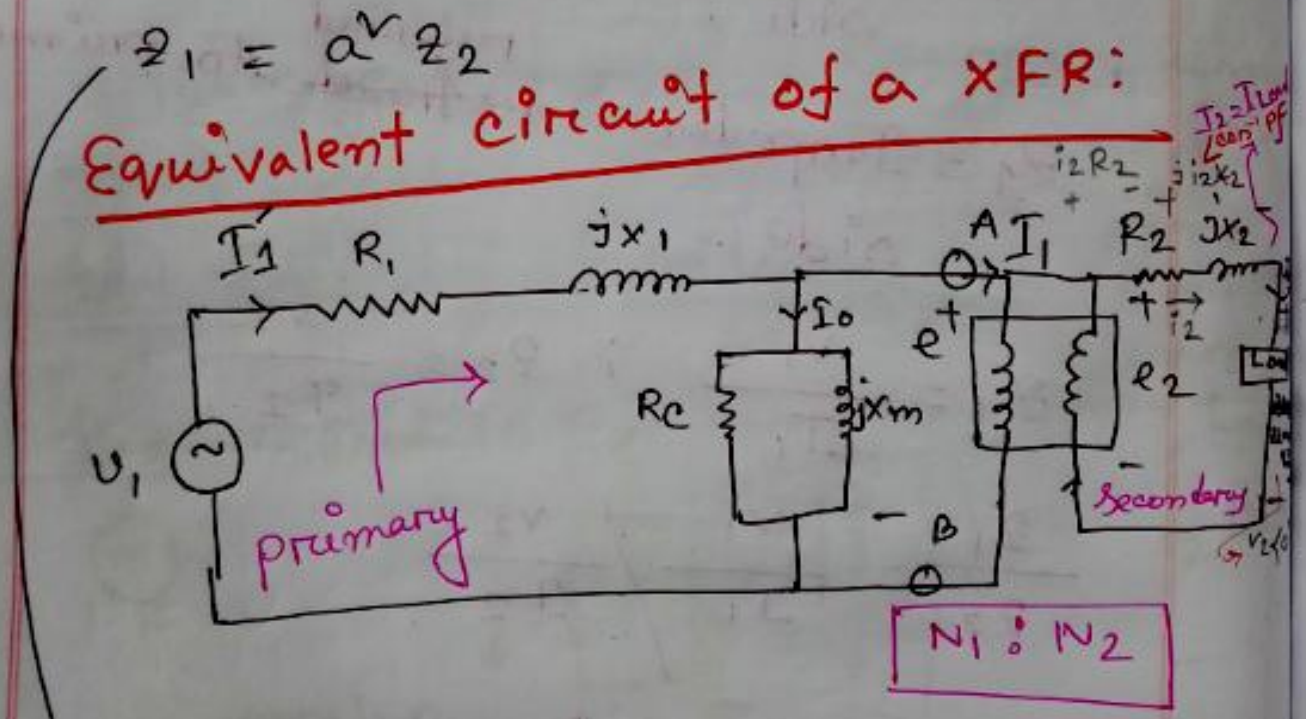


$$Z_2 = \frac{1}{2} Z_1$$

$$\frac{I_2}{I_1} = a$$

$$I_1 \phi =$$

$$I_1' =$$

① Eq. circuit referred to primary side.

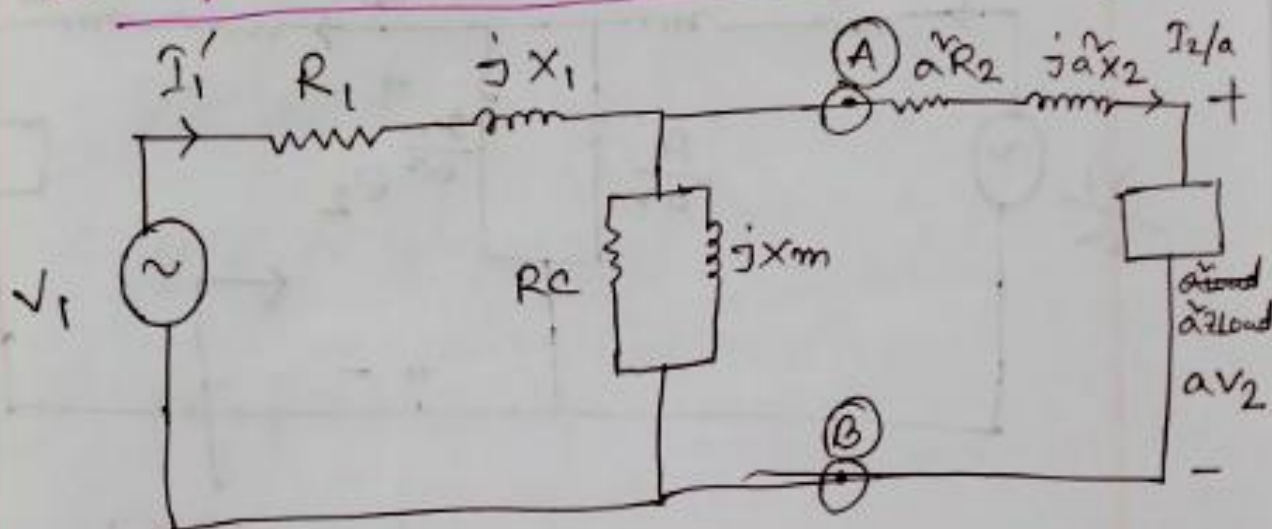

$$E_1 = a E_2$$


$$V_1 = a V_2$$

$$\frac{V_1}{V_2} = a$$

$$V_1 = a V_2$$

$$I_1 = \frac{I_2}{a}$$

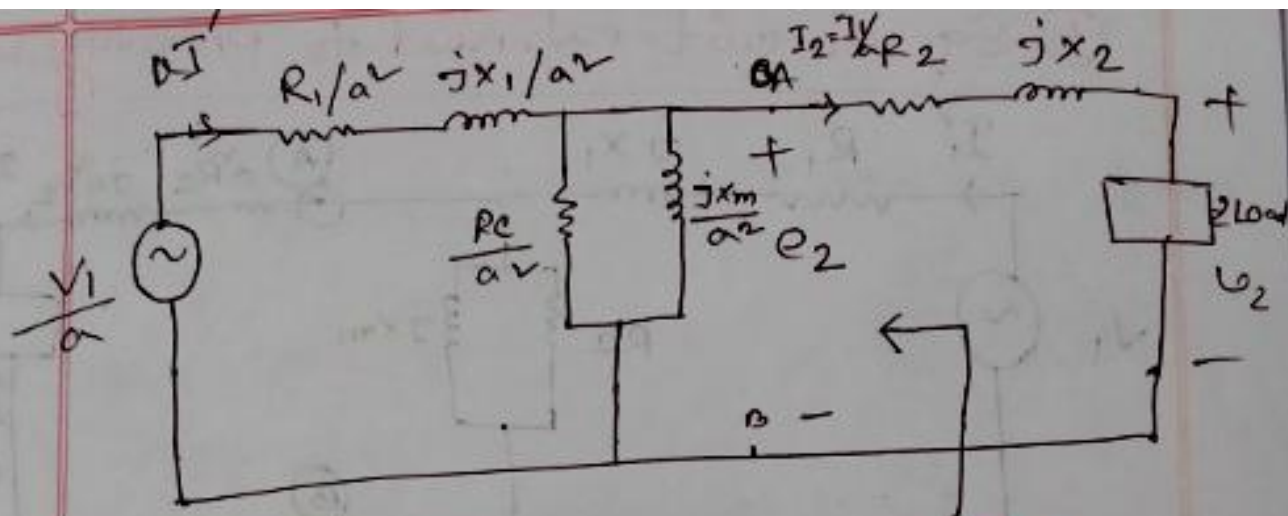② Eq. circuit referred to secondary side.



Phasor Diagram of a XFR:

~~$v = V \sin(\omega t + 0) \rightarrow \text{Triangular}$~~
 ~~$\rightarrow \text{Triangular}$~~

$v = V \sin(\omega t + 0) \rightarrow \text{Trigonometric form}$

$v = V \angle 0^\circ \rightarrow \text{phasor form}$

$i = I \sin(\omega t - \theta) \rightarrow \text{T.F}$

$i = I \angle -\theta$

Rec \rightarrow polar :-

$$z = a + jb \rightarrow \text{Rectangular}$$

$$z = r \angle \theta \rightarrow \text{polar or phasor}$$

$$r = |z| = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

Polar \rightarrow Rec

$$z = r \angle \theta \rightarrow \text{polar}$$

$$z = \underbrace{r \cos \theta}_{\text{real}} + \underbrace{j r \sin \theta}_{\text{Imaginary}}$$

$$v = A \cos \omega t$$

$$v = |v| \angle \theta$$

$$= A \angle 0^\circ$$

* phasor form Draw step: —

(1) Assume/ select a reference vector.

(2) Usually consumer's voltage are considered as reference [reference means \times axis 0° or 2π angle].
 $\theta_2 < 0^\circ$

(3) power factor of consumer. Load to assume/ known, $\theta = \cos^{-1} pf$


(4) Determine all voltage drops and the load current.

(5) Determine all voltage drops and branch current.

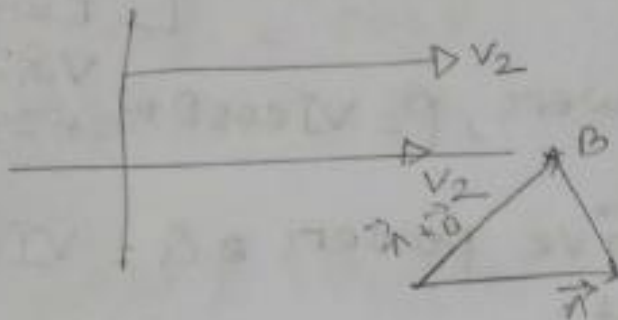(6) Apply KVL and KCL where appropriate.

Most of the load is Inductive. Inductive ^{lag} current ~~lead~~ m.v, capacitor is voltage ~~lead~~ ^{lead} m.v.

reference ^{of} means angle 0 ^{branch current} ^{choice} w.r.t.



power factor
 $\cos \theta$

$$P.f = \cos \theta$$

$$= \cos(\angle \hat{V}, \hat{I})$$

$$\cos \theta = P.f$$


$$\Rightarrow \theta = \cos^{-1} P.f$$

$$V_2 < 0^\circ$$

$$I_2 < 0^\circ \text{ in phase}$$



$$\xrightarrow{I_2} \xrightarrow{V_2}$$

$$I_2 < -\theta$$

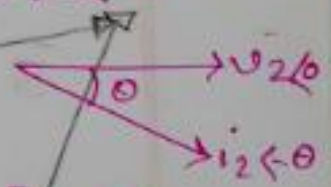

$$I_2 < \theta$$


$$i_2 < \theta$$

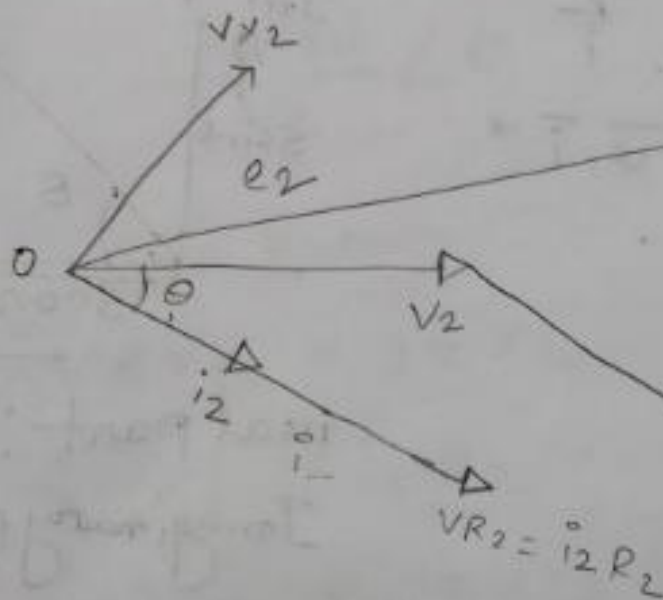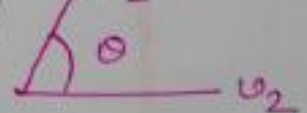

magnitude { Apparent $S = VI$ kVA [\hat{V} Voltage \hat{V} ,
 current \hat{I}]
 Real Power, $P = VI \cos \theta$ W
 Reactive power $Q = VI \sin \theta$ var.

~~Apparent~~:
Real power: \hat{V} AC Voltage \hat{V}
 and AC current \hat{I}

$$\bar{S} = \bar{V} \cdot \bar{I}^*$$

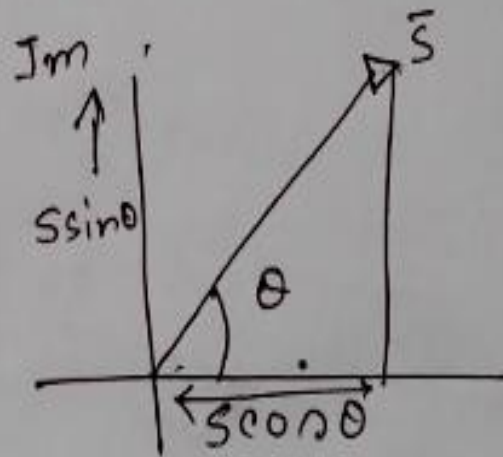

real part: $VI \cos \theta$
 Imaginary part: $VI \sin \theta$

(4) Load \rightarrow Srated

$$pf = \cos \theta$$

$$V_{rated} = V_2$$

lagging \rightarrow cw
leading \rightarrow c.cw.

given,

$$S_{rated} = |V_2| |\dot{i}_2|$$

$$\Rightarrow |\dot{i}_2| = \frac{S_{rated}}{|V_2|}$$

$$\Rightarrow \dot{i}_2 = \frac{S_{rated}}{V_2} \angle \theta$$



(5) (i) $\dot{i}_2 = \text{known}$

$$(ii) \otimes V_{x2} = j \dot{i}_2 X_2$$

$$(iii) V_{R2} = \dot{i}_2 R_2$$

$$(iv) -e_2 + V_{R2} + V_{x2} + V_2 = 0$$
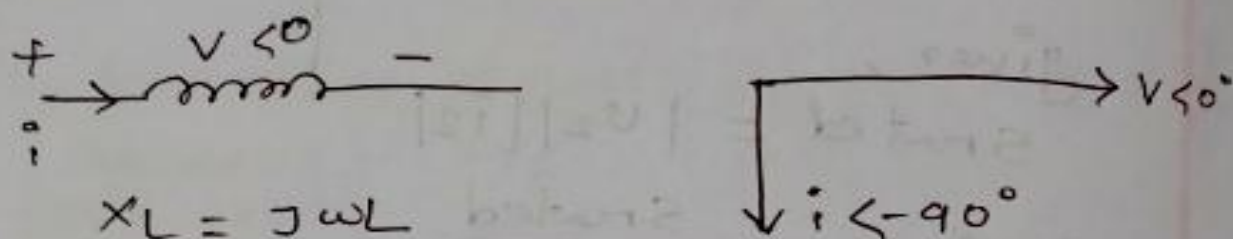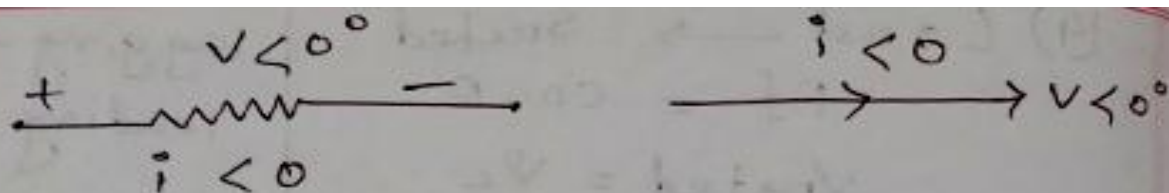
$$e_2 = \overline{V_{R2}} + \overline{V_{x2}} + \overline{V_2}$$



$$X_L = j\omega L$$

$$= \omega L \angle 90^\circ$$

$$i = \frac{V \angle 0^\circ}{\omega L \angle 90^\circ}$$

$$= \frac{V}{\omega L} \angle -90^\circ$$



$$e_2 = V_{R2} + V_{X2} + V_2$$

$$V_{R2} = i_2 R_2$$

$$V_{X2} = jX_2 i_2$$

Lec-6

Phasor diagram of a xfr:-

(1) Step:-

(1) select/ Assume a reference voltage

(2) Usually consumer voltage is considered as reference.


(3) power factor of consumer's load to assume.

(4) Determine the load current.

(5) ~ all the voltage drops and branch current.

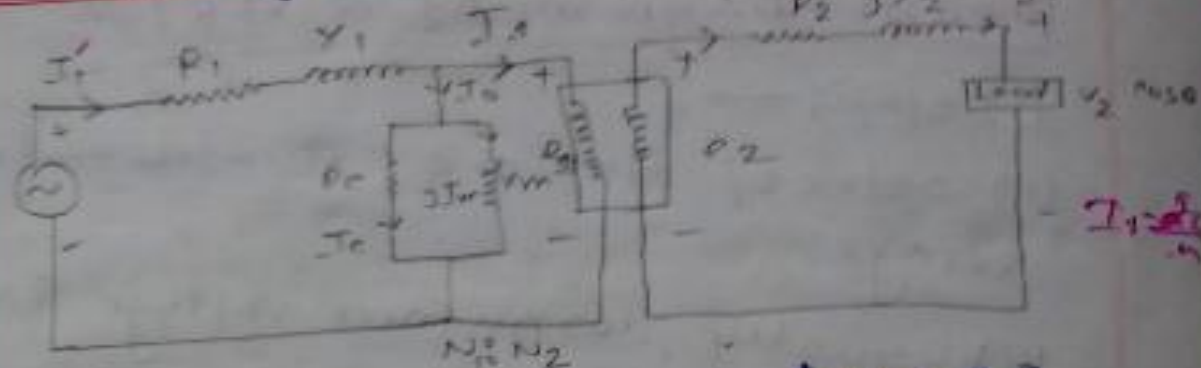(6) Apply KVL/KCL where appropriate.

Always V_2 reference direction નો ધરો,
 અને angle 0 માં રાખો,



(1) \rightarrow

(2) $\rightarrow V_2 < 0^\circ \Rightarrow$


(3) $\rightarrow \cos \theta$ lagging

(4) \rightarrow Load current $I_2 < 0$

(5) (6) \rightarrow KVL $\rightarrow E_2 = V_{R2} + V_{X2} + V_2$

I_c & e_1 same
 phase નો ધરો,





I_m & e_1 નો
 90° lag
 નો ધરો.

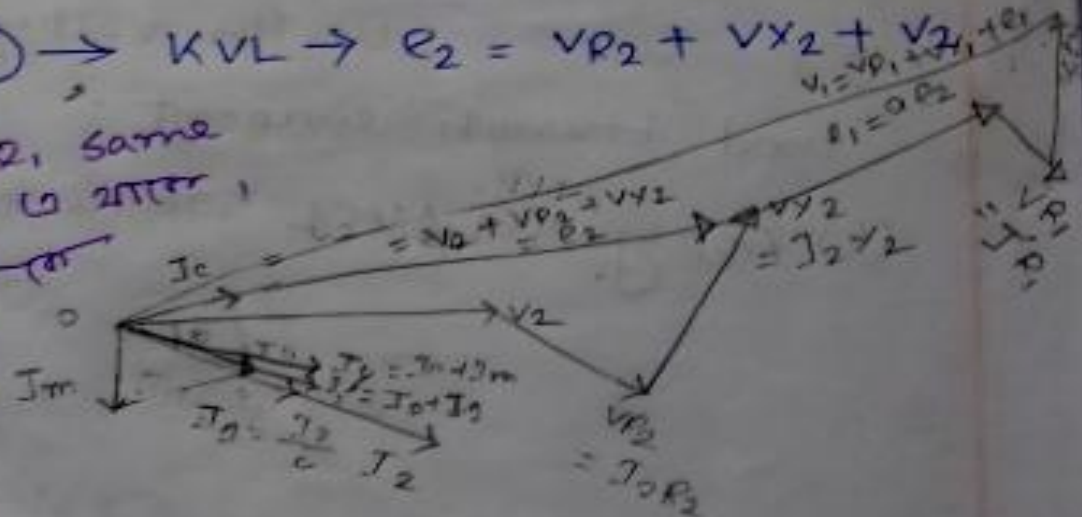


Lag \rightarrow ccw

Lead \rightarrow ccw

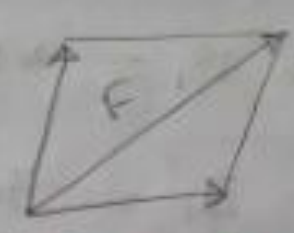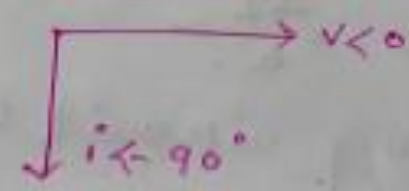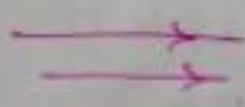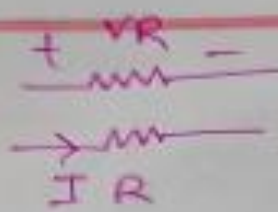Note: KVL Always
 Secondary -
 circuit નો
 નિર્ણય.



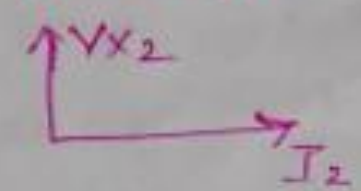Induction is such that reference is taken
 v_2 lead i_2



From circuit:-

$$a = \frac{N_1}{N_2} = \frac{e_1}{e_2}$$

$$\Rightarrow \boxed{e_1 = a e_2}$$

[e_1 & e_2 Always
 in phase & same
 direction but
 magnitude different 2nd]

$$\frac{I_2}{I_1} = a$$

$$\Rightarrow I_1 = \frac{I_2}{a}$$

primary circuit \rightarrow KVL & KCL apply
use this eqn,

$$\text{KVL} \rightarrow V_1 = VR_1 + VX_1 + e_1$$

$$\text{KCL} \rightarrow I_1' = I_0 + I_1$$

$$\Rightarrow VR_1 = I_1' R_1; VX_1 = I_1' X_1$$

$$I_0 = I_c + jI_m$$

$$I_c = \frac{e_1}{R_c}$$


$$I_m = \frac{e_1}{X_m}$$

Approximate Equivalent circuit

$$H = \frac{V_o}{V_i}$$

* અચ્ચત Approximate equivalent circuit નોંધે છે કે અચ્ચત X_c & R_c નો overlook કરવામાં, અચ્ચત બહુ Simple series circuit થાય,

Voltage Regulation:-

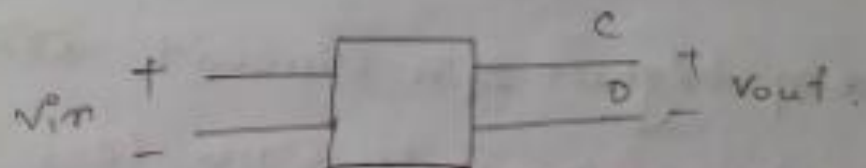

$$VR = \frac{V_{no\ load} - V_{full\ load}}{V_{fl}} \times 100\%$$

* અચ્ચત no load અચ્ચત V_{in} જોડે જાય,

* અચ્ચત full - - - V_{out} - - -

* Loading side કે voltage રાખી -
તમામ તમામ no load કે voltage
રાખી નોંધ 25,

* NO load:

240V and 200V

T.V
 $P = VI \cos \theta$

* $\cos \theta$ is called power factor

* η higher in circuit then

* transformer :- core loss & copper loss.

core loss :- Transformer core is through it flux produce the core loss.

copper loss :- copper wire is through it loss.

Lec:- 7

Transformer Tests:-


(1) open circuit Test (to determine R_c and X_m)


(2) short ~ ~ (To determine R_{eq} and X_{eq})

R_c = core loss reactance


X_m = Magnetizing ~

Ref. to primary side

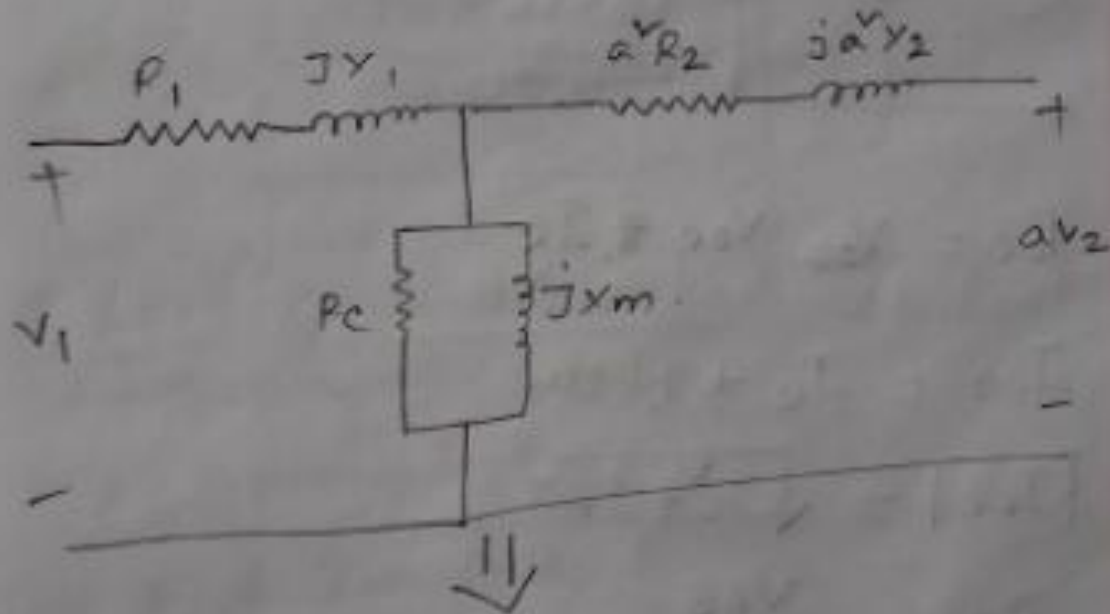

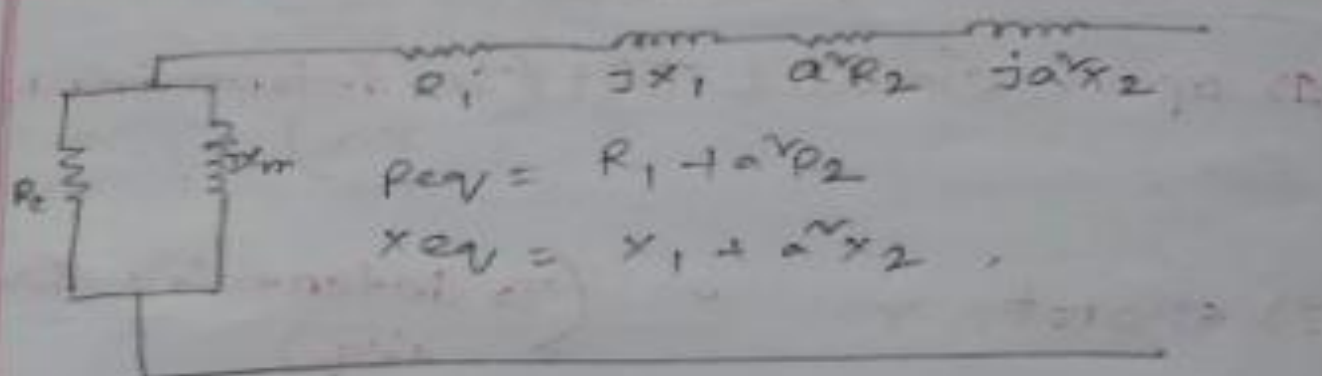

open circuit test

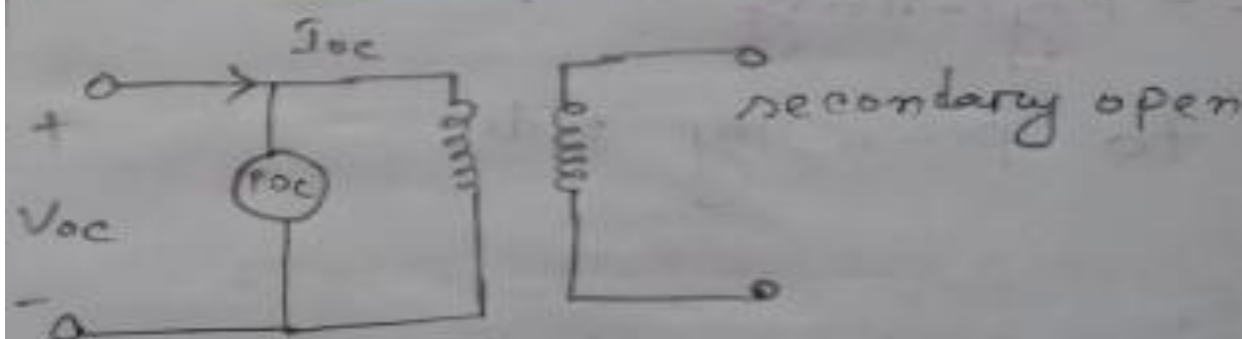

$$P_{oc} = V_{oc} I_{oc}$$

$$I_{oc} = I_c + jI_m$$

$$|I_{oc}| = \sqrt{I_c^2 + I_m^2}$$


$$R_c = \frac{V_{oc}}{I_c}$$

$$X_m = \frac{V_{oc}}{I_m}$$

Re 2m Real power, wt workman fig
measure 2m 2m, Rated current means
voltage apply 2m 2m max output 2m 2m But Rated voltage
7276-

Known V_{oc} , I_{oc} , and P_{oc}

App eq circuit.

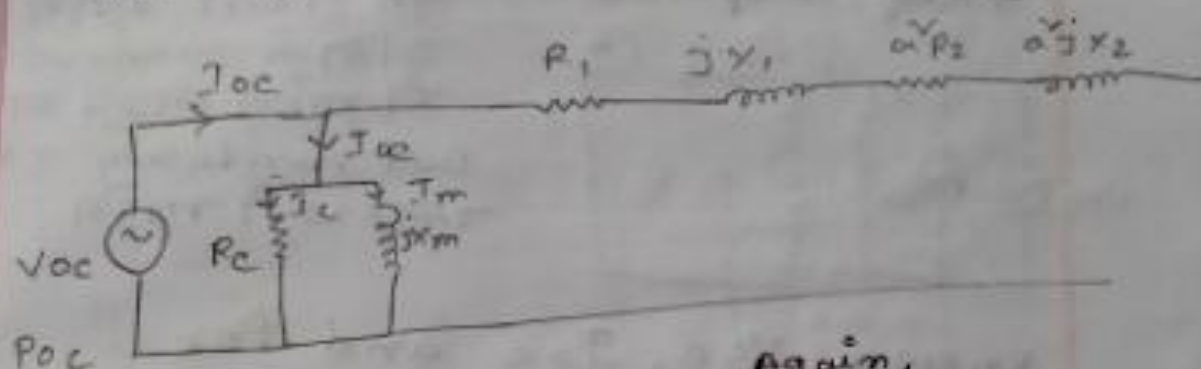

$$I_{oc} = I_c + jI_m$$

$$P_{oc} = V_{oc} I_c$$

$$\Rightarrow I_c = \frac{P_{oc}}{V_{oc}}$$

$$I_{oc} = \sqrt{I_c^2 + I_m^2}$$

$$\Rightarrow I_m = \sqrt{I_{oc}^2 - I_c^2}$$

known.

I_c and I_m are determined.

$$V_{oc} = R_c I_c$$

$$\Rightarrow R_c = \frac{V_{oc}}{I_c}$$


Again,

$$V_{oc} = I_m X_m$$

$$\Rightarrow X_m = \frac{V_{oc}}{I_m}$$

Short circuit test:-

→ R_{eq} , X_{eq} 120
400 I_{sc}

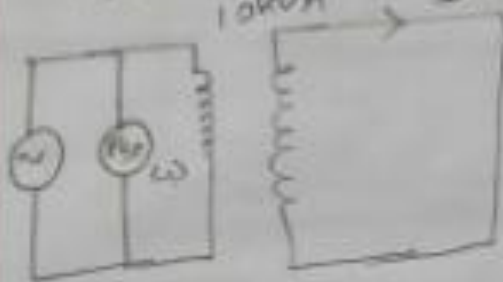

* રાખ્યાન, V થીની એકે
તે short થીના
ત્રીજીની current
તે નીમ નાકુમ થા,
But randomly રાખી
રનાર એકે થીના,

Known V_{sc} , I_{sc} and P_{sc}

$$I_{rated 1} = \frac{10 \text{ KVA}}{400}$$

$$= \frac{10 \times 10^3}{400}$$


$$= 25 \text{ A}$$

$$I_{rated 2} = \frac{10 \text{ KVA}}{120}$$

$$= \frac{10 \times 10^3}{120}$$

$$= 83 \text{ A}$$

equivalent circuit

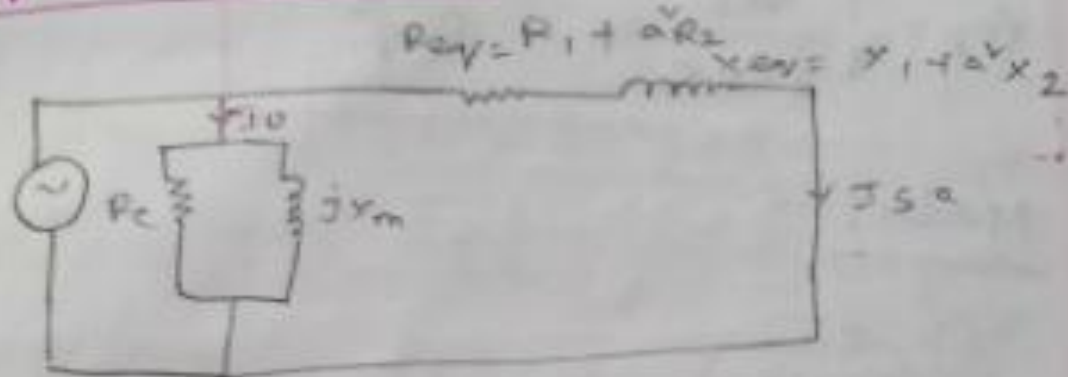

$I_o \rightarrow$ Negligible

$$P_{sc} = I_{sc}^2 \cdot R_{eq}$$

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$V_{sc} = I_{sc} Z_{eq}$$

$$\bar{Z}_{eq} = R_{eq} + jX_{eq}$$

$$|Z_{eq}| = \sqrt{R_{eq}^2 + X_{eq}^2}$$


$$Z_{eq} = \frac{V_{sc}}{I_{sc}}$$

$$\Rightarrow \sqrt{R_{eq}^2 + X_{eq}^2} = \frac{V_{sc}}{I_{sc}}$$

Distribution transformer secondary
440V, 277V
(3 phase).

$$X_{eq} = \sqrt{\frac{V_{sc}^2}{I_{sc}^2} - R_{eq}^2}$$

Math: →

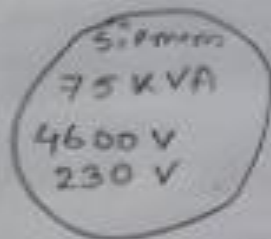

open circuit test: —

$$V_{oc} = 230 \text{ V}$$

$$I_{oc} = 13.04 \text{ V}$$

$$P_{oc} = 521 \text{ W}$$

$$\Rightarrow P_{oc} = V_{oc} \cdot I_{oc}$$

$$\Rightarrow 521 = 230 \cdot I_{oc}$$

$$\Rightarrow I_{oc} = 2.265 \text{ A}$$

$$R_{oc} = \frac{230}{2.265} =$$

$$X_m = \frac{V_{oc}}{I_m}$$

$$\Rightarrow I_m = \sqrt{I_{oc}^2 - I_c^2}$$

$$P_{oc} = V_{oc} \cdot I_c$$

$$\Rightarrow I_c = \frac{P_{oc}}{V_{oc}}$$

$$R_c = \frac{V_{oc}}{I_c}$$

per unit value:-

Base:-

Z_{base}

V_{base}

I_{base}

$S_{base}(kVA)$

→ 2000 KVA 10KV 25%
 ବାଲ 10KV 25%
 ବାଲ 10KV 25%

Actual value
Base value

$$R_{pu} = \frac{R_{eq}}{Z_{base}}$$

$$X_{pu} = \frac{X_{eq}}{Z_{base}}$$

$$V_{pu} = \frac{V}{V_{base}}$$

$$I_{pu} = \frac{I}{I_{base}}$$

* rated current, voltage, power
अङ्कित मान base मान

~~per~~ per system ko jaganidhi Percentage ko-
rakhna hoga.

Lec-8

$$(b) \text{ per unit Resistance } R_{pu} = \frac{R_{eqHS}}{Z_{baseHS}} \\ = \frac{R_{eqLS}}{Z_{baseLS}}$$

$$\text{per unit Reactance, } X_{pu} = \frac{X_{eqHS}}{Z_{baseHS}} \\ = \frac{X_{eqLS}}{Z_{baseLS}}$$

$$\text{per unit Impedance, } Z_{pu} = \frac{\sqrt{R_{eqHS}^2 + X_{eqHS}^2}}{Z_{baseHS}} \\ = \frac{\sqrt{R_{eqLS}^2 + X_{eqLS}^2}}{Z_{baseLS}}$$

HS \rightarrow primary

Referred to side \rightarrow

$$\boxed{R_{eq,HS} = R_1 + a^2 R_2} \Rightarrow \text{Not given}$$

$$\boxed{X_{eq,HS} = x_1 + a^2 x_2} \Rightarrow \text{Not given.}$$

$$Z_{eq,HS} = \sqrt{R_{eq,HS}^2 + X_{eq,HS}^2}$$

$$a = \frac{V_1}{V_2} = \frac{4600}{230} = 20$$

(b) Using short circuit Test Data:

$$V_{sc} = 160.8 \text{ V}$$

$$I_{sc} = 16.3 \text{ A}$$

$$P_{sc} = 1200 \text{ W}$$

$$R_{eq,HS} = \frac{P_{sc}}{I_{sc}^2} = 4.51 \Omega$$

$$Z_{eq,HS} = \frac{V_{sc}}{I_{sc}} = 9.86 \Omega$$

$$X_{eq,HS} = \sqrt{Z_{eq,HS}^2 - R_{eq,HS}^2} = 8.77 \Omega$$

* Transformer is rated power all the same.
base ~~val~~ power 2m rated ~~to~~ power.

$$\begin{aligned} Z_{\text{base HS}} &= \frac{V_{\text{base HS}}}{I_{\text{base HS}}} \\ &= \frac{V_{\text{base HS}}}{\frac{S_{\text{base}}}{V_{\text{base HS}}}} \\ &= \frac{V_{\text{base HS}}^2}{S_{\text{base}}} = \frac{(4600)^2}{(75 \times 10^3)} \\ &= 282.13 \Omega \end{aligned} \quad \left. \begin{array}{l} S_{\text{base}} = \\ \text{Apparent base} \\ \text{power} \end{array} \right\}$$

$$R_{pu} = \frac{4.51}{282.13} = 0.0151$$

$$X_{pu} = \frac{8.77}{282.13} = 0.031$$

$$Z_{pu} = \sqrt{R_{pu}^2 + X_{pu}^2}$$

Per unit Impedance Z_{pu}

$$= \frac{9.86}{282.13} = 0.345$$

19 তারিখ Mid:- syllabus - 12 তারিখ
অর class

(c) Voltage Regulation:-

$$VR = \frac{|V_{nl}| - |V_{fl}|}{|V_{fl}|} \times 100\%$$

$$\Rightarrow PF = \cos \theta$$

$$\Rightarrow \theta = \cos^{-1}(0.75)$$

$$41.40^\circ$$

$$VR = \left\{ \sqrt{(R_{pu} + \cos \theta)^2 + (X_{pu} + \sin \theta)^2} - 1 \right\}$$

$$PF = \cos \theta = 0.75$$

$$\Rightarrow \theta = \cos^{-1}(0.75)$$

$$= \frac{VR}{R_{pu}}$$

$$R_{pu} = 0.0319$$

$$VR = 3.19\%$$

$$BD = 50 \text{ Hg}$$

$$USA = 60 \text{ Hg}$$

2/15 Given,

$$S_{\text{rated}} = 100 \text{ kVA}$$

$$f = 60 \text{ Hz}$$

$$V_{\text{rated}} = 7200 \text{ V}$$

$$V_2 \text{ rated} = 480 \text{ V}$$

$$R_{HS} = 3.06, X_{HS} = 6.05$$

$$X_{mHS} = 17809$$

$$R_{LS} = 0.014, X_{LS} = 0.27$$

$$R_{fCHS} = 71400$$

$$pf = 0.75 \text{ lagging}$$

Generate
→ current supply
mg.

Load current
7.27

$R_{HS} 2\pi \omega L_{HS}$


R_L

Load voltage

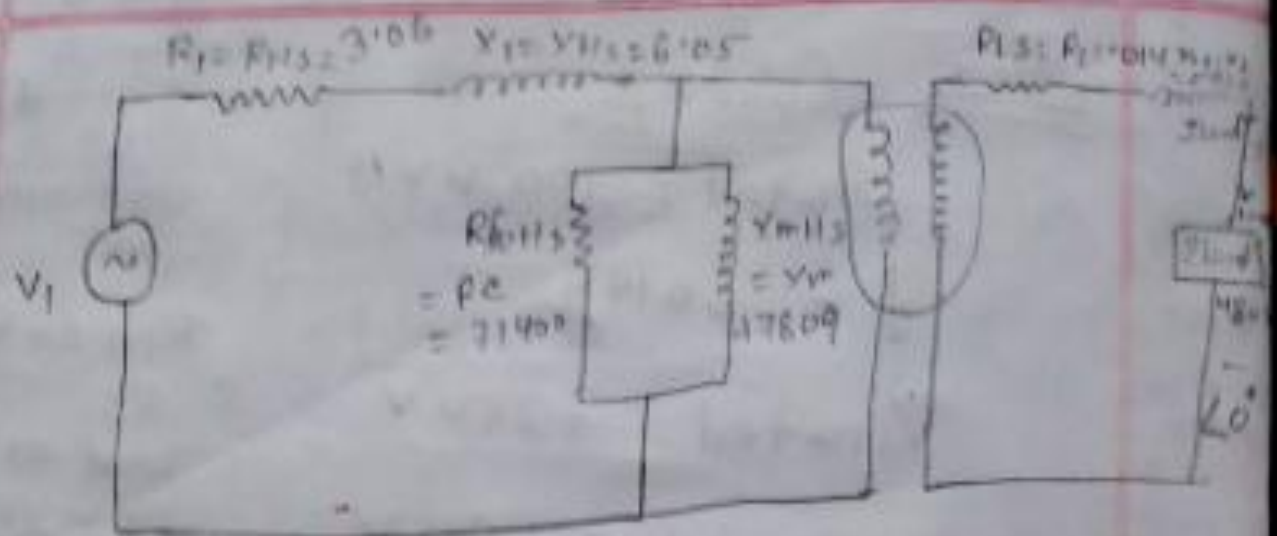7.27

step up or
step down

તમામ પાવર 100kVA ના થાય ત્યારે Rated power supply
અર્થ, Total V_{load}




$Z_{Load} = ?$

Assume load is supplying rated 100kVA

$$Z_{Load} = \frac{V_{Load}}{I_{Load}} = \frac{480}{\frac{S_{rated}}{480}} = \frac{480^2}{\frac{100 \times 10^3 \angle -\cos^{-1} 0.75}{480}}$$
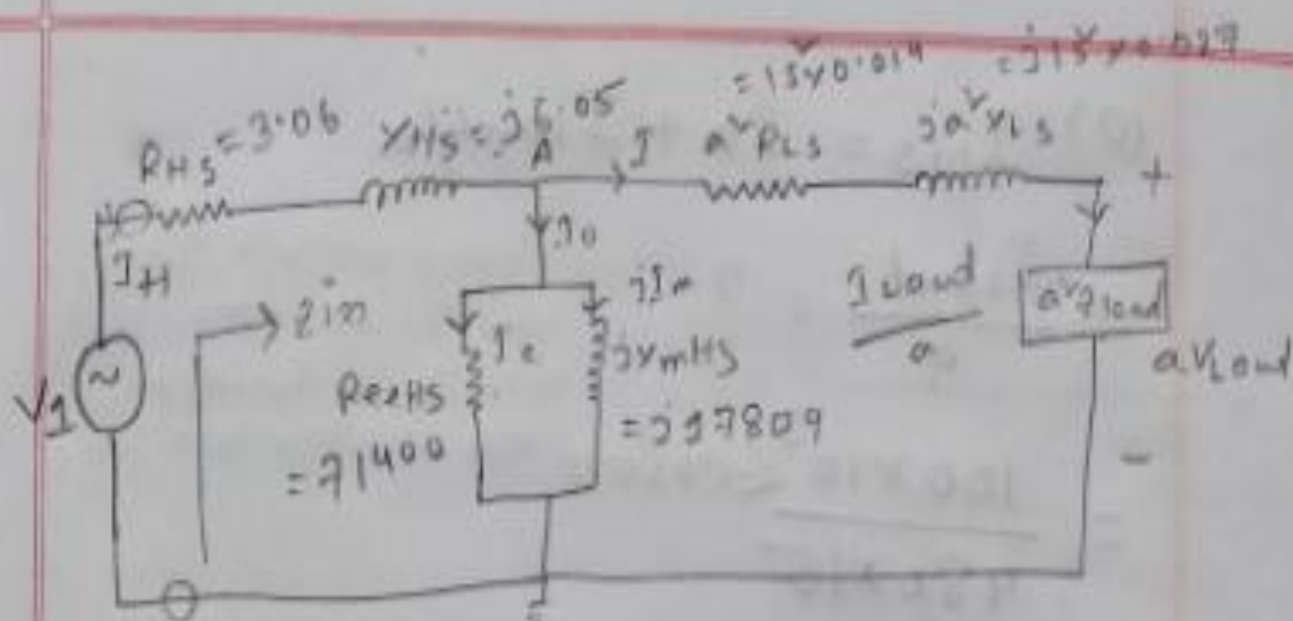
$$I_{Load} = \frac{V_{Load}}{Z_{Load}} = \frac{S_{rated}}{V_{Load}} = \frac{100 \times 10^3}{480} \angle -\cos^{-1} 0.75$$



appropriate eq. circuit reference to HS.

$$(a) a = \frac{7200}{480} = 15$$

$$R_{eqHS} = R_{HS} + a^2 R_{LS}$$

$$X_{eqHS} = X_{HS} + a^2 X_{LS}$$

$$(b) Z_{im} = R_{eqHS} + jX_{eqHS} + a^2 Z_{load}$$

$$(c) I_{HS} = I_0 + I_{Load}/a$$

$$\Rightarrow \frac{I_{Load}}{a} = ? \quad \text{primary circuit total current } I_{HS} \text{ is } I_0 \text{ \& } I_{Load}/a$$

$$= \frac{100 \times 10^3 \angle -0.75^\circ}{480 \times 15}$$

$$(d) V_{in} = V_1 = I_{HS} \times Z_{in}$$

$$= \left(I_0 + \frac{I_{Load}}{a} \right) \times Z_{in}$$

$$I_0 =$$

$$V_A = a V_{Load} + \frac{I_{Load}}{a} (\bar{a}^2 R_{LS} + j \bar{a}^2 X_{LS})$$


$$I_0 = I_c + j I_m = \frac{V_A}{R_{feHS}} + j \frac{V_A}{X_{mHS}}$$

$$I_c = \frac{V_A}{R_{feHS}}$$

$$I_m = \frac{V_A}{X_{mHS}}$$

$$I_{HS} = I_0 + \frac{I_{Load}}{a}$$


$$V_1 = I_{HS} \times Z_{in}$$

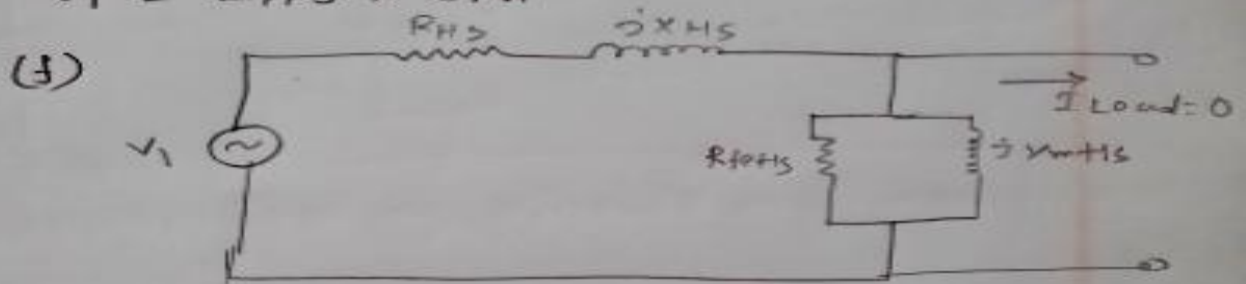

$$Z_{in} = (R_{HS} + jX_{HS} + (R_{feHS} \parallel jX_{mHS}))$$

Lec:-9

Induction Motor/Machine:-

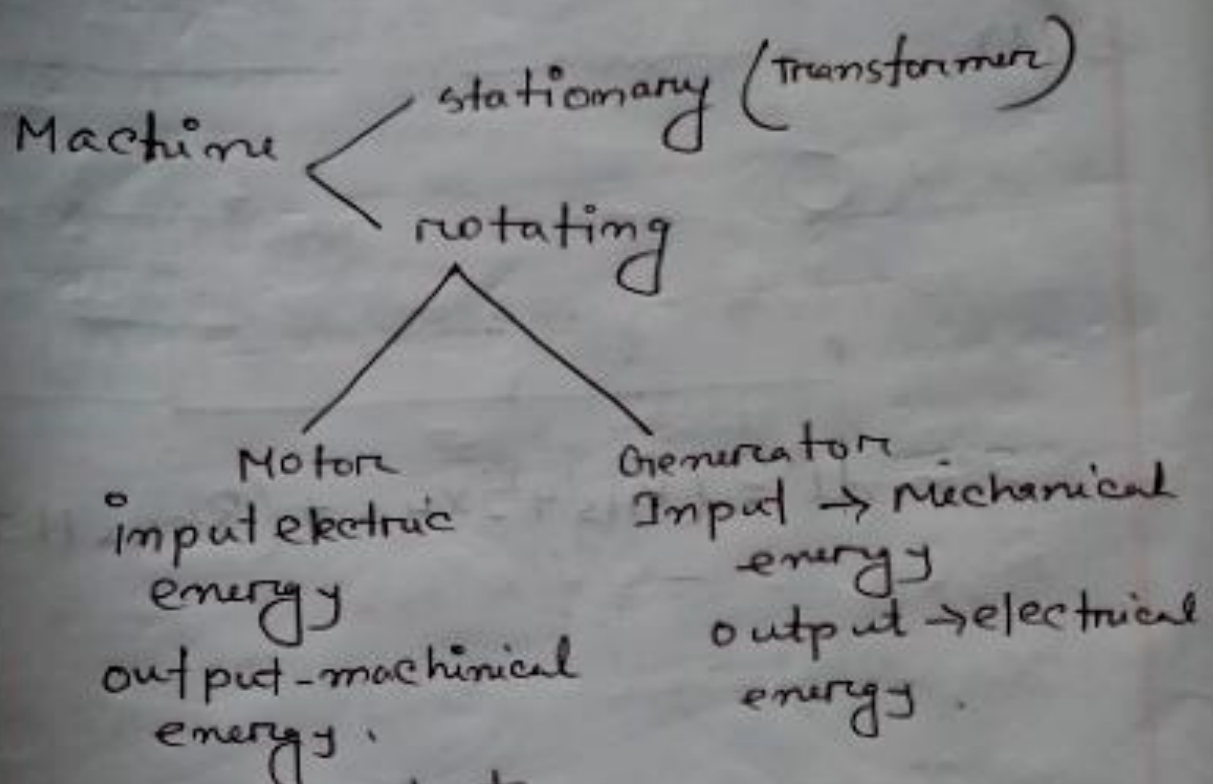

* Load & output
ଟେଡ଼ା ଥାଏ ।

* ଜିଉଲ ଉତ୍ପାଦନ:- base fuel ଥାଏ,
ଅର୍ଥା ଜିଉଲ ଓ ଗାସ,

Motor:- Electrical \longrightarrow Mechanical

Generator:- Mechanical \longrightarrow electrical

Induction

3 phase electrical motor

3 phase w/ grid stator

Inductor motor

stator

rotor



stator

transformer:-

stationary part

stator, which move
rotate with it,

MMF = Magnetomotive
force.

Induction motor is primary side of fixed
stator, secondary side is move rotate with it.

Rotor:- movable moveable part.

Rotor; rotate with stator • 3 rotate with it,

કે Motor નો આ base પર
Induction motor છે


- (1) squirrel cage
- (2) wound round

shelt નાં આંતર જાલા ring નાં આંતર
આંતર, slip ring નાં આંતર 2nd output
collect કરાડે અને,

Principle of operation:

primary 2nd
stator
~~and~~ secondary
rotor.

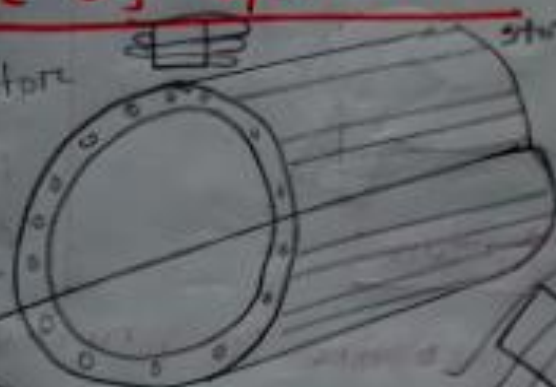rim conductors
inside નાં
જોડા નાં
the conductor
નાં short
નાં




$$V_A = V_m \sin^{\cos} \omega t$$

$$V_B = V_m \sin^{\cos} (\omega t - 120^\circ)$$

$$V_C = V_m \sin^{\cos} (\omega t - 240^\circ)$$
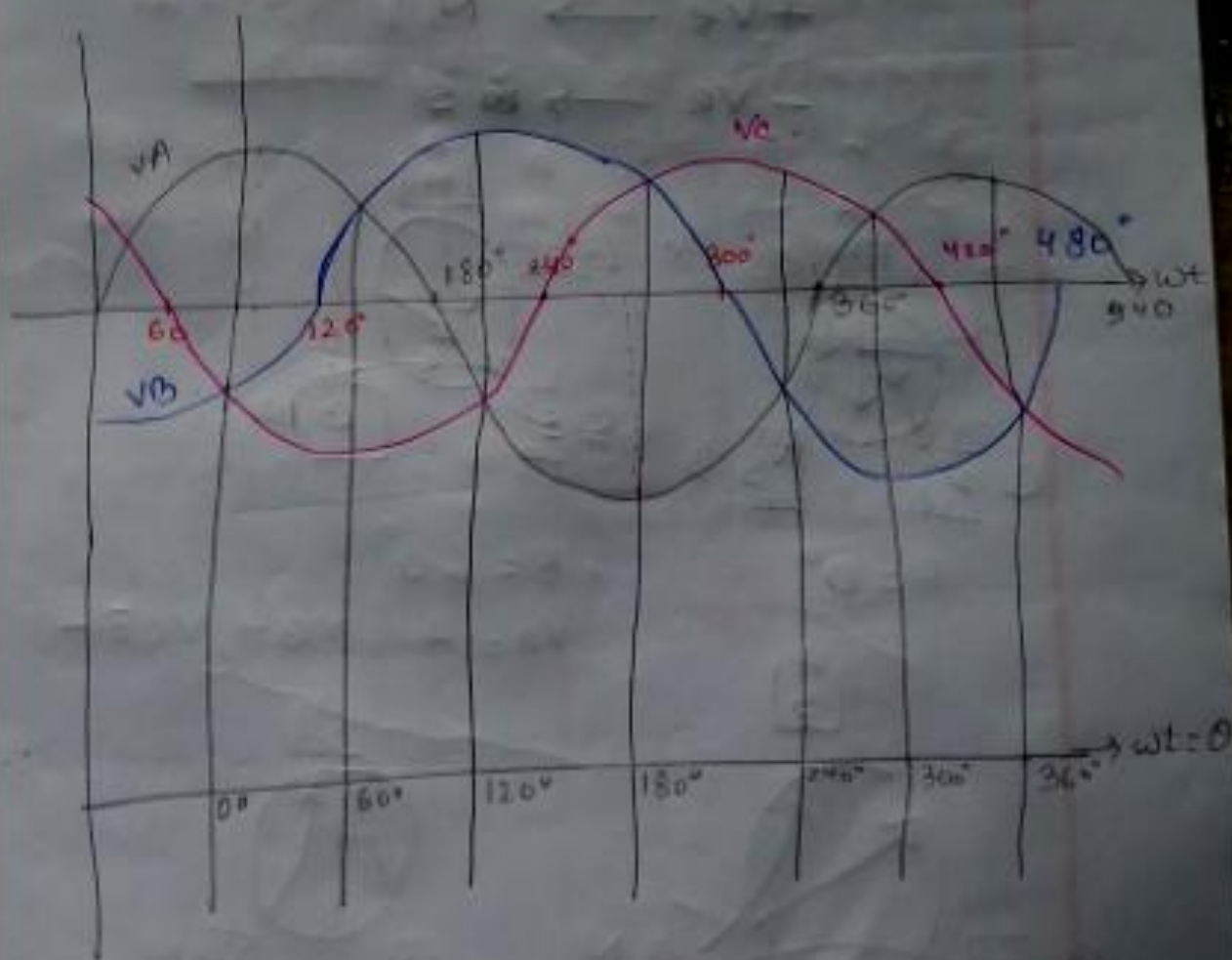
$$= V_m \sin^{\cos} (\omega t + 120^\circ)$$






current voltage current:

+ve \rightarrow N

-ve \rightarrow S



$\theta = 0^\circ$

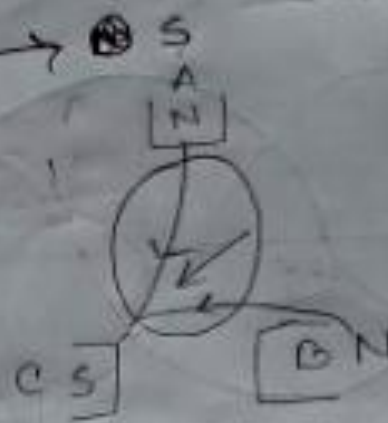

$\theta = 60^\circ$

$V_A = +, V_B = +, V_C = -$




$\theta = 120^\circ$

$V_A = - V_B = +, V_C = -$



$\theta = 180^\circ$


$V_A = - V_B = +, V_C = +$

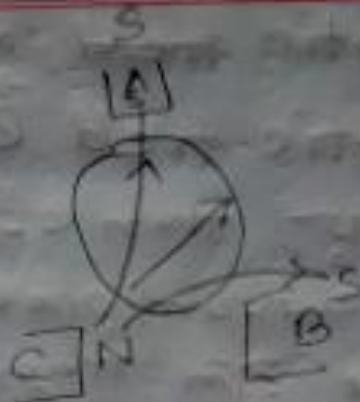

$$\theta = 240^\circ$$

$$V_A = - \quad V_B = -$$

$$V_C = +$$

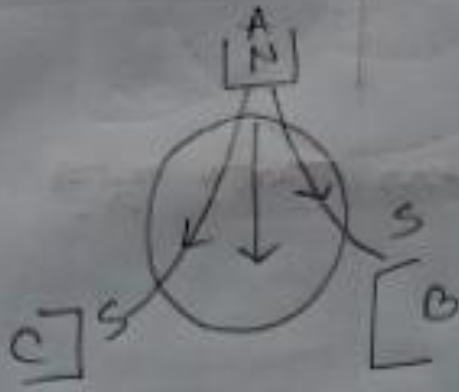


$$\theta = 360^\circ$$

$$V_A = +$$

$$V_B = -$$

$$V_C = -$$

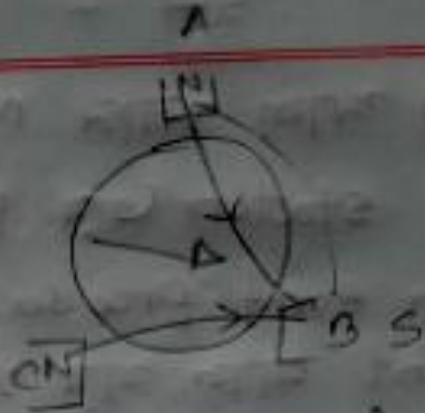

$$\theta = 300^\circ$$

$$V_A = +$$

$$V_B = -$$

$$V_C = +$$



$$\vec{B}_S$$

$$\vec{B}_R$$

$$\vec{\gamma} = k \vec{B}_S \times \vec{B}_R$$

ଉତ୍ତର γ apply ହେଉ
ଉତ୍ତର - Motor ହେଉ

N → current entry
S → " exit.

flux

* Φ આમ જાતે magnetic field produce
જેમ stator ઉપર magnetic field \vec{B}_s
then emf produce થયું, then એવી
short થાત, એવે અને current produce
થયું, current produce થતો magnetic
flux produce થયું, એવે અને
magnetic field શરૂ, ~~which~~
which is \vec{B}_R

$$\therefore \vec{\tau} = k \vec{B}_s \times \vec{B}_R$$

~~$\vec{\tau} = \vec{p} \times \vec{B}$~~

$$\Phi = B A$$

$$\Phi = \text{flux}$$

$\vec{\tau}$ produce થયું, means તેવો ટોર્ક વળ
rotate થાય.


Lec-12

- * Problem base question :-
- * Transformer
 - Equivalent ckt draw
 - short ckt test
 - open " "
 - & Core loss,

phasor diagram :-

math or phasor diagram बना ना समझ
कराव नुकराव नाहे

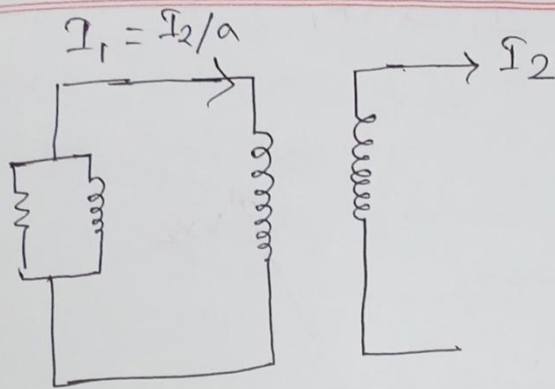
- (1) How a three phase induction works
- (2) How a rotating magnetic field
from म.व.
AC or current flow म.व.



$$\vec{I}_1 = \frac{\vec{I}_2}{a} < 180^\circ$$

(1) phasor Diagram of a 1- Φ XFR

(1) EQ CKT

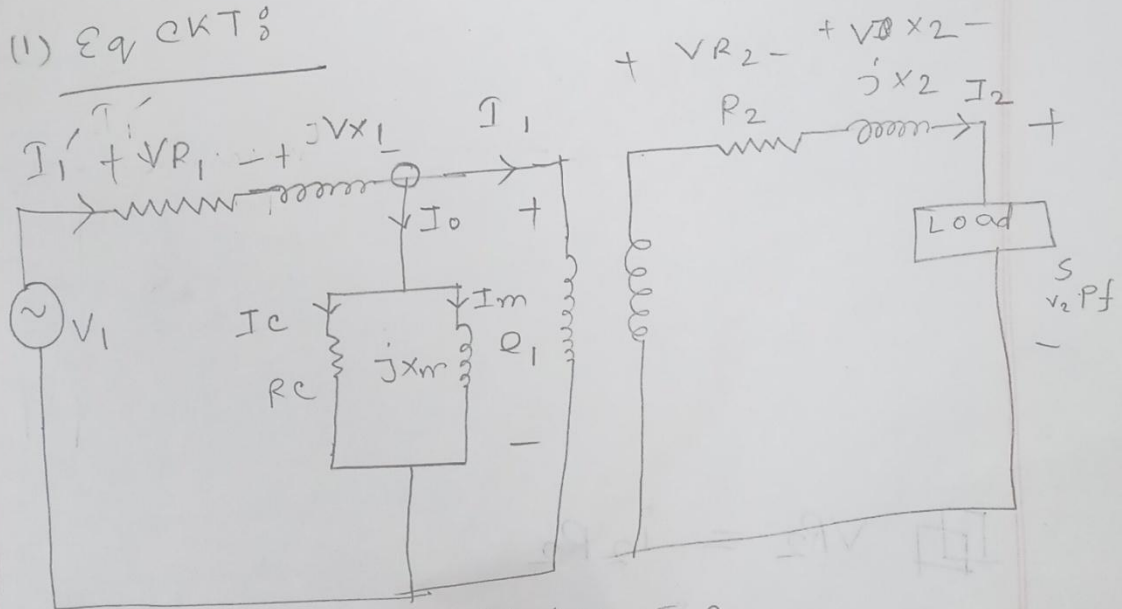

$$\frac{N_1}{N_2} = a$$


$$\frac{E_1}{E_2} = a = \frac{I_2}{I_1}$$

$$\boxed{\square} \theta = \cos^{-1}(\text{P.f.})$$

$$I_2 = \frac{2}{V_2} \angle -\theta$$

E_1 & E_2 same phase
 I_1 & I_2 ~ ~ ~

I_1' & V_{R1}' in phase

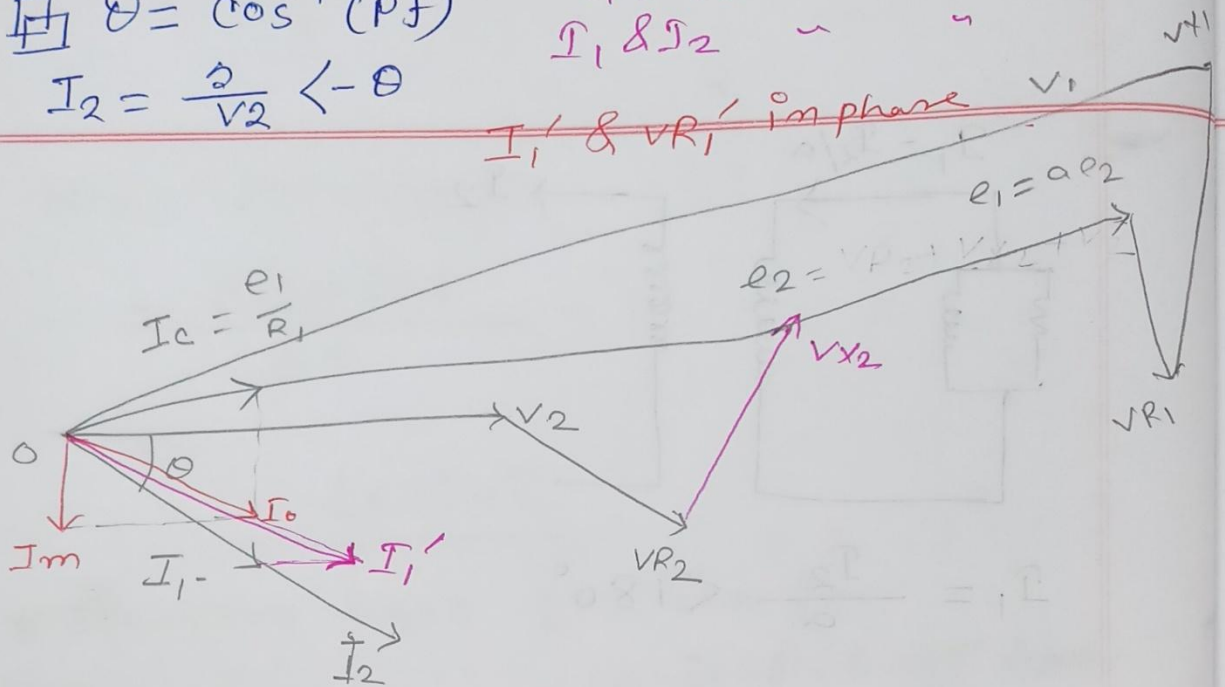

V_2 is the Induction or voltage.

$$\boxed{\square} V_{R2} = I_2 R_2$$

$$\Rightarrow V_{X2} = I_2 X_2$$

$$e_2 = V_{R2} + V_{X2} + V_2$$

$$\boxed{+} I_c = \frac{e_1}{R_c},$$

$$I_m = \frac{e_1}{X_m}$$

$$\bar{I}_0 = \bar{I}_c + \bar{I}_m$$

$$I_c = \frac{e_1}{R_c}, \quad I_m = \frac{e_1}{X_m}$$

$$\begin{aligned} \bar{I}_0 &= \bar{I}_c + \bar{I}_m \\ &= I_c + jX_m \end{aligned}$$

$$\boxed{+} I_1' = \bar{I}_0 + \bar{I}_1$$

$$\boxed{+} V_{R1} = I_1' R_1$$

$$V_{X1} = I_1' X_1$$

$$V_1 = V_{R1} + V_{X1} + V_2$$