



North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code : EEE211

Course Title: Digital Electronics

Section: 01

Experiment Number: 06

Experiment Name: Binary Arithmetic

--

Experiment Date: 14.12.2020

Date of Submission: 21.12.2020

Course Instructor: Fahimul Haque

Submitted To: Fatema Zahra

Experiment Name:

BCD to seven segment decoder.

Objectives:

Learn the conversion & displaying value in a seven segment display.

Theory:


An ABCD to seven segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in an indicator used to display decimal digit in a familiar form.

Each element (a, b, c, d, e, f, g) of the seven segment display is turned on when a logic low is applied to its corresponding input pin.

Equipments:

- Trainer board.
- IC 7447, resistors, etc.
- Resistors
- Seven segment display.
- Wire.

Circuit Diagram:

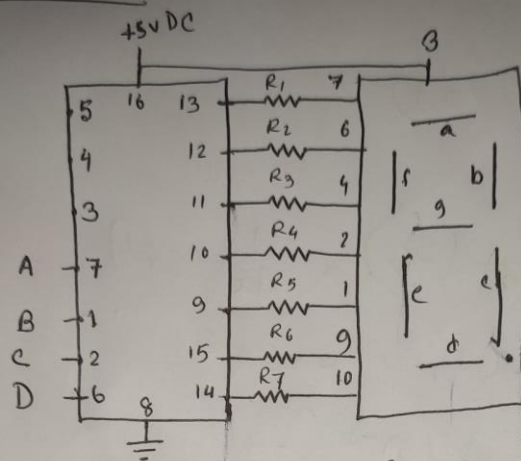

$R_1 \text{ to } R_7 = 220\Omega$.

Table:

Decimal	Inputs				Output						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

for a:

CD \ AB	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	x	x	x	x
10	1	1	x	x

$$\therefore a = C + A + BD + B'D'$$

for b:

CD \ AB	00	01	10	11
00	1	1	1	1
01	1	0	1	0
11	x	x	x	x
10	1	1	x	x

$$b = B' + C'D' + CD$$

for c:

CD \ AB	00	01	10	11
00	1	1	1	0
01	1	1	1	1
11	x	x	x	x
10	1	1	x	x

$$c = C' + D + B$$

for d:

CD \ AB	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	x	x	x	x
10	1	1	x	x

$$d = CD' + A + B'D' + B'C + BC'D$$

for e:

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	x	x	x	x
10	1	0	x	x

$$e = CD' + D'B'$$

for g:

CD \ AB	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	x	x	x	x
10	1	1	x	x

$$g = A + C'B + CD' + C'D'B'$$

for f:

CD \ AB	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	x	x	x	x
10	1	1	x	x

$$f = BC' + C'D' + A + D'B$$

Discussion:

Due to pandemic we are attending in online lab session. Through software simulation we have completed this experiment. This simulation procedure helped us to ~~to~~ learn the use of 7-segment display using basic gates & decoders. It helped us to relate the theoretical knowledge with our practical session.

Attachments:

