


# ETE 211/EEE 211

## **Digital Logic Design**

***Synchronous Sequential Logic -FF***

 
# Sequential Circuits

Every digital system is likely to have combinational circuits, most systems encountered in practice also include **storage elements**, which require that the system be described in term of **sequential logic**.



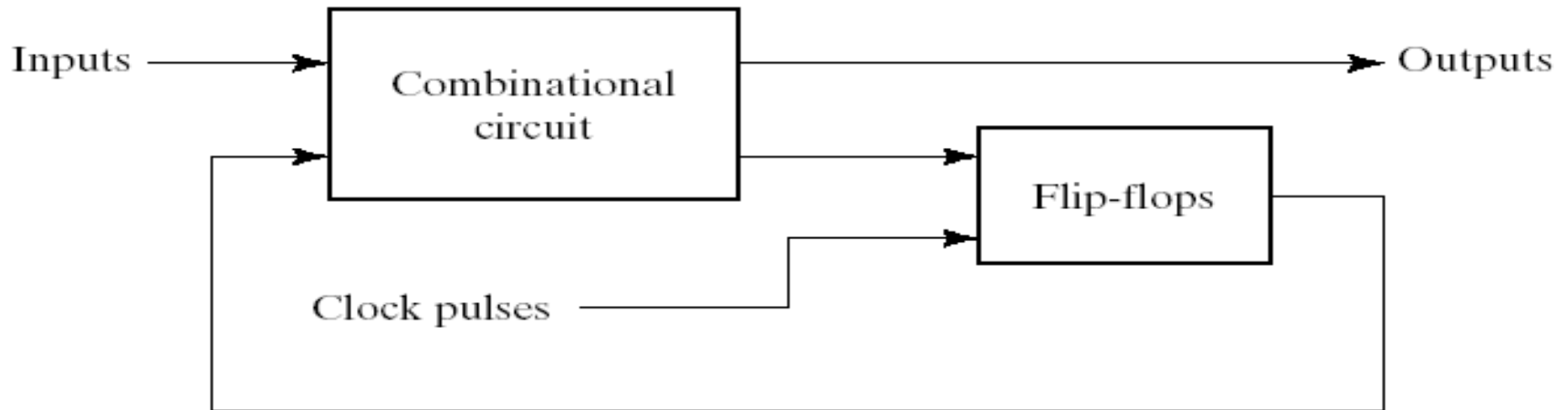
# Synchronous Clocked Sequential Circuit

- A sequential circuit may use many **flip-flops** to store as many bits as necessary.
- The outputs can come either from the combinational circuit or from the flip-flops or both.




(a) Block diagram

 

(b) Timing diagram of clock pulses
 
# SR Latch

The **SR latch** is a circuit with two cross-coupled **NOR gates** or two cross-coupled **NAND gates**. It has two inputs labeled **S** for set and **R** for reset.




(a) Logic diagram

$S$	$R$	$Q$	$Q'$	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$ )
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$ )
1	1	0	0	

(b) Function table

# SR Latch with NAND Gates

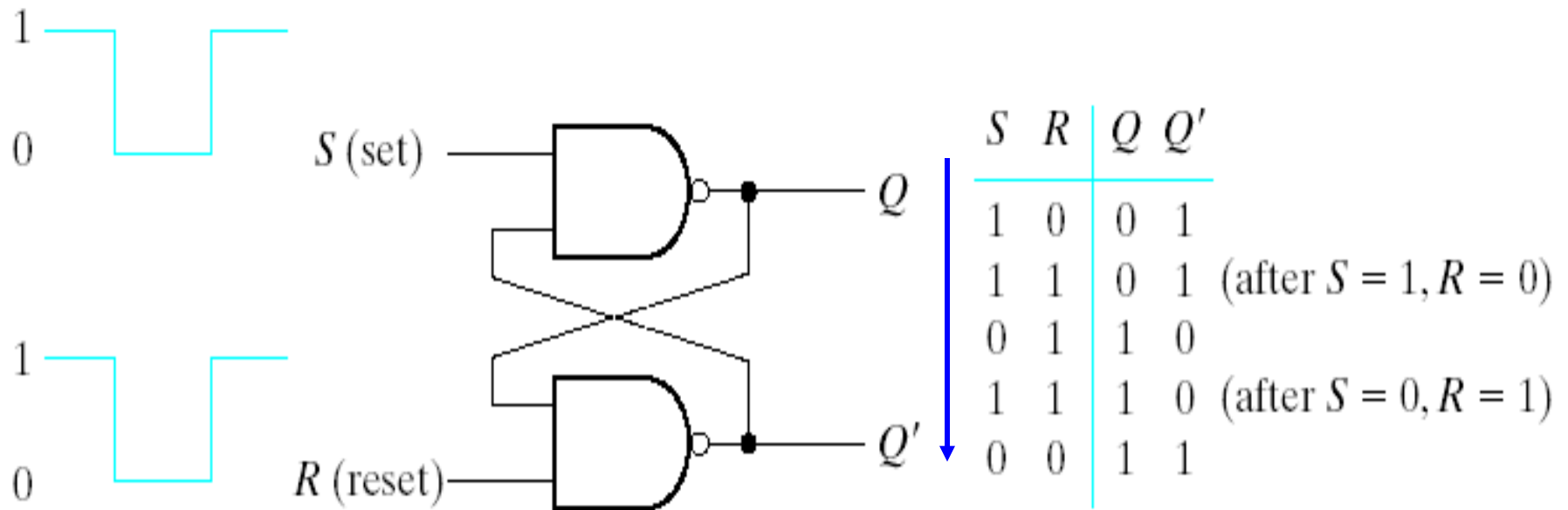


(a) Logic diagram

(b) Function table
 
# SR Latch with Control Input

- The operation of the basic SR latch can be modified by providing an additional control input that determines when the state of the latch can be changed.
- It consists of the **basic SR latch** and **two additional NAND gates**.



(a) Logic diagram


$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

# D Latch

One way to eliminate the undesirable condition of the indeterminate state in SR latch is to ensure that **inputs S and R are never equal to 1 at the same time**.

This is done in the **D latch**.

 

(a) Logic diagram


$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table

 
# Graphic Symbols for latches

A latch is designated by a rectangular block with inputs on the left and outputs on the right.


One output designates the normal output, and the other designates the complement output.



$SR$

 

$\overline{S}\overline{R}$

 

$D$



# Flip-Flops

- The state of a latch or flip-flop is switched by a change in the control input.
- This momentary change is called a **trigger** and the transition it cause is said to trigger the flip-flop.
- The D latch with pulses in its control input is essentially a flip-flop that is triggered every time the pulse goes to the **logic 1 level**.
- As long as the pulse input remains in the level, any changes in the data input will change the output and the state of the latch.

# Clock Response in Latch

***A positive level response*** in the control input allows changes, in the output when the D input changes while the clock pulse stays at logic 1.



(a) Response to positive level




(b) Positive-edge response



(c) Negative-edge response

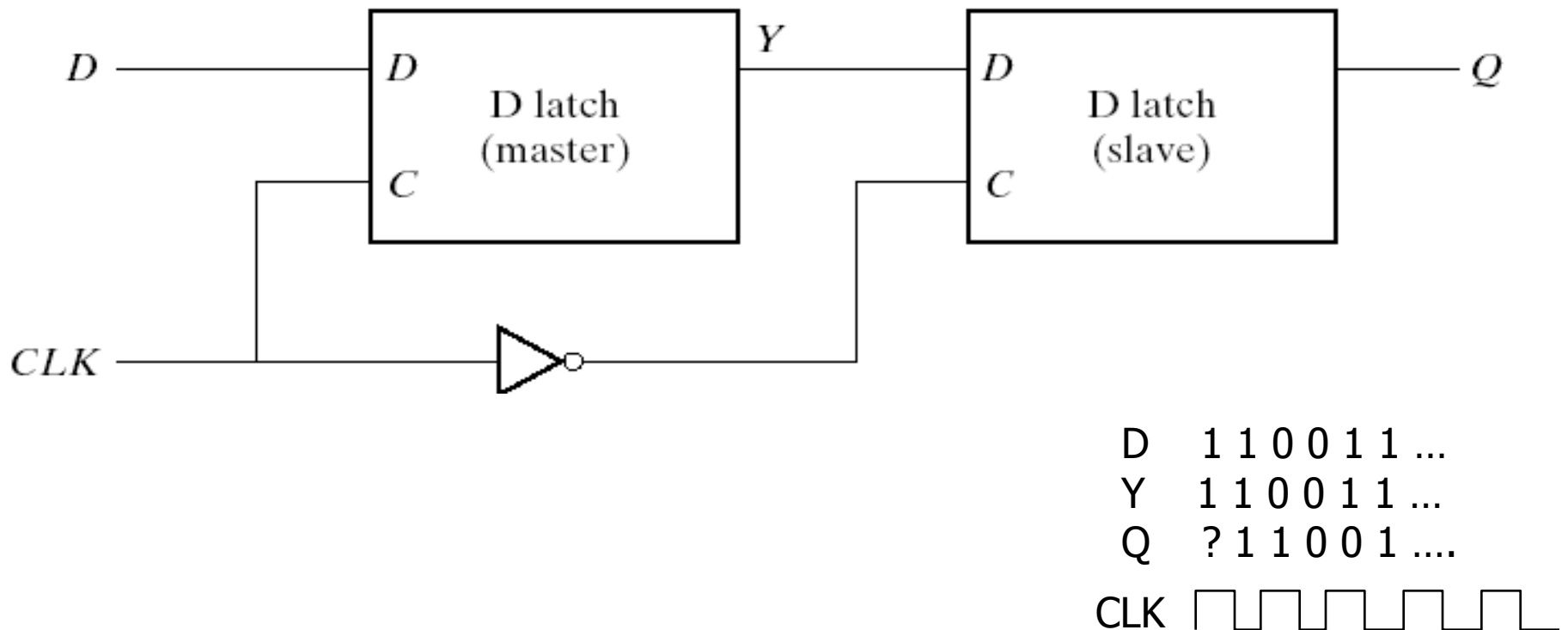
# Edge-Triggered D Flip-Flop

**Master-Slave Flip-Flop:** The **first** latch is called the **master** and the **second** the **slave**. The circuit samples the D input and changes its output Q only at the negative-edge of the controlling clock.



 
# D-Type Positive-Edge-Triggered Flip-Flop


- Another more efficient construction of an edge-triggered D flip-flop uses **three SR latches**.
- Two latches respond to the external D(data) and CLK(clock) inputs.
- The third latch provides the outputs for the flip-flop.


 
# Graphic Symbol for Edge-Triggered D Flip-Flop



(a) Positive-edge

 

(a) Negative-edge

## Other Flip-Flops:

## JK Flip-Flop


There are three operations that can be performed with a flip-flop:

- set it to 1

- reset it to 0

- complement its output.

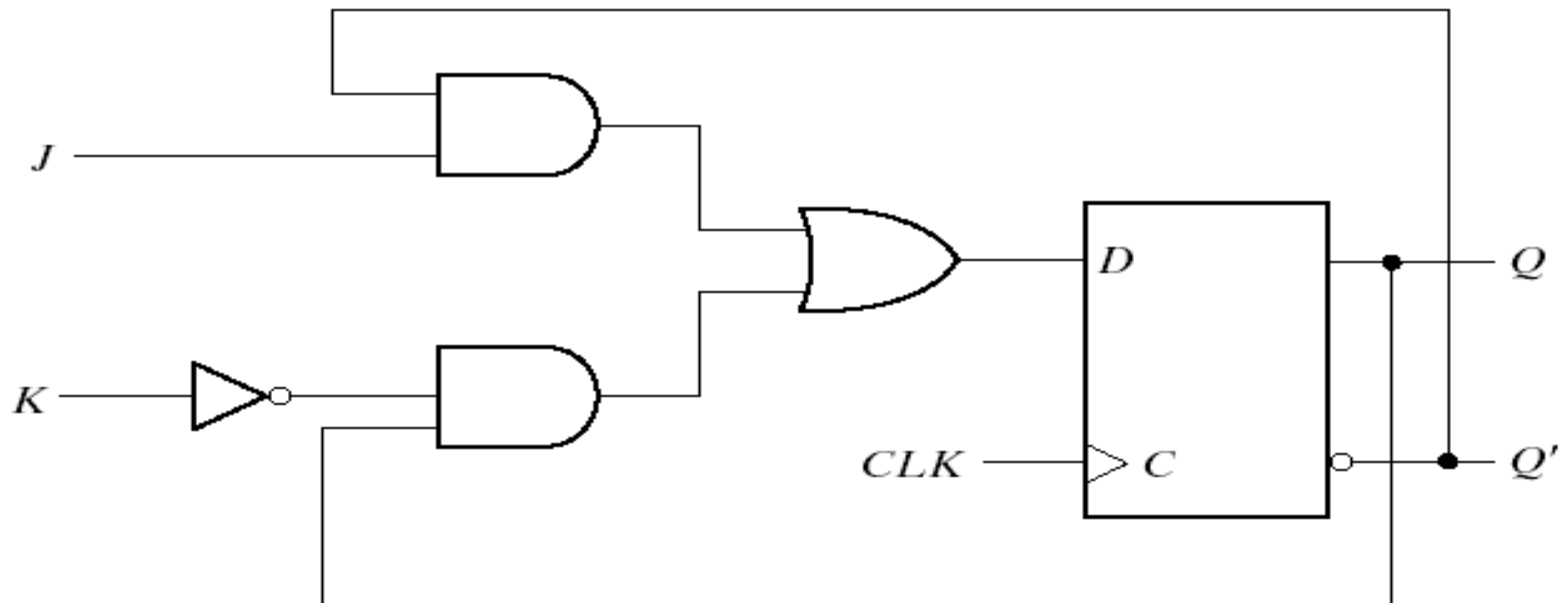
The JK flip-flop performs all three operations. The circuit diagram of a **JK flip-flop** constructed with a **D flip-flop** and **gates**.



# JK Flip-Flop

The J input sets the flip-flop to 1, the K input resets it to 0, and when both inputs are enabled, the output is complemented. This can be verified by investigating the circuit applied to the D input:


$$D = J Q' + K' Q$$

 

Flip-Flop Characteristic Tables			
JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement
 
# T Flip-Flop

The T(toggle) flip-flop is a complementing flip-flop and can be obtained from a JK flip-flop when inputs J and K are tied together.




D Flip-Flop			T Flip-Flop		
$D$	$Q(t + 1)$		$T$	$Q(t + 1)$	
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$Q'(t)$	Complement




# T Flip-Flop

The T flip-flop can be constructed with a D flip-flop and an exclusive-OR gates as shown in Fig. (b). The expression for the D input is

$$D = T \oplus Q = TQ' + T'Q$$

 

(b) From D flip-flop

 

(c) Graphic symbol

# Characteristic Equations

D flip-flop Characteristic Equations

$$Q(t + 1) = D$$

JK flip-flop Characteristic Equations

$$Q(t + 1) = JQ' + K'Q$$


T flip-flop Characteristic Equations

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

# Direct Inputs

- Some flip-flops have asynchronous inputs that are used to force the flip-flop to a particular state independent of the clock.
- The input that sets the flip-flop to 1 is called present or direct set.
- The input that clears the flip-flop to 0 is called clear or direct reset.
- When power is turned on a digital system, the state of the flip-flops is unknown.
- The **direct inputs** are useful for bringing all flip-flops in the system to a known starting state prior to the clocked operation.


# D Flip-Flop with Asynchronous Reset

 

A positive-edge-triggered **D** flip-flop with asynchronous reset

$R$	$C$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

Function Table

 

Symbol