



North South University

Assignment 02

Power Systems

Course Code: EEE362

Section: 02

Course Instructor

Hafiz Abdur Rahman (HZR)

Prepared By

Mohammed Mahmudur Rahman

ID # 152 0386 043

① Given that, $f = 60 \text{ Hz}$

rms value $= 100 \text{ V}$

$$R = 15 \Omega$$

$$I = 0.12 \text{ H}$$

② we know that, $v = v_m \sin(\omega t + \alpha)$

$$\text{for, } t = 0,$$

$$50 = \sqrt{2} \times 100 \sin \alpha$$

$$\Rightarrow \alpha = 20.70^\circ$$

$$\therefore Z = 15 + j2\pi \times 60 \times 0.12$$

$$= 47.66 < 71.66^\circ$$

$$\text{At, } t = 0,$$

$$i_L = - \frac{100 \times \sqrt{2}}{47.66} \sin(\omega t - 71.66^\circ)$$

$$= 2.305 \text{ A}$$

③ Maximum dc component occurs when

$$\sin(\alpha - \theta) = \pm 1$$

$$\text{when, } (\alpha - \theta) = \pm 90^\circ$$

$$\alpha = 161.66^\circ \text{ or } -18.34^\circ$$

$$v = 100\sqrt{2} \sin 161.66^\circ$$

$$= 100\sqrt{2} \sin -18.34^\circ$$

$$= \pm 44.5 \text{ V}$$

(c) No dc component will occur when $\alpha - \theta = 0$
or $\alpha - \theta = 180^\circ$

$$\text{When } \alpha = 71.66^\circ \text{ or } 251.66^\circ$$

$$v = 100\sqrt{2} \sin 71.66^\circ$$

$$= 100\sqrt{2} \sin 251.66^\circ$$

$$= \pm 134.24 \text{ V}$$

(d) For $v = 0$ when $t = 0$ and $\alpha = 0$

0.5 cycles later $\omega t = \pi \text{ rad}$

$$t = \frac{\pi}{2\pi \times 60} = 0.00833 \text{ s}$$

$$i = \frac{100\sqrt{2}}{47.66} \left[\sin(180^\circ - 71.66^\circ) - e^{\frac{-15}{0.12} (0.00833)} \times \sin(-71.66^\circ) \right]$$

$$= \frac{100\sqrt{2}}{47.66} (1 + e^{-1.0461}) \sin(-71.66^\circ)$$

$$= 3.810 \text{ A}$$

similarly

when, 1.5 cycles later: $\omega t = 3\pi$

$$\therefore t = 0.025 \text{ s}$$

$$\therefore i = 2.040 \text{ A}$$

and 5.5 cycles later: $\omega t = 11\pi$

$$\therefore t = 0.09167 \text{ s}$$

$$\therefore i = 2.817 \text{ A}$$

2) Given that:

transformer is rated, 100 MVA, 12 kV

reactance, $X_d'' = 10\%$

$$X_d' = 26\%$$

$$X_d = 130\%$$

$$\text{base current: } \frac{100000}{\sqrt{3} \times 12} = 3207.5 \text{ A}$$

2) The short circuit current:

$$i = \frac{1}{1.3} \times 3207.5$$

$$= 2427 \text{ A}$$

⑥ The symmetrical rms current:

$$i = \frac{1}{j0.10} \times 3207.5 \\ = 16882 \text{ A}$$

⑦ The max possible DC component short circuit current:

$$i = \sqrt{2} \times 16882 \\ = 23874 \text{ A}$$

⑧ The initial symmetrical

⑨ Given that, 100 MVA, 240Y/18 A kV
 $X = 10\%$

⑩ The initial symmetrical rms current in high voltage side

$$I'' = \frac{1.0}{j(0.10 + 0.10)} \\ = -j3.448 \text{ per unit}$$

$$\text{Base } I_{HV} = \frac{100000}{\sqrt{3} \times 240} = 240.6 \text{ A}$$

$$\text{Base } I_{LV} = \frac{1000000}{\sqrt{3} \times 18} = 3207.5 \text{ A}$$

$$\therefore i = 3.448 \times 240.6 \\ = 829.5 \text{ A}$$

$$\textcircled{b} i = 3.448 \times 3207.5 \\ = 11066 \text{ A}$$

④ Given that, $f = 60 \text{ Hz}$; 500 MVA , 2 kV
 $x_d'' = 0.20 \text{ pu}$
 per unit load = 400 MW at 20 kV

Load current,

$$I_{\text{Load}} = \frac{400}{500} = 0.8 \text{ pu}$$

$$E_g'' = 1.0 + 0.8 \times j 0.20 \\ = 1.0 + j 0.16 \text{ pu}$$

∴ The initial symmetrical rms current:

$$I_g'' = \frac{1 + j0.16}{j0.20} = 0.8 - j5.0 \text{ pu}$$

$$= 5.06 \text{ pu}$$

(b) Given that,

The pu reactance of the generator 0.15

The pu reactance of the motor 0.35

The leakage reactance of the transformer 0.10 pu

(c) when the generator is 0.9 pu and 0.8 pf leading.

$$\therefore E_g'' = 0.9 + (0.8 + j0.6)(j0.15)$$


$$= 0.81 + j0.12 \text{ pu}$$

$$\therefore E_m'' = 0.9 + (0.8 + j0.6)(j0.45)$$

$$= 1.17 - j0.32 \text{ pu}$$

$$\therefore I_g'' = \frac{0.81 + j0.12}{j0.25}$$

$$= 0.48 - j3.24 \text{ pu}$$

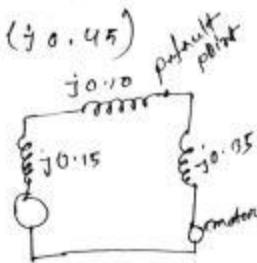

$$\therefore I_{m''} = \frac{1.17 - j0.36}{j0.35} = -1.03 - j3.34 \text{ pu}$$

$$\begin{aligned} \therefore I_f'' &= I_g'' + I_{m''} \\ &= -0.55 - j6.58 \text{ pu} \end{aligned}$$

⑥ By using thevenin's theorem,

$$\begin{aligned} V_f &= 0.9 - (0.8 + j0.6)(j0.1) \\ &= 0.96 - j0.08 \text{ pu} \end{aligned}$$

$$\therefore Z_{th} = \frac{j0.25 \times j0.35}{j0.60} = j0.146 \text{ pu}$$


$$I_f'' = \frac{0.96 - j0.08}{j0.146} = -0.55 - j6.58 \text{ pu}$$

By replacing I_f'' by a current source and then applying the principle of superposition

$$\begin{aligned} I_g'' &= 0.8 + j0.6 + \frac{j0.35}{j0.60} (-0.55 - j6.58) \\ &= 0.48 - j3.24 \text{ pu} \end{aligned}$$

$$\begin{aligned} I_{m''} &= -0.8 - j0.6 + \frac{j0.25}{j0.60} (-0.55 - j6.58) \\ &= -1.03 - j3.34 \text{ pu} \end{aligned}$$

(6)

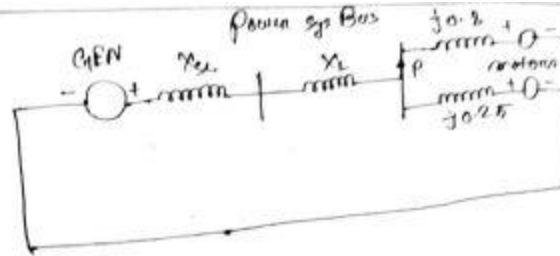

$$\text{Base } Z = \frac{0.48^2}{2} = 0.1152 \Omega$$

$$X_L = \frac{0.083}{0.1152} = 0.72 \text{ per unit}$$


$$X_{se} = \frac{2}{9.6} = 0.208 \text{ per unit}$$

$$X_{th} = \frac{1}{\frac{1}{0.8} + \frac{1}{0.25} + \frac{1}{0.408}} = 0.130 \text{ per unit}$$

$$I_f^a = \frac{\frac{440}{480}}{-j1.30}$$

$$= 7.05 \text{ per unit}$$

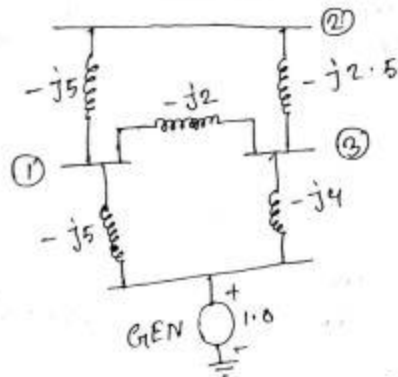(2) Given that, voltage bus (2) is $1.0 \angle 0^\circ \text{ pu}$



$$Y_{bus} = \begin{bmatrix} -j12 & j5 & j2 \\ j5 & -j7.5 & j2.5 \\ j2 & j2.5 & -j8.5 \end{bmatrix}$$

$$\Delta = \frac{1}{-j} \left\{ 12(7.5 \times 8.5 - 2.5 \times 2.5) + 5(-5 \times 8.5 - 2 \times 2.5) - 2[5(-2.5) - (-2 \times 7.5)] \right\}$$

$$= 4307.5$$

for the fault at bus ② the impedance needed
me, $Z_{12} = \frac{\Delta_{21}}{\Delta} = -\frac{j5(-j8.5) - j2.5(j2)}{4307.5}$

$$= \frac{-42.5 - j5}{4307.5}$$

$$= j0.1195$$

$$Z_{22} = \frac{A_{21}}{\Delta} = \frac{-j12(-j8.5) - j2(j2)}{j307.5}$$

$$= \frac{-102 + 4}{j307.5}$$

$$= j0.2465$$

$$Z_{32} = \frac{A_{23}}{\Delta} = \frac{-j12(j2.5) - j5(j2)}{j307.5}$$

$$= \frac{-30 - 10}{j307.5}$$

$$= j0.1006$$

$$\therefore I_f'' = \frac{1.0}{-j0.2465} = -j4.056 \text{ pu}$$

$$V_3 = 1 - \frac{j0.1006}{j0.2465} = 0.502 \text{ pu}$$

$$V_1 = 1 - \frac{j0.1105}{j0.2465} = 0.515 \text{ pu}$$

$$\therefore I_{12}'' = \frac{0.515}{j0.2} = -j2.58 \text{ pu}$$

From generator 1,

$$I_g'' = \frac{1 - 0.515}{j0.2} = -j2.42 \text{ pu}$$