

## Experiment Name:

Parallel RC, RL & RLC circuit.

## Objectives:

- Investigate peak voltage, current & phase relation between the circuit components of parallel RC, RL & RLC circuits.
- Understand & prove KCL for AC circuit.
- Understand the technique to measure current using a current sense resistor.

## Theory:

In parallel circuit voltage across each parallel terminal is same as the source voltage while current is different in each branch.

To measure the current we can use a sense resistor. Its value is comparatively low as than the circuit components & phase angle is same as the V across the resistor.

## Apparatus:

- Resistors:  $1 \times 10k\Omega$ ,  $3 \times 1k\Omega$ ,  $2 \times 3\Omega$ ,  $3 \times 10\Omega$ .
- Capacitors:  $1 \times 10nF$ ,  $1 \times 33nF$ .
- Inductor:  $1 \times 330\mu H$ .
- Bread board.
- Function Generator.
- Oscilloscope.

## Circuit Diagram:

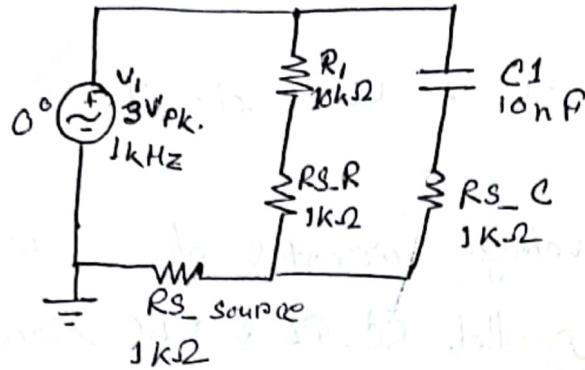


Figure: Parallel RC circuit with sense Resistor.

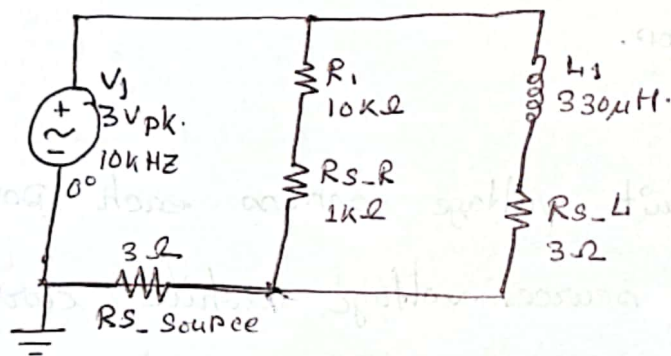


Figure: Parallel RL circuit with sense Resistor

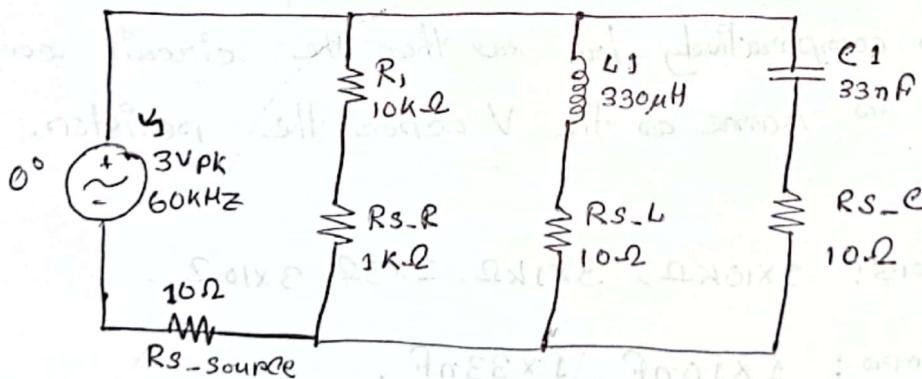


Figure: Parallel RLC circuit with Sense Resistor.

Table 1.1

$R$ (measured)	$C$ (measured)	$X_C$ (Theory) $\frac{1}{2\pi f C}$ ( $\Omega$ )	$Z = \sqrt{R^2 + X^2}$ ( $\Omega$ )	$Z = \tan^{-1}(X/R)$ $\theta$
$R_1 = R_3 = R_4 = 1k\Omega$ $R_2 = 10k\Omega$	10nF	15.915.49		

Table 1.2

	$I_{Peak}$ (Theory)	$\theta$ (Theory)	$V_{(sense)}$ Peak (Measured)	$I_{Peak}$ (Practical)	Delay $\Delta T$ (Measured)	$\theta$ (Pract) $[\Delta T \times f \times 360]$	% Difference (i)	% Difference $\theta$
$i_s$	$6 \times 10^{-4} A$	30	640mV	$6.4 \times 10^{-4} A$	85 $\mu s$	30.6	0.00%	0.02%
$i_R$	1.70mA	30	1.74V	<del>1.74mA</del> 1.74mA	76 $\mu s$	27.36	2.35%	8.8%
$i_C$	$1.02 \times 10^{-3}$	45	1.5V	$1.5 \times 10^{-3}$	120 $\mu s$	43.2	0.0000%	4%

Table 1.3

$R$ (measured) ( $\Omega$ )	$L$ (measured) (H)	$X_L$ (Theory) $(2\pi f L)$ ( $\Omega$ )	$Z = \sqrt{R^2 + X^2}$	$Z = \tan^{-1}(X/R)$ ( $\angle \theta^\circ$ )
	330 $\mu H$	20.73		



Table: 1.4

	$I_{Peak}$ (Theory)	$\theta$ (Theory)	$V_{sense}$ (peak) (Measured)	$I_{Peak}$ (Practical)	Delay $\Delta T$ (Measured)	$\theta$ (Practical) $\Delta T \times f \times 360$	% Difference (i)	% Difference ( $\theta$ )
$i_s$	0.30A	80°	830mV	0.28A	21.8 $\mu$ s	78.48	6.67%	21.9%
$i_R$	$1.90 \times 10^{-3}$	65	1.86V	1.86mA	18.6 $\mu$ s	66.96	2.11%	3.01%
$i_L$	0.85A	81	2.42V	0.81A	22.2 $\mu$ s	79.92	4.71%	1.33%

Table: 1.5

$R(\Omega)$	$C(F)$	$L(H)$	$X_C$ (Theory) $\frac{1}{\omega C} (\Omega)$	$X_L$ (Theory) $\omega L (\Omega)$	$Z = \sqrt{R^2 + X^2}$ ( $\Omega$ )	$Z = \tan^{-1}(X/R)$ $\angle \phi^\circ$
	$33 \times 10^{-9}$	$330 \times 10^{-6}$	80.98	124.41		

Table: 1.6

	$I_{Peak}$ (Theory)	$\theta$ (Theory)	$V_{sense}$ (peak) (Measured)	$I_{Peak}$ (Practical)	Delay $\Delta T$ (Measured)	$\theta$ (Practical) $\Delta T \times f \times 360$	% Difference (i)	% Diff ( $\theta$ )
$i_s$	0.5A	65	4.55V	0.46A	3 $\mu$ s	64.8	8%	0.31
$i_R$	1.4AmA	37	300mV 1.35V	0.03A 1.35mA	799ns 1.66 $\mu$ s	35.856	18.57	3.08
$i_L$	0.06A	18	300mV	0.03A	799ns	17.26	25	4.11
$i_c$	0.17A	70	1.69V	0.169A	3.16 $\mu$ s	68.26	0.59	2.49

### Questions:

① Function of sense resistor is to determine the current by calculation voltage across it. The more the resistance if we used smaller resistance it might burned due to over voltage. This is the disadvantage. Again, On the other, the advantage is that we'll get more perfect values if ~~the~~ for current in case of smaller resistance.

②

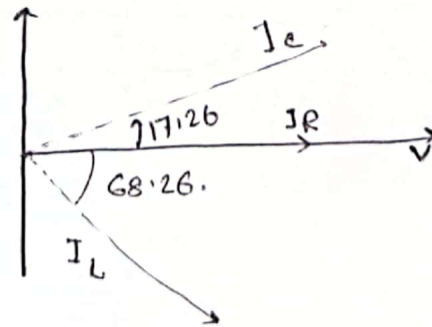


Figure: Phasor diagram for RLC circuit.

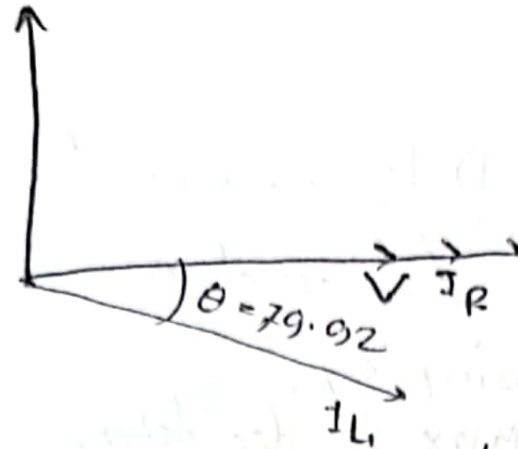


Fig: phasor diagram of RL circuit

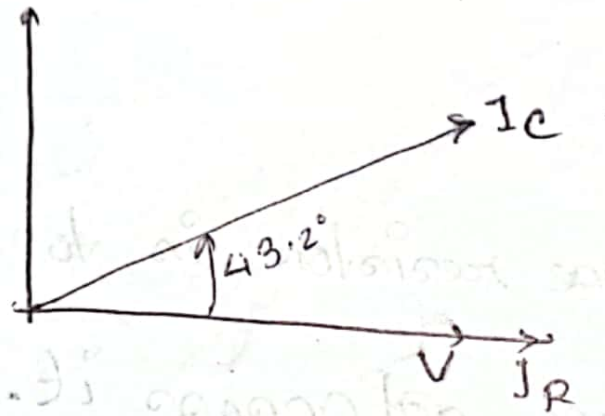


Fig: Phasor diagram of RC circuit

④ As we have completed software simulation due to pandemic, we did not noticed ~~was~~ a huge difference between theoretical and practical values. Rather, it was an acceptable ~~difference~~ error. The cause that ~~may be~~ for this error would be:

① We couldn't determine the exact peak values using cursor.

② There was a fluctuation in oscilloscope values.

③ Unavoidable human error.

### Discussion:

Due to pandemic, we have completed the lab in online. Through software simulation we've completed the circuit & measured the value. The measurement procedure was a bit complex but we've learned from youtube & a honourable instructor. As, the experiment was done in software thus, value of the component was ~~a~~ same as theory & our measured value ~~was~~ ~~at~~ had also minimum percentage of error.