

North South University Department of Electrical & Computer Engineering

LAB REPORT

Course Code: EEE211

Course Title: Digital Electronics

Section: 01

Experiment Number: 04

Experiment Name: Combinational Logic

Experiment Date: 30.11.2020
Date of Submission: 07.12.2020
Course Instructor: Fahimul Haque

Submitted To: Fatema Zahra

Name of Experiment:

lombinational Logic Design.

Objectives:

- Design a complete minimal combinational logic nymem from specification to implementation.
 - Minimize combinational logic circuits using K-maps.
 - Leon various numerical representation systems.
- → 9 mplemento circuito using 1°+ & 2° d canonical minimal forms.


Apparatus:


- + Trainer Board
- Logic gates ICD: 2 & 3 input AND, OR, NOR, NAND.

Theory:


In this lab we have learned orumleer conversion.

3 ina	ry (loded nal		Excess-3					Excess-3				Binary Coded Decimal (BCD			
A B C D				WXYZ			Z	Wein	W	W X		Z	A BOC D			D
0	0	0	0	0	0	1	1		0	0	1	1	0	0	0	0
0	0	0	1	0	1	0	0		0	1	0	0	0	0	0	1
0	0	1	0	0	1	0	1		0	1	0	1	0	0	1	0
0	0	1	1	0	1	1	0		0	1	1	0	0	0	1	1
0	1	0	0	0	(1	1		0	1	1	1	0	1	0	0
0	١	0	1	1	0	0	0		1	0	0	0	0	ŀ	0	1
0	1	1	0	1	0	0	1		1	0	0	1	0	t	1	0
0	1	1	1	1	0	(0		1	0	1	0	0	1	1	1
1	0	0	D	1	0	1	1		1	0	1	1	1	0	0	0
1	0	0	1	1	1	U	0		1	1	0	0	1	0	0	1
X	X	У	Х	×	X	X	X		X	×	X	X	X	X	X	X
×	×	×	. X	X	X	x	X		×	X	x	X	X		X	X
×	χ	X.	X	X	X	X	X		X	X	X	X	X	X	X	
X	x	×	X	X	X	X	X		×	X	X	X	X	×	×	
X	X	X	X	X	X	X	X		×		× >	(X	X	1	-	X
X	X	X	X	X	X	X	X		7	1	1)	X	X	X	×	X

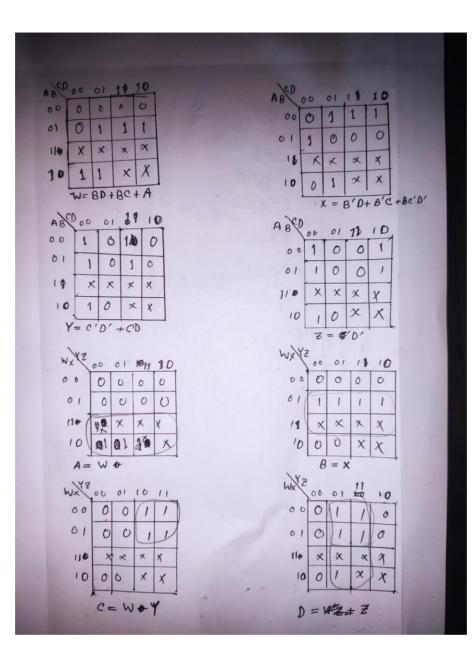

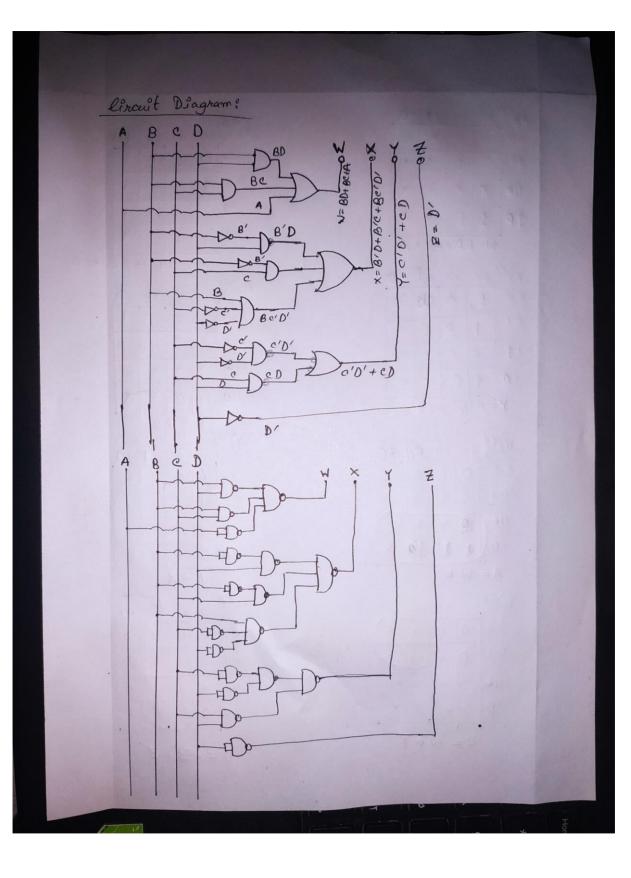

C. (B)

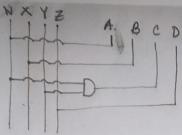

(N+7)'-

Fig: Excens-3 to BCD Circuit diagrams

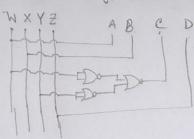


Fig. Excess-3 to BED Ciperist Diagnon uning NOR gates.

Dincussion:

Due to pandemic we are attending the lab online & using software simulation we are completing the expressional. Through this experiment we learned the conversion procedure of number. We also learned to use K-map for output as well; white we used K-map for imput only previously. This lab helped us to relate our theoretical idea with the practical one's.