



North South University

Midterm

Power Systems

Course Code: EEE362

Section: 02

Course Instructor

Hafiz Abdur Rahman (HZR)

Prepared By

Mohammed Mahmudur Rahman

ID # 152 0386 043

Answer to question No :3

Answer to question NO:3.

The value of base KVA, $S_{base} = 50 \text{ KVA}$.

base voltage, $V_{base} = 2400 \text{ V}$.

$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{2400^2}{50 \times 10^3} = 115.2 \Omega.$$

For G_1 ,

$$Z_{g, pu} = \frac{Z_{actual}}{Z_{base}} \text{ where } Z_{actual} = \text{actual impedance.} \quad \text{..... (1)}$$

$$Z_{actual} = Z_{old, p.u.} \times Z_{base}$$

Substitute $j0.2 \text{ p.u.}$ for $Z_{old, p.u.}$

$$Z_{actual} = (j0.2) \left(\frac{2400^2}{10^4} \right) = j115.2 \Omega$$

Substitute $j115.2 \Omega$ for Z_{actual} & 115.2Ω for Z_{base} .

$$Z_{g, pu} = \frac{j115.2}{115.2} \text{ p.u.} = j \text{ p.u.}$$

For G_2 ,

$$Z_{g2, pu} = \frac{Z_{actual}}{Z_{base}} \quad \text{..... (2)}$$

$$Z_{actual} = (j0.2) \left(\frac{2400^2}{20 \times 10^3} \right) = j57.6 \Omega.$$

$$Z_{g2, pu} = \frac{j57.6}{115.2} \text{ p.u.} = \frac{1}{2} j \text{ p.u.}$$

Calculating actual impedance of the transformer by the rated values from p.u value.

$$Z_{\text{actual}} = j0.1 \left(\frac{2400^2}{40 \times 10^3} \right) = j14.4 \Omega$$

$$Z_{\text{p.u.}} = \frac{j14.4}{115.2} \text{ p.u.} = j0.125$$

for Transformer T_2 .

$$Z_{\text{actual}} = (j0.1) \left(\frac{10000^2}{80 \times 10^3} \right) = j125 \Omega$$

$$Z_{\text{base 2}} = \frac{V_{\text{base}}^2}{S_{\text{base}}}$$

$$\Rightarrow Z_{\text{base 2}} = \frac{(0600)^2}{50 \times 10^3}$$

$$= 1843.2 \Omega$$

[Substituting 0.6 kV for V_{base} & 50 kVA for S_{base}]

Substituting $j125 \Omega$ for Z_{actual} & 1843.2Ω for $Z_{\text{base 2}}$.

$$Z_{2 \text{ p.u.}} = \frac{j125}{1843.2} \text{ p.u.} = 0.068 j \text{ p.u.}$$

Hence, $Z_{\text{p.u.}} = \frac{Z_{\text{actual}}}{Z_{\text{base 2}}}$ for the expression per unit value of the transmission line impedance.

Substitute $(50 + j200) \Omega$ for Z_{actual} & 1843.2Ω for $Z_{\text{base 2}}$

$$Z_{p.u.} = \frac{50 + j200}{1843.2} \text{ p.u.}$$

$$= 0.027 + 0.1085j \text{ p.u.}$$

Substitute 25 KVA for KVA_{actual} & 50 KVA for KVA_{base} .

$$KVA_{p.u.} = \frac{25}{50} \text{ p.u.} = 0.5 \text{ p.u. rating}$$

Calculating the per unit voltage of motor:


$$K.V_{p.u.} = \frac{KV_{actual}}{KV_{base}}$$

$$KV_{base} = \frac{5 \times 10^3}{10 \times 10^3} (9600) \\ = 4.8 \text{ KV.}$$

Substitute 4 KV for KV_{actual} & 4.8 KV for KV_{base} .

$$K.V_{p.u.} = \frac{4}{4.8} \text{ p.u.}$$

$$= 0.833 \text{ p.u.}$$

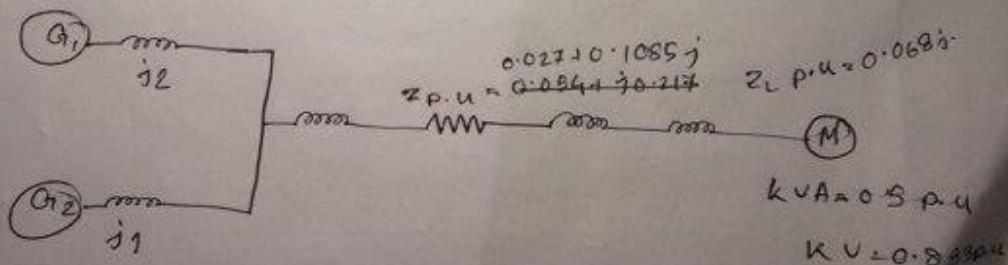

Answer to question NO: 2.

The base MVA in the γ circuit is 20 MVA

$$V_{\text{base } Z} = \frac{138}{\alpha} = 69 \text{ kV.}$$

$$Z_{\text{base } Z} = \frac{69^2}{10} = 476.1 \Omega.$$

Determine the p.u impedance.

$$Z_{\text{p.u}} = \frac{Z}{Z_{\text{base } Z}} = \frac{200}{476.1} = 0.420 \text{ p.u.}$$

Determining base impedance in circuit γ .

$$Z_{\text{base } \gamma} = \frac{V_{\text{base } \gamma}^2}{S_{\text{base}}} = \frac{138^2}{10} = 1269.6 \Omega$$

Determining the load impedance referred to γ -circuit.

$$Z_{\gamma} = (2)^2 \times 500 = 2000 \Omega.$$

$$\therefore Z_{\text{p.u}} = \frac{2000}{1269.6} = 1.557 \text{ p.u.}$$

$$V_{\text{base } x} = 138 \text{ kV.}$$

$$= 138 \left(\frac{1}{10} \right) = 13.8 \text{ kV.}$$

$$Z_{\text{base } x} = \frac{(13.8)^2}{10} = 12.69 \Omega.$$

$$\text{Here } Z_{\gamma} = a_1^2 \cdot Z_{\gamma} = \left(\frac{1}{10} \right)^2 (2000) = 20 \Omega.$$

$$\therefore Z_{\text{p.u}} = \frac{Z_{\gamma}}{Z_{\text{base } x}} = \frac{20}{12.69} = 1.575 \text{ p.u.}$$

Answer to Question No: 4

Answer to question NO: 4.

Choosing generator rating as the base MVA & KV
i.e. 25 MVA, 13.8 KV.

Generator Reactance $X_{gd} = 15.1 = 0.15 \text{ pu}$.

Transformer T_1 : 25 MVA = 13.2 / 69 KV, 114.
25 MVA, 13.8 KV are base.

New transformer reactance:

$$X_{T1\text{new}} = X_{T1\text{old}} \times \frac{\text{MVA}_{\text{new}}}{\text{MVA}_{\text{old}}} \times \left(\frac{\text{KV}_{\text{old}}}{\text{KV}_{\text{new}}} \right)^2$$

$$= 0.11 \times \left(\frac{25}{25} \right) \times \left(\frac{19.2}{13.8} \right)^2$$

$$X_{T1\text{new}} = 0.1 \text{ p.u.}$$

Both Transformers ratings are same.

$$\therefore X_{T1\text{new}} = X_{T2\text{new}} = 0.1 \text{ p.u.}$$

transmission reactance $X_{T2} = X_{T1} \times \frac{\text{MVA}}{\text{KV}^2}$

For, 13.2 KV - 69 KV


13.8 KV \rightarrow ?

$$\frac{69 \times 13.8}{13.2} = 72.13 \text{ KV.}$$


$$X_{T2} = 69 \times 25 / 72.13^2 = 0.3122 \text{ pu.}$$

$$\text{Motor reactance} = X_{md} = 0.15 \times \frac{25}{15} \times \left(\frac{19.2}{13.8} \right)^2 = 0.24 \text{ p.u.}$$

Finally, equivalent single line diagram

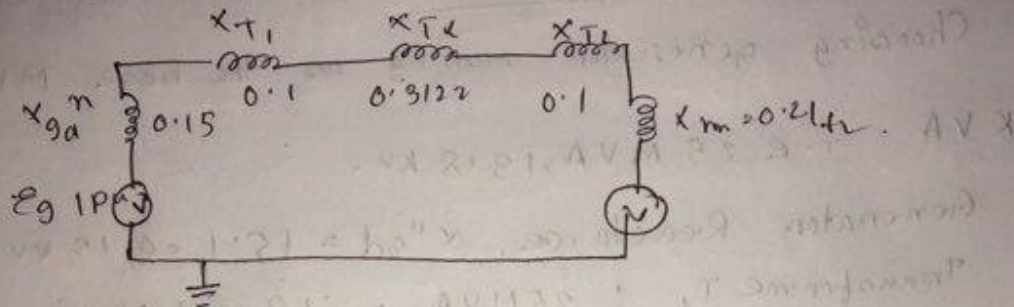

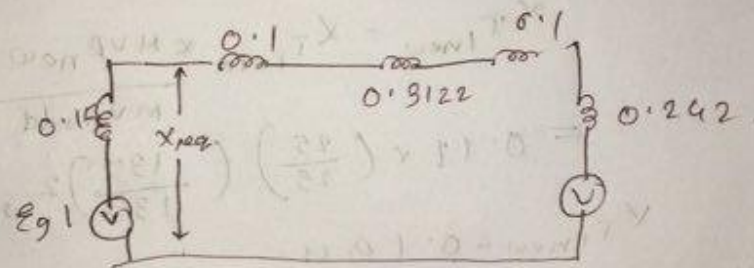3 phase fault is occurred on at the generator bus A. Then circuit is changed as below.



$$i_f = \frac{E_g}{X_{eq}}$$

$$X_{eq} = 0.15 \parallel (0.1 + 0.3122 + 0.1 + 0.242)$$

$$= 0.15 \parallel 0.7546$$

$$= 0.1251$$

$$\text{Subst fault current} = \frac{1}{0.1251} = 7.99 \text{ p.u.}$$

$$\text{Base Current} = \frac{\text{Rated MVA}}{\text{Rated kV}}$$

$$\frac{25}{\sqrt{3} \times 13.8} = 1.0459$$

$$\therefore I_D = 1045.9 \text{ A}$$

transient fault current in amperes

$$I_f = I_f(\text{pu}) \times I_D$$

$$= 7.99 \times 1045.9$$

$$= 8356.9 \text{ A} = 8.3569 \text{ kA}$$