



## Lab 3: Loading Effect of Voltage Divider Circuit

### Objective:


- ☐ To analyze how the voltage divider circuit behaves when there is no load resistance connected.
- ☐ Evaluate the performance of voltage divider circuit due to loading.

### List of Equipment:

- ☐ Trainer Board
- ☐ DMM
- $2 \times 560\Omega$  resistors
- $1 \times (0-10k\Omega)$  variable resistor

### Introduction:

Voltage Divider circuit provides a simple way to convert a DC voltage to another lower DC voltage. Consider the following voltage divider circuit.

 

**Figure 1:** A voltage divider on the left, and potentiometer on the right.

The voltage drop across  $R_2$  is the output voltage,  $V_{out}$ .  $V_{out}$  is less than  $V_{in}$  because the total voltage across  $R_1$  and  $R_2$  must add up to  $V_{in}$ . A potentiometer can also be used to change  $V_{out}$  by changing the resistance  $R_2$ . As the value of  $R_2$  is changed, it allows the output voltage to be adjusted from 0 to  $V_{in}$ .

In Figure 1, there is no output load ( $R_L$ ) connected in parallel to  $R_2$  hence we call it a No-Load circuit.

According to Voltage Divider Rule:  $V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$  (1)

- ☐ Say  $V_{in}=5v$  and you need  $V_{out}= 3v$ . How would you set the values of  $R_1$  and  $R_2$  ?

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Choice of resistor value should follow the ratio:  $\frac{R_1}{R_2} = \frac{2}{3}$

One possible combination:  $R_1=2k$  and  $R_2=3k$

- ☐ Now say we connect an output load,  $R_3$  in parallel to  $R_2$  :

 


Figure 2: With Output Load Connected.

⇒ Do you think keeping the values of resistors same would still give  $V_{out}=3v$  from  $V_{in}=5v$ ?  
Let's check:

Since you have a Load resistance parallel to  $R_2$ , your Voltage divider formula to find  $V_{out}$  is:

$$V_{out} = V_{in} \frac{(R_2 // R_3)}{R_1 + (R_2 // R_3)} \quad (2)$$

Let  $R_3 = 10k$ .

$R_2 // R_3 = 2.31k$

→  $V_{out} = 2.68v$

So, our Designed value was 3v, but connecting a load resistor reduced it to 2.68v.

### Design Criteria:

To minimize the loading effect, choose the load resistor to be much larger than its parallel resistor.

If  $R_3$  is much greater than  $R_2$  then  $R_2 // R_3$  (parallel combination of  $R_2$  and  $R_3$ ) is approximately equal to  $R_2$

### Circuit Diagram:

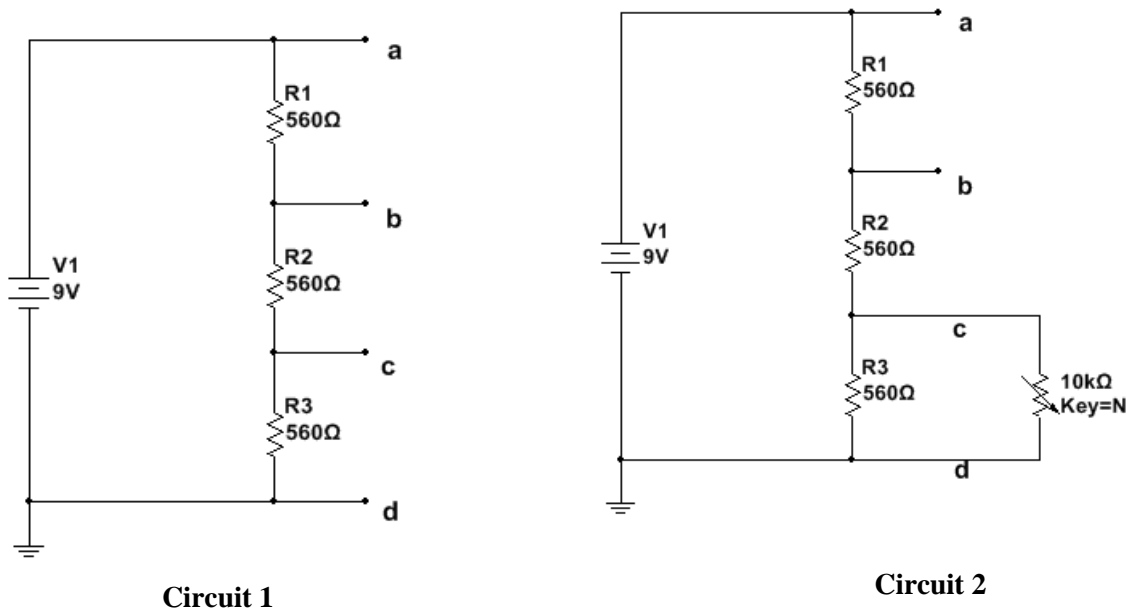


Figure C.1



	Circuit 1	Circuit 2 (R4= 1K $\Omega$ )	Circuit 2 (R4= 4K $\Omega$ )	Circuit 2 (R4= 7K $\Omega$ )	Circuit 2 (R4= 10K $\Omega$ )
<b>R<sub>T</sub></b>					
<b>E</b>					
<b>I</b>					
<b>V<sub>R1</sub></b>					
<b>V<sub>R2</sub></b>					
<b>V<sub>R3</sub></b>					
<b>V<sub>R4</sub></b>	xxxxxxxxxxxx				
<b>I<sub>R1</sub></b>					
<b>I<sub>R2</sub></b>					
<b>I<sub>R3</sub></b>					
<b>I<sub>R4</sub></b>	xxxxxxxxxxxx				
Table C.1					

### C.3 Report

1. Theoretically analyse circuits in figure C.1 using voltage divider rule and obtain all the theoretical values of Table C.1
2. Calculate the percentage of errors of all the measurements.
3. Compare and comment on the theoretical and experimental values.
4. Discuss on the loading effect of voltage divider circuit.



### Procedure:

1. Construct the voltage divider circuit as shown in figure above.
2. Measure the unloaded output voltage  $V_{out}$ . Record the value in Table 1.
3. Connect 10 k $\Omega$  variable load resistor, parallel with  $R_2$  to the circuit. (Connect 1 middle pin of variable resistor and one of the other pins).
4. Change the value of the variable resistor according to Table 1, and record  $V_{out}$  for each resistor value in Table 1.

### Data Collection for Exp 3 :

Group No. \_\_\_\_\_

Instructor's Signature \_\_\_\_\_

Table 1:

RL	Vout (Measured)	Vout (Calculated)	%Error
0			
1k			
4k			
7k			
10k			

### Report Question:

1. Showing all steps in details, calculate the value of  $V_{out}$  for each load resistor.
2. Calculate the percentage of errors of all the measurements.
3. Compare and comment on the theoretical and experimental values.
4. Discuss on the loading effect of voltage divider circuit.