

Digital Logic Design :

Lecture 6

"Don't care" conditions,

use of "don't care" conditions to simplify an expression.

Inputs				Output
A	B	C	D	Y
0	0	0	0	X
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

AB \ CD				
	00	01	11	10
00	X			
01			1	
11	X	X	X	X
10	1	1	X	X


Without don't cares

$$Y = A\bar{E}\bar{B} + \bar{A}BCD$$

with don't cares

$$Y = A + BCD$$



Combinational Logic Circuit

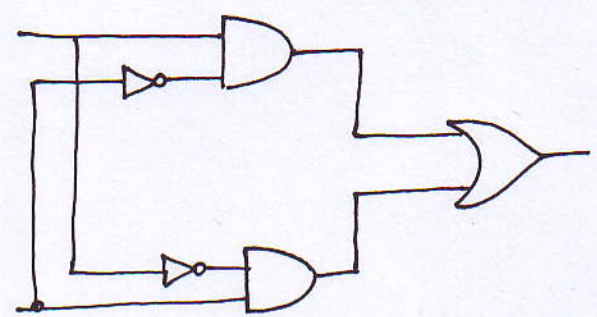

$$Y = A\bar{B} + \bar{A}B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


$$\therefore Y = A \oplus B$$

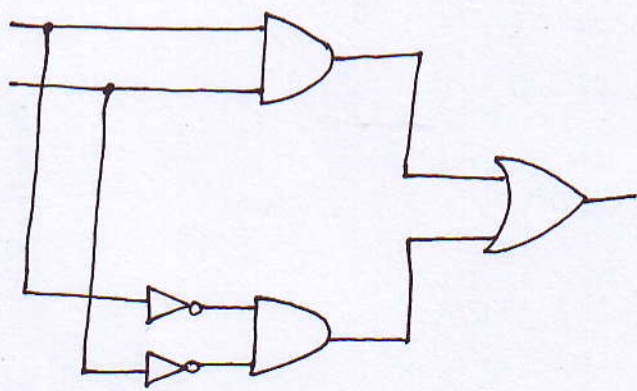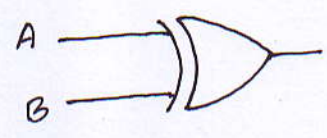

$$Y = AB + \bar{A}\bar{B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = \overline{A \oplus B}$$

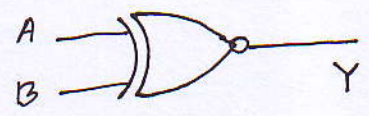

The universal property of NAND and NOR gates.

Truth table for 2 input NAND gate

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

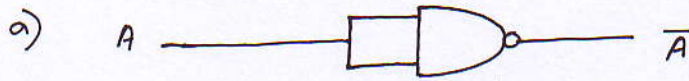


fig : A NAND gate used as an inverter

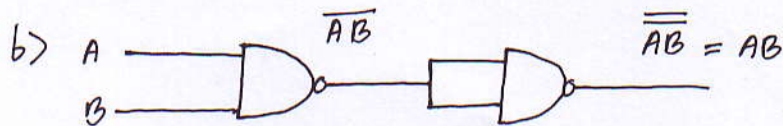


fig : Two NAND gates used as an AND gate

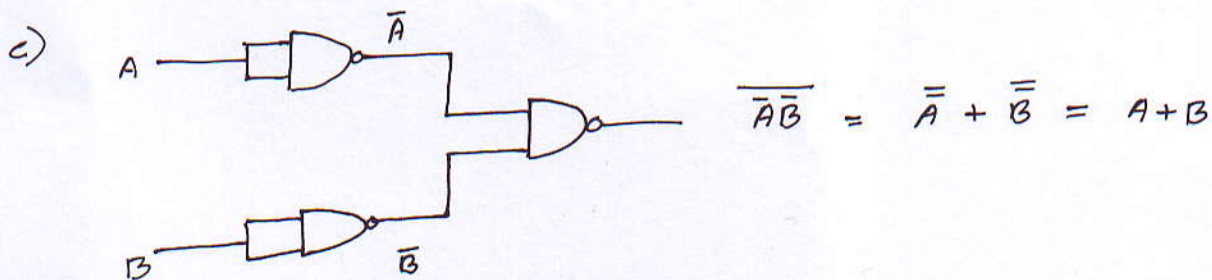


fig : Three NAND gates used as an OR gate

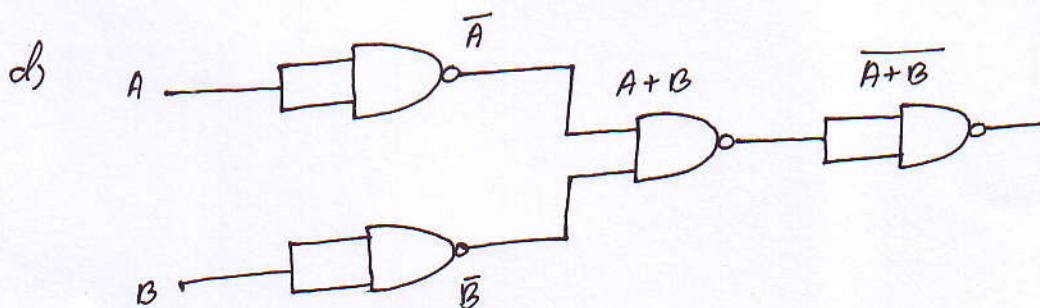


fig : Four NAND gates used as NOR gate

The NOR Gate as a universal Logic element

Truth table for 2 input NOR Gate



Fig : a NOR gate used as an inverter

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

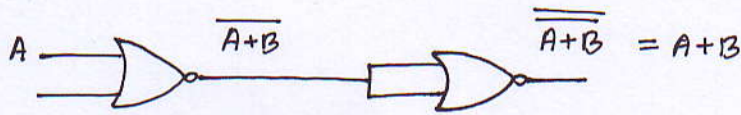


Fig : Two NOR gates used as an OR gate

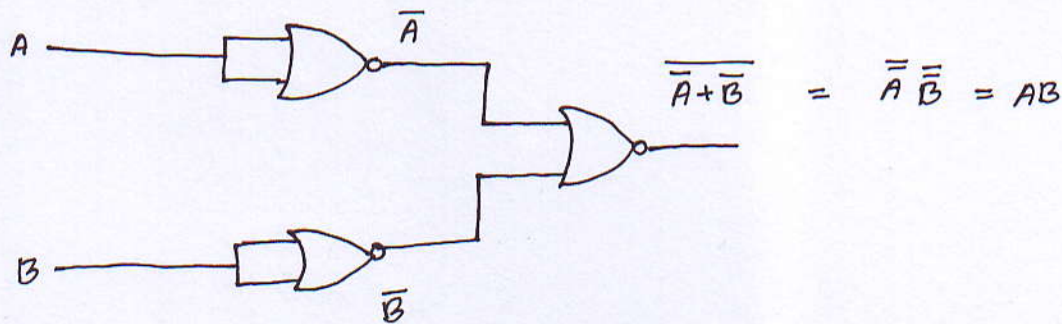


Fig : Three NOR gates used as an AND gate

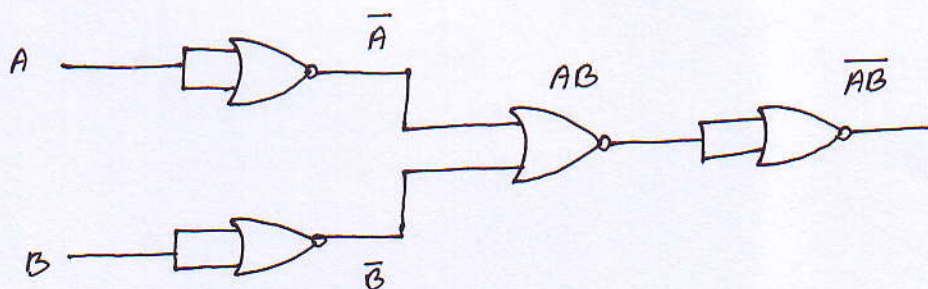


Fig : Four NOR gates used as a NAND gate

Simplify the Boolean Function in

a) Sum of products and

b) Product of sum form

$$F(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10)$$

a)

		CD			
		00	01	11	10
AB	00	0 1	1 1	3	2 1
	01	4	5 1	7	6
	11	12	13	15	14
	10	8 1	9 1	11	10 1

$$F = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}\bar{C}D$$

In product of maxterms, F can be expressed as

$$F(A, B, C, D) = \pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

b)

		CD			
		00	01	11	10
AB	00			0	
	01	0		0	0
	11	0	0	0	0
	10			0	

$$\bar{F} = CD + AB + B\bar{D}$$

$$F = \overline{CD + AB + B\bar{D}}$$

$$= (\bar{C}\bar{D})(\bar{A}\bar{B})(\bar{B} + D)$$

$$= (\bar{C} + \bar{D})(\bar{A} + \bar{B})(\bar{B} + D)$$

Exercise

$$F(A, B, C, D) = \sum (5, 7, 8, 10, 11, 14, 15)$$

$$d = \sum (0, 12, 13)$$

Combinational Logic using NAND and NOR gates :

NAND gate :

using De Morgan's rule

$$\overline{AB} = \underbrace{\bar{A} + \bar{B}}_{\text{Negative OR}}$$



Fig : Two graphic symbols for NAND gate

$$\overline{A+B} + \bar{A}\bar{B}$$

Negative AND

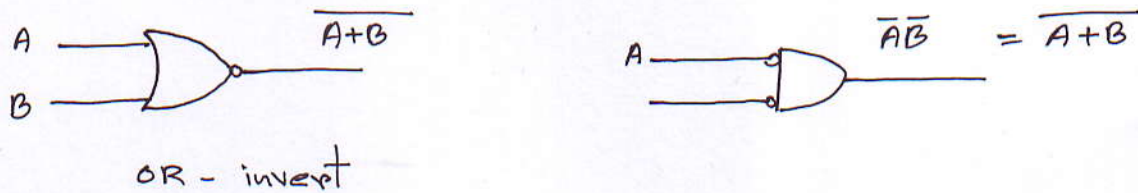


Fig : Two graphic symbols for NOR gate